

# Design of an Amplifier for Sensor Interfaces

Anurag Mangla

Electrical and Electronics Engineering

*anurag.mangla@epfl.ch*

*Supervised by*

Dr. Marc Pastre


Prof. Maher Kayal



# Outline


- Introduction
- Need for high gain
- Gain enhancement methods
  - Cross-coupled current mirror
  - Regulated current source
- Design methodology for high-gain op-amp
- Simulation Results
- Summary

# Sensors

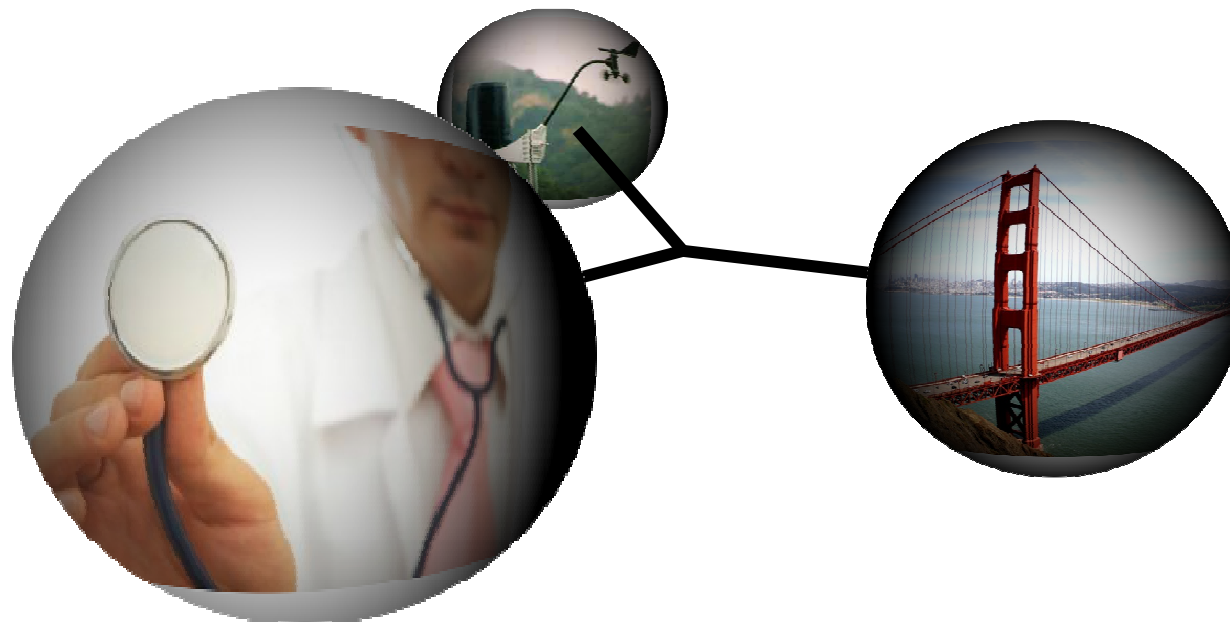


Healthcare Monitoring

# Sensors

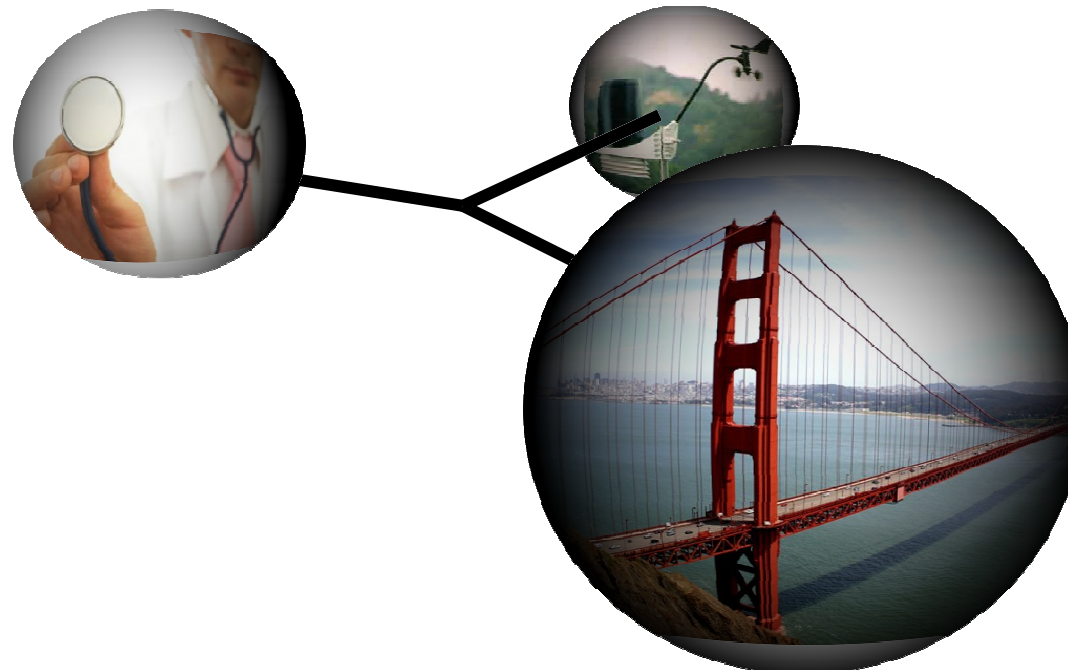

Structural Monitoring

# Sensors

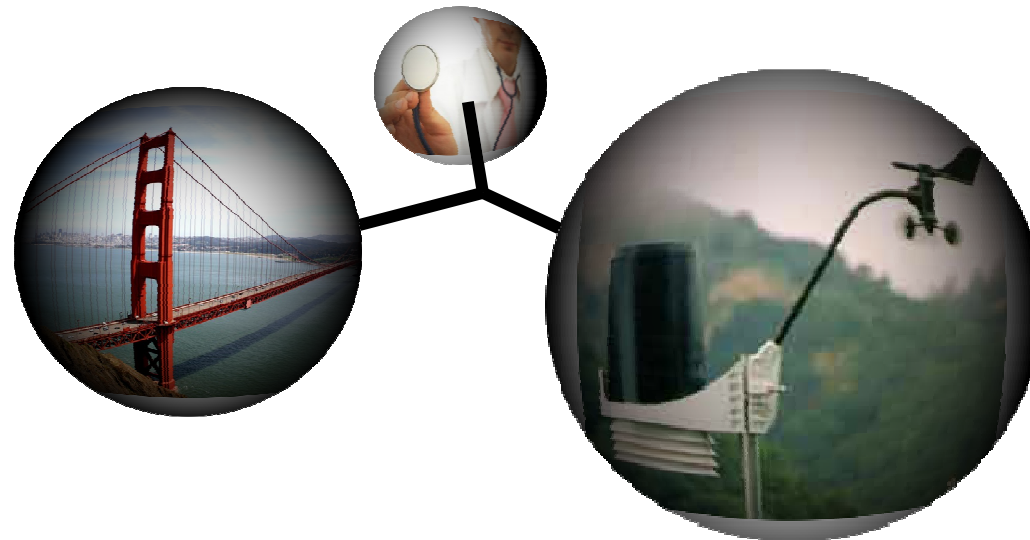

Weather & Agricultural  
Monitoring

# ...even in the iPhone


**Accelerometer**

**Capacitive touch sensor**




**CCD sensors**

# The Role of Amplifiers

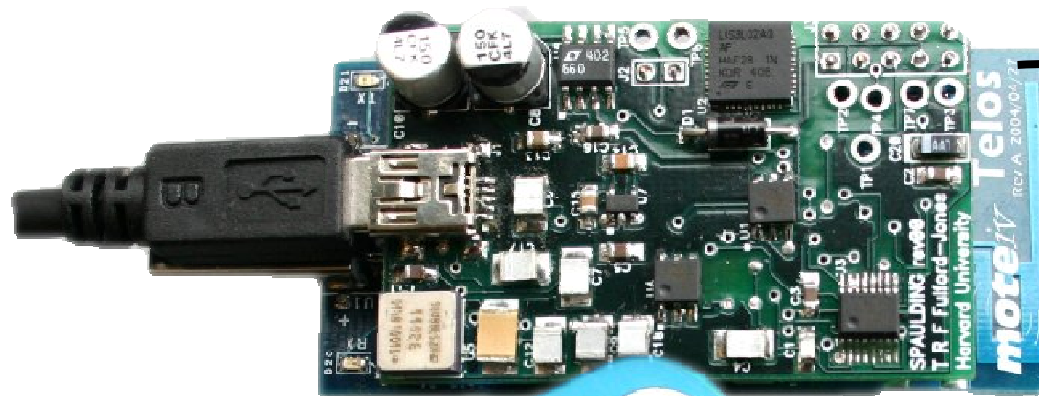

Circuitry for  
Signal Conditioning/  
Processing/Transmission

**Signal amplification required**

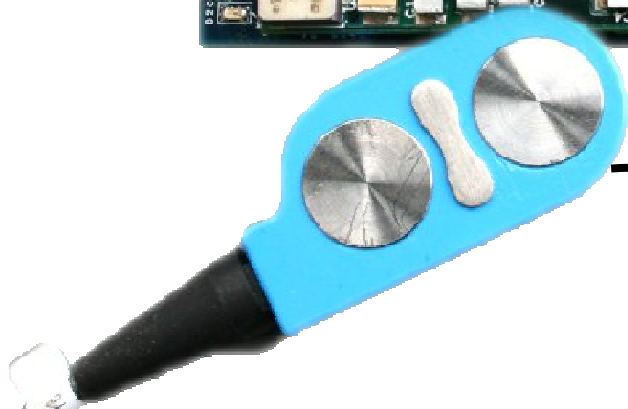

Sensor  
Produces low-level signal



# Target Design Specifications


- **Gain:**  $>120$  dB
- **Noise:**  $< 10\text{nV}/\sqrt{\text{Hz}}$
- **GBW:** Configurable
  - high speed
  - low speed
- **Power Consumption:** Low but variable


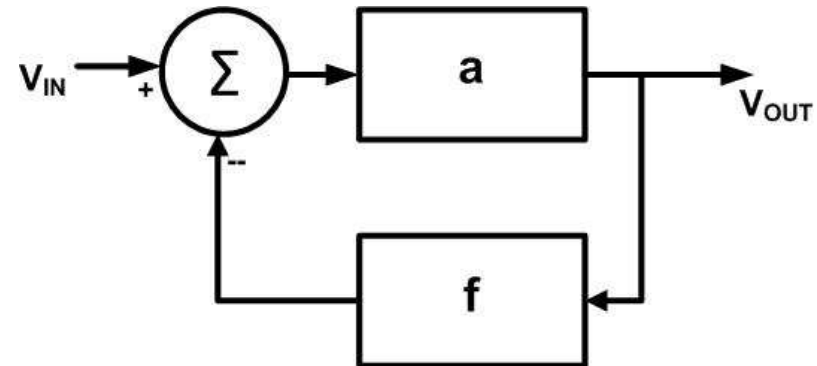
# The Need for High Gain


$$A = \frac{a}{1 + af}$$

$$A \approx \frac{1}{f} \quad \text{for } af \gg 1$$




$$\frac{dA}{A} = \frac{da}{a} \left( \frac{1}{1 + af} \right) \quad \text{-> desensitization}$$

# Classical Miller Amplifier

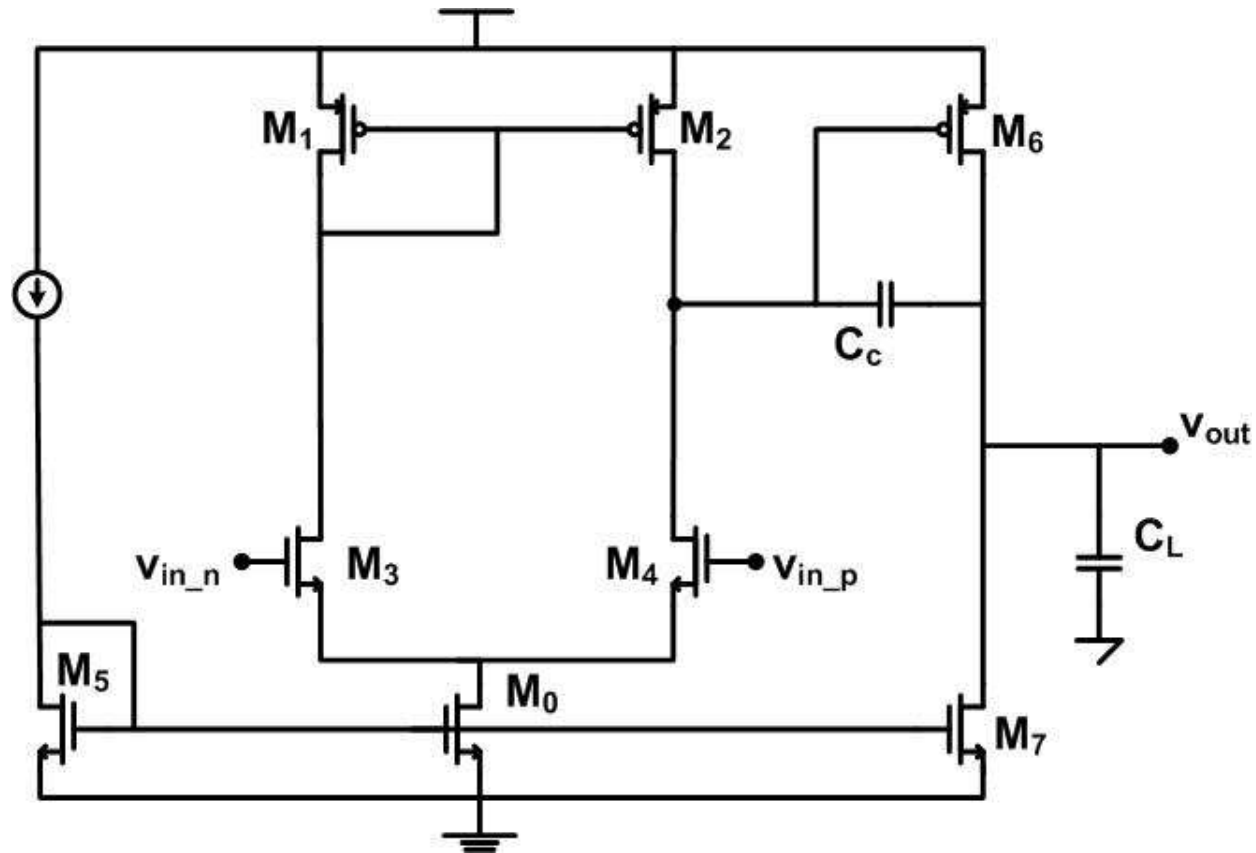

# Classical Miller Amplifier

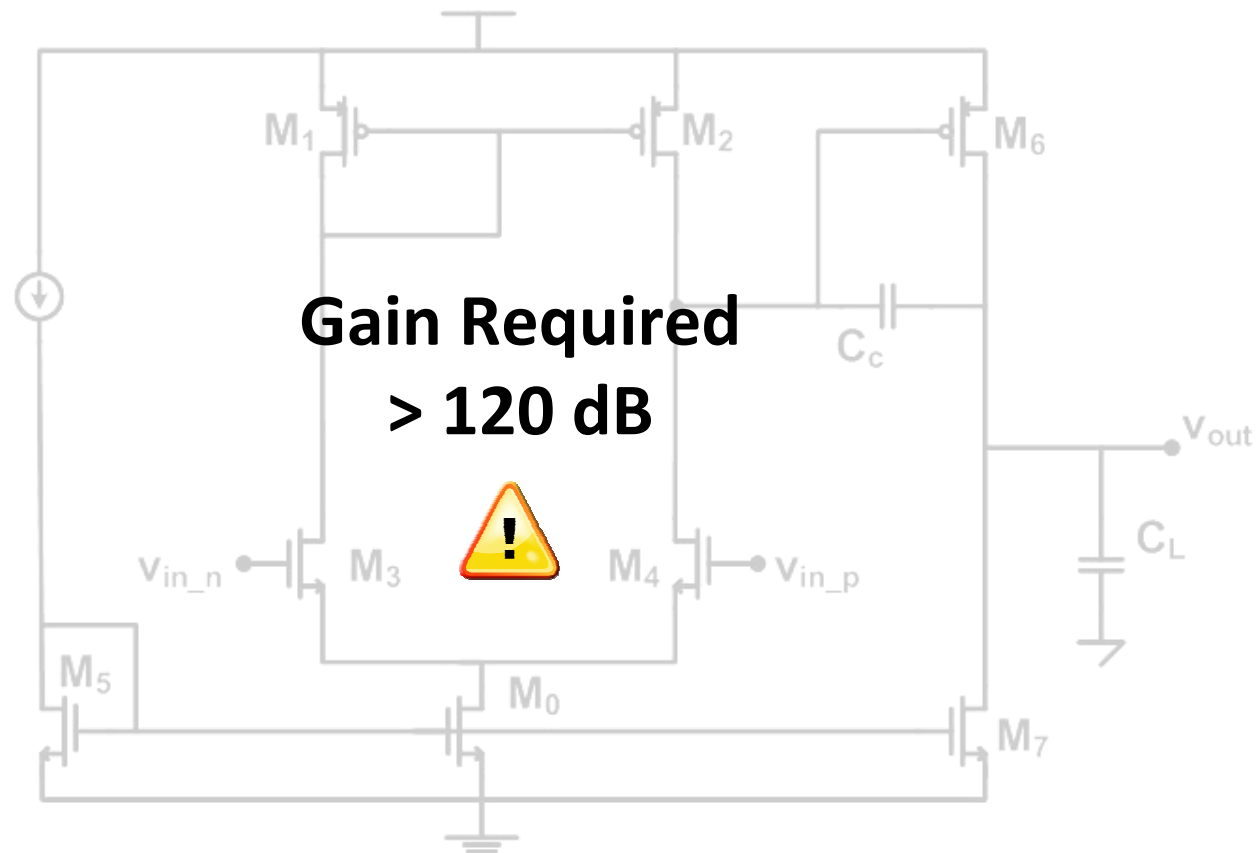

# Gain Enhancement: Options

- Modify first stage
  - Cascode load
  - Folded-cascode
  - Cross-coupled current mirror
  - Regulated current source

# Gain Enhancement: Options

- Modify first stage
  - Cascode: **Reduced voltage headroom**
  - Folded-cascode
  - Cross-coupled current mirror
  - Regulated current source


# Gain Enhancement: Options

- Modify first stage
  - Cascode: Reduced voltage headroom
  - Folded-cascode: Higher power consumption
  - Cross-coupled current mirror
  - Regulated current source

# Gain Enhancement: Options


- Modify first stage
  - Cascode: Reduced voltage headroom
  - Folded-cascode: Higher power consumption
  - Cross-coupled current mirror
  - Regulated current source

# Gain Enhancement: Cross Coupled Load

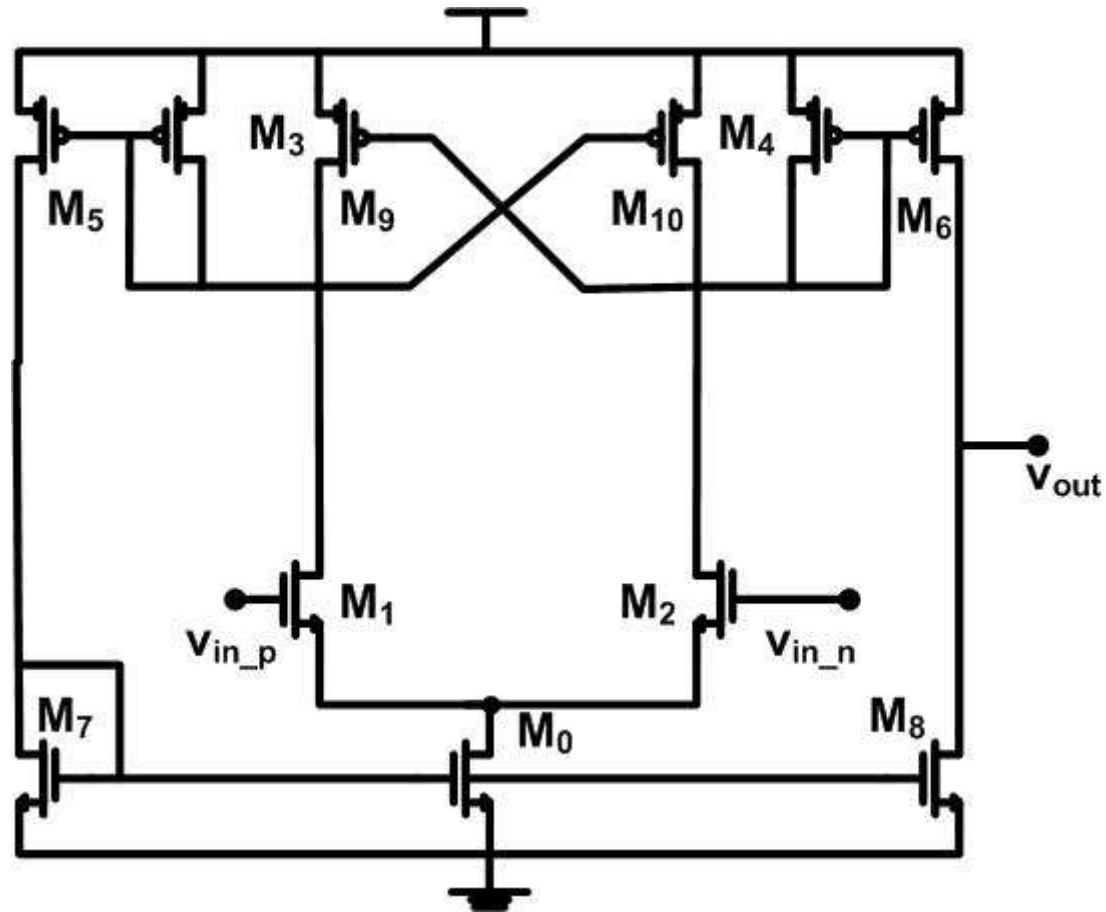



# Cross Coupled Current Mirror Load

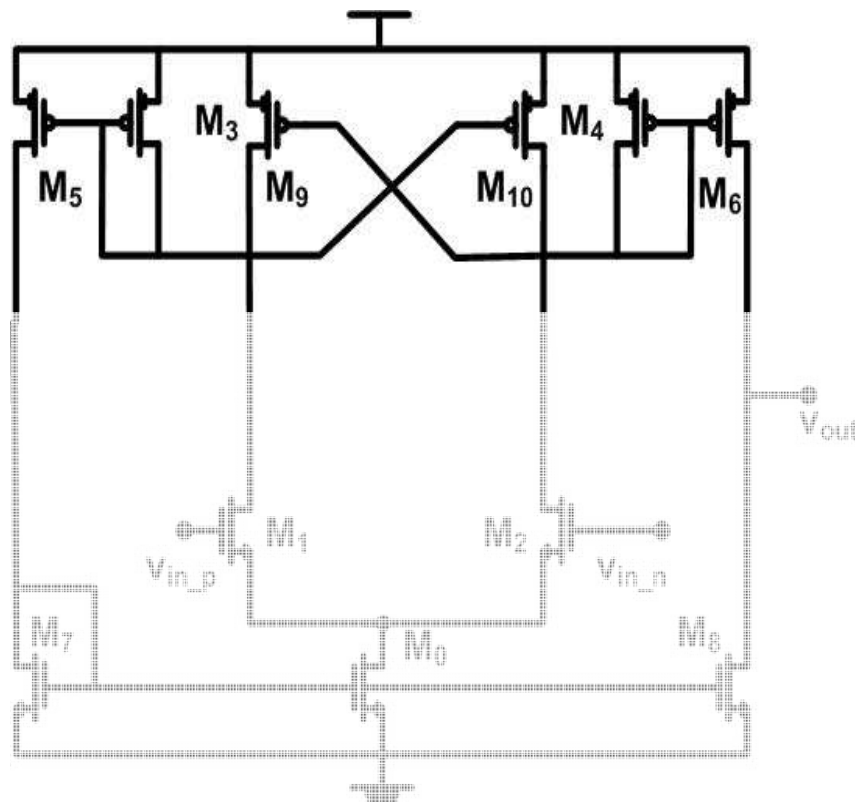

$$G = A \left( \frac{1}{1 - \eta} \right)$$

$$\eta = \frac{\Delta I_3}{\Delta I_{10}} = \frac{G_{m9}}{G_{m3}} \quad \text{Loop Gain}$$

$$G_m = \frac{G_{m1}}{1 - \eta} \quad \text{Effective Transconductance}$$

# Cross Coupled Load: Stability Issues

$$\eta = \frac{\Delta I_3}{\Delta I_{10}} = \frac{G_{m9}}{G_{m3}}$$

$$G = A \left( \frac{1}{1 - \eta} \right)$$

- If  $\eta \rightarrow 1$ , amplifier can become **unstable**
- If  $\eta \rightarrow 0$ , no gain improvement
- Critical value of  $\eta$  needs to be chosen

# Cross Coupled Load: Stability Issues

$$\frac{1}{1-\eta} = \frac{1}{1-(1-3\sigma)} = \frac{1}{3\sigma}$$

$$\eta = \frac{G_{m9}}{G_{m3}} \approx \sqrt{\frac{I_{F3}}{I_{F9}}}$$

$$\sigma_{\eta}^2 = \frac{1}{4}\eta^2(\sigma_{ID3}^2 + \sigma_{ID9}^2) + \sigma_{I_{spec3}}^2 + \sigma_{I_{spec9}}^2$$

- 1/ 3σ : max. possible gain enhancement
- Susceptible to instability due to **mismatch**
- Very carefully matched design required


# Gain Enhancement: Options

- Modify first stage
  - Cascode: Reduced voltage headroom
  - Folded-cascode: Higher power consumption
  - Cross-coupled current mirror: Susceptible to instability
  - Regulated current source


# Gain Enhancement: Options

- Modify first stage
  - Cascode: Reduced voltage headroom
  - Folded-cascode: Higher power consumption
  - Cross-coupled current mirror: Susceptible to instability
  - Regulated current source


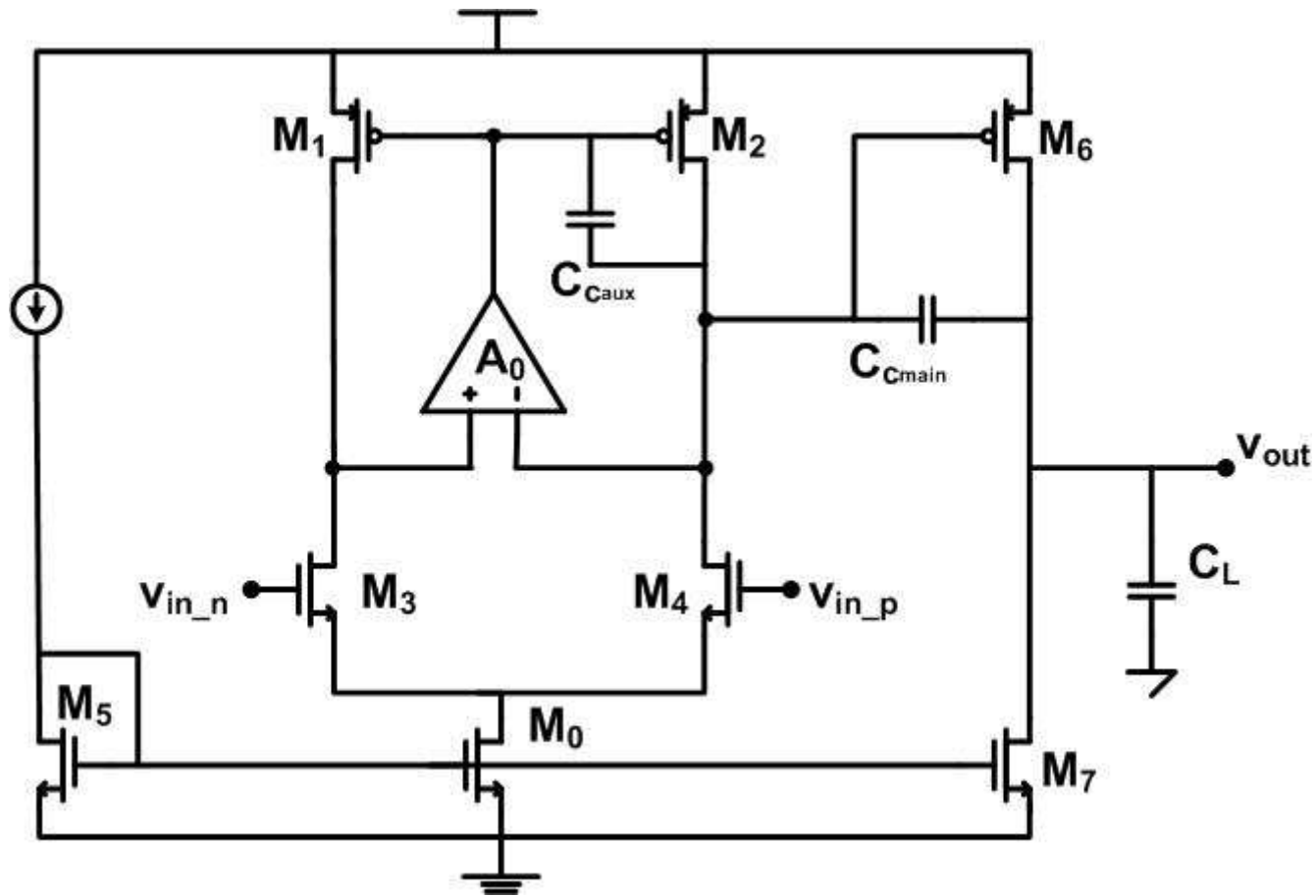
# Gain Enhancement: Regulated Current Source


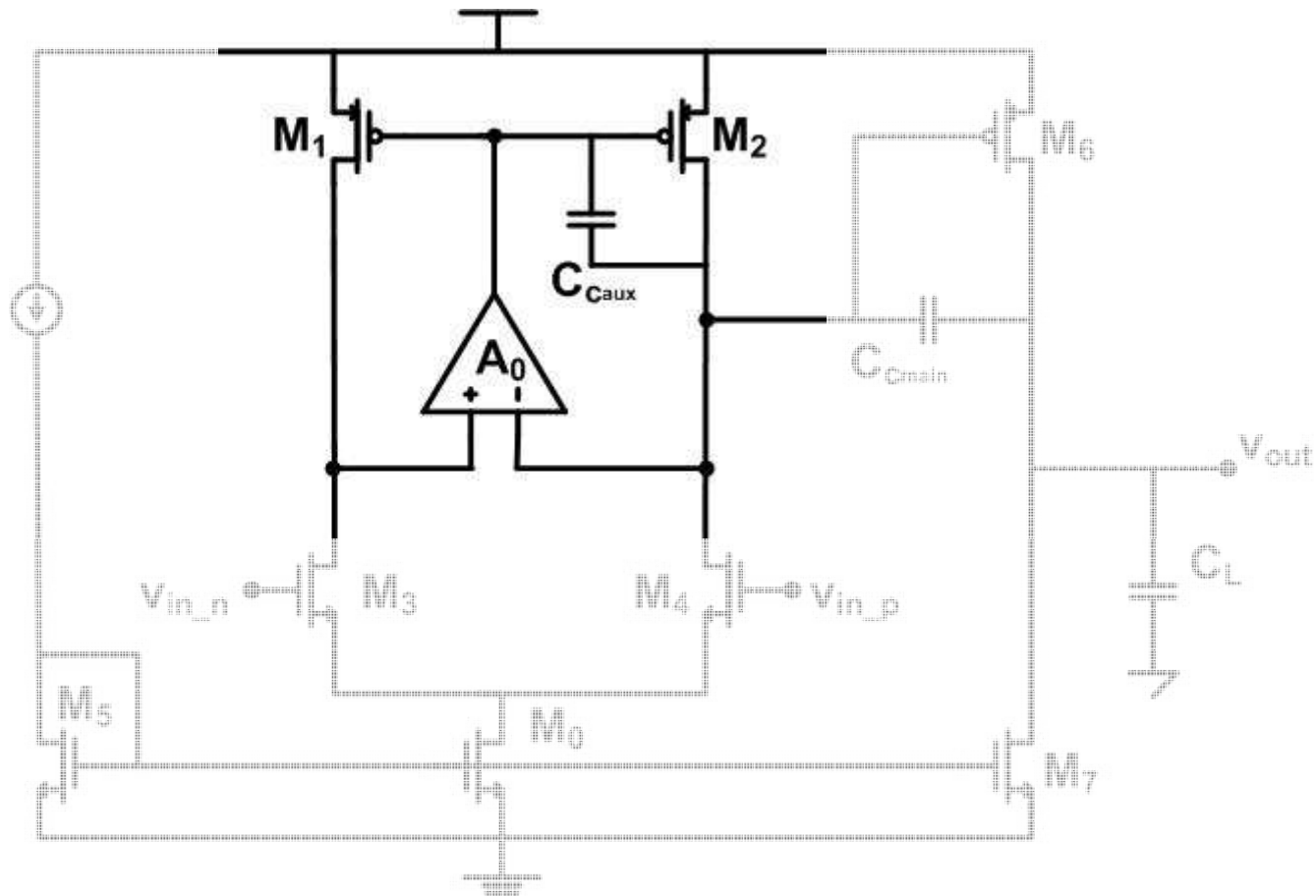
# Gain Enhancement: Regulated Current Source



# Regulated Current Source

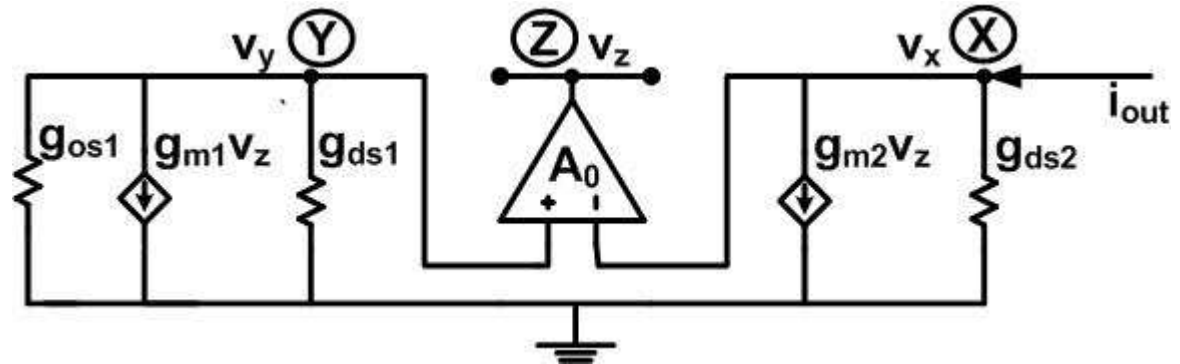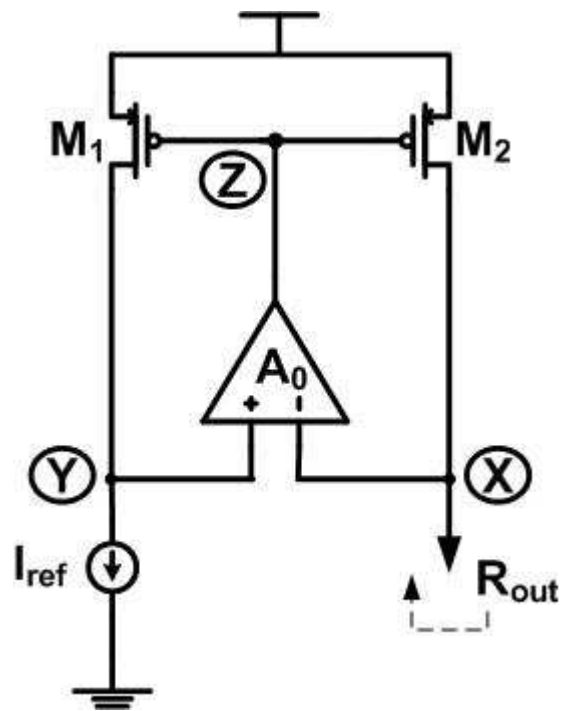


$V_x$  tracks  $V_y$

$$R_{out} \approx -1/g_{os}$$



# Regulated Current Source

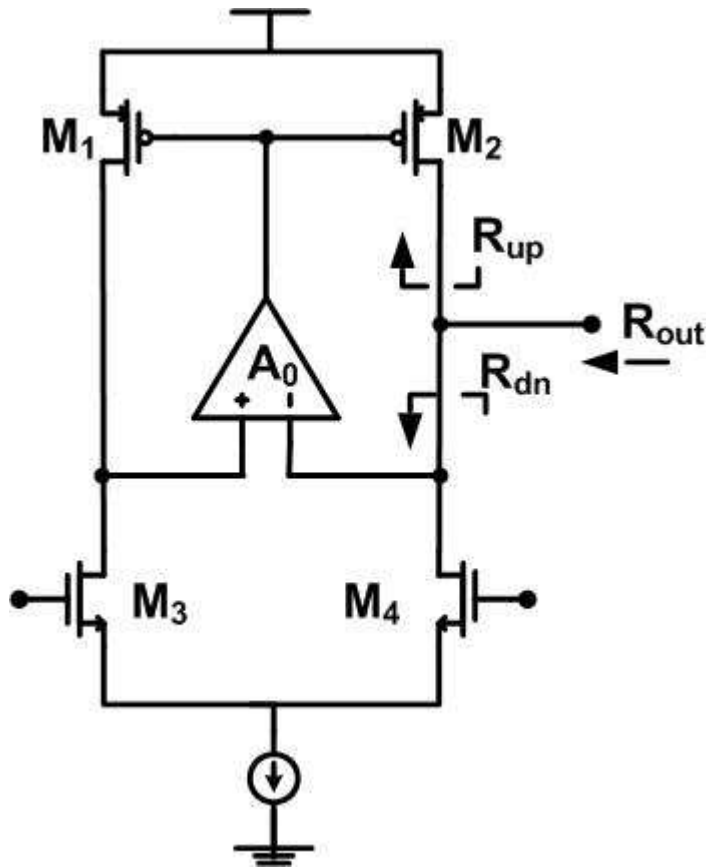


$$R_{up} \approx \frac{1}{g_{dsM_3}}$$


$$R_{dn} = \frac{1}{g_{dsM_4}}$$

$$R_{out} \rightarrow \infty$$


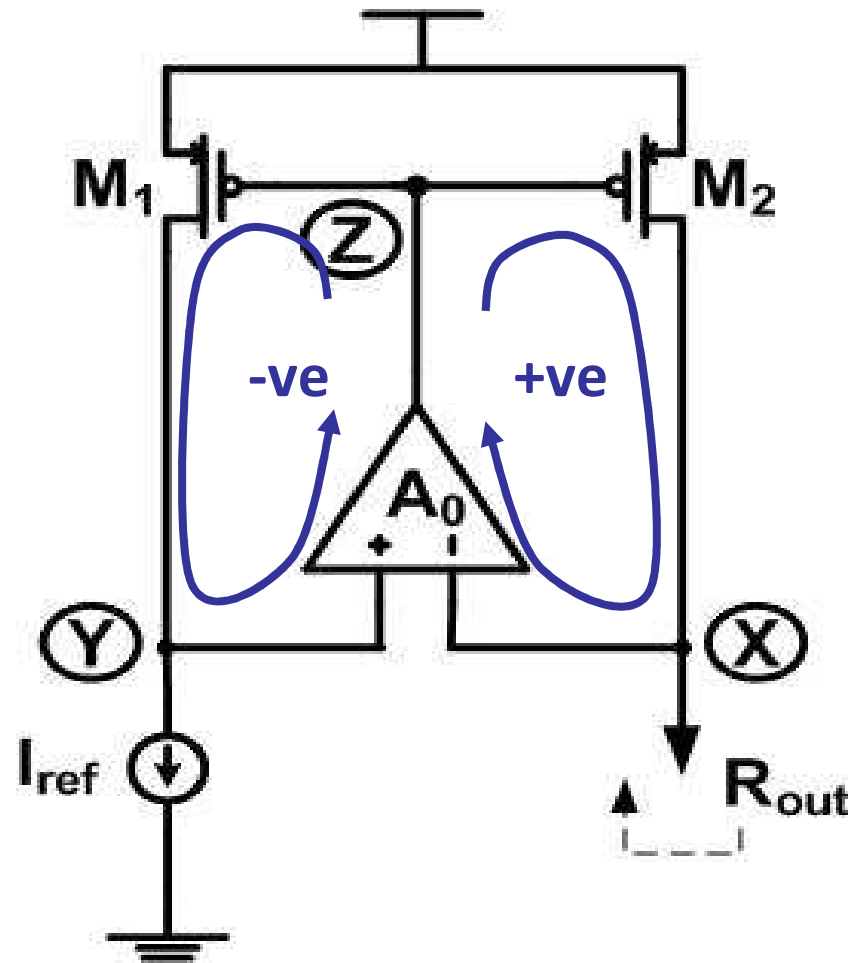
# Regulated Current Source: Stability issues





# Instability: A Detour

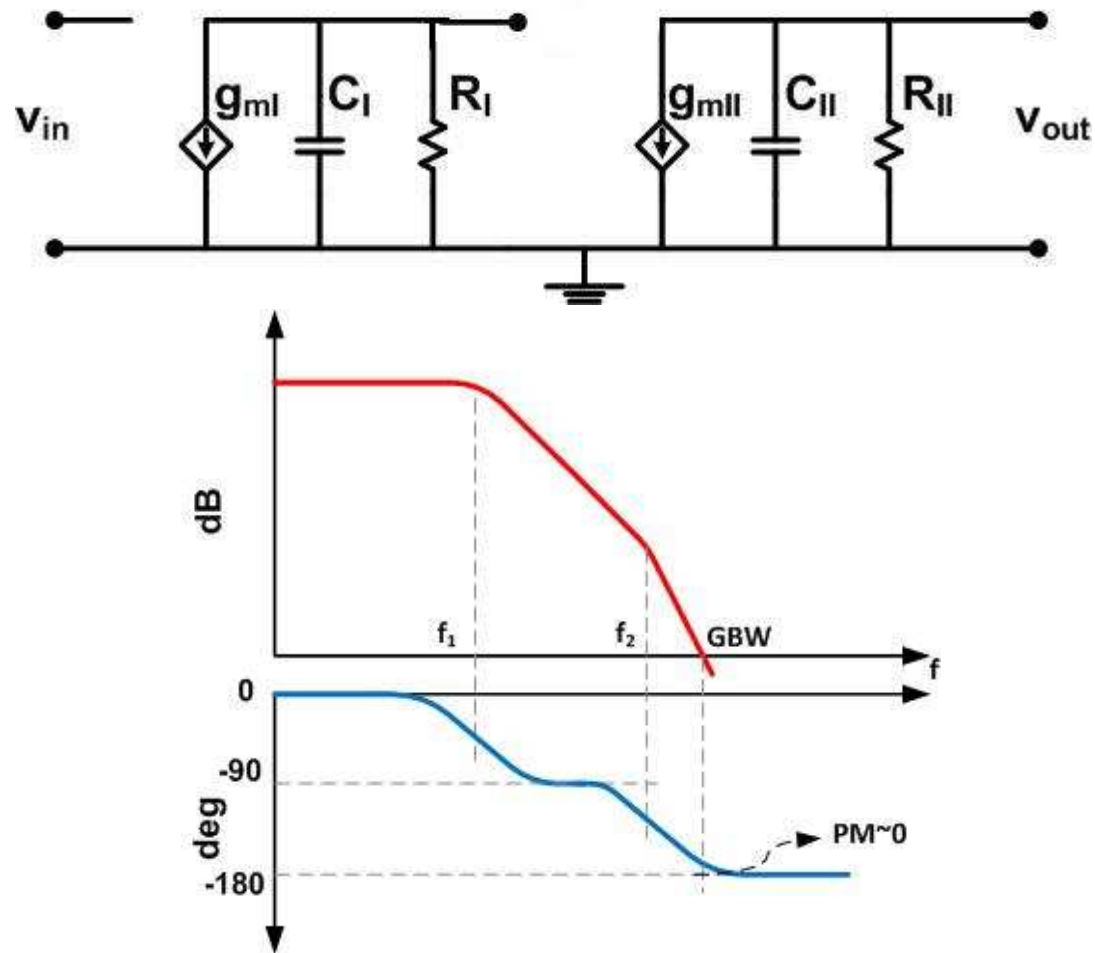



# Compensation

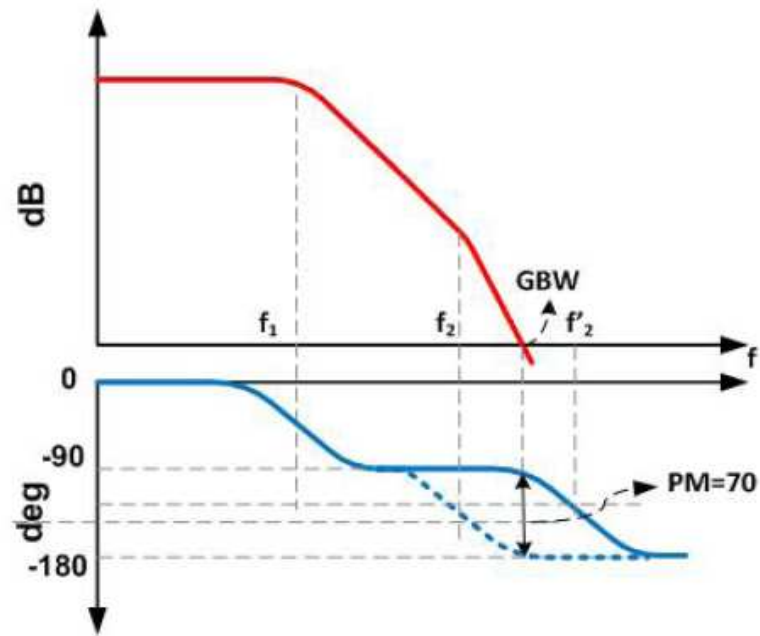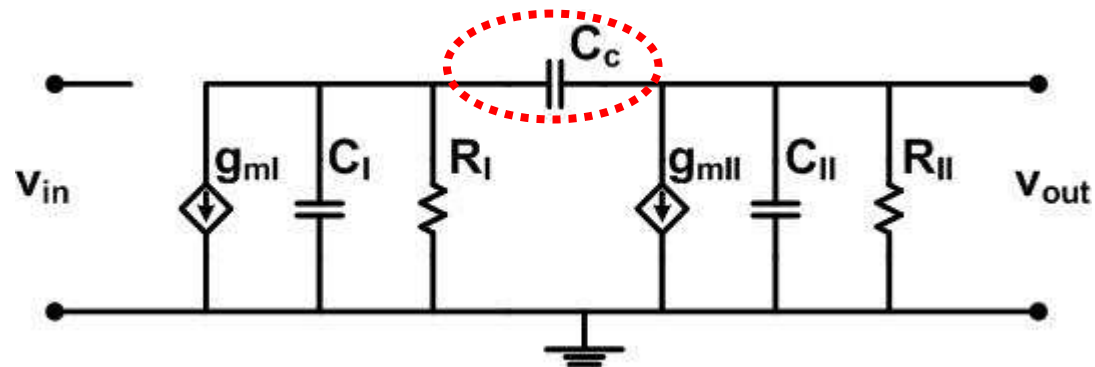


# Compensation

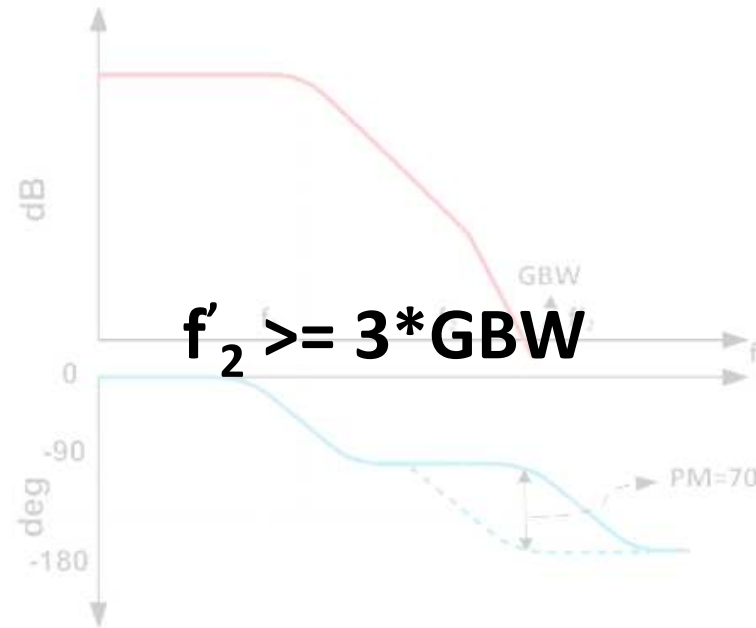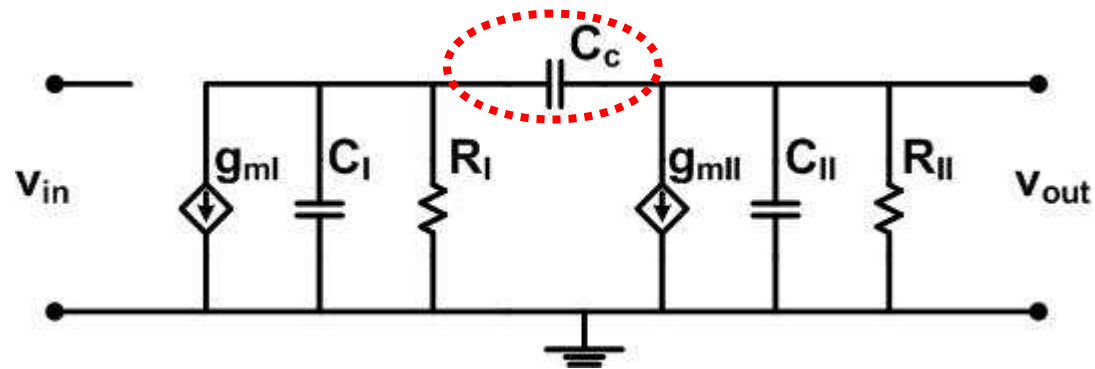

# Compensation

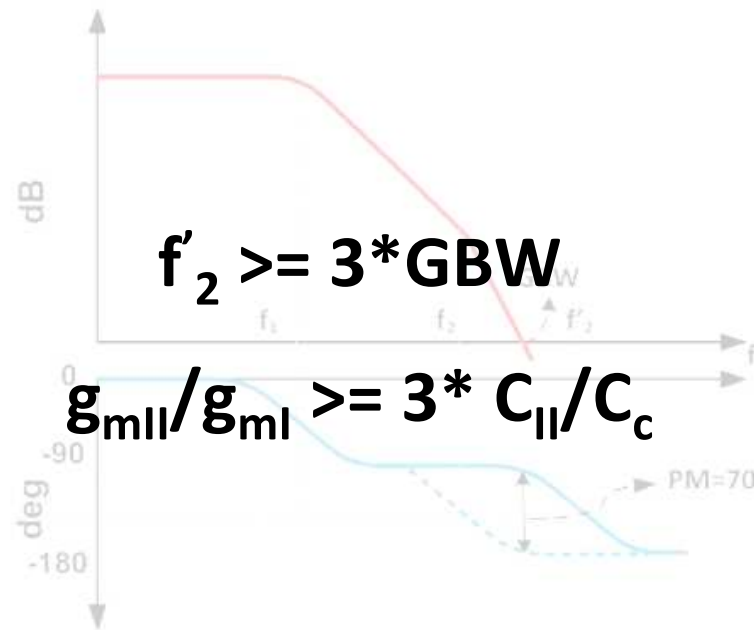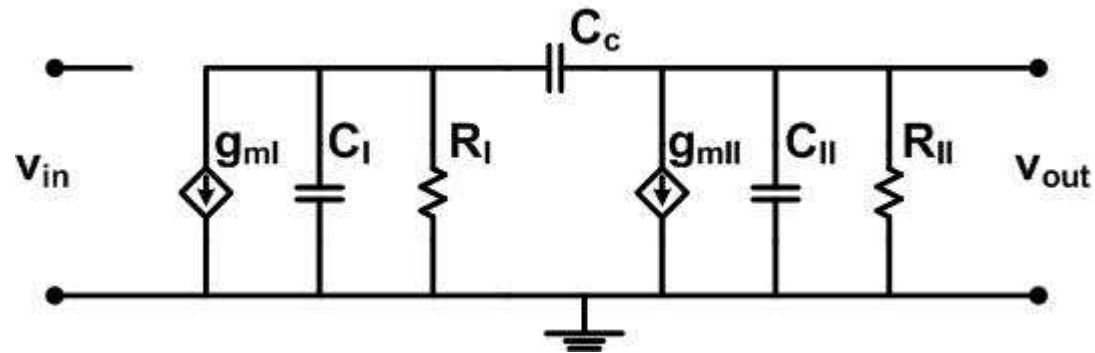
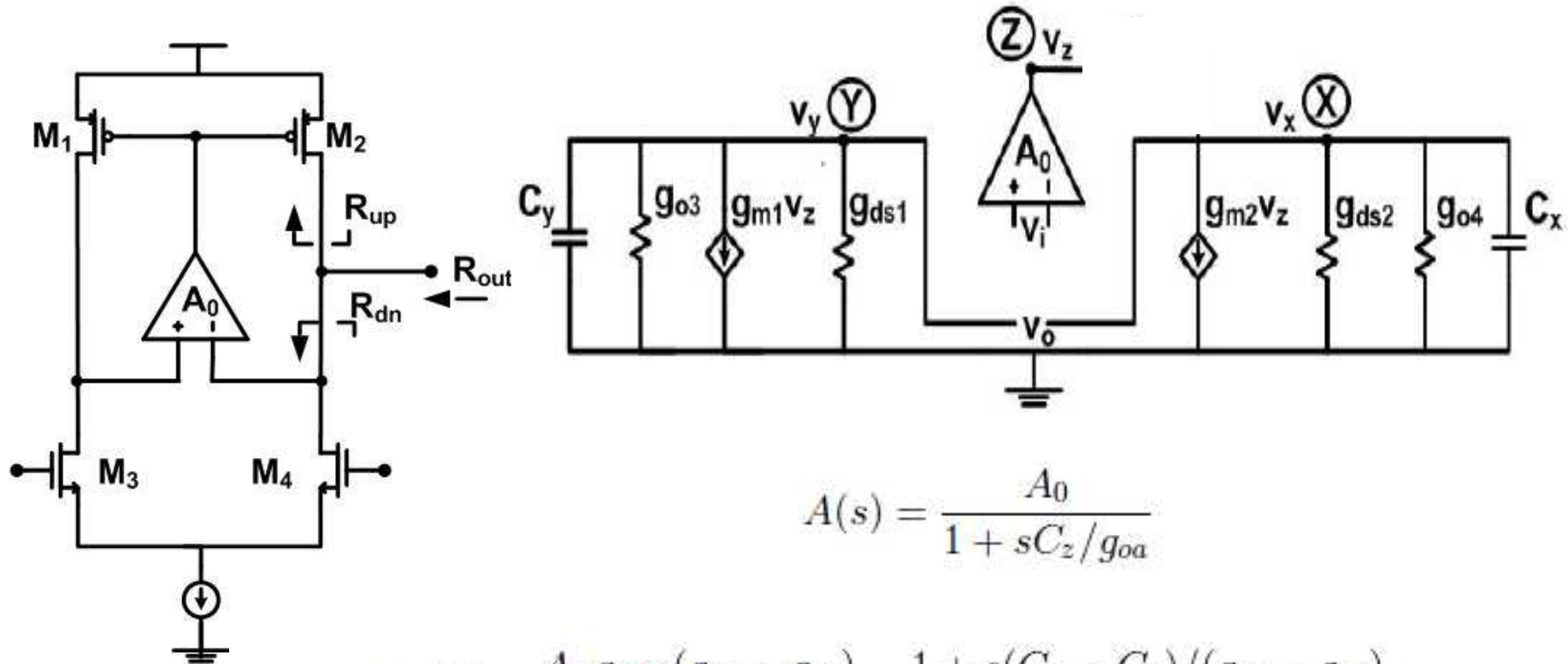
# Regulated Current Source: Stability issues




$$A(s) = \frac{A_0}{1 + sC_z/g_{oa}}$$

$$H_{OL}(s) = \frac{A_0 g_{m12}(g_{o4} - g_{o3})}{g_{ds12}(g_{ds12} + g_{o4})} \cdot \frac{1 + s(C_x - C_y)/(g_{o4} - g_{o3})}{(1 + s/p_x)(1 + s/p_y)(1 + s/p_z)}$$


where  $p_x = (g_{o3} + g_{ds12})/C_x$ ,  $p_y = (g_{ds12} + g_{o3})/C_y$  and  $p_z = g_{oa}/C_z$ .
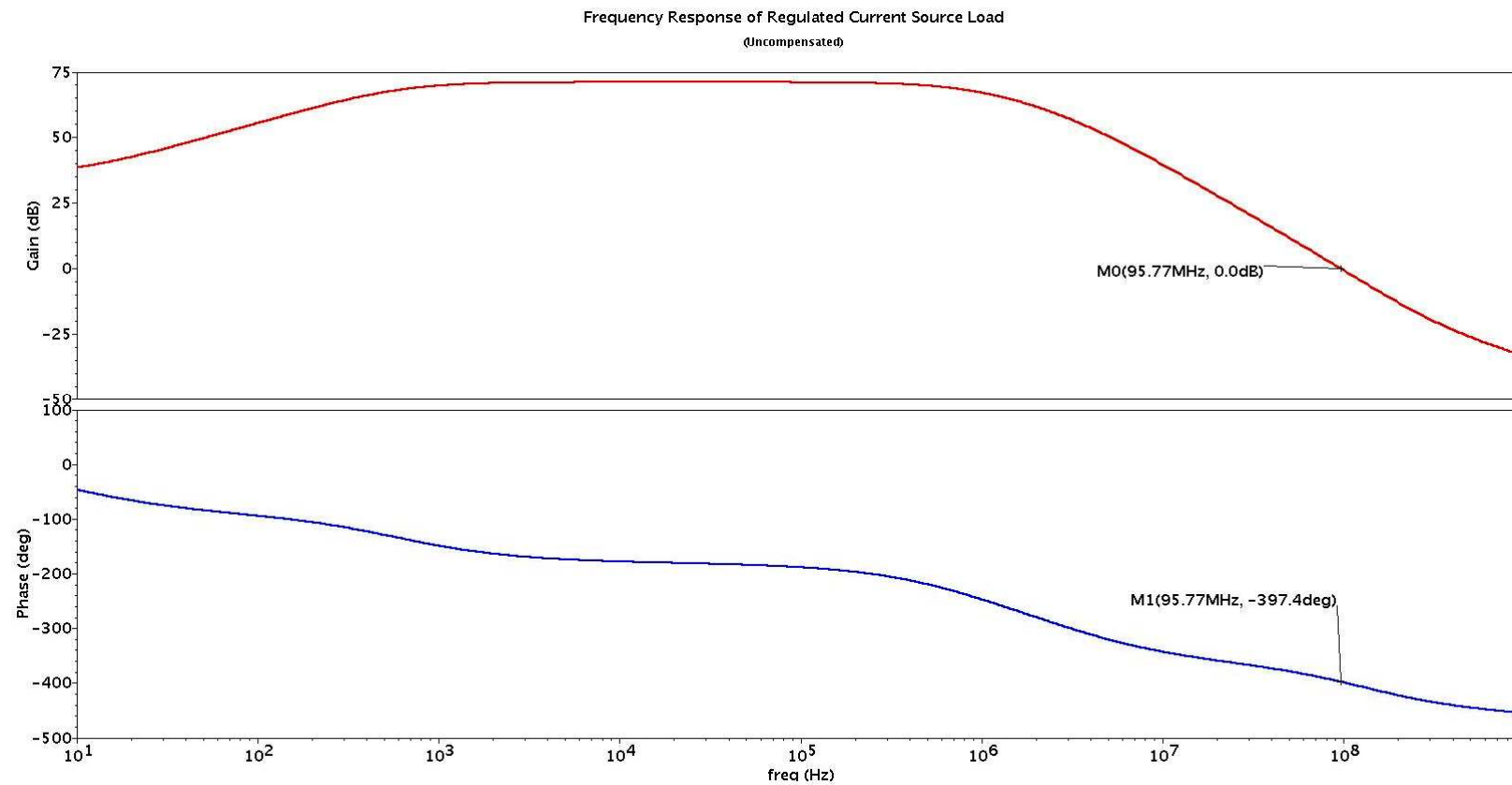
# Regulated Current Source: Stability issues




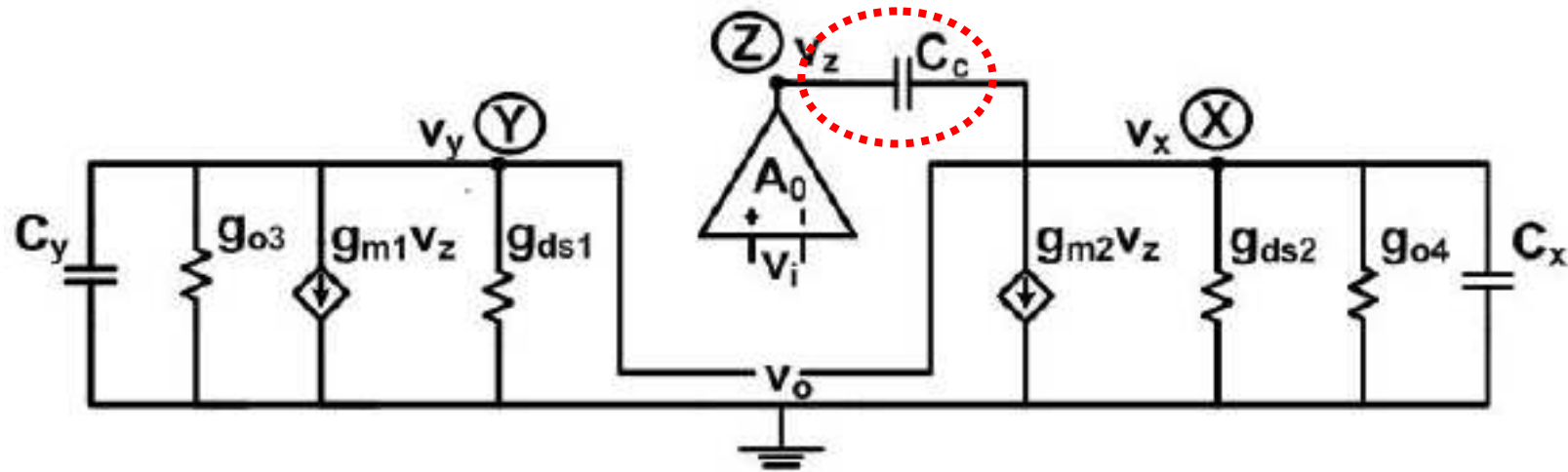
# Regulated Current Source: Stability issues



$$H_{OL}(s) = \frac{A_0 g_{m12}(g_{o4} - g_{o3})}{(g_{ds12} + g_{o3})(g_{ds12} + g_{o4})} \cdot \frac{(1 - s/z_1)(1 + s/z_2)}{(1 + s/p'_x)(1 + s/p_y)(1 + s/p'_z)}$$


where  $p'_x = g_{m12}/(C_x + C_y)$ ,

$p'_z = g_{o4}g_{ds12}/g_{m12}C_c$ ,


$z_1 = (g_{o4} - g_{o3}) \cdot g_{m12}/C_c (g_{m12} + g_{o4})$  and

$z_2 = g_{m12}/C_x$ .
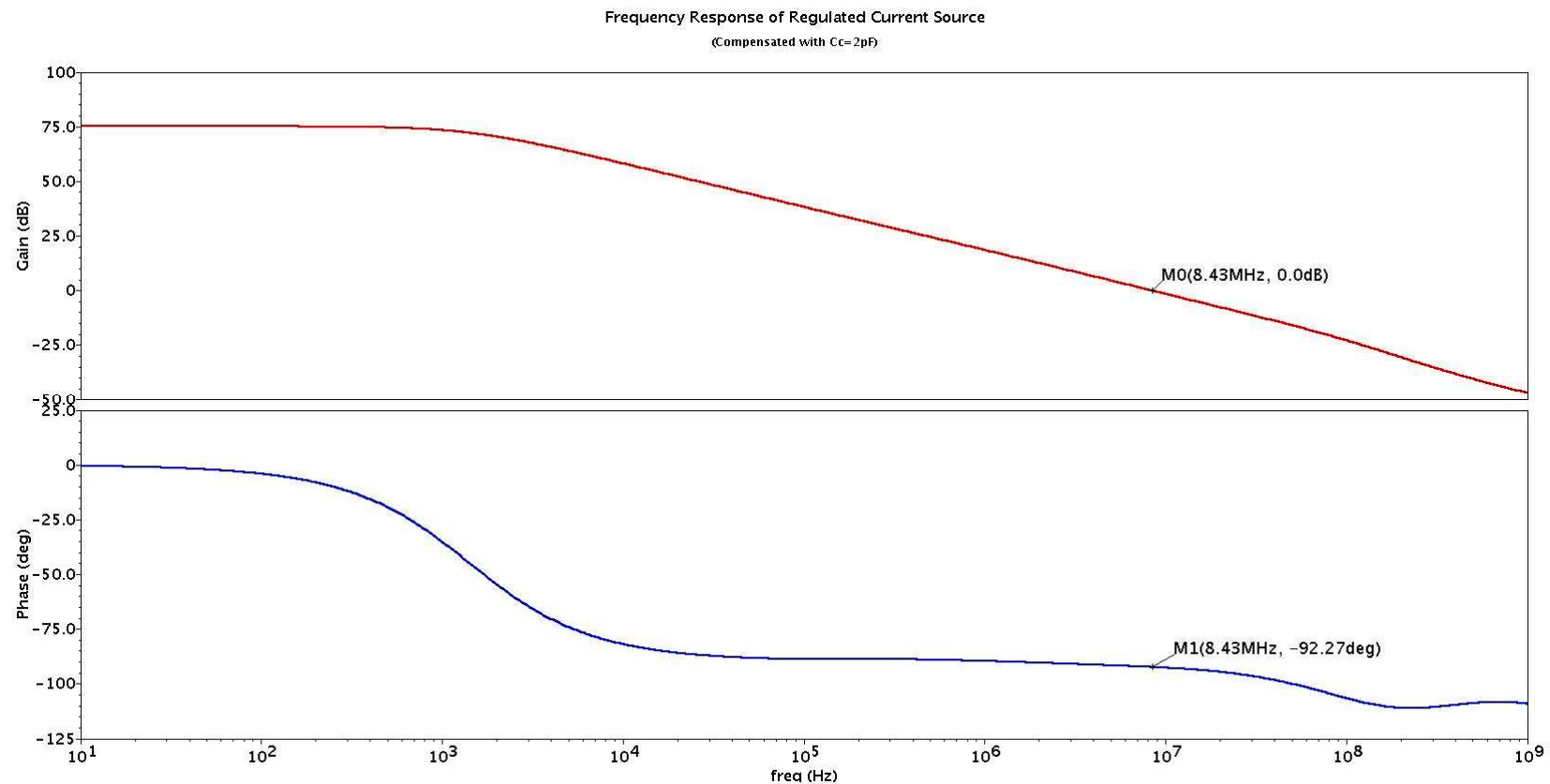
# Regulated Current Source: Stability issues



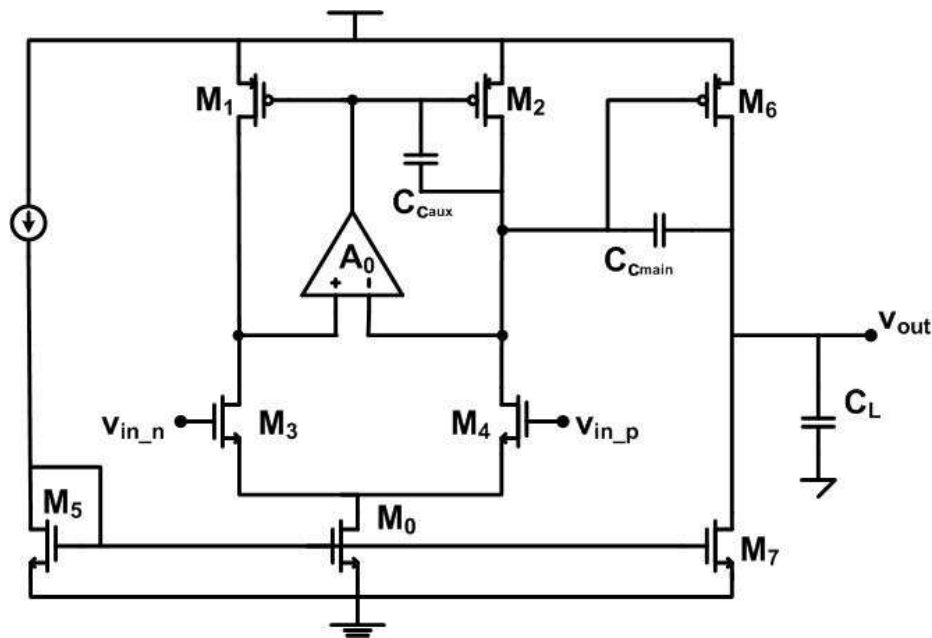
# Regulated Current Source: Stability issues





For stability:

$$p_z' \gg GBW_{main}$$
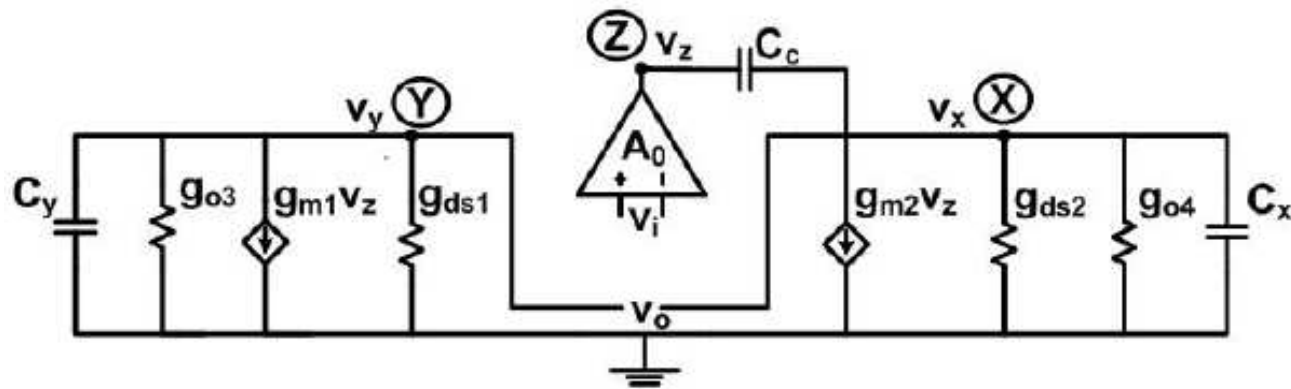
$$\frac{g_{oa}g_{ds12}}{g_{m12}C_c} \gg GBW_{main}$$


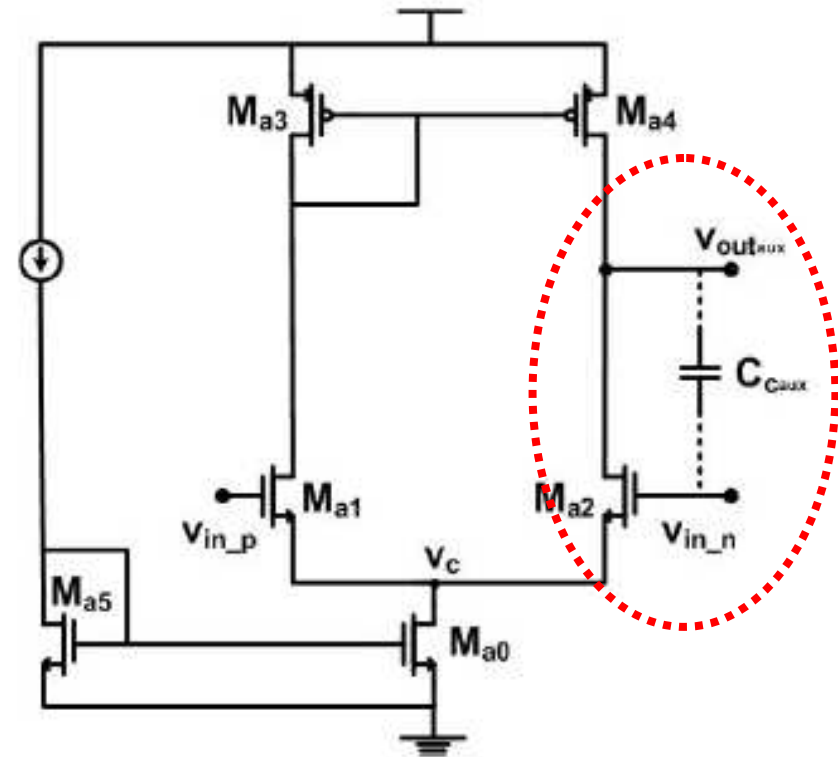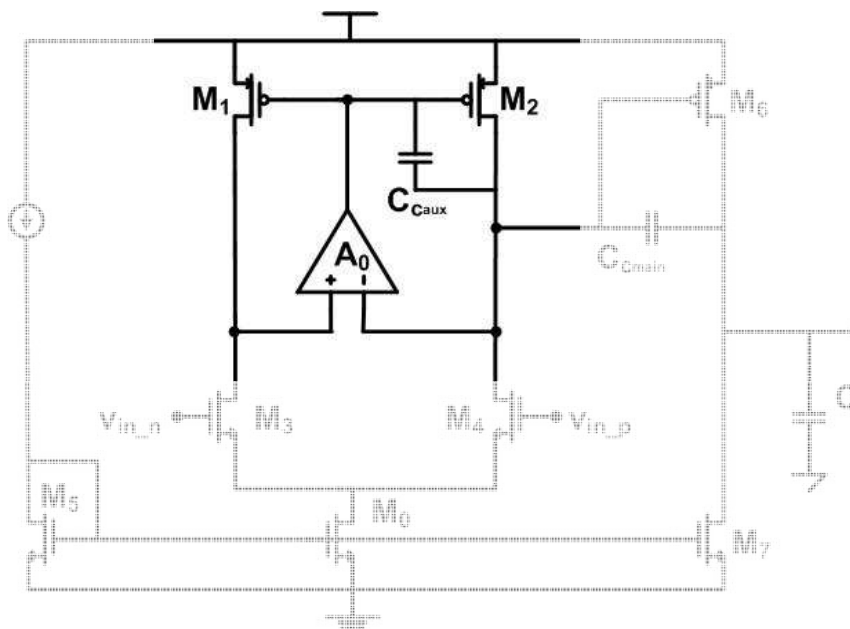
# Regulated Current Source: Stability issues



For stability:

$$\frac{g_{oa}g_{ds12}}{g_{m12}C_c} \gg GBW_{main} \quad \rightarrow \quad \frac{g_{ma12}g_{ds12}}{g_{m12}C_{caux}} \gg GBW_{main}$$


# Regulated Current Source: Stability issues

$$\frac{g_{m12}g_{ds12}}{g_{m12}C_{c_{aux}}} \gg GBW_{main}$$


$$GBW_{aux} = \frac{g_{m12}}{C_{c_{aux}}}$$

$$GBW_{aux} \geq 4 GBW_{main}$$

- Stability condition

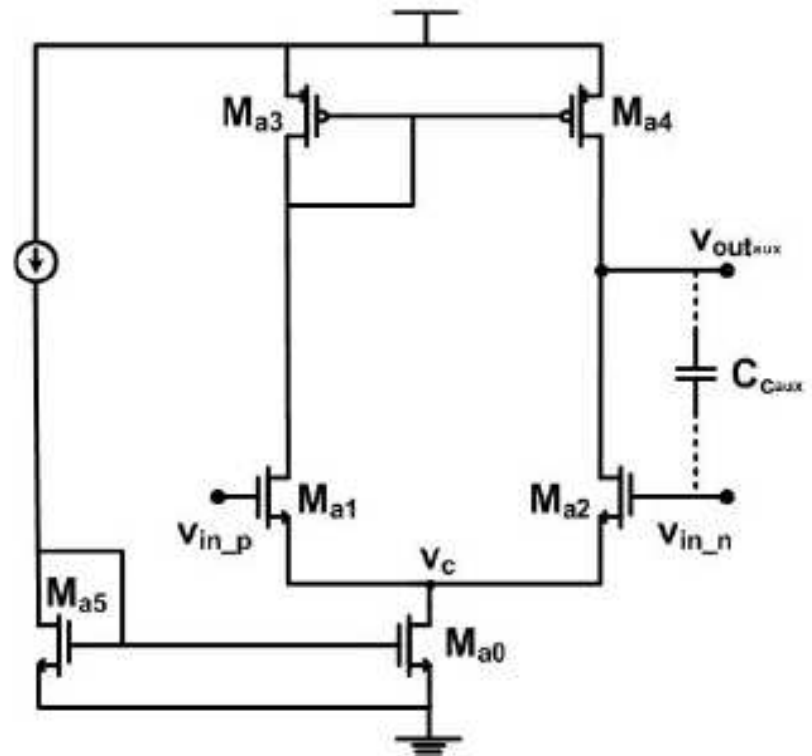

# Regulated Current Source: Gain

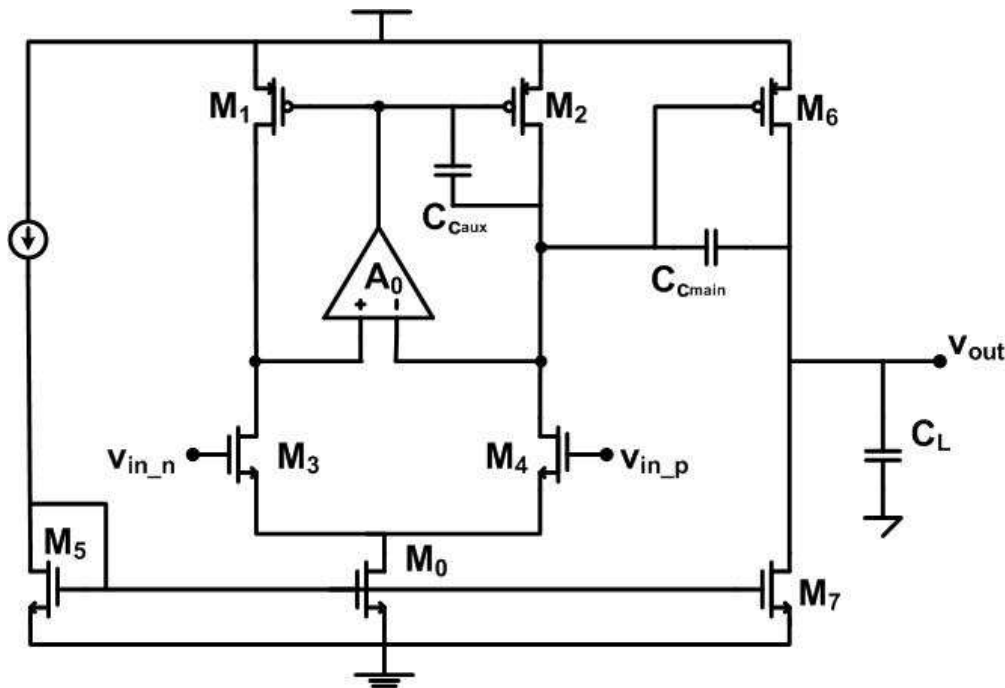

$$A_I = \frac{v_{out1}}{v_{in_{aux}}} \cdot \frac{v_{in_{aux}}}{v_{in}}$$

$$= \frac{A_0 g_{m2} g_{m34}}{(g_{ds2} + g_{ds4})^2}$$


$$A_{II} = \frac{g_{m6}}{g_{ds6} + g_{ds7}}$$

$$A_{total} = \frac{A_0 g_{m2} g_{m34}}{(g_{ds2} + g_{ds4})^2} \cdot \frac{g_{m6}}{g_{ds6} + g_{ds7}}$$

# Gain Enhancement: Options

- Modify first stage
  - Cascode: Reduced voltage headroom
  - Folded-cascode: Higher power consumption
  - Cross-coupled current mirror: Susceptible to instability
  - Regulated current source:
    - High gain
    - High dynamic
    - Can be systematically stabilized

# The Op-Amp: Design Methodology

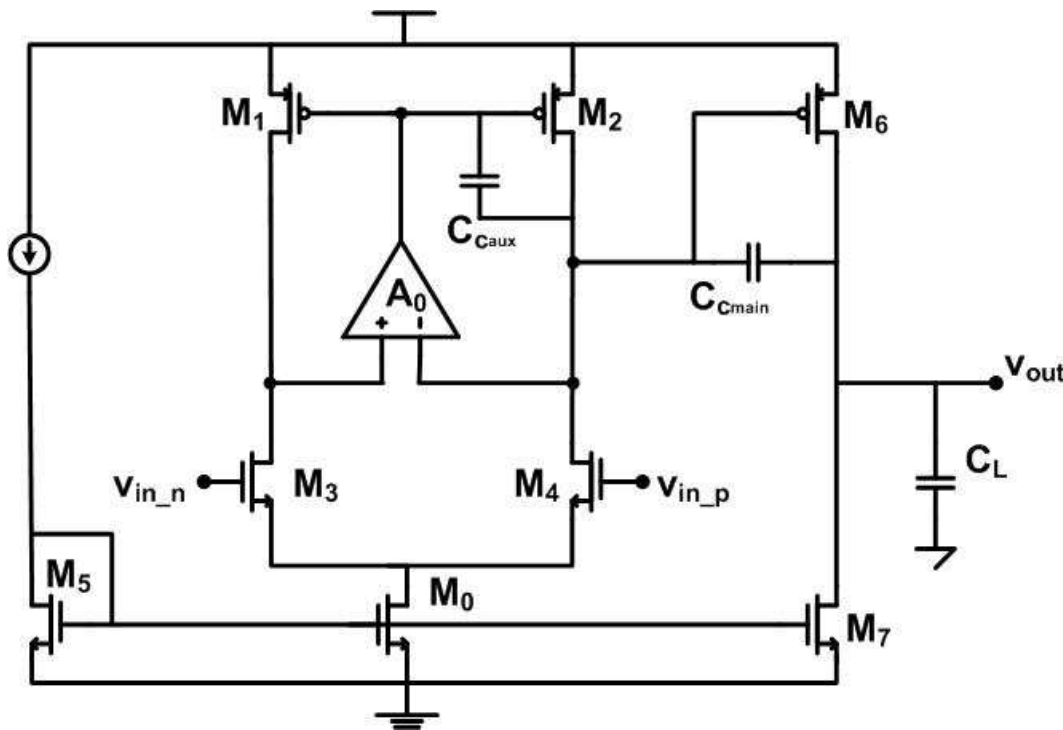

$$GBW_{total} = \frac{g_{m34}}{C_c}$$

$$\frac{g_{m6}}{g_{m34}} \geq 3 \frac{C_L}{C_c}$$

$$GBW_{aux} \geq 4 GBW_{total}$$


$$A_{total} = \frac{A_0 g_{m2} g_{m34}}{(g_{ds2} + g_{ds4})^2} \cdot \frac{g_{m6}}{g_{ds6} + g_{ds7}}$$



# The Op-Amp: Design Methodology

- Constraints
  - Gain
  - Power
  - GBW
  - Load capacitance
  - Variable power/speed
- Decisions/Discretion
  - Current allocation between stages
  - Gain allocation between stages
- Tools
  - Design equations
  - $g_m/I_D$  method


# The Op-Amp: Layout

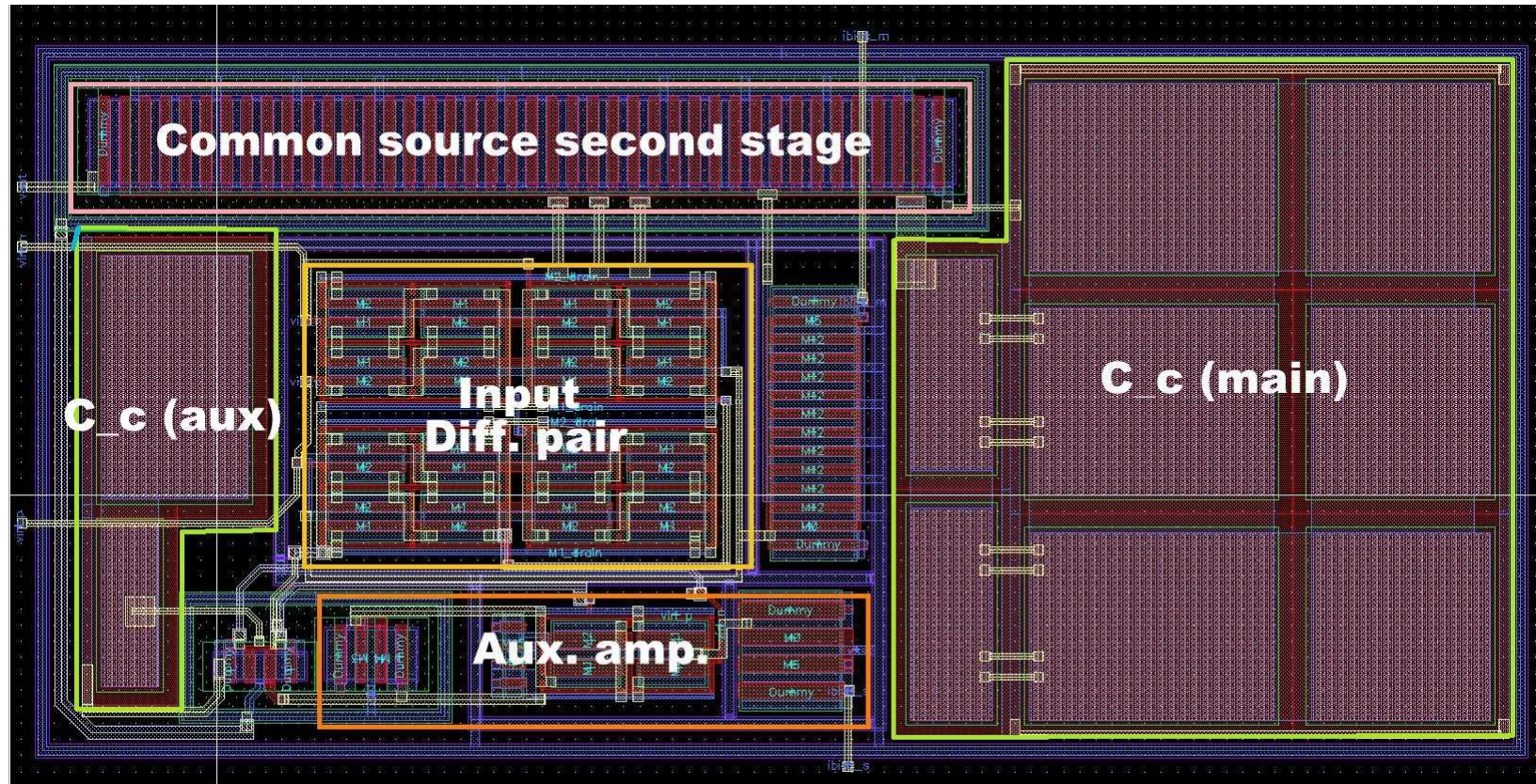


Area= 0.16 mm<sup>2</sup>
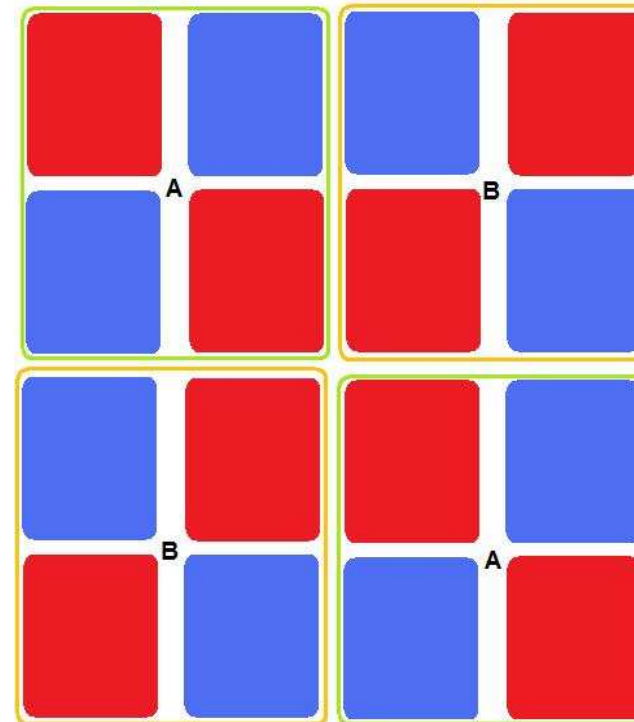
# Layout Considerations


- Large device sizes
- Minimum distance b/w devices
- Symmetrical layout
- Same orientation
- Same environment
- Multi-finger transistors
- Common-centroid layout



# Layout: PIP vs. MOSCAP

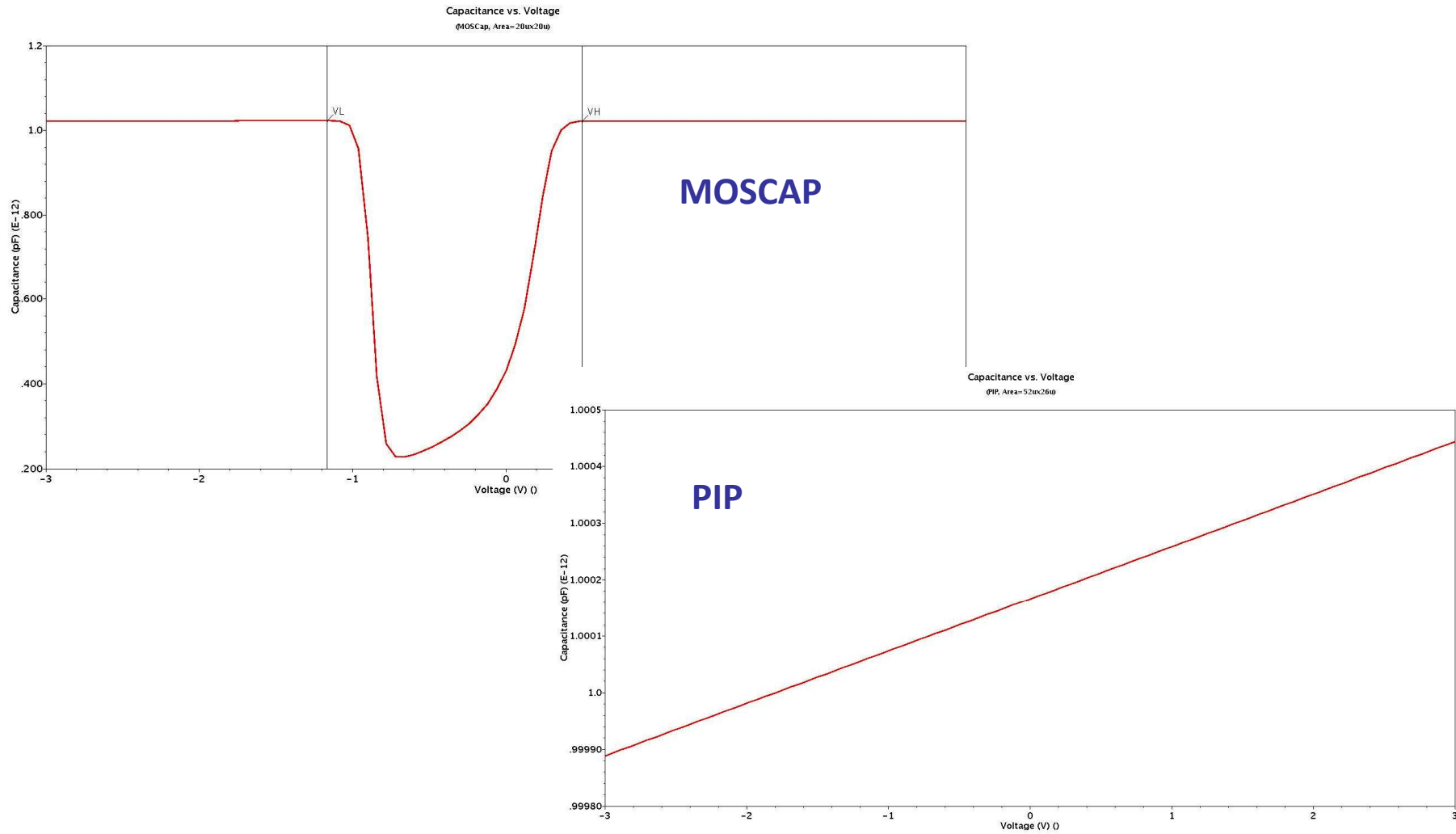


# Simulation Results: Frequency Response

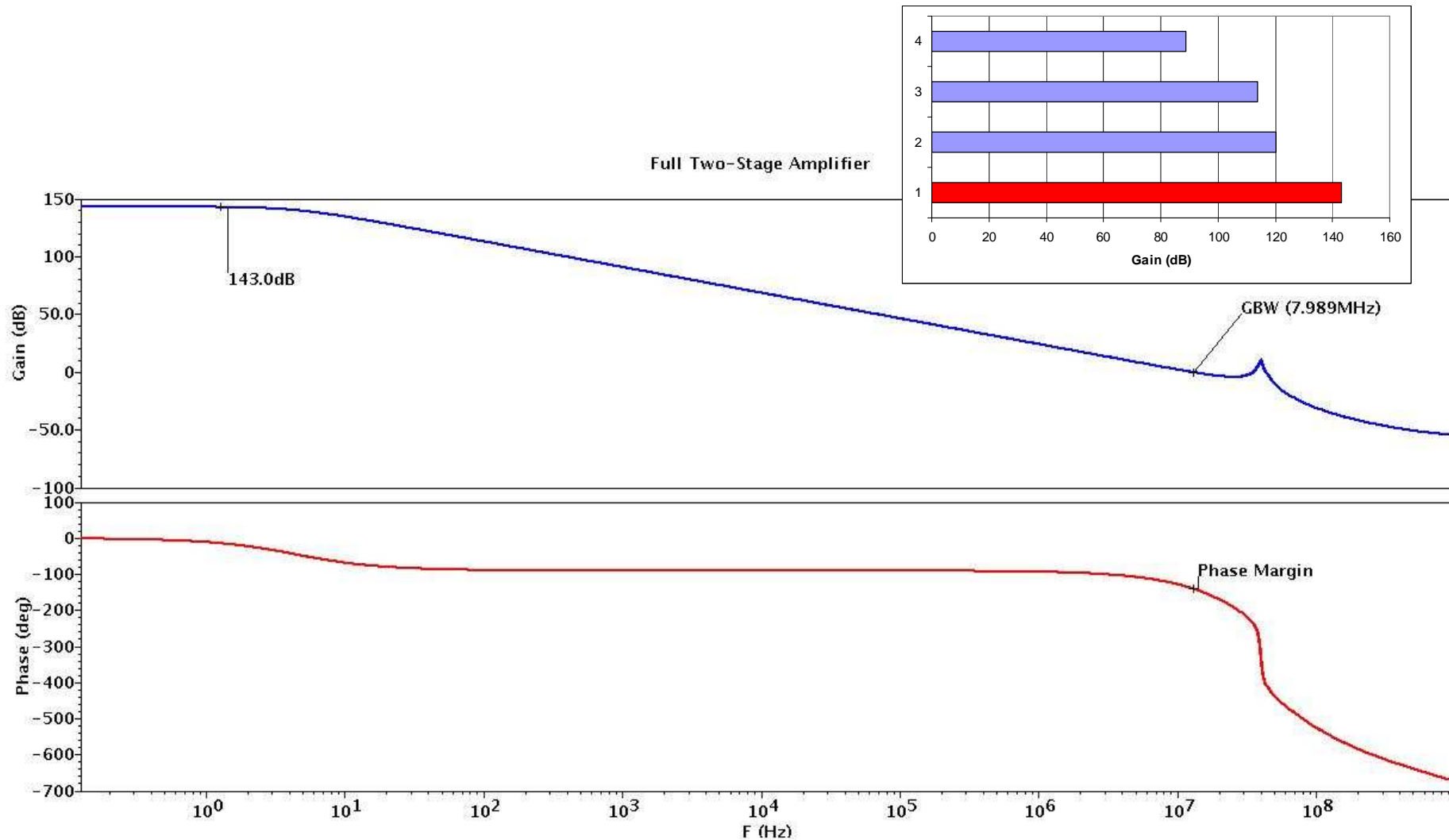


[1] This work [2] Ivanov, IEEE Trans. Ckts & Sys. 2007 [3] Zhang, IEEE APCCAS 2008 [4] Yang, IEEE Conf. on Sensors 2006

# Simulation Results: Transient Response

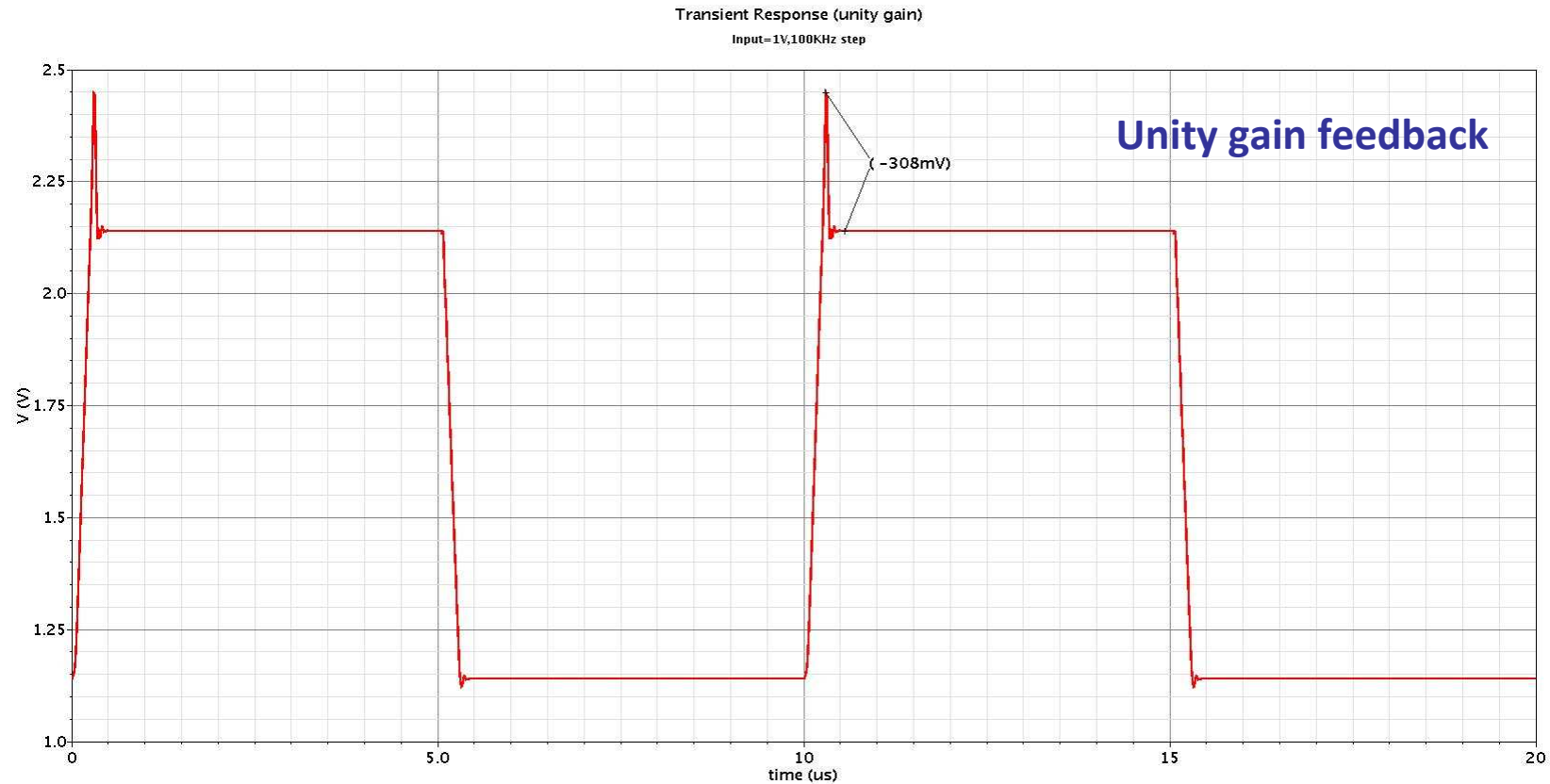


**Slew Rate = 4.90 V/us**  
**Settling time = 150 ns**

# Simulation Results: Transient Response

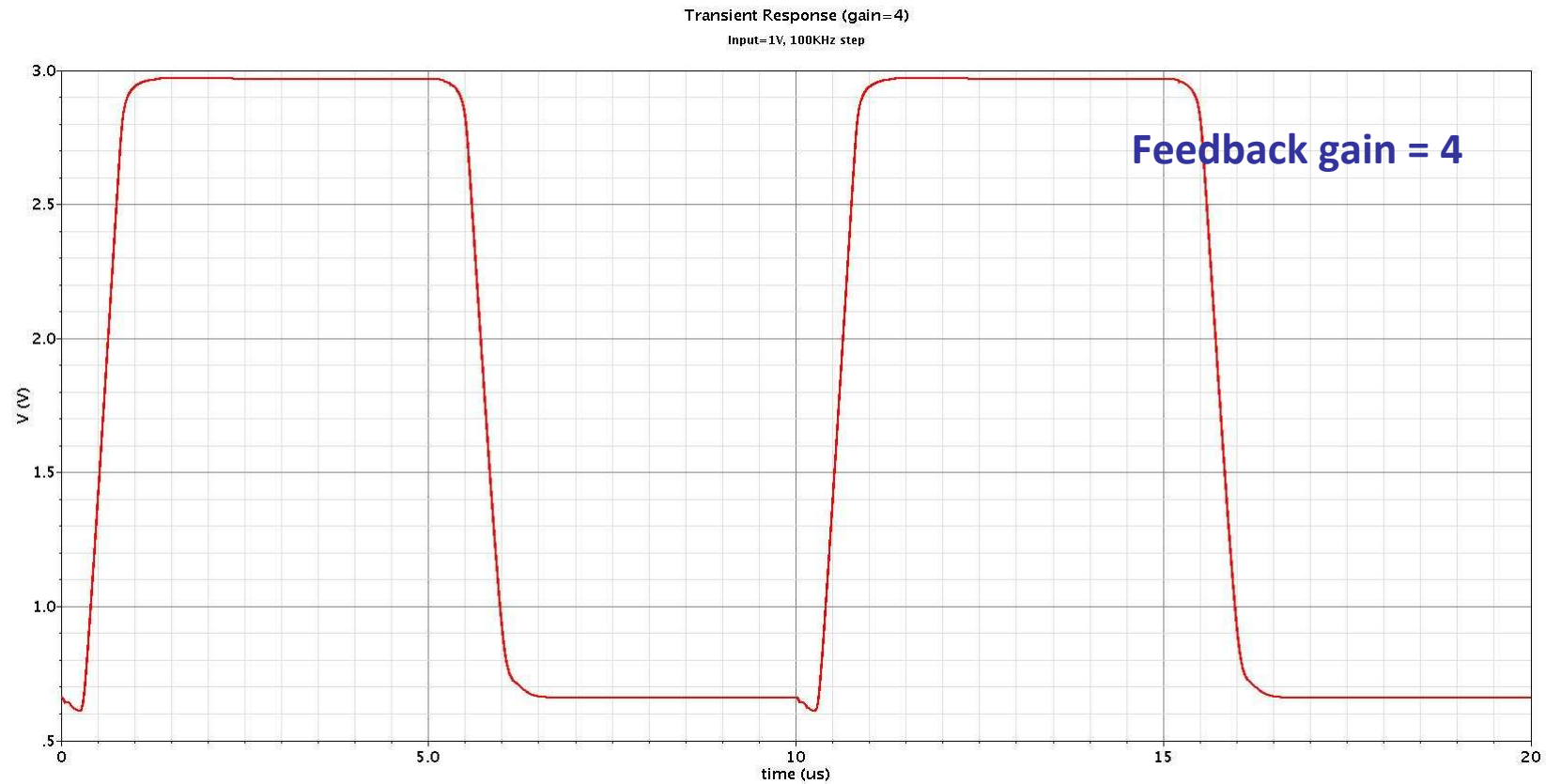


# Simulation Results: CMRR

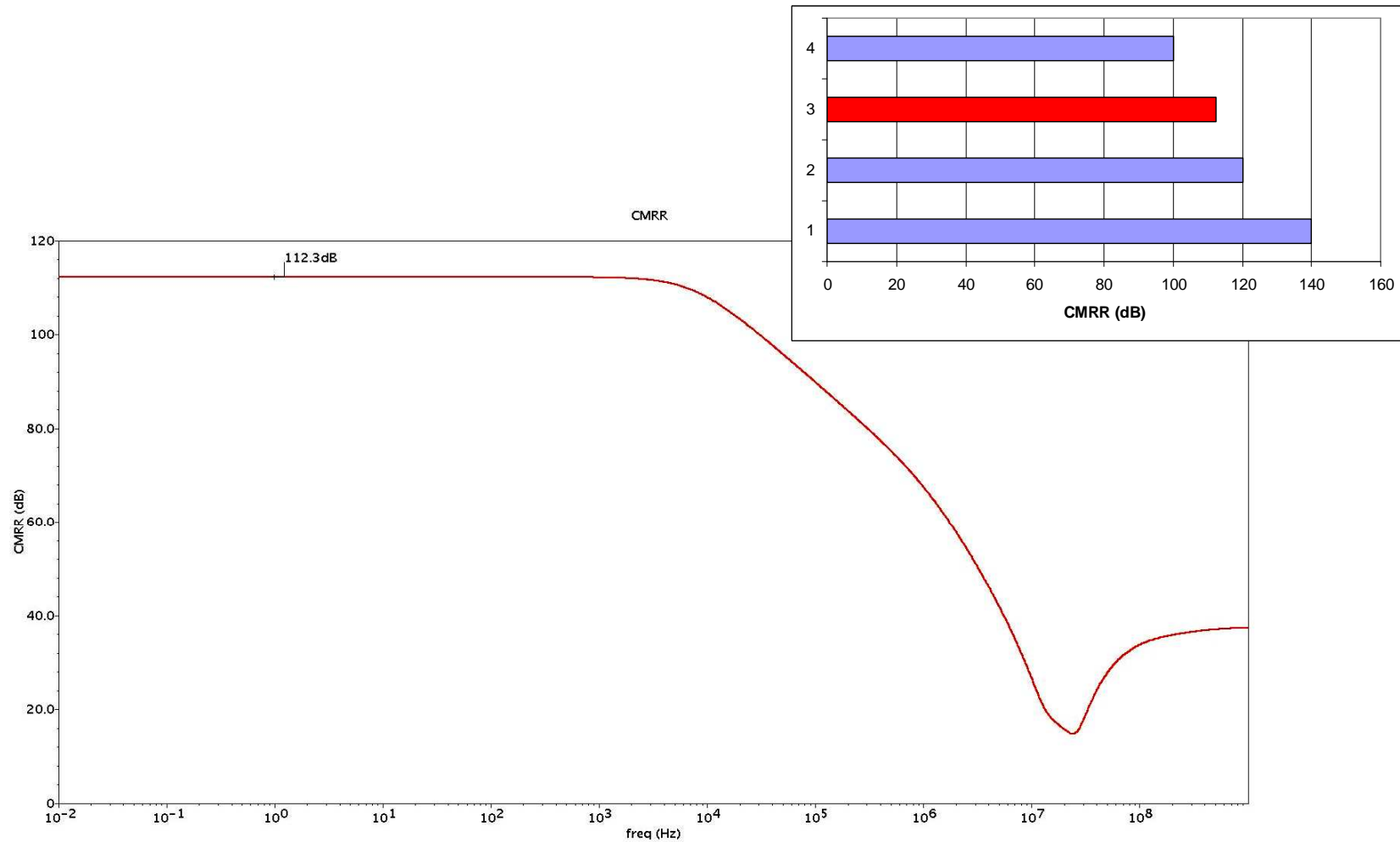

[1] Pertijs, ISSCC 2009 [2] Zhang, IEEE APCCAS 2008 [3] This work [4] Ivanov, IEEE Trans. Ckts & Sys. 2007




# Simulation Results: PSRR

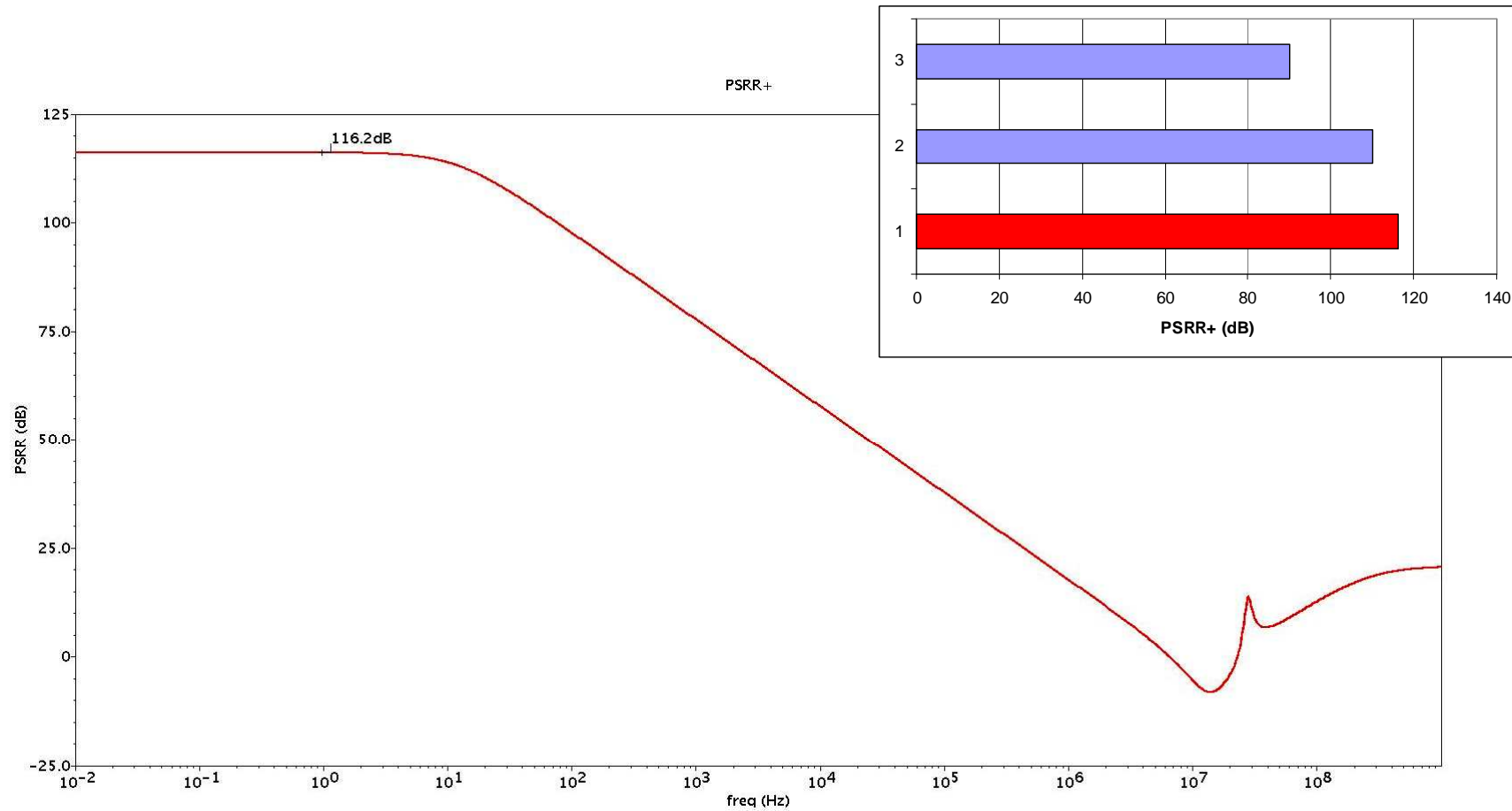


[1] This work [2] Zhang, IEEE APCCAS 2008 [3] Ivanov, IEEE Trans. Ckts & Sys. 2007

# Simulation Results: Noise

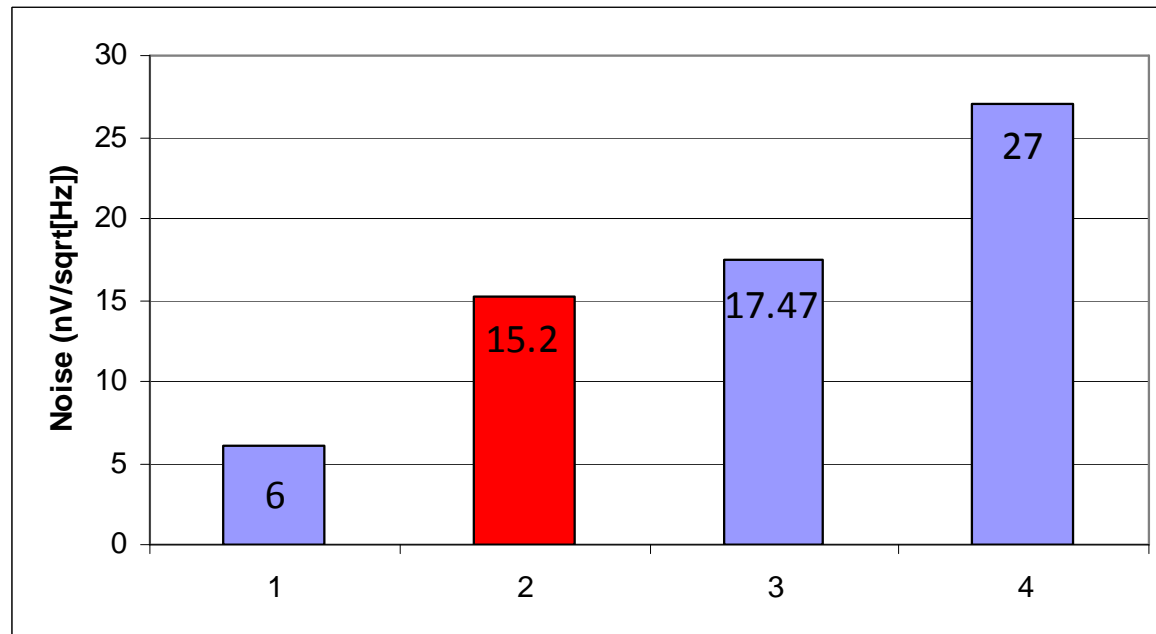


[1] Ivanov, IEEE Trans. Ckts & Sys. 2007 [2] This work [3] Zhang, IEEE APCCAS 2008 [4] Pertijs, ISSCC 2009

# Simulation Results: Power Consumption

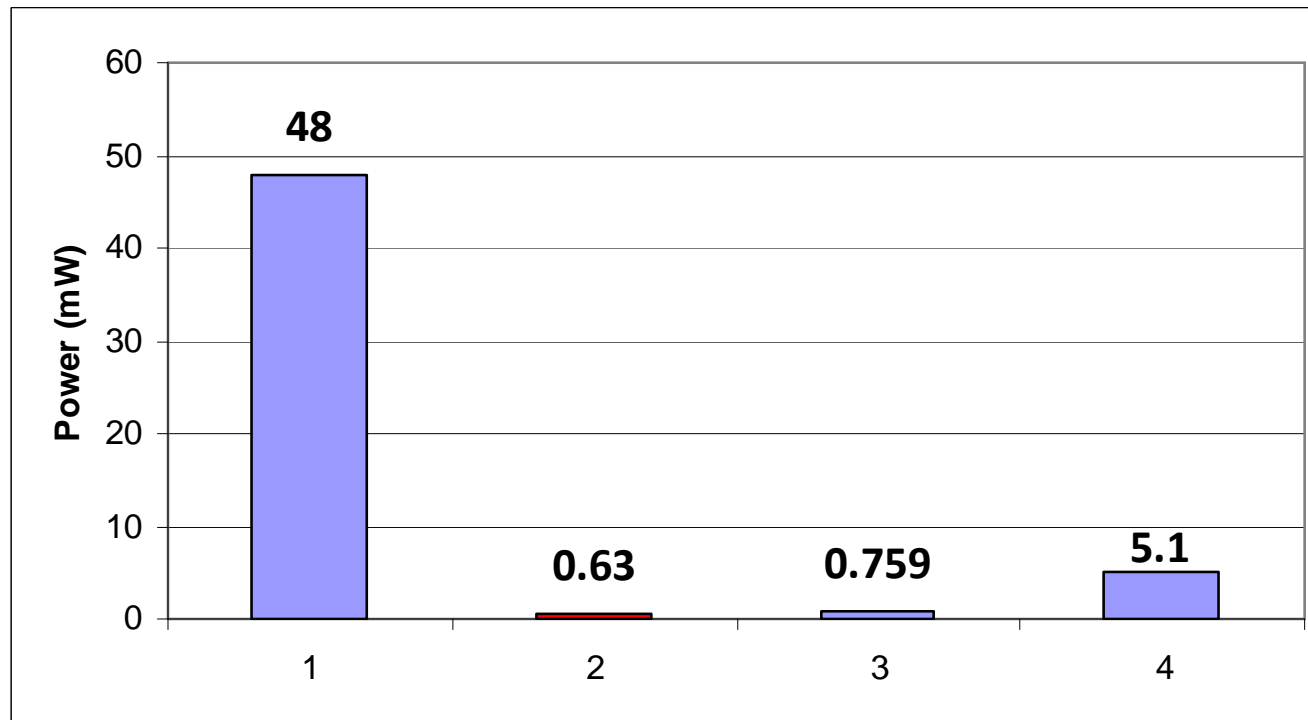

[1] Ivanov, IEEE Trans. Ckts & Sys. 2007 [2] This work [3] Zhang, IEEE APCCAS 2008 [4] Pertijs, ISSCC 2009

# Simulation Results: Low Speed Mode

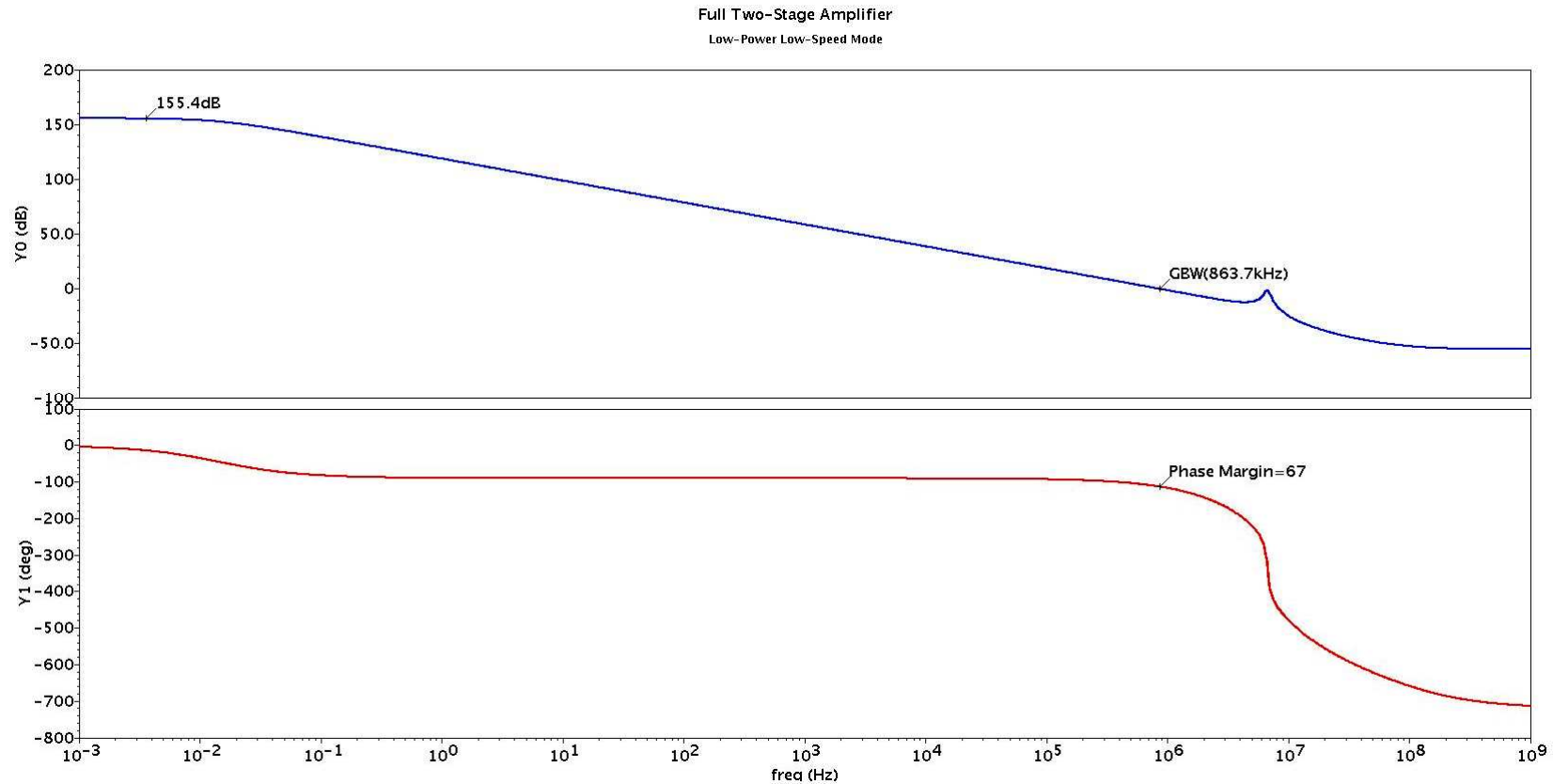

Power Consumption = 69  $\mu$ W

# Performance Summary

Parameter	High Speed	Low Speed
Supply Voltage (V)	3.0	3.0
Quiescent Current ( $\mu\text{A}$ )	210	23
DC Gain (dB)	143	155.4
GBW (MHz) (10 pF load)	7.98	0.86
Slew Rate (V/ $\mu\text{s}$ )	4.90	0.49
Settling time (ns)	150	2.7e3
Noise at 100 KHz (nV/ $\sqrt{\text{Hz}}$ )	15.2	51.7
CMRR (dB)	112.3	121.8
PRSR+ (dB)	116.2	126.1
PSRR- (dB)	121.7	130.6
Phase Margin (deg)	41	67
Output Swing (V)	2.78	2.78
Offset (mV) (100 run MC simulation)	1.95	4.37

# Achievements

- Analysis of cross-coupled current mirror load
  - Gain
  - Stability
- Analysis of regulated current source load
  - Gain
  - Stability
- Unified design methodology for two-stage op-amp with regulated current source
- Complete op-amp design