

Majority-based Synthesis for Digital Nano-Technologies

Giovanni De Micheli



Outline


- **Introduction**
- **Technological innovations and motivation**
 - Emerging nanotechnologies and devices
- Design with emerging technologies
 - Physical and logic synthesis
- The majority paradigm in logic synthesis
 - Models, algorithms and tools
- Conclusions

The emerging nano-technologies


- *Enhanced* silicon CMOS is likely to remain the main manufacturing process in the medium term
 - The 10 and 7nm technology nodes are planned
- What are the candidate technologies for the 5nm node and beyond?
 - Silicon Nanowires (SiNW)
 - Tunneling FETs (TFET)
 - Carbon Nanotubes (CNT)
 - 2D devices (flatronics)
- What are the common denominators from a design standpoint?

22 nm Tri-Gate Transistors

32 nm Planar Transistors

 


22 nm Tri-Gate Transistors

 


[Courtesy: M. Bohr]

FinFETs versus SiNW FETs

 


Double gate SiNW FET

 

- *Electrostatic doping*
- **Electrically program** the transistor to either **p-type** or **n-type**

Silicon Nanowire Transistors

 
- Gate all around transistors
- Double gate to control polarity



(c) Giovanni De Micheli

[Courtesy: De Marchi, EPFL] 7


Device I_d/V_{cg}

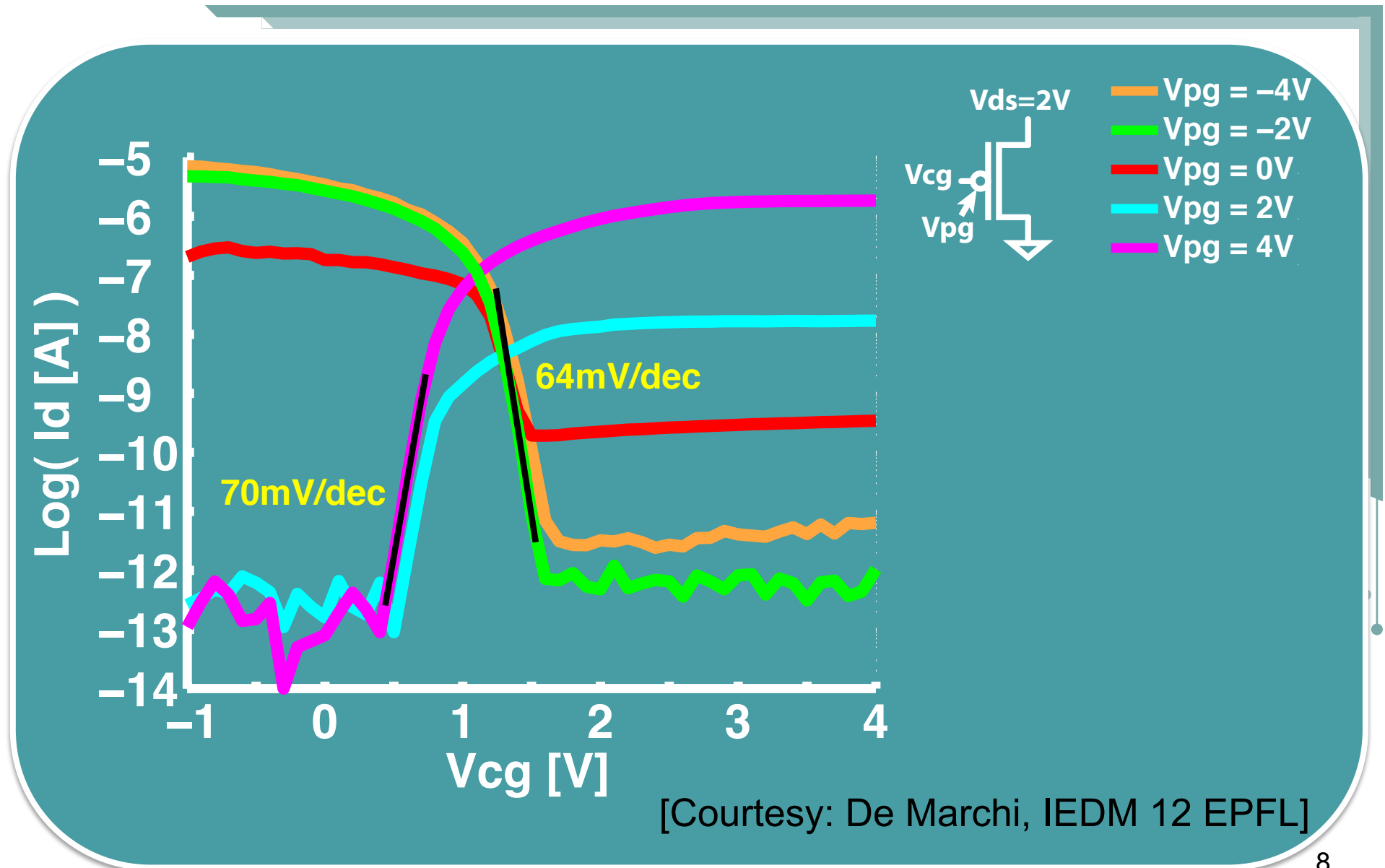

Logic level abstraction

- Three terminal transistors are switches
 - A loaded transistor is an *inverter*
- Controllable-polarity transistors compare two values
 - A loaded transistor is an *exclusive or* (EXOR)
- The intrinsic higher computational expressiveness leads to more efficient data-path design
- The larger number of terminals must be compensated by smart wiring

Modeling various emerging nanogates

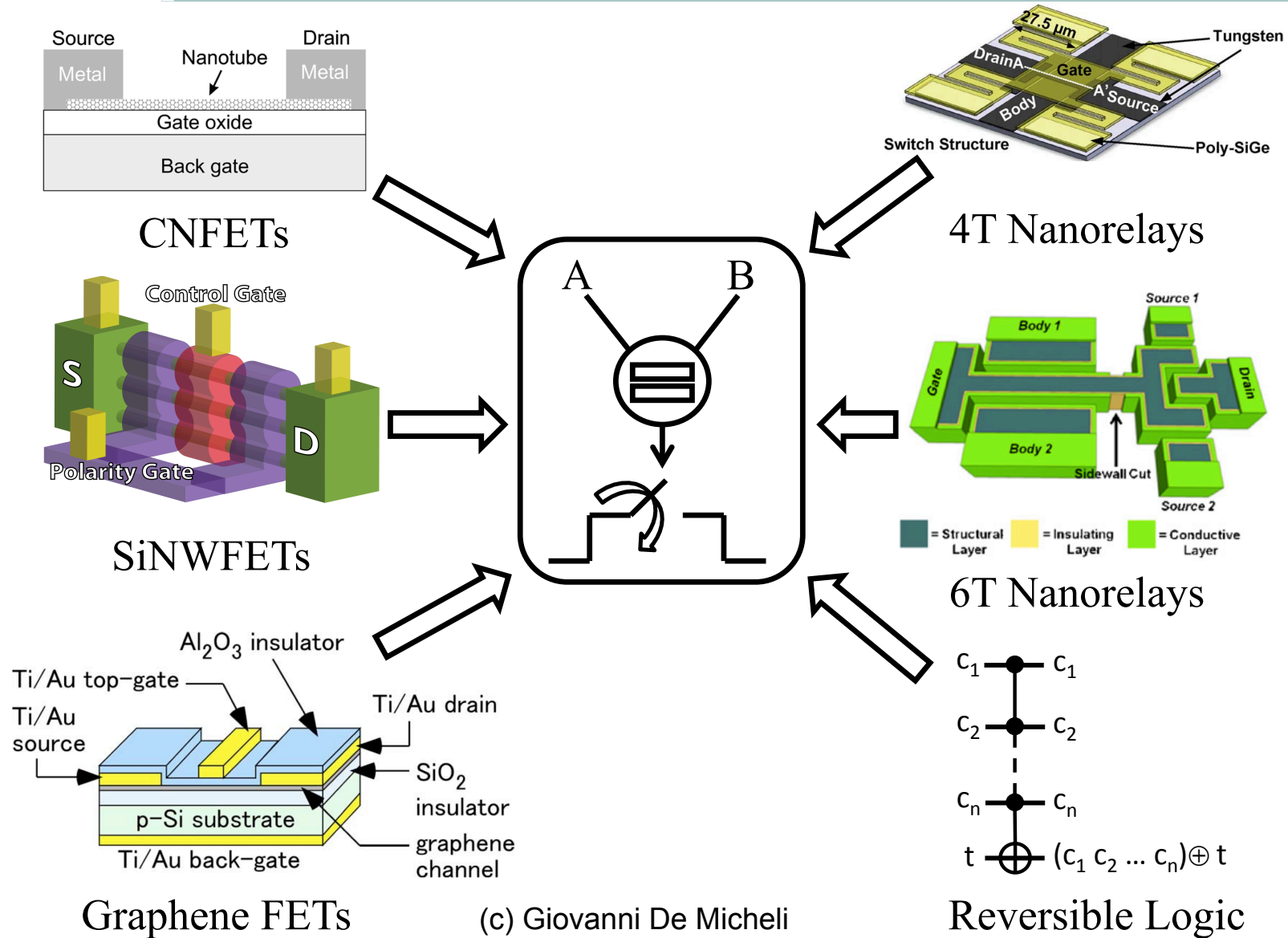



Outline

- Introduction
- Technological innovations and motivation
 - Emerging nanotechnologies and devices
- **Design with emerging technologies**
 - **Physical and logic synthesis**
- The majority paradigm in logic synthesis
 - Models, algorithms and tools
- Conclusions

Logic cell design


- CMOS complementary logic is efficient only for negative-unate functions (INV, NAND, NOR...etc)
- Controllable-polarity logic is efficient for all functions
- Best for XOR-dominated circuits (binate functions)

Negative Unate functions

  

Similar to regular CMOS


Binate functions

 


Only 4 transistors when compared to 8 transistors with a regular CMOS

Physical design



 
- Sea of Tiles: Homogeneous array of Tiles



Dumbbell-stick diagrams

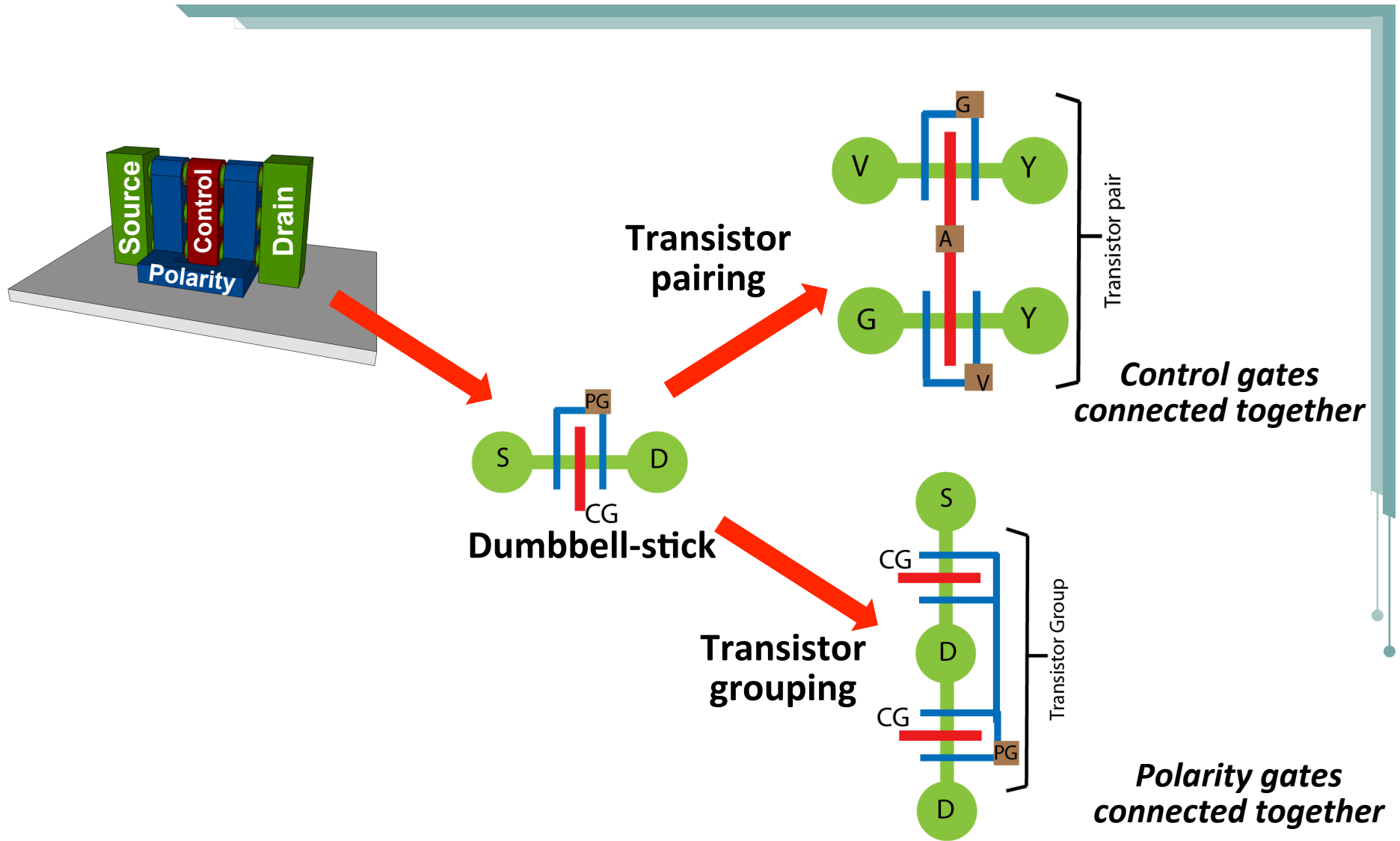

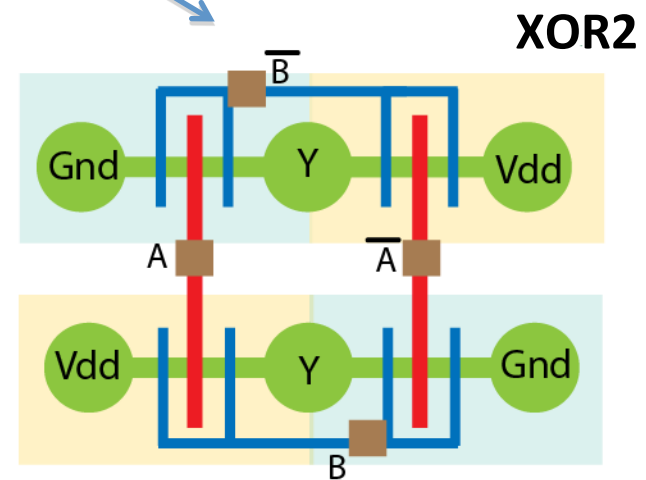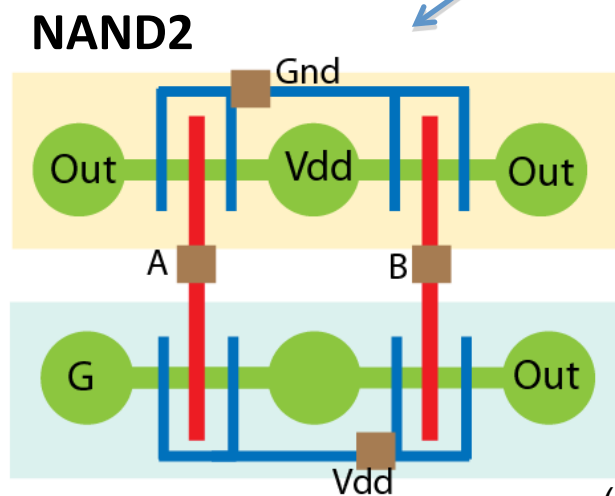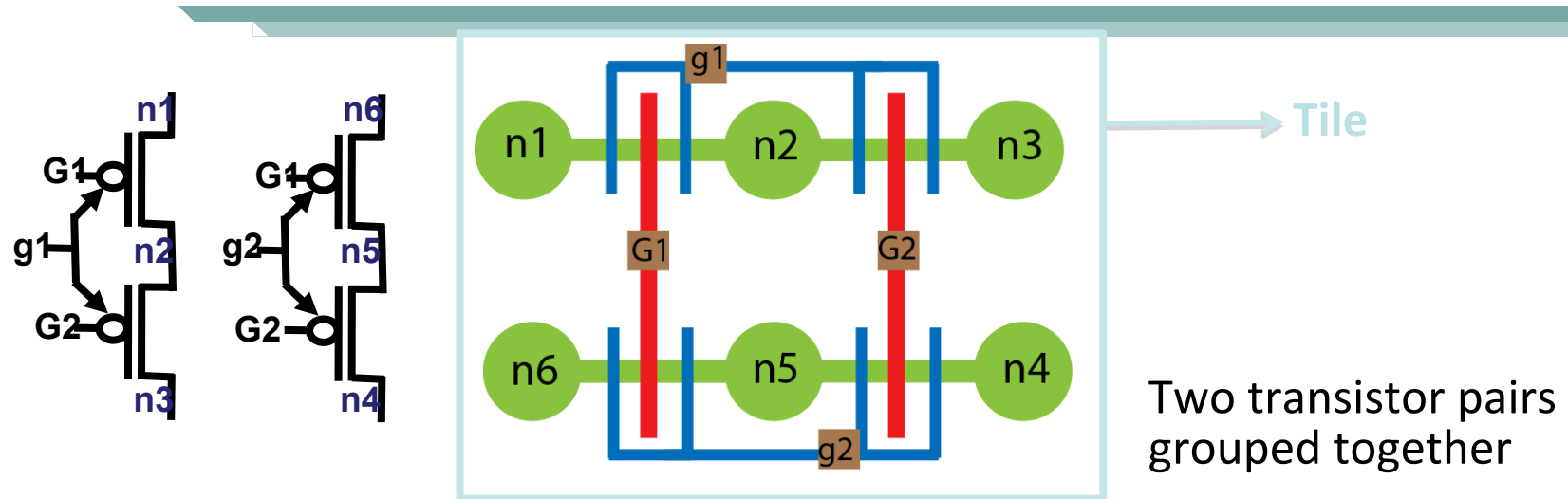Layout abstraction and regularity with *Tiles*




(c) Giovanni De Micheli

[Courtesy: Bobba, DAC 12]

Biconditional Binary Decision Diagrams

- Native **canonical** data structure for logic design
- *Biconditional* expansion:

 
$$f(v, w, \dots, z) = (v \oplus w) f(w', w, \dots, z) + (v \oplus \bar{w}) f(w, w, \dots, z)$$



- Each BBDD node:
 - Has two branching variables
 - Implements the *biconditional* expansion
 - Reduces to Shannon's expansion for single-input functions


BBDD: Examples

 a) $f = a \oplus b \oplus c \oplus d \oplus e \oplus g$




$\pi = (a, b, c, d, e, g)$

 b) $f = ab + (a \oplus b)(c \bar{\oplus} d)$




$\pi = (a, b, c, d)$

c) $f = ab + bc + ac$

 

$\pi = (a, b, c)$

d) $f = (a \bar{\oplus} b)(b + c)$

 


$\pi = (a, b, c)$

- The BDD counterparts for these examples have about 50% more nodes!


Why BBDDs ?

- BBDDs are the representation of choice for controllable-polarity devices
 - Direct mapping to transistor structures
- BBDDs are very effective for standard CMOS, especially for design of arithmetic circuits
- BBDDs are proven to be more compact for:
 - Adders:
 - BBDD best size: $3n + 1$
 - BDD best size: $5n + 2$
 - Majority:
 - BBDD size: $0.25 (n^2 + 7)$
 - BDD size: $\lceil 0.5n \rceil (n - \lceil 0.5n \rceil + 1) + 1$

Efficient Direct Mapping of BBDD Nodes

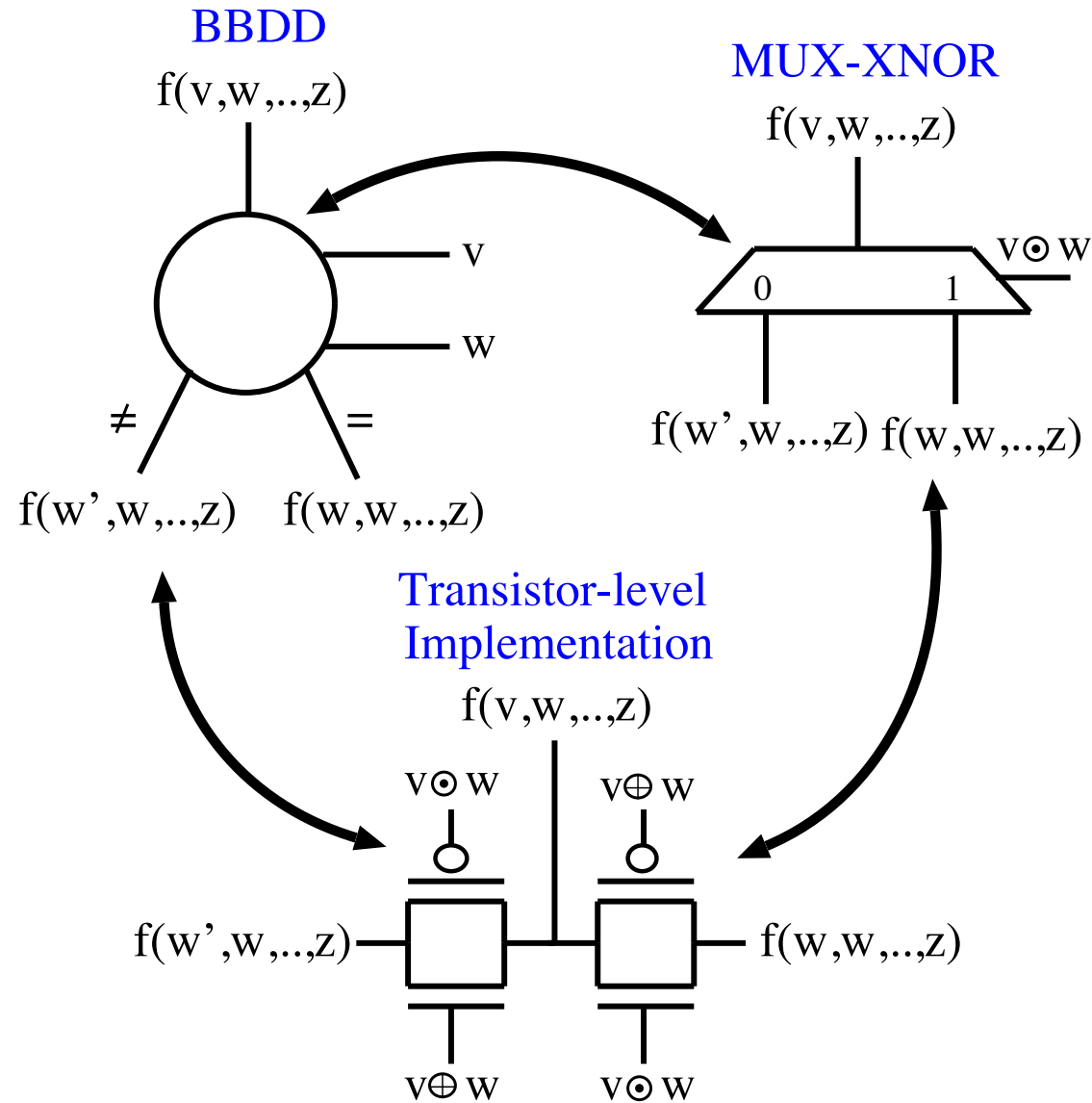

BBDDs are Compact (Majority Function)

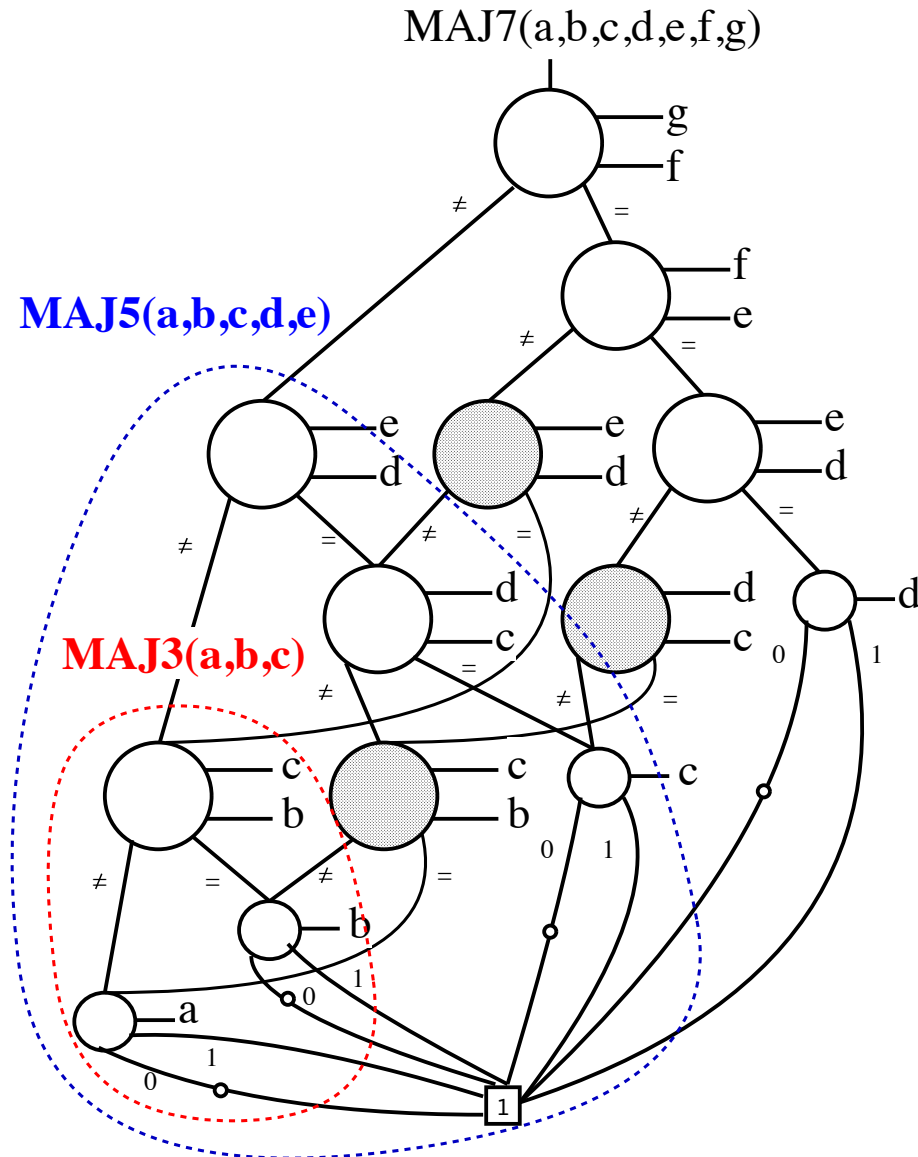

Number of nodes
of MAJ(n):

$$0.25(n^2 + 7)$$

MAJ(3): 4 (including sink)

MAJ(5): 8 (including sink)


MAJ(7): 14 (including sink)

....

The BBDD optimization tool


- Unique table to store BBDD nodes
- Recursive formulation of Boolean operations
- Performance-oriented memory management
- Chain variable reordering

<http://lsi.epfl.ch/BBDD>

 

Experimental results

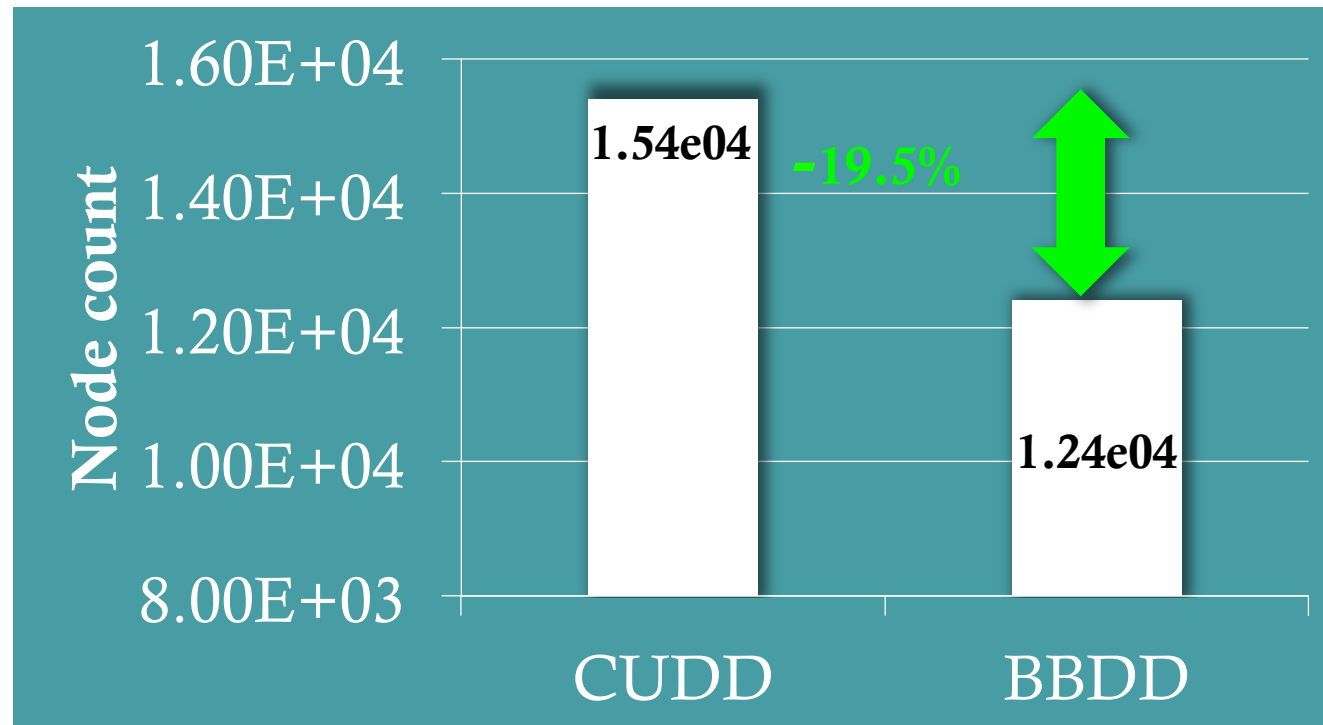- We implemented a BBDD package in C language
 - Comparison with CUDD (BDD)
- Both CUDD and BBDD first build the DDs and then apply sifting (no dynamic reordering)




Also **1.63x** speedup for arithmetic intensive circuits

Outline

- Introduction
- Technological innovations and motivation
 - Emerging nanotechnologies and devices
- Design with emerging technologies
 - Physical and logic synthesis
- **The majority paradigm in logic synthesis**
 - **Models, algorithms and tools**
- Conclusions

Why Majority Logic?

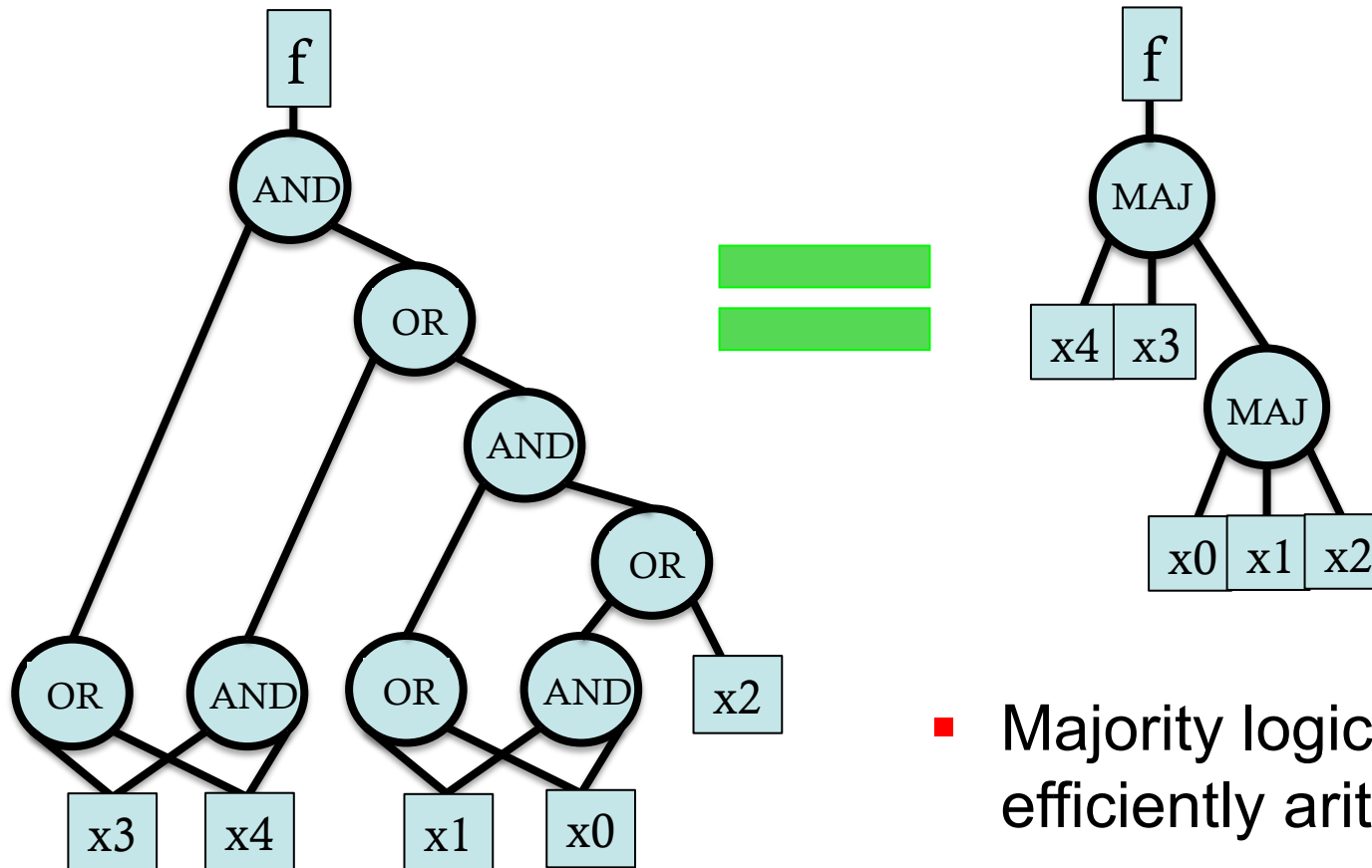- Majority logic is a powerful generalization of AND/ORs
 - $\text{MAJ}(a,b,c)=ab+ac+bc$. $\text{MAJ}(a,b,1)=a+b$. $\text{MAJ}(a,b,0)=ab$.
- Unlocks optimization opportunities not apparent before



- Majority logic handles efficiently arithmetic circuits

Synthesis Motivation for Majority

MCNC.GENLIB + MIN3

```

module ANDOR (
  x0, x1, x2, x3, x4,
  z0 );
input x0, x1, x2, x3, x4;
output z0;
wire n6, n7, n8, n9, n10, n11;
  nor2 g0(.a(x4), .b(x3), .O(n6));
  nand2 g1(.a(x4), .b(x3), .O(n7));
  inv1 g2(.a(n7), .O(n8));
  inv1 g3(.a(x0), .O(n9));
  nand2 g4(.a(n9), .b(n8), .O(n10));
  inv1 g5(.a(x2), .O(n11));
  nand2 g6(.a(x1), .b(x0), .O(n12));
  nand2 g7(.a(n12), .b(n11), .O(n13));
  nand2 g8(.a(n13), .b(n10), .O(n14));
  aoi21 g9(.a(n14), .b(n7), .c(n6), .O(z0));
endmodule

```

Area=18 Delay=4.60

```

module MAJ (
  x0, x1, x2, x3, x4,
  z0 );
input x0, x1, x2, x3, x4;
output z0;
wire n6, n7, n8, n9, n10, n11;
  inv1 g1(.a(x3), .O(n6));
  inv1 g2(.a(x4), .O(n7));
  min3 g3(.a(x2), .b(x1), .c(x0), .O(n8));
  min3 g4(.a(n8), .b(n7), .c(n6), .O(z0));
endmodule
module MAJ2 (
  x0, x1, x2, x3, x4,
  z0 );
  nand2 g5(.a(x4), .b(x3), .O(n11));
  nand2 g6(.a(n11), .b(n10), .O(z0));
endmodule

```

Area=12 Delay=3.20

Area ↓ Delay =

Area ↓ Delay ↓

How to Exploit Majority Logic?

We want good and scalable methods for manipulating MAJ

State-of-the-art


- AND-OR Inverter Graphs (AOIGs)
- Use traditional Boolean algebra axioms and theorems to manipulate & optimize AOIGs

For majority

- Majority Inverter Graphs (MIGs)
- New Boolean algebra to deal natively with majority and inverters


Majority-Inverter Graph

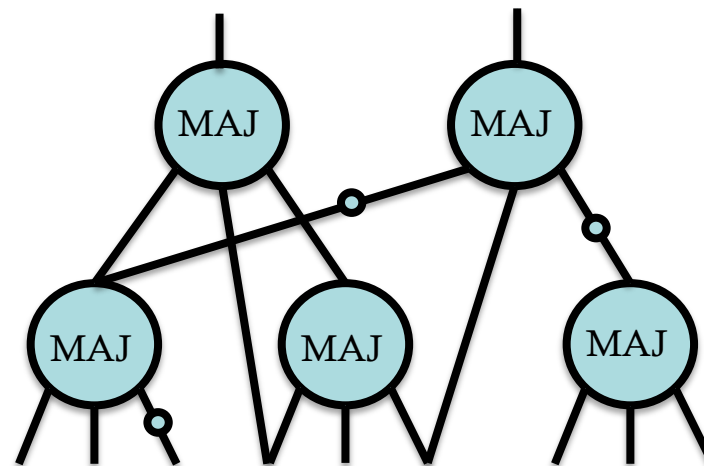Definition: An MIG is a logic network consisting of 3-input majority nodes and regular/complemented edges



MIG Properties

AOIGs → MIGs

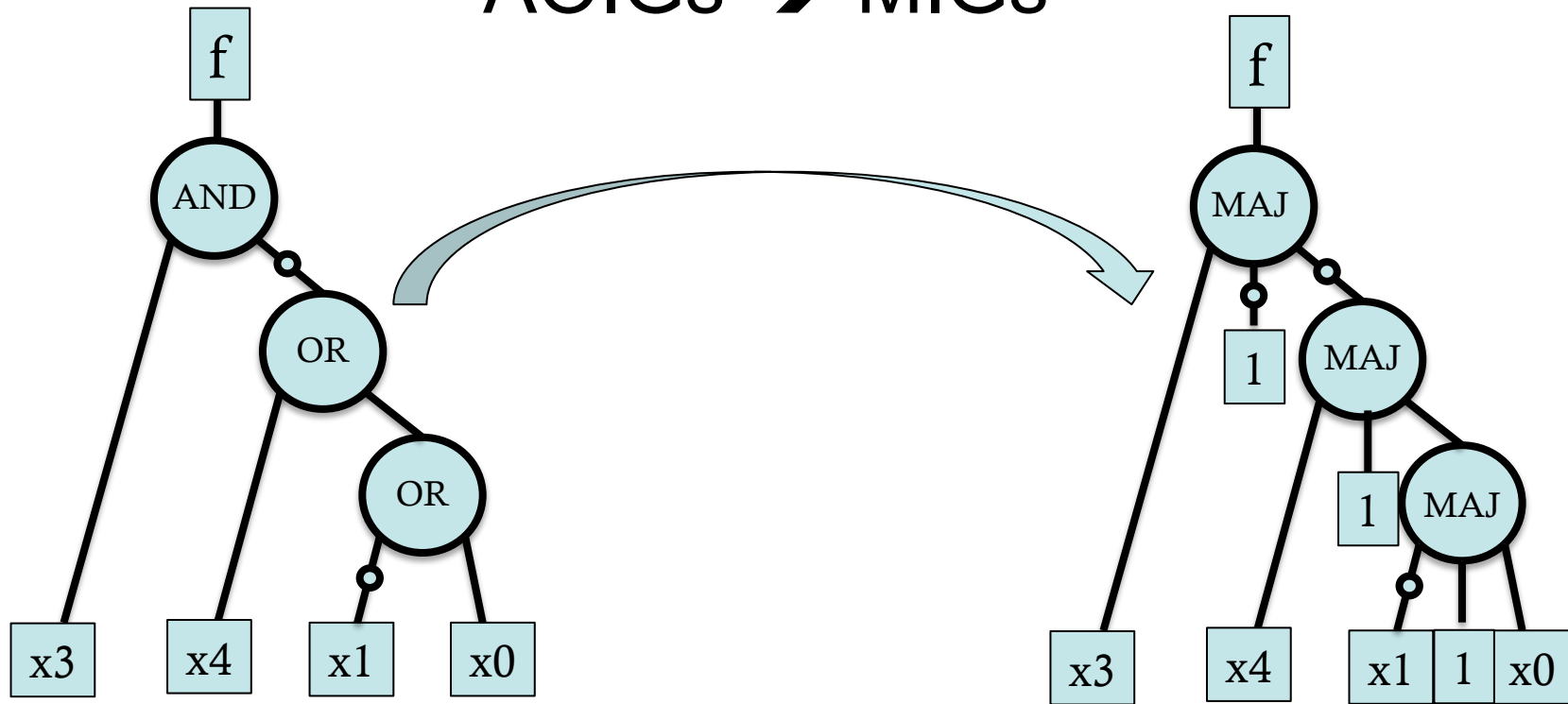

MIGs **include** AOIGs **include** AIGs


Manipulating MIGs: MIG Boolean Algebra

- Ω {
- 1- **Commutativity**: $M(x, y, z) = M(y, x, z) = M(z, y, x)$
 - 2- **Majority**: $\text{if}(x = y), M(x, y, z) = x = y$
 $\text{if}(x = y'), M(x, y, z) = z$
 - 3- **Associativity**: $M(x, u, M(y, u, z)) = M(z, u, M(y, u, x))$
 - 4- **Distributivity**: $M(x, y, M(u, v, z)) = M(M(x, y, u), M(x, y, v), z)$
 - 5- **Inverter Propagation**: $M'(x, y, z) = M(x', y', z')$

Theorem: $(B, M, ', 0, 1)$ subject to axioms in Ω is a Boolean algebra


MIG Boolean Algebra

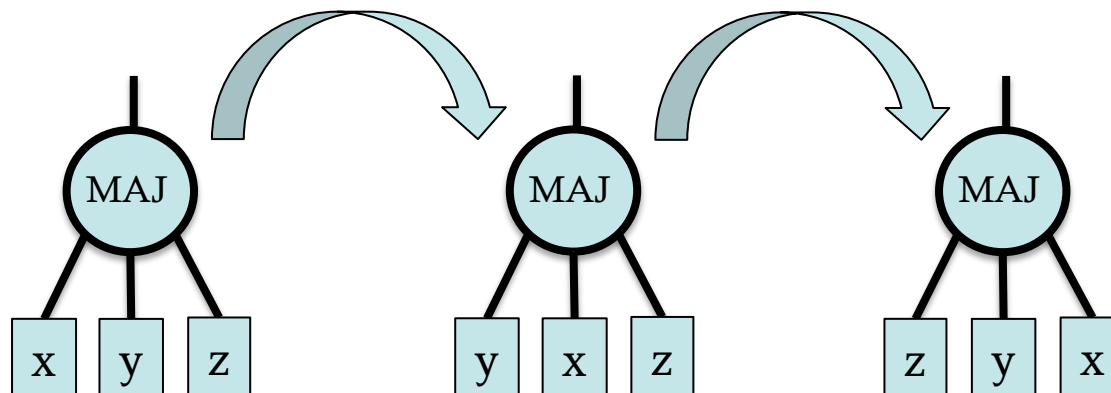- 1- **Commutativity:** $M(x, y, z) = M(y, x, z) = M(z, y, x)$
- 2- Majority: $\text{if}(x = y), M(x, y, z) = x = y$
 $\text{if}(x = y'), M(x, y, z) = z$
- 3- Associativity: $M(x, u, M(y, u, z)) = M(z, u, M(y, u, x))$
- 4- Distributivity: $M(x, y, M(u, v, z)) = M(M(x, y, u), M(x, y, v), z)$
- 5- Inverter Propagation: $M'(x, y, z) = M(x', y', z')$




MIG Boolean Algebra

 - 1- Commutativity: $M(x, y, z) = M(y, x, z) = M(z, y, x)$
- 2- **Majority**: $\text{if}(x = y), M(x, y, z) = x = y$
 $\text{if}(x = y'), M(x, y, z) = z$
- 3- Associativity: $M(x, u, M(y, u, z)) = M(z, u, M(y, u, x))$
- 4- Distributivity: $M(x, y, M(u, v, z)) = M(M(x, y, u), M(x, y, v), z)$
- 5- Inverter Propagation: $M'(x, y, z) = M(x', y', z')$




MIG Boolean Algebra

 - 1- Commutativity: $M(x, y, z) = M(y, x, z) = M(z, y, x)$
- 2- Majority: $\text{if}(x = y), M(x, y, z) = x = y$
 $\text{if}(x = y'), M(x, y, z) = z$
- 3- **Associativity**: $M(x, u, M(y, u, z)) = M(z, u, M(y, u, x))$
- 4- Distributivity: $M(x, y, M(u, v, z)) = M(M(x, y, u), M(x, y, v), z)$
- 5- Inverter Propagation: $M'(x, y, z) = M(x', y', z')$




MIG Boolean Algebra

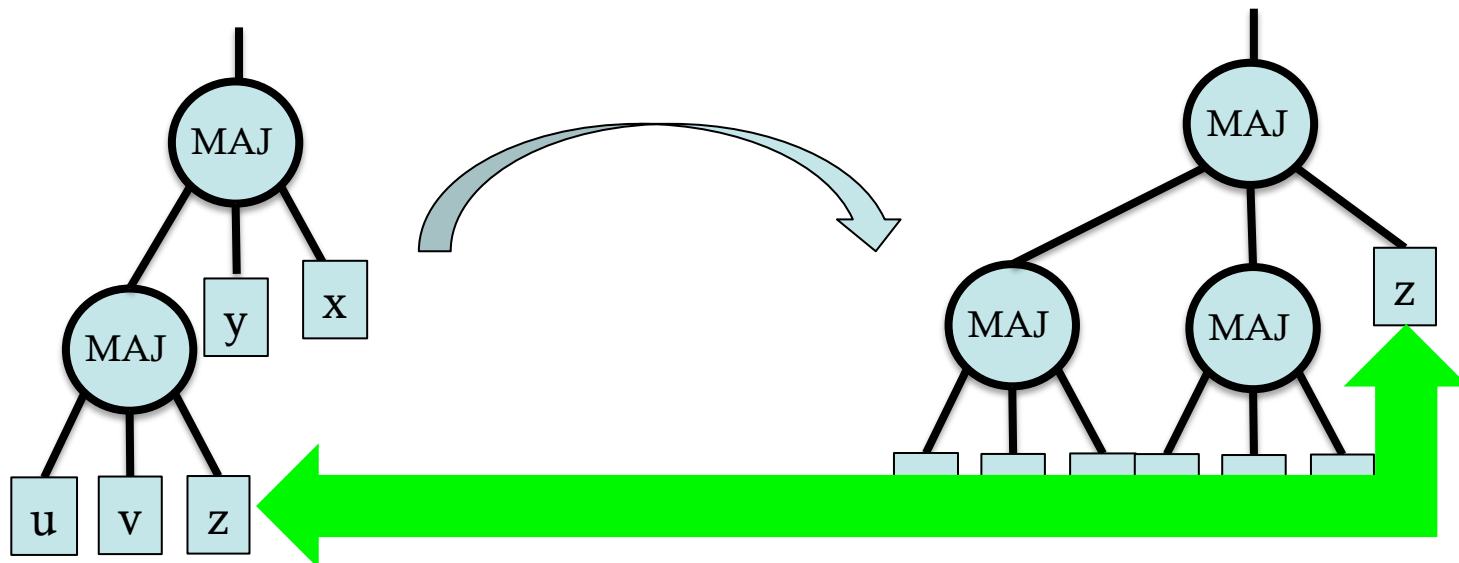- 1- Commutativity: $M(x, y, z) = M(y, x, z) = M(z, y, x)$
- 2- Majority: $if(x = y), M(x, y, z) = x = y$
 $if(x = y'), M(x, y, z) = z$
- 3- Associativity: $M(x, u, M(y, u, z)) = M(z, u, M(y, u, x))$
- 4- **Distributivity**: $M(x, y, M(u, v, z)) = M(M(x, y, u), M(x, y, v), z)$
- 5- Inverter Propagation: $M'(x, y, z) = M(x', y', z')$



MIG Boolean Algebra

 - 1- Commutativity: $M(x, y, z) = M(y, x, z) = M(z, y, x)$
- 2- Majority: $\text{if}(x = y), M(x, y, z) = x = y$
 $\text{if}(x = y'), M(x, y, z) = z$
- 3- Associativity: $M(x, u, M(y, u, z)) = M(z, u, M(y, u, x))$
- 4- Distributivity: $M(x, y, M(u, v, z)) = M(M(x, y, u), M(x, y, v), z)$
- 5- **Inverter Propagation:** $M'(x, y, z) = M(x', y', z')$



Properties

- The Boolean algebra with axioms Ω is:
 - Sound:
 - If a formula is derivable from Ω , then it is valid
 - Complete:
 - Each valid formula is derivable from Ω

- Any MIG configuration is reachable from any other equivalent MIG configuration

Enhancing Ω

- Powerful macro-transformations: Ψ
- Serve as shortcut to longer sequences in Ω
- Define: $z_{x/y}$ as replace x by y in all appearances in z

$$\Psi \left\{ \begin{array}{l} \text{1- **Relevance:** } M(x, y, z) = M(x, y, z_{x/y'}) \\ \text{2- **Complementary Associativity:Substitution:**$$

Optimizing MIGs

$$\Omega \left\{ \begin{array}{l} 1- \text{Commutativity: } M(x, y, z) = M(y, x, z) = M(z, y, x) \\ 2- \text{Majority: } \text{if}(x = y), M(x, y, z) = x = y \\ \quad \text{if}(x = y'), M(x, y, z) = z \\ 3- \text{Associativity: } M(x, u, M(y, u, z)) = M(z, u, M(y, u, x)) \\ 4- \text{Distributivity: } M(x, y, M(u, v, z)) = M(M(x, y, u), M(x, y, v), z) \\ 5- \text{Inverter Propagation: } M'(x, y, z) = M(x', y', z') \end{array} \right.$$

- By using Ω and Ψ we optimize an MIG
- What we really care about?
- Area \rightarrow MIG size
- Delay \rightarrow MIG depth
- Power \rightarrow MIG switching activity

MIG Size Optimization

- How to reduce the number of nodes in an MIG?
- Let's see what comes handy from Ω :

1- Commutativity: $M(x, y, z) = M(y, x, z) = M(z, y, x)$

2- **Majority**: if $(x = y)$, $M(x, y, z) = x = y$

if $(x = y')$, $M(x, y, z) = z$


3- Associativity: $M(x, u, M(y, v, z)) = M(M(x, y, u), M(x, y, v), z)$

4- **Distributivity**: $M(x, y, M(u, v, z)) = M(M(x, y, u), M(x, y, v), z)$

5- Inverter Propagation: $M'(x, y, z) = M(x', y', z')$

MIG Size Optimization

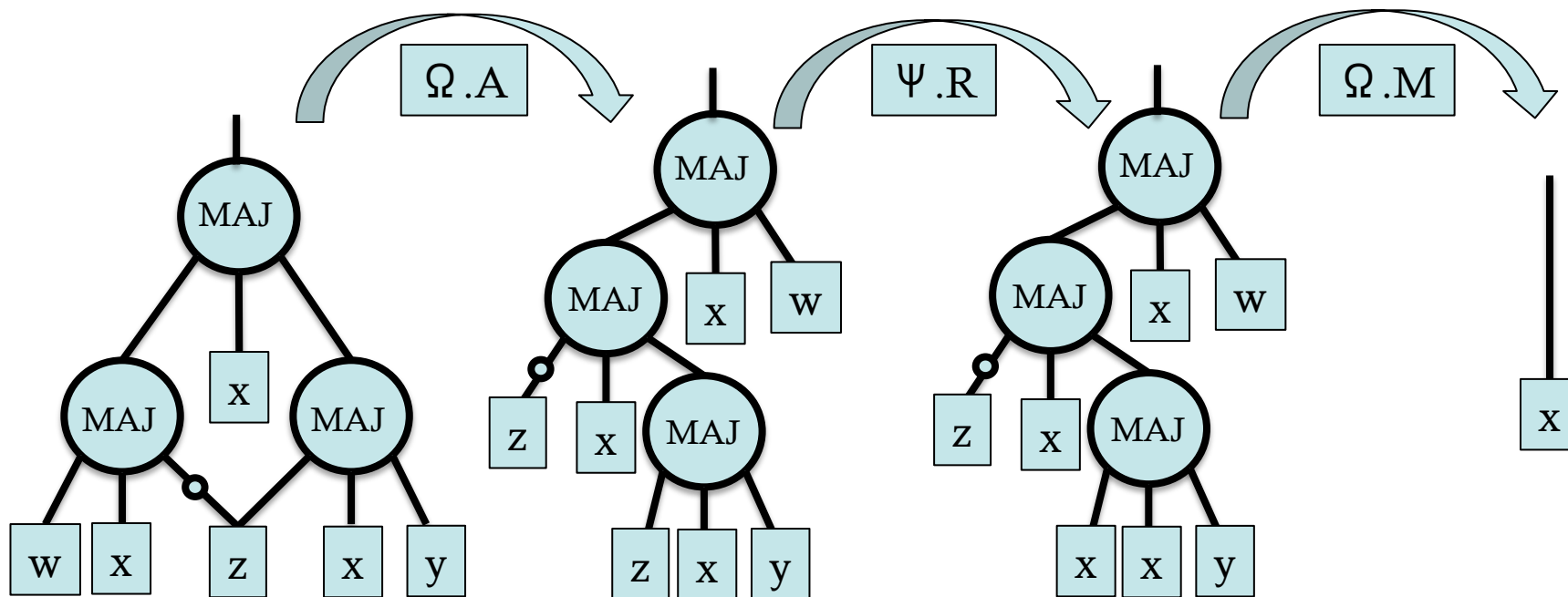- How to enable majority and distributivity laws for node reduction?
- Other rules from Ω and Ψ to reshape the MIG
- Reshape rationale: move closer similar/equivalent variables/nets




MIG Depth Optimization

- How to reduce the depth of an MIG?
- Let's see what comes handy from Ω :

- 1- Commutativity: $M(x, y, z) = M(y, x, z) = M(z, y, x)$
 - 2- **Majority**: $\text{if}(x = y), M(x, y, z) = x$
 $\text{if}(x = y'), M(x, y, z) = z$
 - 3- **Associativity**: $M(x, u, M(y, u, z)) = M(z, u, M(y, u, x))$
 - 4- **Distributivity**: $M(x, y, M(u, v, z)) = M(M(x, y, u), M(x, y, v), z)$
 - 5- Inverter Propagation: $M'(x, y, z) = M(x', y', z')$
-

MIG Depth Optimization

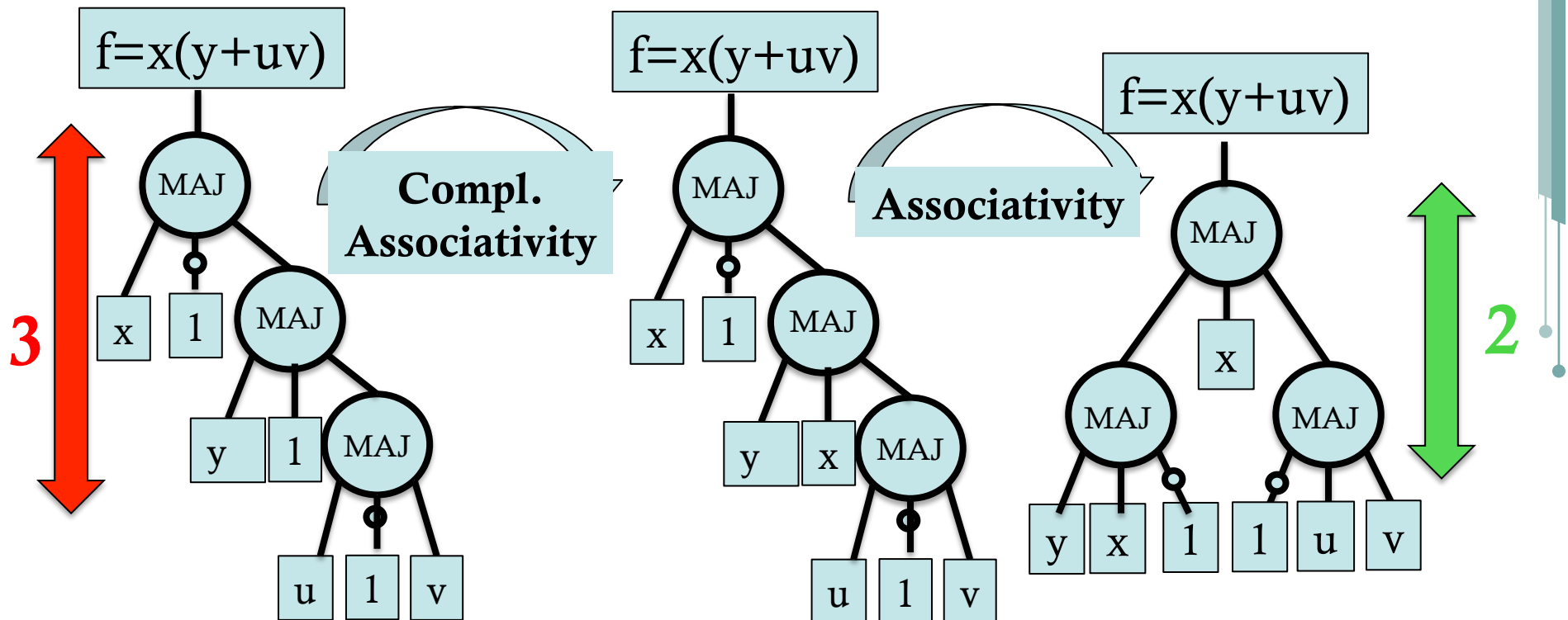- Rationale: move critical variables closer to the outputs via associativity, distributivity and majority rules
- Reshaping the MIG with other Ω rules




MIG Depth Optimization: Adders

8-bit adder: original

8-bit adder: MIG

Adder type	Inputs	Outputs	Original AIG		Optimized MIG	
			Size	Depth	Size	Depth
2-op 32 bit	64	33	352	96	610	12
2-op 64 bit	128	65	704	192	1159	11
2-op 128 bit	256	129	1408	384	14672	19
2-op 256 bit	512	257	2816	768	7650	16
3-op 32 bit	96	32	760	68	1938	16
4-op 64 bit	256	66	1336	136	2212	18

 

MIG Activity Optimization


- How to reduce the switching activity of an MIG?
- We want to make the switching probability of nodes close to 0
- Solution: substitute variables with $p \sim 0.5$ with other having $p \sim 0$ or $p \sim 1$
- How to make this? Let's see what comes handy from Ψ :

Ψ {

- 1- **Relevance:** $M(x, v, z) = M(x, v, z)$
- 2- **Comp** **if** $|p(x) - 0.5| > |p(u) - 0.5|$
 $M(x, u, M(y, u', z)) = M(x, u, M(y, x, z))$
- 3- **Subst** **if** $|p(u) - 0.5| > |p(v) - 0.5|$
 $M(x, y, z)$ **+ extra nodes overhead**
 $M(v, M(v', M_{v/u}(x, y, z), u), M(v', M_{v/u'}(x, y, z), u'))$

MIG Activity Optimization

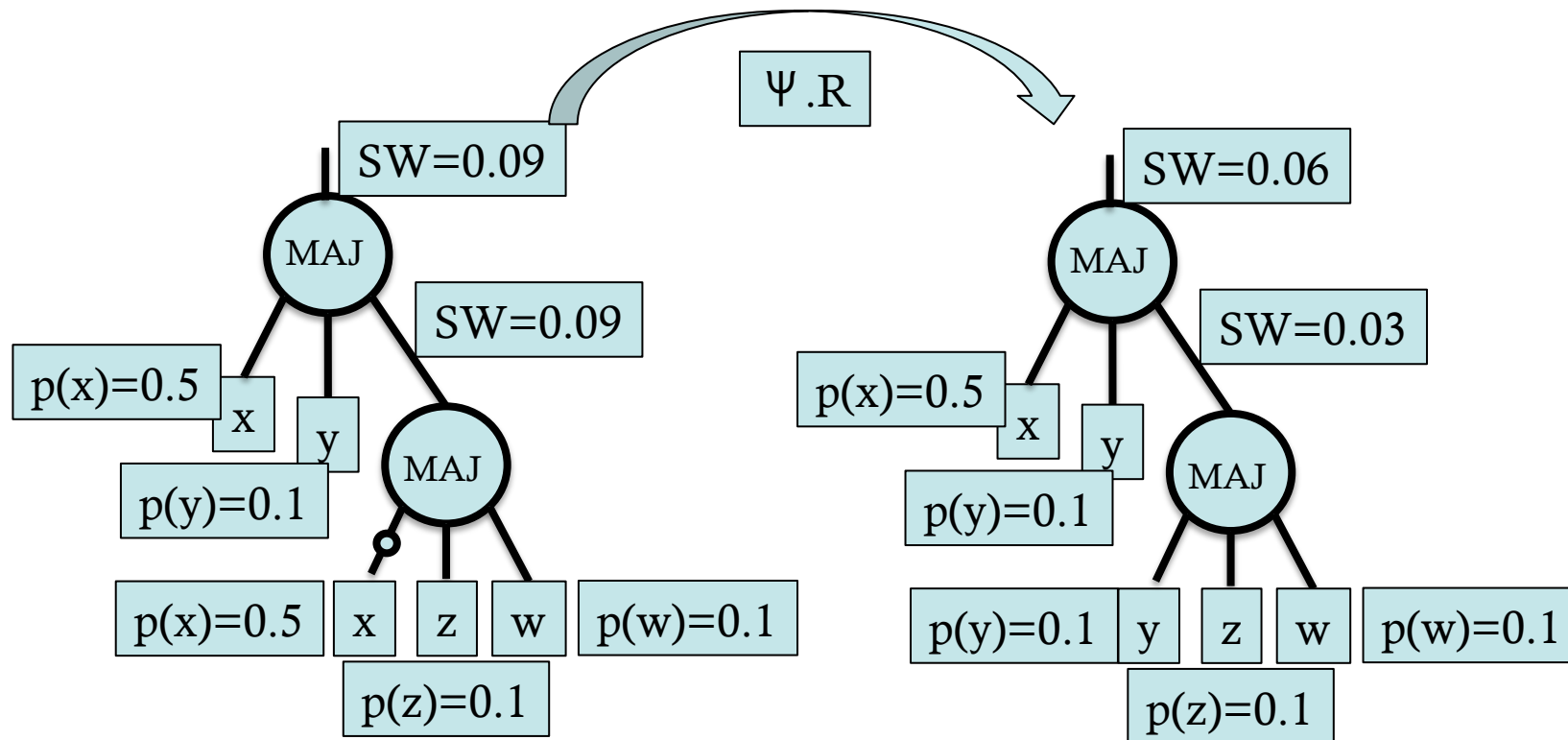
- How to enable switching activity reduction?
- Rationale: same as size and activity but oriented at reducing the switching probability



Majority-based synthesis: MIGthy

- **MIGthy**: a logic manipulation package for MIG
 - *MIGthy* reads and writes Verilog
 - Different optimization strategies (depth/area/activity)
 - Hybrid optimization: depth-oriented interlaced with area/power recovery phases
- MCNC, IWLS'05, arithmetic HDL benchmarks
 - Comparison with ABC, BDS and commercial synthesis tool
 - First set of experiments: pure logic optimization
 - Second set of experiments: complete design flow (logic optimization + technology mapping + physical design)

Experimental Results: MCNC circuits

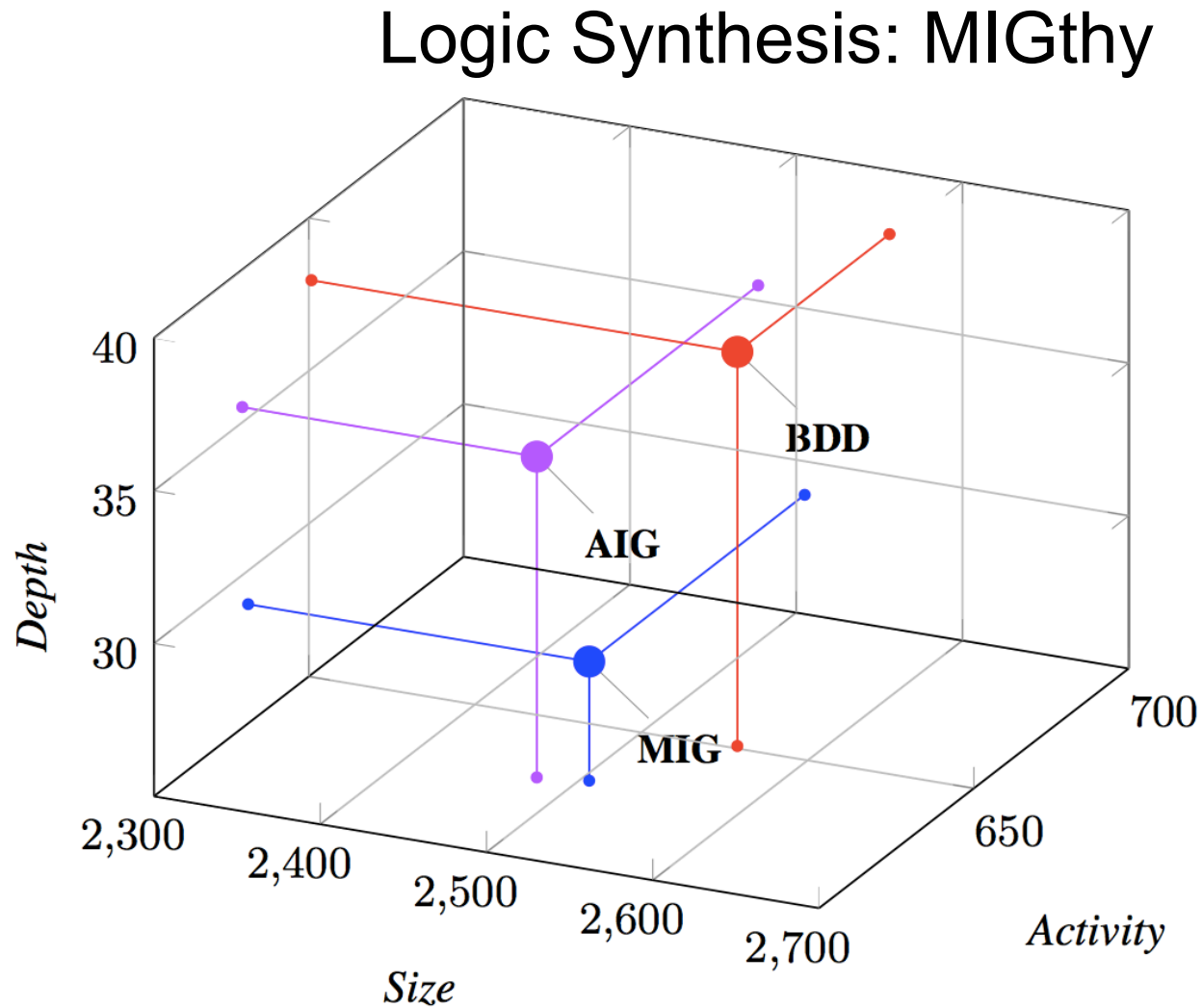

**MIGs & AIGs
better than BDDs**

**MIGs size &
activity ~ AIGs**

**MIGs depth
-20% w.r.t AIGs**

CMOS Design Results

Advanced 22nm CMOS
MIG as front-end to LS & PD

Well-established 90nm CMOS
MIG as front-end to LS & PD

Behavioral

```
module div32 (a, b, quotient_uns, quotient_tc, remainder_uns, remainder_tc);  
  
    parameter width = 32;  
  
    input [width-1:0] a, b;  
    output [width-1:0] quotient_uns, remainder_uns;  
    output signed [width-1:0] quotient_tc, remainder_tc;  
  
    // operators for quotient and remainder  
    assign quotient_uns = $unsigned(a) / $unsigned(b);  
    assign quotient_tc = $signed(a) / $signed(b);  
    assign remainder_uns = a % b;  
    assign remainder_tc = $signed(a) % $signed(b);  
endmodule
```

Area: 0.21 mm²
Delay: 11.22 ns
GC: 37k

MIG


```
assign w0 = (w39266 & w27196) | (w39266 & w42866) | (w27196 & w42866);  
assign w1 = w44100 & w4464;  
assign w2 = ~w19966 & w27946;  
assign w3 = ~w22044 & ~w30809;  
assign w4 = w42722 & ~b[26];  
assign w5 = (~w30032 & w19016) | (~w30032 & w47192) | (w19016 & w47192);  
assign w6 = ~w26074 & w5179;  
assign w7 = (w42822 & w16131) | (w42822 & w16107) | (w46131 & w16107);  
assign w8 = ~w35174 & w16835;  
assign w9 = ~w45553 & w4052;  
assign w10 = ~w14416 & w204;  
assign w11 = (~w16181 & w36731) | (w16181 & w16835);  
assign w12 = (w27179 & w4052);  
assign w13 = (w2836 & w204);  
assign w14 = ~w2529 & w36731;  
assign w15 = (w43756 & w36731);  
assign w16 = ~w44399 & w36731;  
assign w17 = ~w22912 & w36731;  
assign w18 = ~w30302 & w36731;  
assign w19 = (~w23777 & w50584);  
assign w20 = w26809 & w50584;  
assign w21 = (~w43756 & w3953);  
assign w22 = ~w36188 & w11507;  
assign w23 = ~w33838 & ~w16188;  
assign w24 = ~w38787 & w19348;  
assign w25 = w42096 & w20651;  
assign w26 = (w45543 & w39924) | (w45543 & w25446) | (w39924 & w25446);  
assign w27 = ~w34177 & w38267;  
assign w28 = ~w10074 & ~w29118;  
assign w29 = w25495 & w32055;  
assign w30 = (w48190 & w13546) | (w48190 & w19290) | (w13546 & w19290);
```

Area: 0.18 mm²
Delay: 10.10 ns
GC: 24k

All circuits underwent formal verification with success

Both circuits underwent formal verification with success

Modeling various emerging nanogates

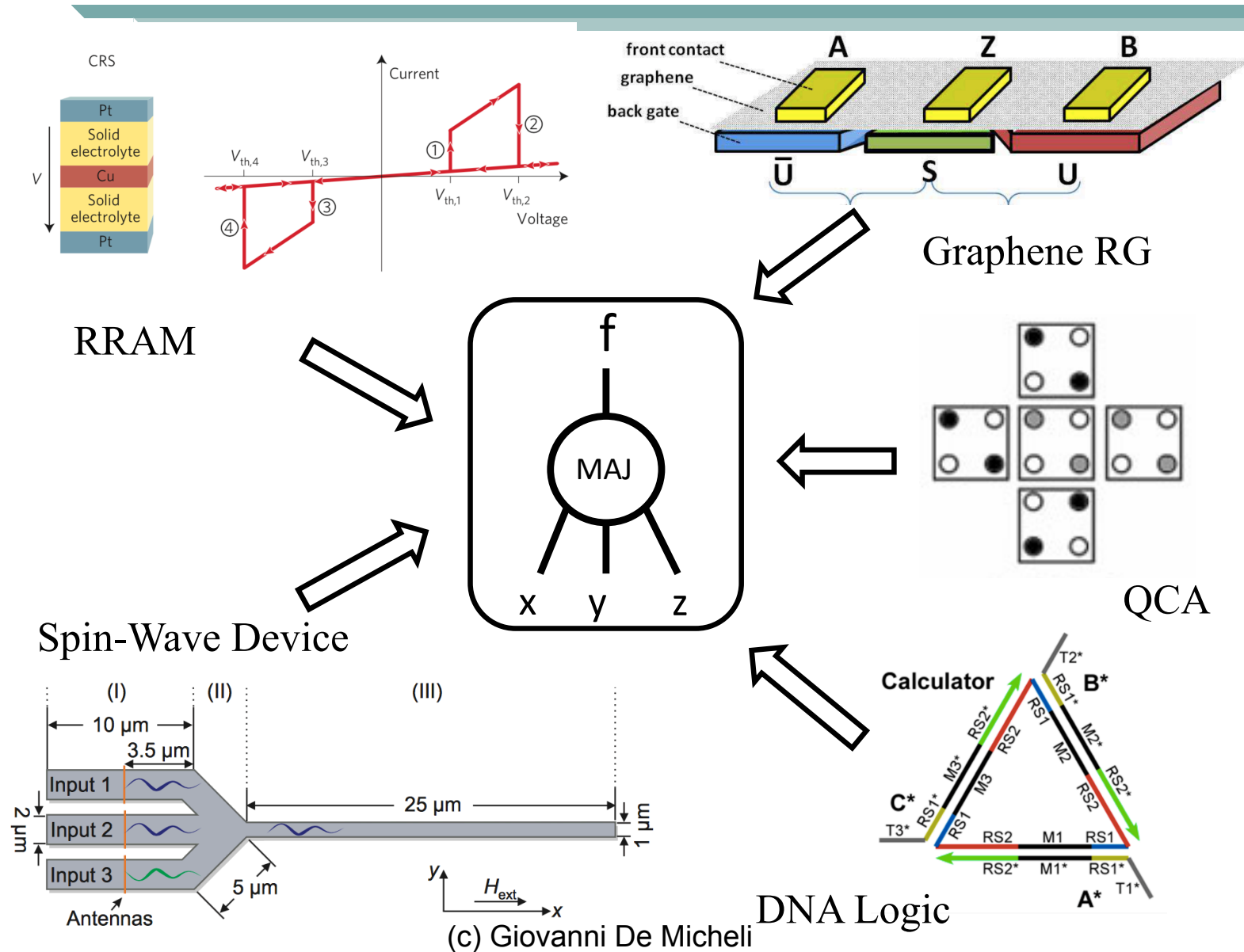

Nanotechnology Design

Spin Wave Device

feature size 21 nm

Behavioral

```

module div32 (a, b, quotient_uns, quotient_tc, remainder_uns,
remainder_tc);
parameter width = 32;
input [width-1:0] a, b;
output [width-1:0] quotient_uns;
output signed [width-1:0] quotient_tc;
output [width-1:0] remainder_uns;
output signed [width-1:0] remainder_tc;
// operators for unsigned and signed integers
assign quotient_uns = a / b;
assign quotient_tc = $signed(a) / $signed(b);
assign remainder_uns = a % b;
assign remainder_tc = $signed(a) % $signed(b);
endmodule
    
```

Area: 4863 μm^2
Delay: 5.32 ns
GC: 35k

DG-SiNWFET 22 nm

Divisor 32-bit IP

MIG

```

assign w0 = (w39266 & w27196) | (w39266 & w42866) | (w27196 & w42866);
assign w1 = w44100 & w4464;
assign w2 = ~w19966 & w27946;
assign w3 = ~w22044 & ~w30809;
assign w4 = w42722 & ~b[26];
assign w5 = (~w30032 & w19016) | (~w30032 & w47192) | (w19016 & w47192);
assign w6 = ~w26074 & w5179;
assign w7 = (w42822 & ~w46131) | (w42822 & w16107) | (~w46131 & w16107);
assign w8 = ~w3517;
assign w9 = ~w4555;
assign w10 = ~w144;
assign w11 = (~w162318 & w16835);
assign w12 = (w271 & w4052);
assign w13 = (w283 & w39204);
assign w14 = ~w252 & w36731;
assign w15 = (w437 & w36731);
assign w16 = ~w443;
assign w17 = ~w229;
assign w18 = ~w303;
assign w19 = (~w23 & w50584);
assign w20 = w2680;
assign w21 = (~w43 & w3953);
assign w22 = ~w36188 & w11587;
assign w23 = ~w33838 & ~w16188;
assign w24 = ~w38787 & w19348;
assign w25 = w42096 & w20651;
assign w26 = (w45543 & w39924) | (w45543 & w25446) | (w39924 & w25446);
assign w27 = ~w34177 & w38267;
assign w28 = ~w10074 & ~w29118;
assign w29 = w25495 & w32055;
assign w30 = (w48190 & w13546) | (w48190 & w19290) | (w13546 & w19290);
    
```

Area: 6115 μm^2
Delay: 3.55 ns
GC: 43k

Average	212/176	90.02	9.07	0.53	89.60	11.02	0.53
---------	---------	-------	------	------	-------	-------	------

MIGs Summary

- Majority-Inverter Graphs with their Boolean algebra push further the capabilities of contemporary logic synthesis
- Improvements at the design level for general benchmarks but also for highly-optimized units (div32)
- Promising results for CMOS (22nm and 90nm nodes) and even better results for DG-SiNWFET nanotechnology with enhanced device functionality
- MIGs unveil efficient design opportunities unseen by state-of-art synthesis techniques

Outline

- Introduction
- Technological innovations and motivation
 - Emerging nanotechnologies and devices
- Design with emerging technologies
 - Physical and logic synthesis
- The majority paradigm in logic synthesis
 - Models, algorithms and tools
- **Conclusions**

Conclusions

- Emerging nano-technologies with enhanced-functionality devices increase computational density
- New design, synthesis and verification methods stem from new abstractions of logic devices
- Current logic synthesis is based on specific heuristics: new models with stronger properties lead us to better methods and tools for both CMOS and emerging devices

Never stop exploring!

Huayna Potosi – 6088m
August 29, 2015



Thank you

