



# MODULAR MULTILEVEL CONVERTERS OPERATING PRINCIPLES AND APPLICATIONS

**Prof. Dražen Dujčić, Stefan Milovanović**

École Polytechnique Fédérale de Lausanne (EPFL)  
Power Electronics Laboratory (PEL)  
Switzerland



**EPFL**



# INTRODUCTION

*Non technical one...*





## Prof. Drazen Dujic

### Experience:

2014 – today	École Polytechnique Fédérale de Lausanne (EPFL), Lausanne, Switzerland
2013 – 2014	ABB Medium Voltage Drives, Turgi, Switzerland
2009 – 2013	ABB Corporate Research, Baden-Dättwil, Switzerland
2006 – 2009	Liverpool John Moores University, Liverpool, United Kingdom
2003 – 2006	University of Novi Sad, Novi Sad, Serbia

### Education:

2008	PhD, Liverpool John Moores University, Liverpool, United Kingdom
2005	M.Sc., University of Novi Sad, Novi Sad, Serbia
2002	Dipl. Ing., University of Novi Sad, Novi Sad, Serbia




## Mr. Stefan Milovanovic

### Education:

2020	PhD, École Polytechnique Fédérale de Lausanne (EPFL), Lausanne, Switzerland
2016	M.Sc., School of Electrical Engineering, University of Belgrade, Belgrade, Serbia

# POWER ELECTRONICS LABORATORY AT EPFL

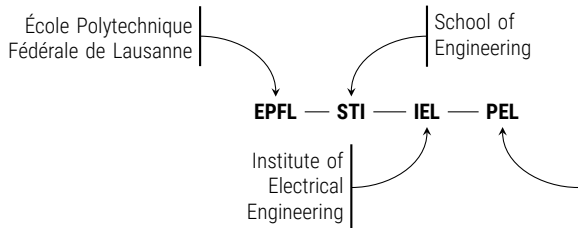

- ▶ Online since February 2014
- ▶ 12 PhD, 1 Scientist, 1 Postdoc, 1 Secretary
- ▶ <http://pel.epfl.ch>



Competence Centre



YOU ARE

BY SCHOOL

ABOUT EPFL

Directory


EPFL · STI · IEL · PEL

English

## POWER ELECTRONICS LABORATORY PEL

★ People Research Facilities Publications Education Student Projects News Awards Contact

Share:

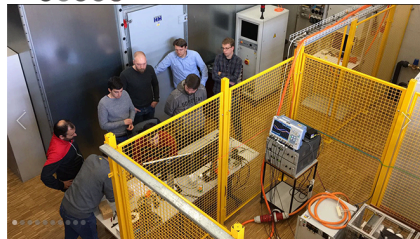

### Key Interests

electrical energy generation, conversion, storage  
medium voltage applications  
high power electronic converters  
high performance variable speed drives  
modelling, simulation, design, optimization, control  
power semiconductors, advanced magnetics

### CONTACT

Laboratory Director  
Prof. Drazen Dujic

Secretary  
Maria Anitua

Address  
EPFL STI IEL PEL  
ELD 131 (Bâtiment ELRO)  
Station 11  
CH-1015 Lausanne  
[Show on campus map](#)

Tel: +41 (0) 21 693 26 28  
Fax: +41 (0) 21 693 26 00

### PEL Research Interests


The research interests of the Power Electronics Laboratory are in the broad area of the Electrical Energy Generation, Conversion and Storage. In particular, we are interested into High Power Electronics Technologies for Medium Voltage applications, those operating with voltages in kV range, currents in kA range and powers in MW range. Power Electronics is one of the key-enabling technologies for the future energy systems, as it offers unprecedented flexibility for the integration and control of various electrical sources, storage elements or loads into the grid. This is equally valid for the present-day AC grids as well as for emerging concepts of DC grids, or inevitable mix of both in the near future.

To achieve controllable, reliable and efficient electrical energy conversion by means of advanced power electronic converters, we optimally use, but also influence and drive forward, advancements in different areas. These multidisciplinary considerations include: power semiconductors (e.g. Si, SiC, GaN), passive components (e.g. magnetics), insulation materials, mathematical modeling, simulations and optimization of power electronic systems, advanced control methods, etc.

# RESEARCH FOCUS


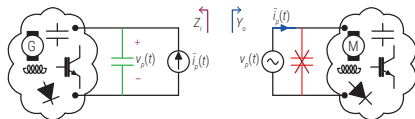
## MVDC Technologies and Systems

- ▶ System Stability
- ▶ Protection Coordination
- ▶ Power Electronic Converters



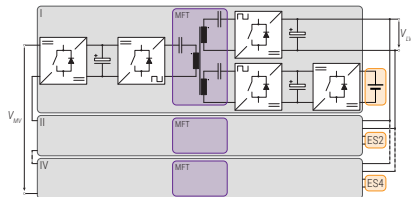
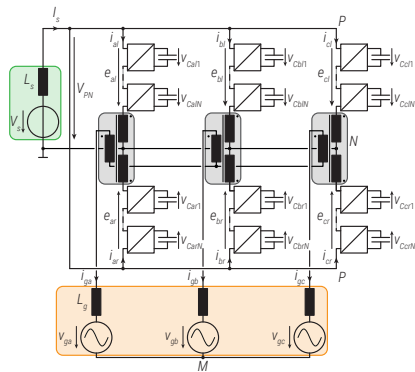
## High Power Electronics

- ▶ Multilevel Converters
- ▶ Solid State Transformers
- ▶ Medium Frequency Conversion


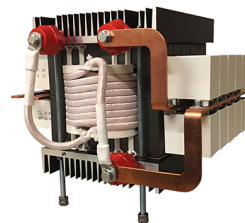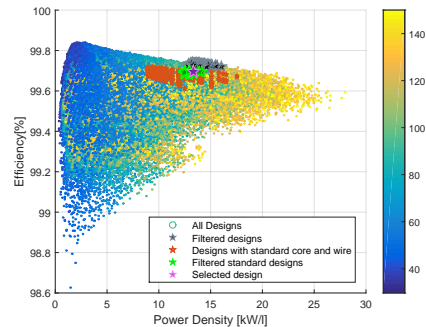
## Components

- ▶ Semiconductor devices
- ▶ Magnetics
- ▶ Modeling, Characterization



# MVDC POWER DISTRIBUTION NETWORKS

## MVDC Power Distribution Networks

- ▶ Feasibility (Applications)
- ▶ System Level Gains
- ▶ Dynamic Stability

## Conversion


- ▶ Passive, Efficient and Stable
- ▶ Flexible, Modular and Scalable
- ▶ Efficient

## Protection

- ▶ DC Breaker?
- ▶ Fault Current Limiting by Converters
- ▶ Protection Coordination



▲ Power electronics constituents

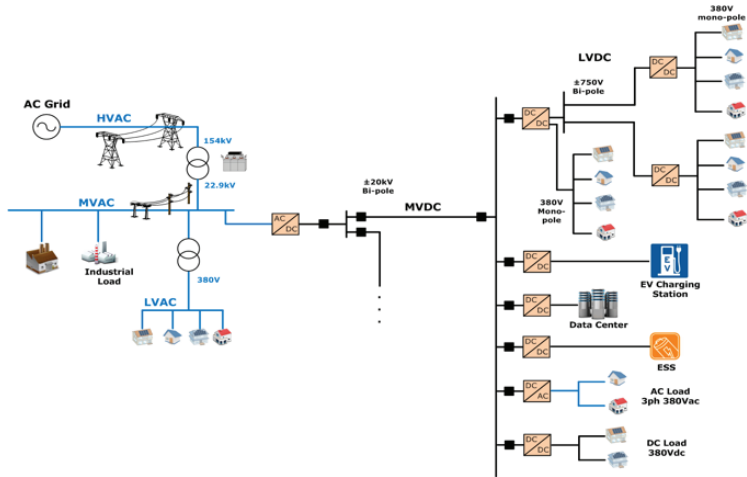

▲ Possible future MVDC grids and its links with existing grids

## Before the Coffee

### 1) Introduction and Motivation - MVDC

- ▶ MVDC Applications and Technologies
- ▶ MVDC Conversion Technologies
- ▶ Solid State Transformers

### 2) Modular Multilevel Converter Fundamentals

- ▶ Operating principles
- ▶ Modeling and Control
- ▶ Performance Benchmark

### 3) MMC Modulation Methods

- ▶ Carrier-based PWM, SVPWM
- ▶ Centralized vs. Distributed PWM
- ▶ SHE and OPPs



## After the Coffee

### 4) High Power MMCs

- ▶ Branch Energy Balancing
- ▶ Power Extension
- ▶ Pulse Width Modulation

### 5) High Power DC-DC Conversion

- ▶ MMC-based DAB Topologies
- ▶ Quasi-Two-Level Converters
- ▶ Design and Control

### 6) MMC Research Platform

- ▶ MMC system level design
- ▶ MMC RT-HIL development
- ▶ Questions and Discussion


⇒ Tutorial pdf can be downloaded from: (Source: [https://pe1.epfl.ch/publications\\_talks\\_en](https://pe1.epfl.ch/publications_talks_en))

# MVDC TECHNOLOGIES AND SYSTEMS

*Future electrical energy generation, conversion and storage technologies*
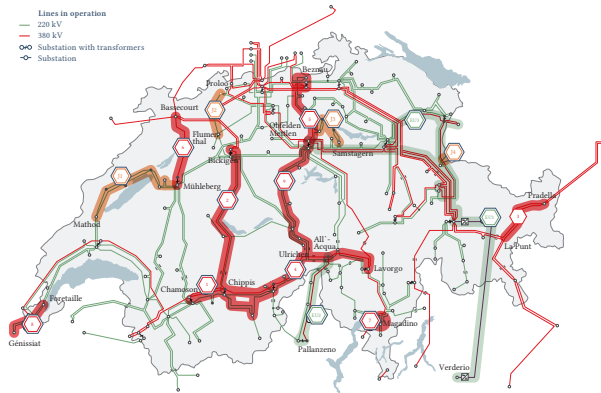
## SwissGrid infrastructure

- ▶ Existing infrastructure (220 – 380kV, 50 Hz) is ageing (2/3 built ~ 1960)
- ▶ Large PHSPs commissioned ⇒ sufficient capacity required
- ▶ Lengthy procedures for new overhead lines construction (low social acceptance, impact on landscape)




## MVDC grids

- ▶ Might be a good candidate w/ underground cable
- ▶ Suited for medium-scale energy collection

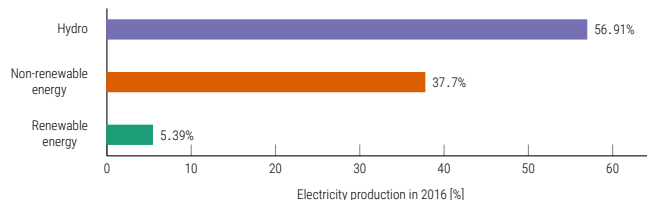
## Swiss energy landscape

- ▶ Annual consumption 60 TWh
- ▶ Nuclear phase out by 2050


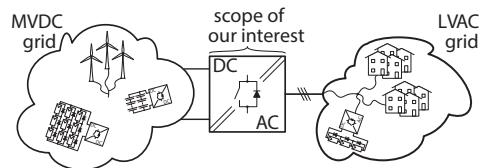
## Swiss Competence Centers for Energy Research (SCCERs)

- ▶ Government supported initiative
- ▶ SCCER-FURIES for future grids
- ▶ Explore ways to interconnect a MVDC grid w/ a LVAC grid




- ▲ Future energy systems with MVDC and LVAC grids

# WHY DC?


- ▶ No reactive power

Example: @  $\cos(\varphi) = 0.95$



$$\frac{P}{Q} \approx \frac{3}{1}$$

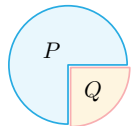


- ▶ No constraints imposed upon transmission distance
  - ▶ Transmission capacity increase
  - ▶ Lower transmission losses
  - ▶ Alleviated stability problems
- 
- ▶ No skin effect ( $R_V \downarrow \Rightarrow P_V \uparrow$ )
  - ▶ Cheaper solution ("Break-even distance")
  - ▶ Underwater cable transmission
  - ▶ No need for synchronization (Marine applications)
  - ▶ Direct integration of Renewable Energy Sources
  - ▶ Challenges  $\Rightarrow$  DC Transformer/Protection?

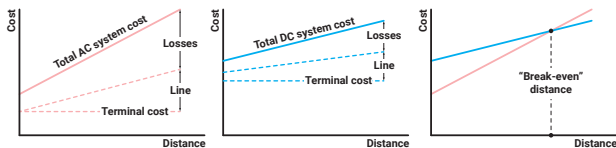

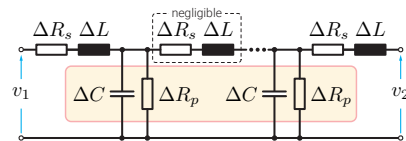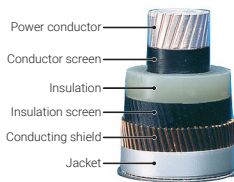▲ Cost comparison between AC and DC systems



▲ High voltage cable

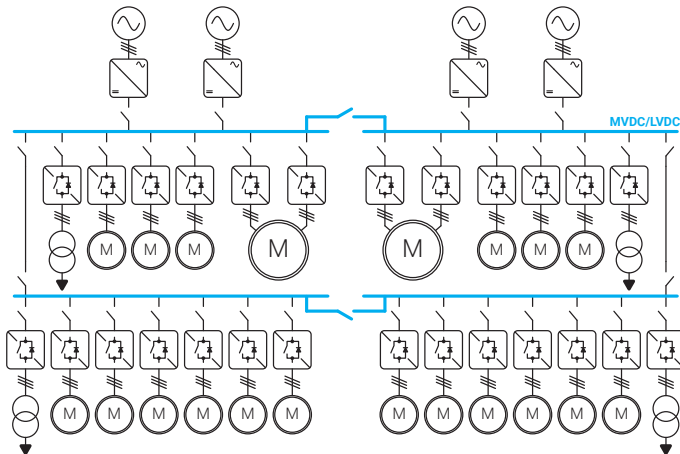

▲ DC Ship distribution system - frequency decoupling through a DC distribution



# TREND TOWARDS DC

## Bulk power transmission

- ▶ Break even distance against AC lines
- ▶ ~ 50 km for subsea cables or 600 km for overhead lines
- ▶ Long history since 1950s
- ▶ Interconnection of asynchronous grids



- ▲ From mercury arc rectifiers to modern HVDC systems

## LVDC ships

- ▶ Variable frequency generators  $\Rightarrow$  maximum efficiency of the internal combustion engines
- ▶ Commercial products by ABB & Siemens



- ▲ Specialized vessels with LVDC distribution

## Datacenters

- ▶ 380 V<sub>dc</sub>
- ▶ DC loads (including UPS)
- ▶ Expected efficiency increase

## Large PV powerplants

- ▶ 1500 V<sub>dc</sub> PV central inverters
- ▶ Higher number of series-connected panels per string



- ▲ 1500V PV inverter - step towards the MVDC

## Open challenges

- ▶ DC breaker
- ▶ Conversion blocks missing
- ▶ Protection coordination

# TREND TOWARDS DC

## Bulk power transmission

- ▶ Break even distance against AC lines
- ▶ ~ 50 km for subsea cables or 600 km for overhead lines
- ▶ Long history since 1950s
- ▶ Interconnection of asynchronous grids



- ▲ From mercury arc rectifiers to modern HVDC systems

## LVDC ships

- ▶ Variable frequency generators ⇒ maximum efficiency of the internal combustion engines
- ▶ Commercial products by ABB & Siemens



- ▲ Specialized vessels with LVDC distribution

## Datacenters

- ▶ 380 V<sub>dc</sub>
- ▶ DC loads (including UPS)
- ▶ Expected efficiency increase

## Large PV powerplants

- ▶ 1500 V<sub>dc</sub> PV central inverters
- ▶ Higher number of series-connected panels per string



- ▲ 1500V PV inverter - step down to the MVDC

## Open challenges

- ▶ DC breaker
- ▶ Conversion blocks missing
- ▶ Protection coordination

dc beneficial for medium / high power applications

# EMERGING MVDC APPLICATIONS

## Installations

- ▶ ABB HVDC Light demo: 4.3 km/ $\pm 9$  kV<sub>dc</sub> [1]
- ▶ Tidal power connection: 16 km/10 kV<sub>dc</sub> (based on MV3000 & MV7000) [2]



- ▶ Unidirectional oil platform connection in China: 29.2 km/ $\pm 15$  kV<sub>dc</sub> [3]

## Projects


- ▶ Angle DC: conversion of 33 kV MVac line to  $\pm 27$  kV MVdc [4]

## Universities

- ▶ Increased number of laboratories active in high power domain
- ▶ China, Europe, USA,...
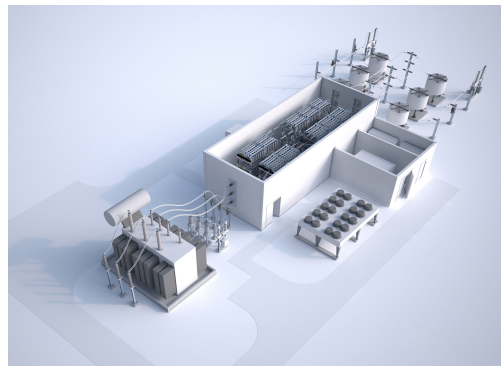
## Products

- ▶ Siemens MVDC Plus
  - ▶ 30 - 150 MW
  - ▶ < 200 km
  - ▶ <  $\pm 50$  kV<sub>dc</sub>



- ▶ RXPE Smart VSC-MVDC
  - ▶ 1 - 10 MVar
  - ▶  $\pm 5$  -  $\pm 50$  kV<sub>dc</sub>
  - ▶ 40 - 200 km

# EMERGING MVDC APPLICATIONS

## Installations

- ▶ ABB HVDC Light demo: 4.3 km/ $\pm 9$  kV<sub>dc</sub> [1]
- ▶ Tidal power connection: 16 km/10 kV<sub>dc</sub> (based on MV3000 & MV7000) [2]



- ▶ Unidirectional oil platform connection in China: 29.2 km/ $\pm 15$  kV<sub>dc</sub> [3]

## Projects


- ▶ Angle DC: conversion of 33 kV MVac line to  $\pm 27$  kV MVdc [4]

## Universities

- ▶ Increased number of laboratories active in high power domain
- ▶ China, Europe, USA,...
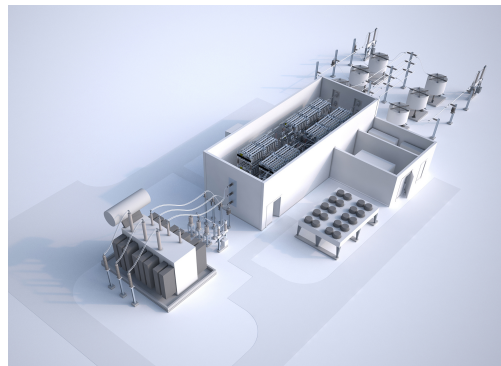
## Products

- ▶ Siemens MVDC Plus
  - ▶ 30 - 150 MW
  - ▶ < 200 km
  - ▶ <  $\pm 50$  kV<sub>dc</sub>




- ▶ RXPE Smart VSC-MVDC
  - ▶ 1 - 10 MVar
  - ▶  $\pm 5$  -  $\pm 50$  kV<sub>dc</sub>
  - ▶ 40 - 200 km

⇒ MVDC is gaining momentum!

# TREND TOWARDS HIGHLY MODULAR CONVERTER TOPOLOGIES

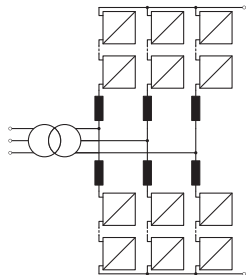
## HVDC

- ▶ Decoupled semiconductor switching frequency from converter apparent switching frequency
- ▶ Improved harmonic performance  $\Rightarrow$  less / no filters
- ▶ Series-connection of semiconductors still possible
- ▶ Fault blocking capability depending on cell type




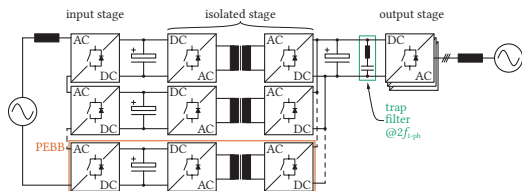
## Solid-state transformers (SSTs)

- ▶ Power density increase w/ conversion & isolation at higher frequency
- ▶ Grid applications / traction transformer w/ different optimization objectives
- ▶ MFT design / isolation are the bottlenecks



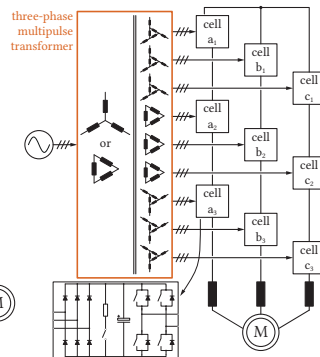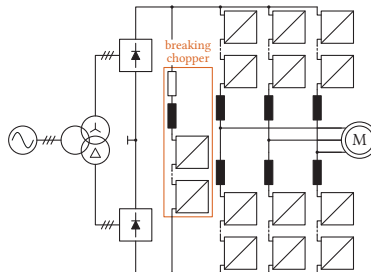
## MV drives

- ▶ Monolithic ML topologies (NPC, NPP, FC, ANPC) are not scalable
- ▶ Robicon drive  $\rightarrow$  everyone offers it
- ▶ Siemens & Benschaw: MMC drive
- ▶ Low  $dv/dt \Rightarrow$  motor friendly


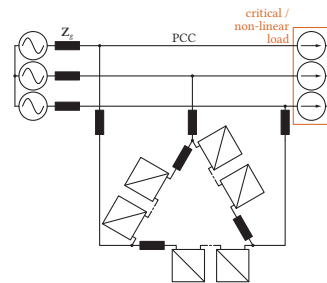
## FACTS


- ▶ SFC for railway inertias (direct catenary connection)
- ▶ STATCOM
- ▶ BESS (split batteries)



# TREND TOWARDS HIGHLY MODULAR CONVERTER TOPOLOGIES

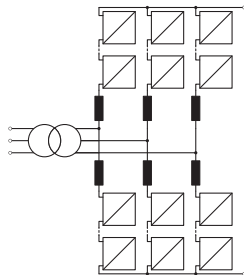
## HVDC

- ▶ Decoupled semiconductor switching frequency from converter apparent switching frequency
- ▶ Improved harmonic performance  $\Rightarrow$  less / no filters
- ▶ Series-connection of semiconductors still possible
- ▶ Fault blocking capability depending on cell type


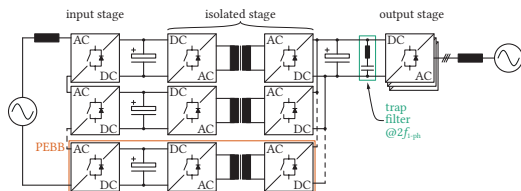
## Solid-state transformers (SSTs)



- ▶ Power density increase w/ conversion & isolation at higher frequency
- ▶ Grid applications / traction transformer w/ different optimization objectives
- ▶ MFT design / isolation are the bottlenecks



$\Rightarrow$  Modularity provides obvious benefits in high power applications!

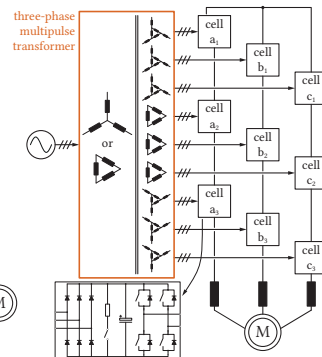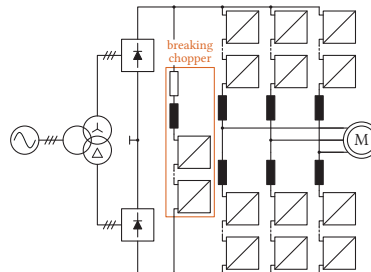
## MV drives

- ▶ Monolithic ML topologies (NPC, NPP, FC, ANPC) are not scalable
- ▶ Robicon drive  $\rightarrow$  everyone offers it
- ▶ Siemens & Benschaw: MMC drive
- ▶ Low  $dv/dt \Rightarrow$  motor friendly


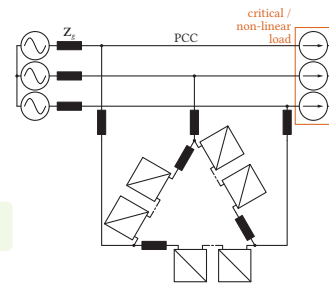
## FACTS

- ▶ SFC for railway inertias (direct catenary connection)
- ▶ STATCOM
- ▶ BESS (split batteries)



# SOLID STATE TRANSFORMER FOR TRACTION (ABB - 1.2MW PETT)

## Characteristics


- ▶ 1-Phase MVAC to MVDC
- ▶ Power: 1.2MVA
- ▶ Input AC voltage: 15kV, 16.7Hz
- ▶ Output DC voltage: 1500 V
- ▶ 9 cascaded stages (n + 1)
- ▶ input-series output-parallel
- ▶ double stage conversion

## 99 Semiconductor Devices

- ▶ HV PEBB: 9 x (6 x 6.5kV IGBT)
- ▶ LV PEBB: 9 x (2 x 3.3kV IGBT)
- ▶ Bypass: 9 x (2 x 6.5kV IGBT)
- ▶ Decoupling: 9 x (1 x 3.3kV Diode)
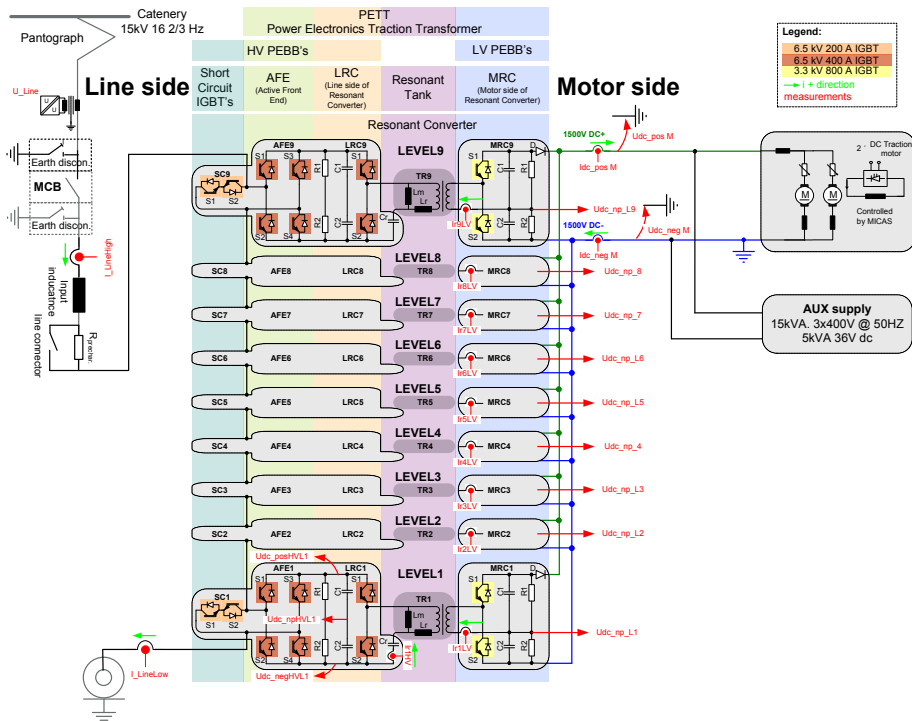
## 9 MFTs

- ▶ Power: 150kW
- ▶ Frequency: 1.75kHz
- ▶ Core: Nanocrystalline
- ▶ Winding: Litz
- ▶ Insulation / Cooling: oil




▲ ABB PETT scheme [5], [6]

# SOLID STATE TRANSFORMER FOR TRACTION - DESIGN


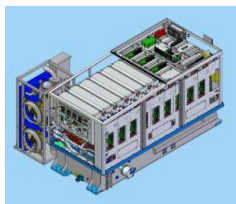
## Retrofitted to shunting locomotive

- ▶ Replaced LFT + SCR rectifier
- ▶ Propulsion motor - 450kW
- ▶ 12 months of field service
- ▶ No power electronic failures
- ▶ Efficiency around 96%
- ▶ Weight:  $\approx 4.5$  t



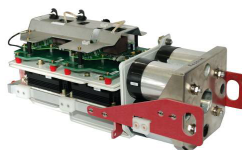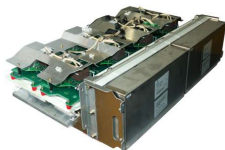
## Technologies

- ▶ Standard 3.3kV and 6.5kV IGBTs
- ▶ De-ionized water cooling
- ▶ Oil cooling/insulation for MFTs
- ▶  $n + 1$  redundancy
- ▶ IGBT used for bypass switch


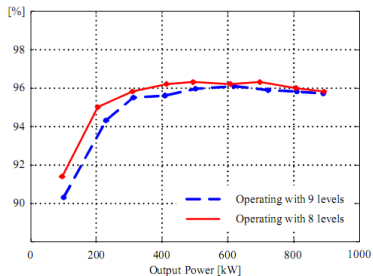
## Displayed at:

- ▶ Swiss Museum of Transport
- ▶ <https://www.verkehrshaus.ch>



▲ ABB PETT prototype [5], [6]



# MEDIUM OR LOW FREQUENCY CONVERSION?

## MVDC integration challenge

- ▶ MVDC-LVAC galvanically isolated conversion system

## Desired conversion features


- ▶ High efficiency
- ▶ Galvanic isolation
- ▶ Modularity
- ▶ Scalability
- ▶ Reliability
- ▶ Availability

## Laboratory prototype ratings

- ▶  $S = 0.5 \text{ MVA}$
- ▶  $N_{\text{cells}} = 6 \times 16$
- ▶  $V_{\text{dc}} = 10 \text{ kV}$
- ▶  $V_{\text{ac}} = 400 \text{ V}$
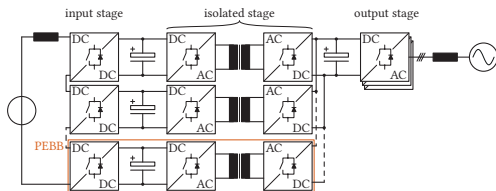
## SST approach


- ▶ VSI on LVAC side of SST reduces efficiency by  $\approx 2\%$  (!) [7]
- ▶ Drawn solution is not the unique possibility



▲ Generic SST illustration for MVDC-LVAC conversion
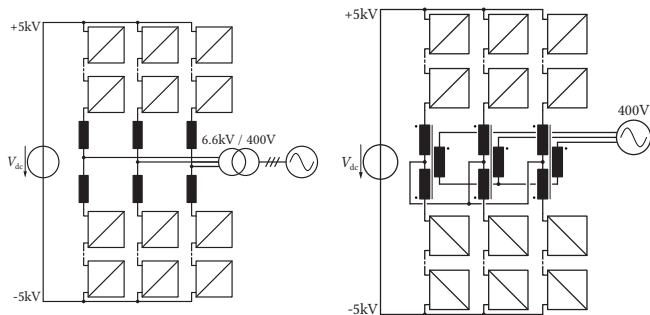
## MMC

- ▶ Solution with MMC + LFT has higher efficiency



## Research opportunities

1. MMC topological variations and control methods
2. Modulation and branch balancing methods
3. Integration of branch inductances into the transformer structure: **GIMC**
4. Virtual Submodule Concept for fast cell loss estimation method [8]
5. MMC cell design optimization [9]

# MEDIUM OR LOW FREQUENCY CONVERSION?

## MVDC integration challenge

- ▶ MVDC-LVAC galvanically isolated conversion system

## Desired conversion features


- ▶ High efficiency
- ▶ Galvanic isolation
- ▶ Modularity
- ▶ Scalability
- ▶ Reliability
- ▶ Availability

## Laboratory prototype ratings

- ▶  $S = 0.5 \text{ MVA}$
- ▶  $N_{\text{cells}} = 6 \times 16$
- ▶  $V_{\text{dc}} = 10 \text{ kV}$
- ▶  $V_{\text{ac}} = 400 \text{ V}$
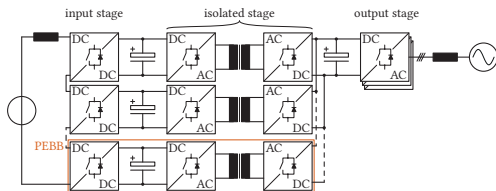
## SST approach


- ▶ VSI on LVAC side of SST reduces efficiency by  $\approx 2\%$  (!) [7]
- ▶ Drawn solution is not the unique possibility



▲ Generic SST illustration for MVDC-LVAC conversion
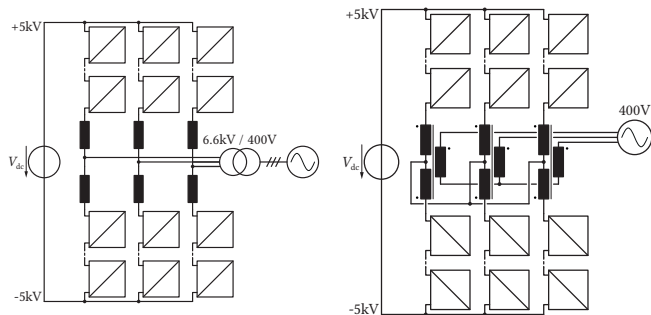
## MMC

- ▶ Solution with MMC + LFT has higher efficiency



## Research opportunities

1. MMC topological variations and control methods
2. Modulation and branch balancing methods
3. Integration of branch inductances into the transformer structure: **GIMC**
4. Virtual Submodule Concept for fast cell loss estimation method [8]
5. MMC cell design optimization [9]

⇒ The choice is not always obvious and greatly depends on the application requirements and constraints!

# MODULAR MULTILEVEL CONVERTER

*Fundamental operating principles, modeling, power equations*

# NOMENCLATURE

## Cell (Submodule)

- ▶ Controllable devices (semiconductors)
- ▶ Energy storage element (capacitor)

## Branch

- ▶ Controllable current / voltage source
- ▶ A string of cells (submodules)
- ▶ One reactor

## Phase-leg


- ▶ Comprising two branches

## AC terminals

- ▶ Connection to a grid (with or without transformer) or a load (e.g., ac machine)
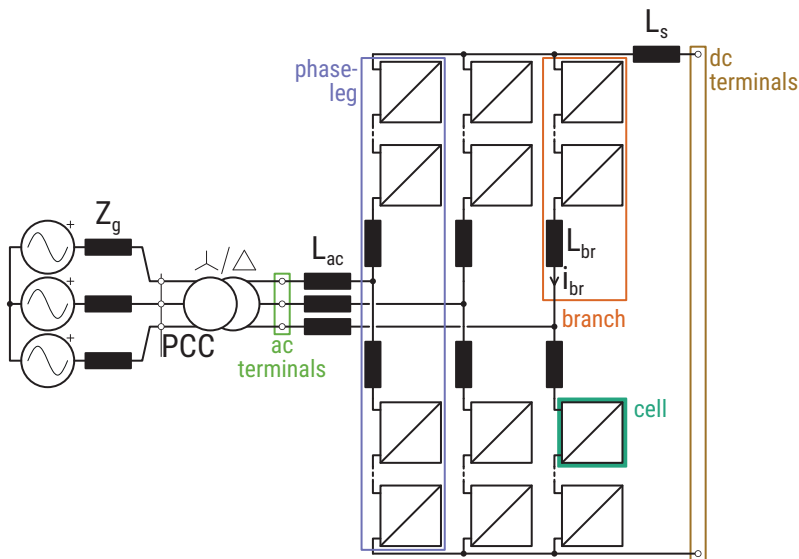
## DC terminals

- ▶ Connection to transmission line (overhead line or cable), load or other converter (back-to-back)



▲ Modular multilevel converter connected to an ac grid through a transformer




Functionality wise, only  $L_{br}$  is required!

# SUBMODULE TYPES
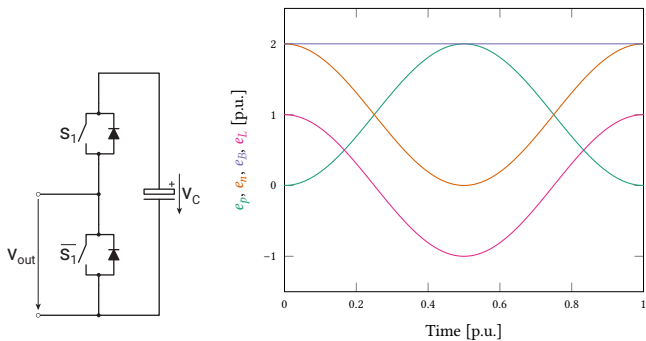
## Unipolar cell


- ▶ Best for efficiency
- ▶ No fault blocking capability
- ▶ 2-level output voltage



▲ Unipolar (half-bridge) Submodule
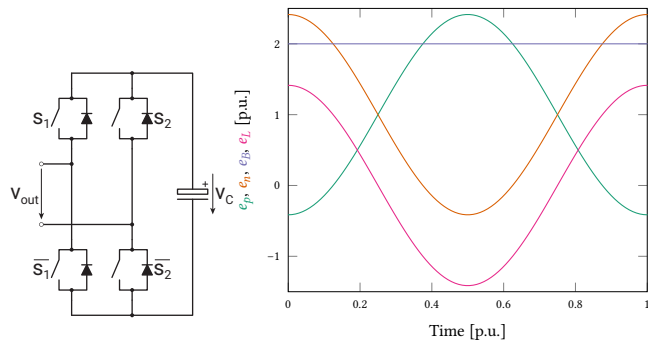
## Bipolar cell

- ▶ Fault blocking capability
- ▶ Conduction losses double
- ▶ 3-level output voltage



▲ Bipolar (full-bridge) Submodule

Many other variations and advanced cell types have been reported...

# MATHEMATICAL MODELING

## KVL equations


$$\frac{V_{dc}}{2} = e_p + L_{br} \frac{d}{dt} i_p - M_{br} \frac{d}{dt} i_n + R_{br} i_p + L_g \frac{d}{dt} (i_p - i_n) + R_g (i_p - i_n) + v_g + v_{CM}$$

$$\frac{V_{dc}}{2} = e_n + L_{br} \frac{d}{dt} i_n - M_{br} \frac{d}{dt} i_p + R_{br} i_n - L_g \frac{d}{dt} (i_p - i_n) - R_g (i_p - i_n) - v_g - v_{CM}$$

where  $e_x = \sum_{i=1}^{N_{cells}} s_{xi} v_{Cxi}$  (switched model) or  $e_x = m_x v_{C\Sigma x}$  (average model)
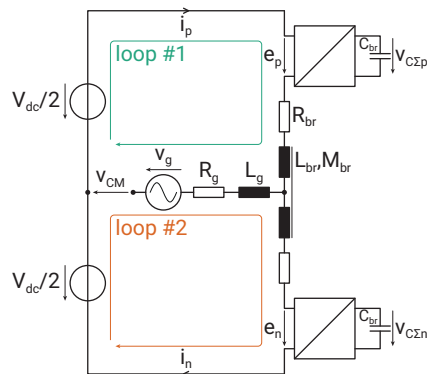
## Submodule capacitor voltages

$$\frac{d}{dt} \begin{bmatrix} v_{C\Sigma p} \\ v_{C\Sigma n} \end{bmatrix} = \frac{1}{C_{br}} \begin{bmatrix} m_p & 0 \\ 0 & m_n \end{bmatrix} \begin{bmatrix} i_p \\ i_n \end{bmatrix}$$



▲ Single-phase MMC for modeling

## First transformation

$$\begin{bmatrix} i_{circ} \\ i_g \end{bmatrix} = \begin{bmatrix} 1/2 & 1/2 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} i_p \\ i_n \end{bmatrix} \quad \Leftrightarrow \quad \begin{bmatrix} i_p \\ i_n \end{bmatrix} = \begin{bmatrix} 1 & 1/2 \\ 1 & -1/2 \end{bmatrix} \begin{bmatrix} i_{circ} \\ i_g \end{bmatrix}$$

$$\begin{bmatrix} e_B \\ e_L \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ -1/2 & 1/2 \end{bmatrix} \begin{bmatrix} e_p \\ e_n \end{bmatrix} \quad \Leftrightarrow \quad \begin{bmatrix} e_p \\ e_n \end{bmatrix} = \begin{bmatrix} 1/2 & -1 \\ 1/2 & 1 \end{bmatrix} \begin{bmatrix} e_B \\ e_L \end{bmatrix}$$


## Second transformation

$$\begin{bmatrix} v_{C\Sigma}^{\Sigma} \\ v_{C\Sigma}^{\Delta} \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ -1/2 & 1/2 \end{bmatrix} \begin{bmatrix} v_{C\Sigma p} \\ v_{C\Sigma n} \end{bmatrix} \quad \Leftrightarrow \quad \begin{bmatrix} v_{C\Sigma p} \\ v_{C\Sigma n} \end{bmatrix} = \begin{bmatrix} 1/2 & -1 \\ 1/2 & 1 \end{bmatrix} \begin{bmatrix} v_{C\Sigma}^{\Sigma} \\ v_{C\Sigma}^{\Delta} \end{bmatrix}$$

$$\begin{bmatrix} m_{\Sigma} \\ m_{\Delta} \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ -1/2 & 1/2 \end{bmatrix} \begin{bmatrix} m_p \\ m_n \end{bmatrix} \quad \Leftrightarrow \quad \begin{bmatrix} m_p \\ m_n \end{bmatrix} = \begin{bmatrix} 1/2 & -1 \\ 1/2 & 1 \end{bmatrix} \begin{bmatrix} m_{\Sigma} \\ m_{\Delta} \end{bmatrix}$$
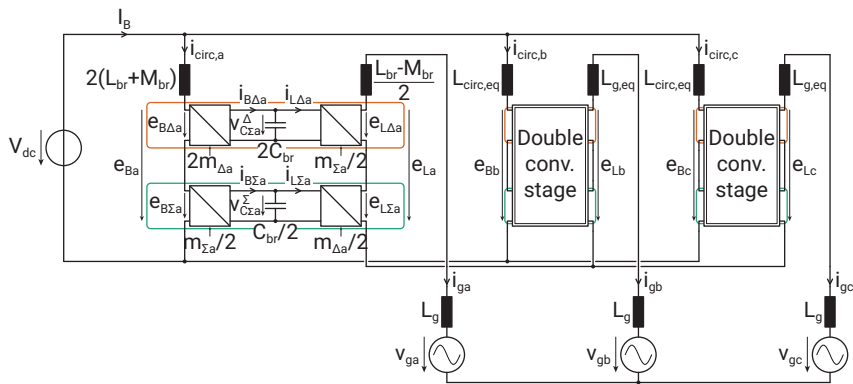
# DECOUPLED MODEL

$$\frac{d}{dt} \begin{bmatrix} i_{\text{circ}} \\ i_g \\ \Sigma V_{C\Sigma} \\ \Delta V_{C\Sigma} \end{bmatrix} = \begin{bmatrix} -\frac{R_{br}}{L_{br}-M_{br}} \mathbb{1}_3 & -\frac{R_{br}/2+R_g}{L_{br}+M_{br}+2L_g} \mathbb{1}_3 & \frac{(L_{br}+L_g)M_{lp}+(M_{br}+L_g)M_{ln}}{2(L_{br}-M_{br})(L_{br}+2L_g+M_{br})} & -\frac{(L_{br}+L_g)M_{lp}-(L_g+M_{br})M_{ln}}{(L_{br}-M_{br})(L_{br}+2L_g+M_{br})} \\ -\frac{R_{br}}{L_{br}-M_{br}} \mathbb{1}_3 & \frac{R_{br}/2+R_g}{L_{br}+2L_g+M_{br}} \mathbb{1}_3 & \frac{(L_{br}+L_g)M_{ln}+(L_g+M_{br})M_{lp}}{2(L_{br}-M_{br})(L_{br}+2L_g+M_{br})} & -\frac{(L_{br}+L_g)M_{ln}-(L_g+M_{br})M_{lp}}{(L_{br}-M_{br})(L_{br}+2L_g+M_{br})} \\ \frac{1}{C_{br}} M_{lp} & \frac{1}{2C_{br}} M_{lp} & -\frac{1}{2C_{br}R_{esr}} \mathbb{1}_3 & \frac{1}{C_{br}R_{esr}} \mathbb{1}_3 \\ \frac{1}{C_{br}} M_{ln} & -\frac{1}{2C_{br}} M_{ln} & -\frac{1}{2C_{br}R_{esr}} \mathbb{1}_3 & -\frac{1}{C_{br}R_{esr}} \mathbb{1}_3 \end{bmatrix} \begin{bmatrix} i_{\text{circ}} \\ i_g \\ \Sigma V_{C\Sigma} \\ \Delta V_{C\Sigma} \end{bmatrix} + \begin{bmatrix} \frac{3}{4(L_{br}-M_{br})} \mathbb{1}_{3 \times 1} & -\frac{1}{2(L_{br}+2L_g+M_{br})} \mathbb{1}_3 \\ \frac{1}{4(L_{br}-M_{br})} \mathbb{1}_{3 \times 1} & -\frac{3}{2(L_{br}+2L_g+M_{br})} \mathbb{1}_3 \\ \mathbb{0}_{3 \times 1} & \mathbb{0}_3 \\ \mathbb{0}_{3 \times 1} & \mathbb{0}_3 \end{bmatrix} \begin{bmatrix} V_{dc} \\ V_g + V_{CM} \mathbb{1}_{3 \times 1} \end{bmatrix}$$



▲ Decoupled MMC model with main and secondary paths

# POWER EQUATIONS (I)

$$e_{p/n}(t) = \frac{V_{dc}}{2} \mp (v_g(t) + v_{CM}(t)) - \left( R_{br} i_{p/n}(t) + L_{br} \frac{d}{dt} i_{p/n}(t) - M_{br} \frac{d}{dt} i_{n/p}(t) \right)$$
$$i_{p/n}(t) = \frac{I_{dc}}{3} \pm \frac{i_g(t)}{2} + i_{circ}(t)$$

where

$V_{dc}$	the dc-link voltage
$v_g(t) = k_{ac} \frac{V_{dc}}{2} \cos\left(\omega t - \frac{2\pi(k-1)}{3}\right)$	the ac grid voltage
$v_{CM}(t) = \sum_i \hat{v}_{CM,i} \cos(i3\omega t)$	the CM voltage
$I_{dc}$	the dc-link current
$i_g(t) = \hat{i}_g \cos\left(\omega t + \varphi - \frac{2\pi(k-1)}{3}\right)$	the ac grid current
$i_{circ}(t) = \sum_{i \neq l} \hat{i}_{circ,i} \cos\left(l2\omega t + \theta_l - \frac{2\pi(k-1)}{3}\right)$	the circulating current

with  $k \in \{1, 2, 3\}$  the phase number.



# POWER EQUATIONS (II)

**Generic formulation**  $p_{p/n}(t) = e_{p/n}(t)i_{p/n}(t)$

$$p_{p/n}(t) = \frac{V_{dc}I_{dc}}{6} \pm \frac{V_{dc}i_g(t)}{4} + \frac{V_{dc}i_{circ}(t)}{2} \mp \frac{I_{dc}(v_g(t) + v_{CM}(t))}{3} - \frac{i_g(t)(v_g(t) + v_{CM}(t))}{2} \mp i_{circ}(t)(v_g(t) + v_{CM}(t)) - \left( R_{br}i_{p/n}(t)^2 + L_{br}i_{p/n}(t)\frac{d}{dt}i_{p/n}(t) - M_{br}i_{p/n}(t)\frac{d}{dt}i_{n/p}(t) \right)$$

**Transformation**

$$\begin{bmatrix} p_{\Sigma} \\ p_{\Delta} \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ -1/2 & 1/2 \end{bmatrix} \begin{bmatrix} p_p \\ p_n \end{bmatrix}$$

►  $p_{\Sigma}$  only contains even harmonics

►  $p_{\Delta}$  only contains odd harmonics

$$p_{\Sigma}(t) = \frac{V_{dc}I_{dc}}{3} + V_{dc}i_{circ}(t) - i_g(t)(v_g(t) + v_{CM}(t)) - 2 \left[ R_{br}(i_p(t)^2 + i_n(t)^2) + L_{br} \left( i_p(t)\frac{d}{dt}i_p(t) + i_n(t)\frac{d}{dt}i_n(t) \right) - M_{br} \left( i_p(t)\frac{d}{dt}i_n(t) + i_n(t)\frac{d}{dt}i_p(t) \right) \right]$$

$$p_{\Delta}(t) = -\frac{V_{dc}i_g(t)}{8} + \frac{I_{dc}(v_g(t) + v_{CM}(t))}{6} + \frac{i_{circ}(t)(v_g(t) + v_{CM}(t))}{2}$$

## Reminder



Zero net energy balance  $\int_0^T p_{\Sigma} dt = 0$

**Insight provided**

- Circulating current optimization (in steady state!)
- Converter energy requirement
- Converter safe operating area (a bit optimistic though)

# CIRCULATING CURRENT OPTIMIZATION (I)

- ▶ First discussed in [10].
- ▶ Without passives!

## W/o circulating current

$$p_{\Sigma}(t) = \frac{I_{dc}V_{dc}}{3} - \hat{i}_g \cos(\omega t + \varphi)v_{CM}(t) - \frac{\hat{i}_g\hat{v}_g \cos(\varphi)}{2} - \frac{\hat{i}_g\hat{v}_g \cos(2\omega t + \varphi)}{2} + \underbrace{i_{circ}(t)}_{=0} V_{dc}$$
$$\Rightarrow I_{dc} = \frac{3\hat{i}_g\hat{v}_g \cos(\varphi)}{2V_{dc}}$$

## W/o common mode

$$p_{\Sigma}(t) = \frac{V_{dc}I_{dc}}{3} + V_{dc}i_{circ}(t) - \frac{\hat{i}_g\hat{v}_g \cos(\varphi)}{2} - \frac{\hat{i}_g\hat{v}_g \cos(2\omega t + \varphi)}{2} = 0$$
$$\Rightarrow I_{dc} = \frac{3\hat{i}_g\hat{v}_g \cos(\varphi)}{2V_{dc}}$$
$$\Rightarrow i_{circ}(t) = \frac{\hat{i}_g\hat{v}_g \cos(2\omega t + \varphi)}{2V_{dc}}$$


## W/ common mode

$$p_{\Sigma}(t) = -\hat{i}_g \cos(\omega t + \varphi)v_{CM}(t) - \frac{\hat{i}_g\hat{v}_g \cos(\varphi)}{2} - \frac{\hat{i}_g\hat{v}_g \cos(2\omega t + \varphi)}{2} + i_{circ}(t)V_{dc} + \frac{I_{dc}V_{dc}}{3} = 0$$
$$\Rightarrow I_{dc} = \frac{3\hat{i}_g\hat{v}_g \cos(\varphi)}{2V_{dc}}$$
$$\Rightarrow i_{circ}(t) = \frac{\hat{i}_g [2 \cos(\omega t + \varphi)v_{CM}(t) + \hat{v}_g \cos(2\omega t + \varphi)]}{2V_{dc}}$$

which means 2<sup>nd</sup> and 4<sup>th</sup> harmonics (at least!)


# CIRCULATING CURRENT OPTIMIZATION (II)

W/o common mode

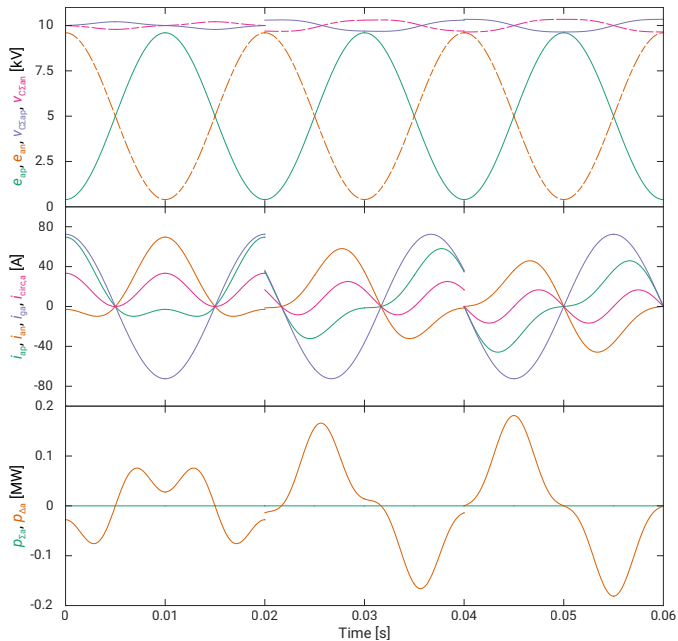

▲ MMC relevant waveforms without injection of the common mode voltage

W/ common mode

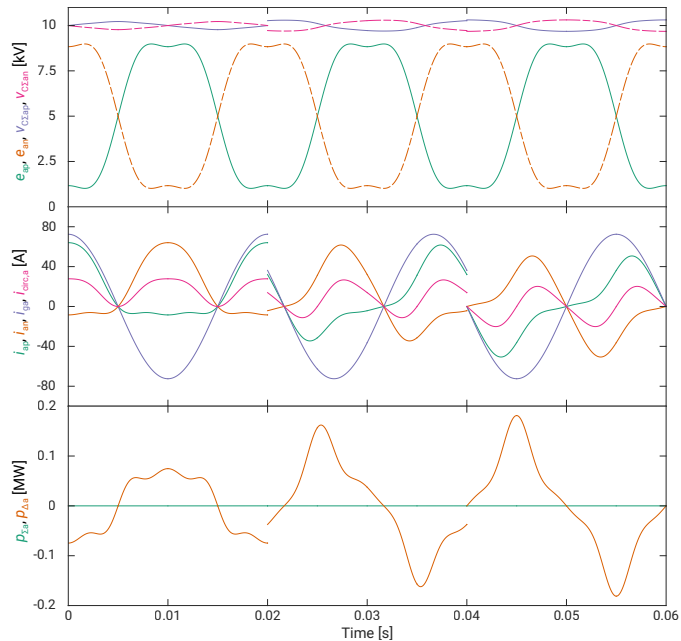

▲ MMC relevant waveforms with injection of the common mode voltage

# BRANCH CAPACITANCE SELECTION

## Branch energy ripples

$$\Delta W_{br,+} = \frac{1}{2} C_{br} v_{C\Sigma,max}^2 - \frac{1}{2} C_{br} v_{C\Sigma0}^{*2} \quad \rightarrow$$

$$\Delta W_{br,-} = \frac{1}{2} C_{br} v_{C\Sigma0}^{*2} - \frac{1}{2} C_{br} v_{C\Sigma,min}^2 \quad \rightarrow$$


$$C_{br} = \frac{2\Delta W_{br,+}}{[(1 + \varepsilon_{v_{C\Sigma}})^2 - 1] v_{C\Sigma0}^{*2}}$$

$$C_{br} = \frac{2\Delta W_{br,-}}{[1 - (1 - \varepsilon_{v_{C\Sigma}})^2] v_{C\Sigma0}^{*2}}$$

Energy requirement  $k_{ac} = 0.9$ ,  $v_{C\Sigma0}^* = V_{dc}$  and  $\varepsilon_{v_{C\Sigma}} = 10\%$

Case #	CM	2 <sup>nd</sup> (+ 4 <sup>th</sup> ) harmonic	Energy requirement [kJ/MVA]
1	○	○	45.6
2	○	●	46.3
3	●	○	27.2
4	●	●	24.8

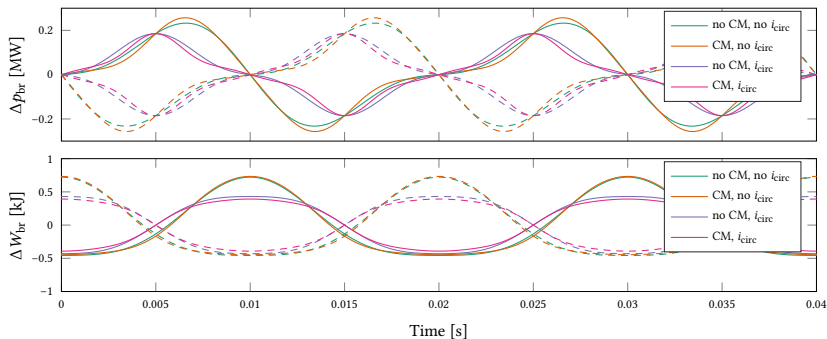Time domain waveforms  $\varphi = -\pi/2$  (worst case)



# MMC CONTROL METHODS

*Similarities and differences with other voltage source converters*


# MMC CONTROL LAYERS

## Two modes of operation:

1. Current source mode (also called inverter mode): transferring active power from the dc terminals to the ac terminals
2. Voltage source mode (also called rectifier mode): transferring active power from the ac terminals to the dc terminals

## Two sets of state variables:

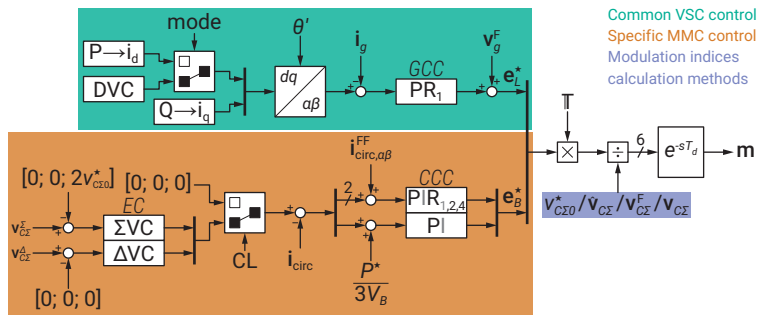1. **External** state variables (dc-link voltage, grid currents, etc.): knowledge from VSC control is reused
2. **Internal** state variables (capacitor voltages, circulating currents): specific MMC control




▲ Overall MMC control structure

# COMMON CONTROL LOOPS WITH OTHER VSC'S


## HVDC light

- ▶ 2-level or 3-level
- ▶ Series-connected StakPak IGBTs
- ▶ Low switching frequency (no multiplication factor since it is a macro switch)
- ▶ Large filters for grid code compliance

## SOA derivation

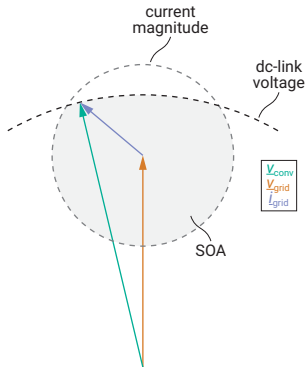


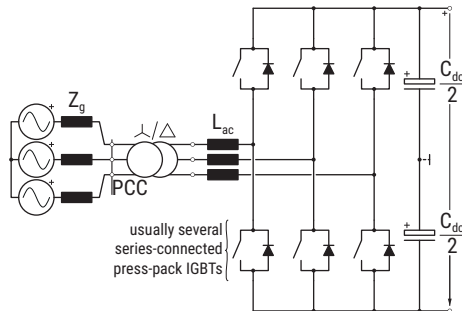Details about the control loops and their tuning can be found in: Amirnaser Yazdani and Reza Iravani. *Voltage-Sourced Converters in Power Systems: Modeling, Control, and Applications*. Wiley-IEEE Press, 2010



## P/Q diagram for the considered design


- ▶  $|V_{conv}| \leq V_{dc}/\sqrt{3}$  (CM injection)
- ▶  $I_{g,max} = 1$  kA (semi. devices)

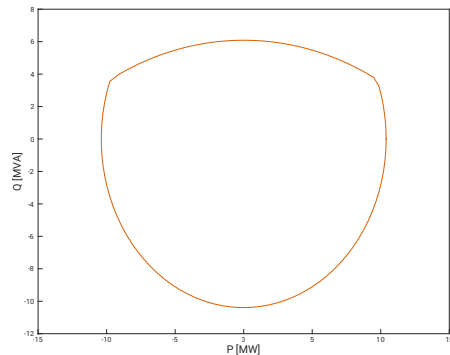

# COMMON CONTROL LOOPS WITH OTHER VSC'S: POSITIVE/NEGATIVE SEQUENCE EXTRACTION (PNSE)
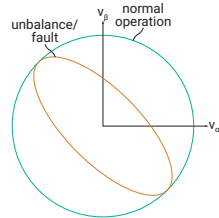
## Aim


- ▶ Retrieve the positive and negative grid voltage sequences (in order to handle grid unbalances/faults)



- ▲ Unbalanced grid conditions
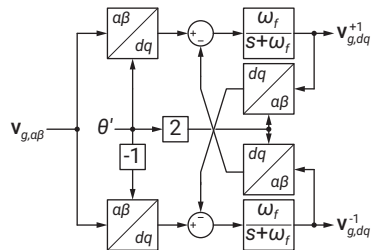
## Decoupled Double Synchronous Reference Frame (DDSRF) [12]


- ▶ Implementation in  $dq$  frame
- ▶ LPF to remove oscillations at twice the frequency



- ▲ Decoupled Double Synchronous Reference Frame
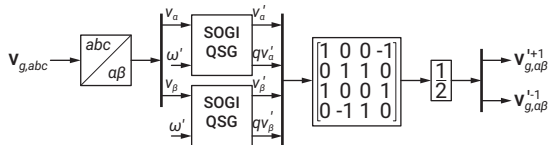
## Double Second-Order Generalized Integrator (DSOGI)

- ▶ Implementation in  $a\beta$  frame
- ▶ No additional filters required (with SOGI, LPF on  $\alpha$  and notch on  $\beta$ )



- ▲ Double Second-Order Generalized Integrator

October 23, 2019




# COMMON CONTROL LOOPS WITH OTHER VSC'S: PHASE-LOCKED LOOP (PLL)

## Aim

- ▶ Retrieve the grid frequency
- ▶ Retrieve the grid angle (esp. for control in  $dq$  frame)
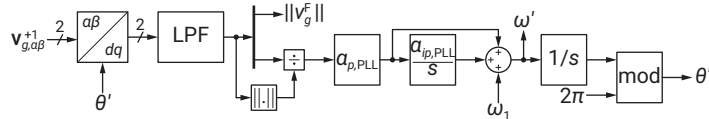
## $dq$ PLL

- ▶ Align with  $d$  axis by setting  $q$  component to 0
- ▶ Slow tuning to avoid instabilities




- ▲ Simple Phase Locked Loop scheme for 3-phase system

# COMMON CONTROL LOOPS WITH OTHER VSC'S: GRID CURRENT CONTROL (GCC)
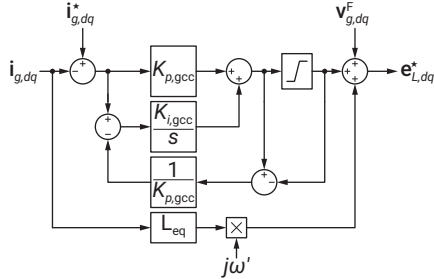
## PI in $dq$ frame


- ▶ Track dc components in a rotating reference frame
- ▶ Delay compensation by phase advance in the inverse Park transform



- ▲ Proportional Integral regulator in  $dq$  frame
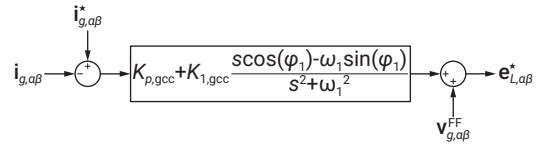
## PR in $\alpha\beta$ frame [13]

- ▶ Track ac components in a stationary reference frame
- ▶ Delay compensation with  $\varphi_h = h\omega_1 T_d$




- ▲ Proportional Resonant regulator in  $\alpha\beta$  frame


# COMMON CONTROL LOOPS WITH OTHER VSC'S: DIRECT VOLTAGE CONTROL (DVC)
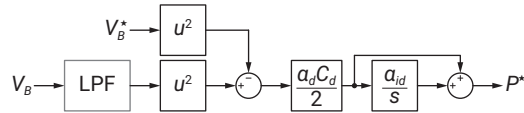
## Voltage control

- ▶ Based on the energy rather than the voltage information to be linear
- ▶ Sets the active power reference to the converter controlling the dc voltage
- ▶ Energy instead of voltage control in order to be linear



▲ DC voltage control

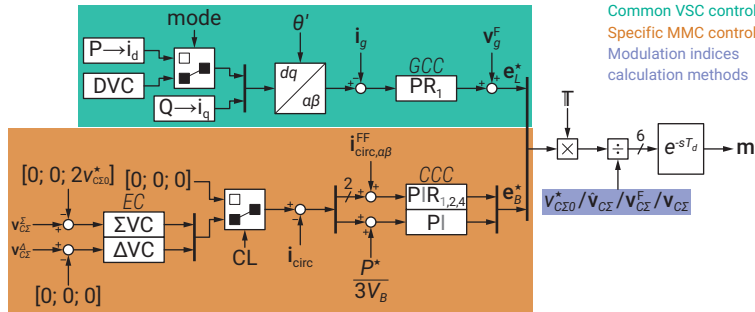


▲ Overall MMC control structure

# MMC SPECIFIC CONTROL LOOPS: ENERGY CONTROL (EC)


1. **Horizontal balancing:** shift energy between phase-legs using a CM current component
2. **Vertical balancing:** shift energy between branches using a fundamental ac current component
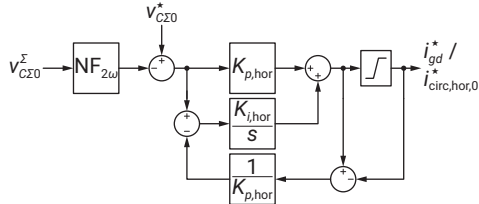
## Horizontal balancing

- Redistribution the CM component (i.e., the dc current for a dc/ac MMC) with the zero component




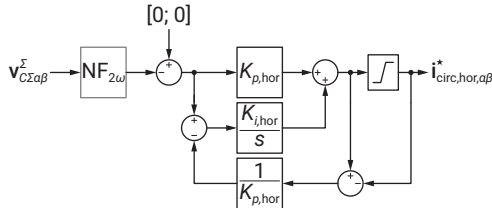- Optimization of the capacitor voltage ripple with the  $\alpha\beta$  components in case notch filters are disabled



## Vertical balancing


- Using a fundamental ac component

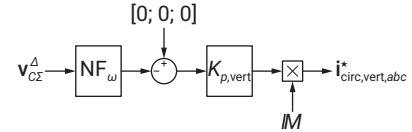

- Major contribution by [14] to cancel the circulating currents from vertical balancing at the dc terminals

$$M = \begin{bmatrix} \cos(\theta_L) & \frac{-\sin(\theta_L)}{\sqrt{3}} & \frac{\sin(\theta_L)}{\sqrt{3}} \\ \frac{\sin(\theta_L - 2\pi/3)}{\sqrt{3}} & \cos(\theta_L - 2\pi/3) & \frac{-\sin(\theta_L - 2\pi/3)}{\sqrt{3}} \\ \frac{-\sin(\theta_L + 2\pi/3)}{\sqrt{3}} & \frac{\sin(\theta_L + 2\pi/3)}{\sqrt{3}} & \cos(\theta_L + 2\pi/3) \end{bmatrix}$$

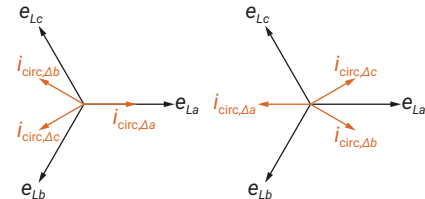where  $\theta_L$  is the load current angle




# MMC SPECIFIC CONTROL LOOPS: CIRCULATING CURRENT CONTROL (CCC)


It has been shown in the power equations that the circulating current contains multiple low harmonic frequency components:

- ▶ **DC:** power exchange with the dc terminal, i.e., horizontal balancing
- ▶ **Fundamental AC:** vertical balancing
- ▶ **Second harmonic:** main component to be suppressed / controlled for capacitor voltage ripple reduction in steady-state
- ▶ **Fourth harmonic:** for capacitor voltage ripple reduction in steady-state with CM injection

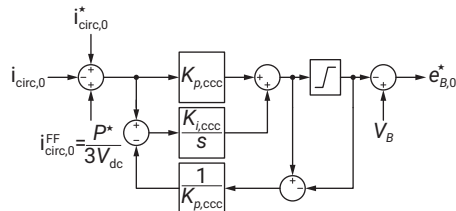PI and multiple R controllers are the best suited candidates to deal with these multiple harmonic components [15]



▲ Zero-sequence control

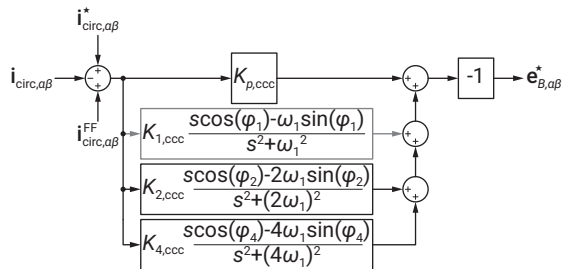


▲  $\alpha\beta$ -sequence control
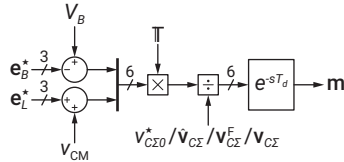
# MODULATION INDEX CALCULATION METHODS (I): DIRECT MODULATION

- ▶ The modulation indices are calculated from the *desired* dc average value
- ▶ The energy controllers **are disabled**
- ▶ The odd harmonics and integrator on dc component in the circulating current control **are disabled**
- ▶ Rely on self balancing of the branch energies [16]

$$m_p = \frac{V_B/2 - e_B^*/2 - e_L^*}{V_{C\Sigma 0}^*}$$
$$m_n = \frac{V_B/2 - e_B^*/2 + e_L^*}{V_{C\Sigma 0}^*}$$




- ▲ Direct modulation principles

# MODULATION INDEX CALCULATION METHODS (II): OPEN-LOOP CONTROL

- ▶ The modulation indices are calculated from *estimates* of the summed branch capacitors in steady-state [17]
- ▶ The energy controllers **are disabled**
- ▶ The odd harmonics and integrator on dc component in the circulating current control **are disabled**
- ▶ Self energy balance achieved [18]

$$m_p = \frac{V_B/2 - e_B^*/2 - e_L^*}{\hat{v}_{C\Sigma p}}$$
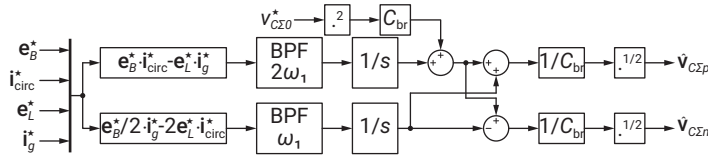
$$m_n = \frac{V_B/2 - e_B^*/2 + e_L^*}{\hat{v}_{C\Sigma n}}$$




▲ Open-loop control
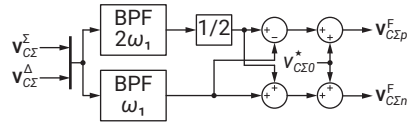
# MODULATION INDEX CALCULATION METHODS (III): HYBRID VOLTAGE CONTROL

- ▶ The modulation indices are calculated from *filtered values* of the summed branch capacitors measurements
- ▶ The energy controllers **are disabled**
- ▶ The odd harmonics and integrator on dc component in the circulating current control **are disabled**
- ▶ Self energy balance achieved [19]

$$m_p = \frac{V_B/2 - e_B^*/2 - e_L^*}{v_{C\Sigma p}^F}$$
$$m_n = \frac{V_B/2 - e_B^*/2 + e_L^*}{v_{C\Sigma n}^F}$$



▲ Hybrid voltage control



## MODULATION INDEX CALCULATION METHODS (IV): CLOSED-LOOP CONTROL

---

- ▶ The modulation indices are calculated from the *actual measurements* of the summed branch capacitors
- ▶ The energy controllers **are enabled**
- ▶ The odd harmonics in the circulating current control **are enabled**




This is by far the most complex control implementation, but at the same time the only method suitable for reaching the best dynamics.


# MMC CONTROL PERFORMANCE BENCHMARK

*Inverter and Rectifier modes of operation...*


# CURRENTS IN INVERTER MODE

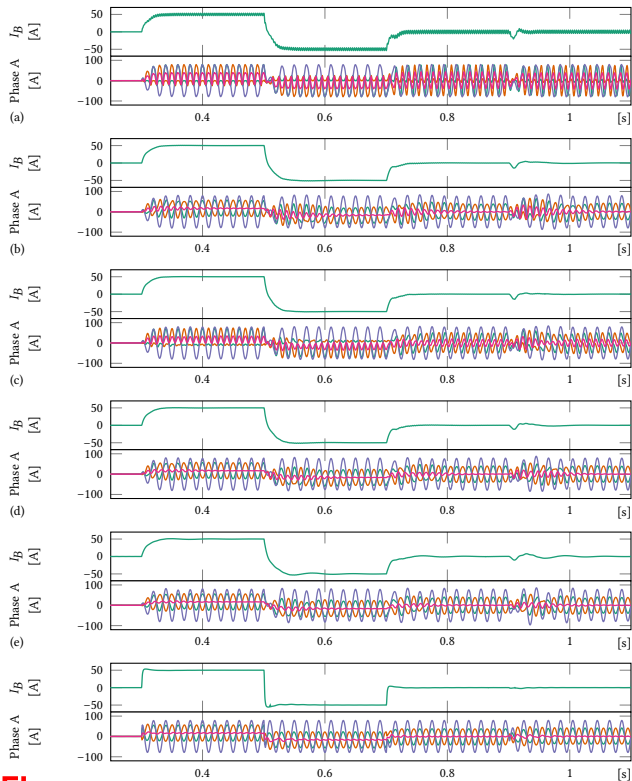


## No CCC

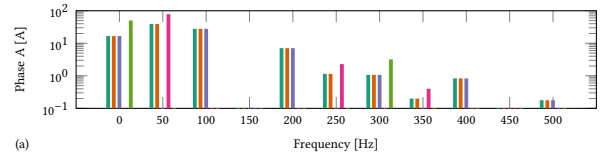


## CCSC / CCC dc circ

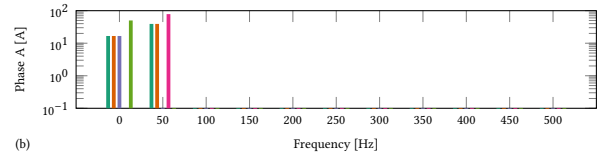


## CCSC / CCC + 2nd circ inj

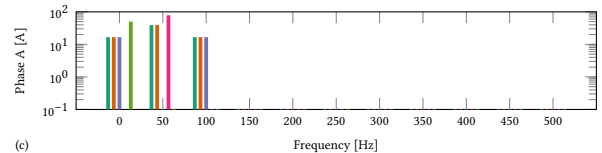


# CURRENTS IN INVERTER MODE

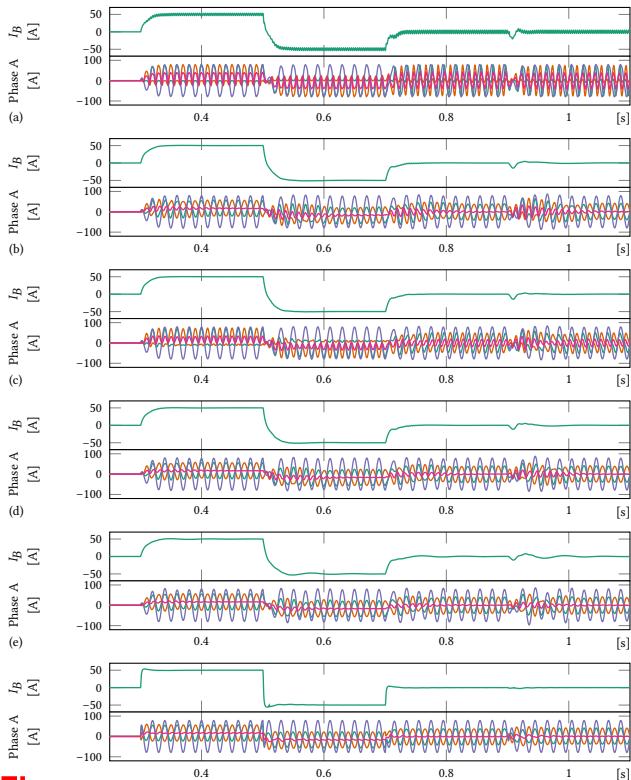


## No CCC

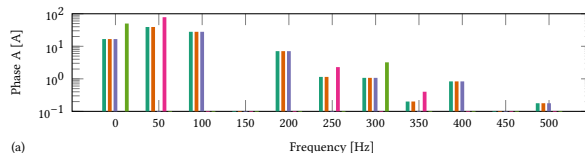

## CCSC / CCC dc circ






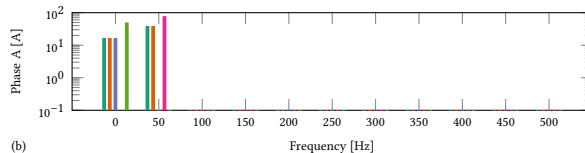


## CCSC / CCC + 2nd circ inj

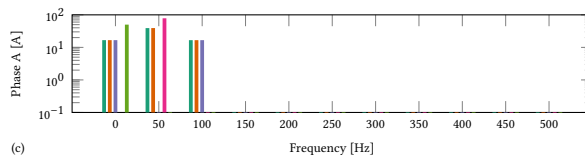

➔ CCSC / CCC **mandatory** to cancel low order harmonics

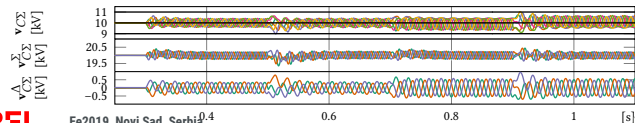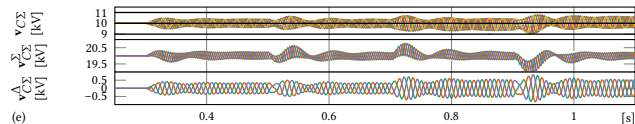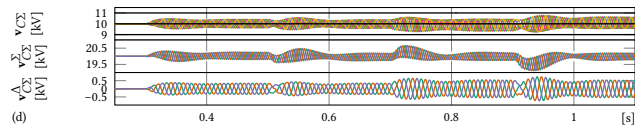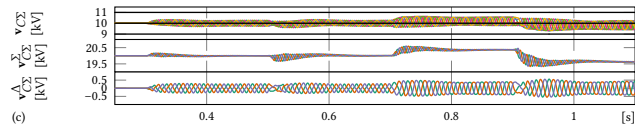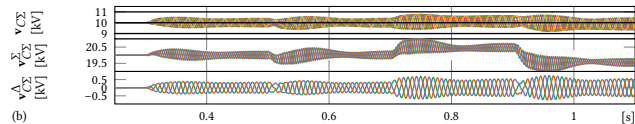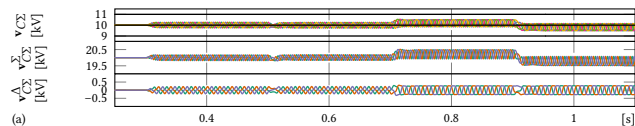
# SUMMED CAPACITOR VOLTAGES IN INVERTER MODE



## Few comments:

- ▶ With the direct modulation,  $v_{C\Sigma}^{\Sigma}$  is not properly controller on reactive power steps (it settles to a value close to  $V_{C\Sigma 0}^*$ )
- ▶ With the direct modulation w/o CCSC, the energies are shifted between the phase-legs (thanks to the uncontrolled circulating current)  $\Rightarrow$  smallest capacitor voltage ripples are observed
- ▶ The self-balancing is more performant than the closed-loop energy balancing (it takes 3 fundamental periods to rebalance the voltages), however consequence is that  $v_{C\Sigma}^{\Sigma}$  dynamics are sluggish (increased voltage variation & lightly damped oscillatory response)
- ▶ BPFs tuning is affecting the performance of the hybrid voltage control method
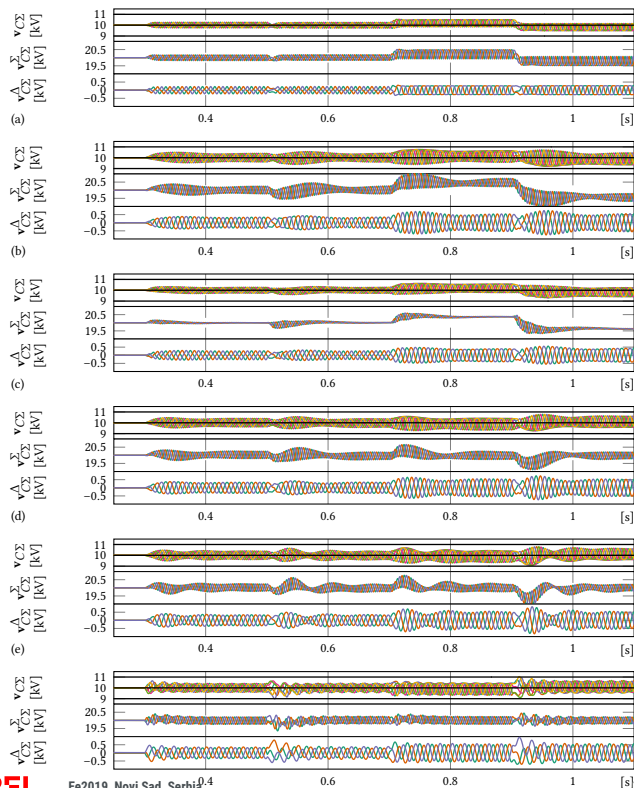
# SUMMED CAPACITOR VOLTAGES IN INVERTER MODE




## Few comments:

- ▶ With the direct modulation,  $v_{C\Sigma}^*$  is not properly controller on reactive power steps (it settles to a value close to  $V_{C\Sigma 0}^*$ )
- ▶ With the direct modulation w/o CCSC, the energies are shifted between the phase-legs (thanks to the uncontrolled circulating current)  $\Rightarrow$  smallest capacitor voltage ripples are observed
- ▶ The self-balancing is more performant than the closed-loop energy balancing (it takes 3 fundamental periods to rebalance the voltages), however consequence is that  $v_{C\Sigma}^*$  dynamics are sluggish (increased voltage variation & lightly damped oscillatory response)
- ▶ BPFs tuning is affecting the performance of the hybrid voltage control method

$\Rightarrow$  the branch energy control offers mitigated performances


# PQ TRACKING IN INVERTER MODE

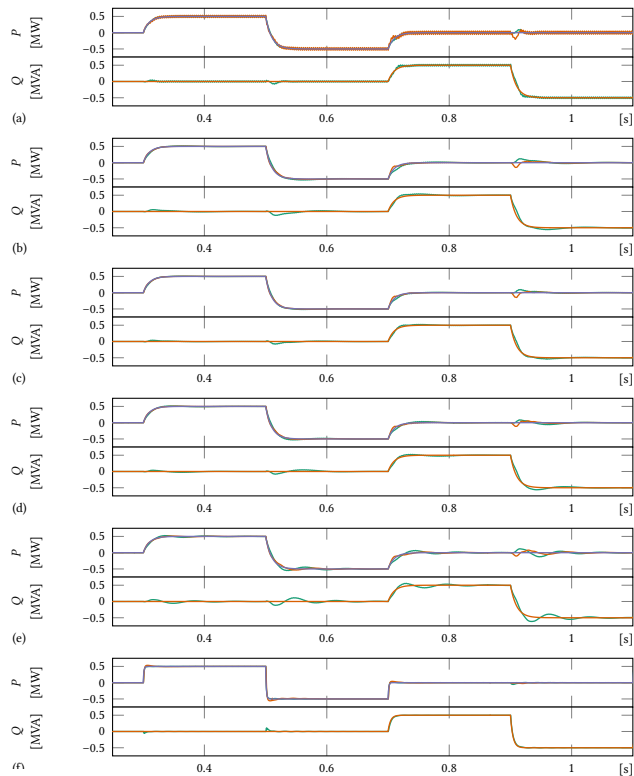

## Few comments:

- ▶ LPF filter bandwidth 100 rad/s for self-balancing methods
- ▶ Low-order harmonics with direct modulation w/o CCSC
- ▶ Lightly damped oscillatory response with the hybrid voltage control method
- ▶ Dynamics are increased to 300 rad/s for the closed-loop control method without controller optimization
- ▶ Power decoupling is not perfect

# PQ TRACKING IN INVERTER MODE

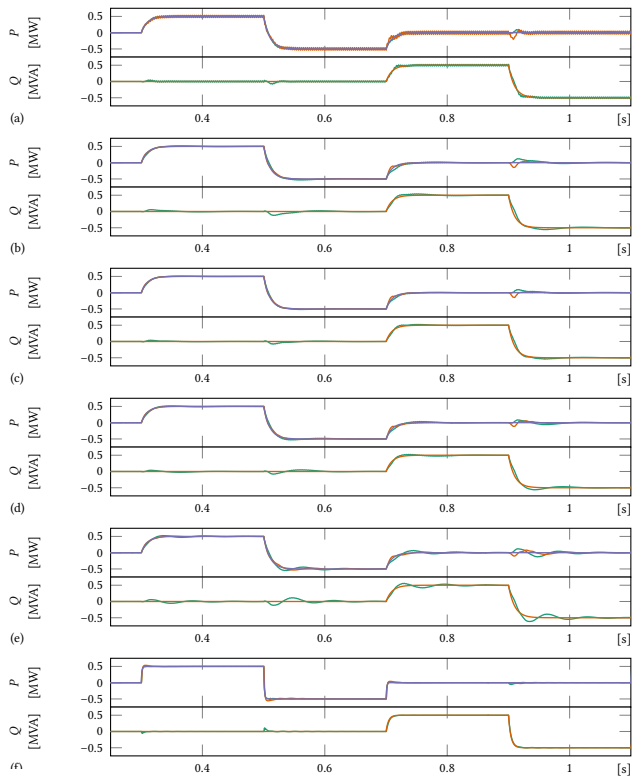

## Few comments:


- ▶ LPF filter bandwidth 100 rad/s for self-balancing methods
- ▶ Low-order harmonics with direct modulation w/o CCSC
- ▶ Lightly damped oscillatory response with the hybrid voltage control method
- ▶ Dynamics are increased to 300 rad/s for the closed-loop control method without controller optimization
- ▶ Power decoupling is not perfect

⇒ clear advantage of the closed-loop control method for highly dynamic applications




# OPERATION IN RECTIFIER MODE

## Open-circuit


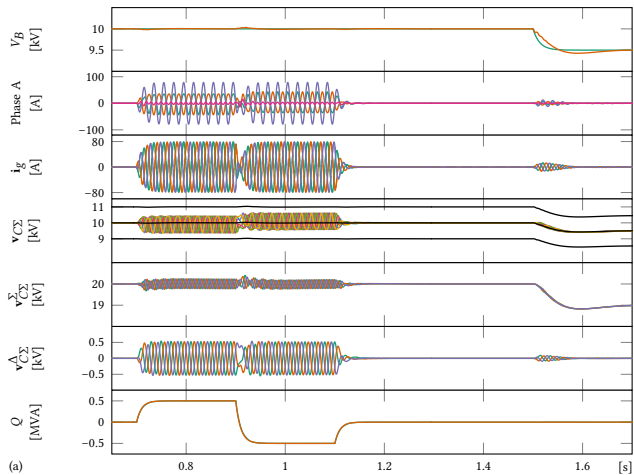


► Circulating currents are canceling out at the terminals


## Current source

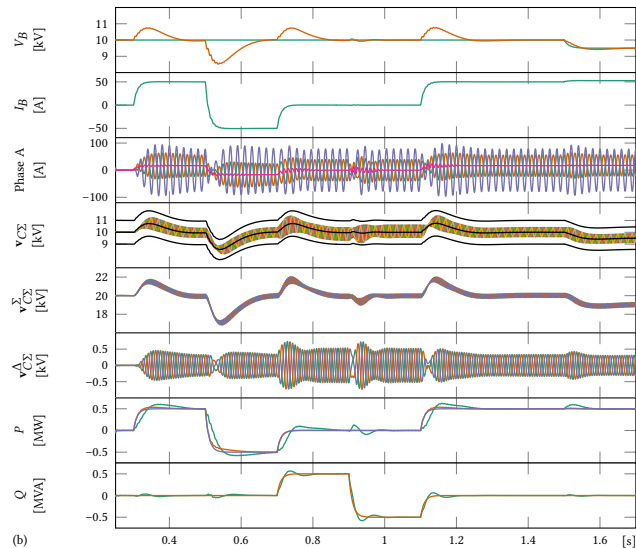





# CONTROL METHOD PERFORMANCE RATING

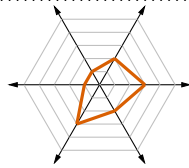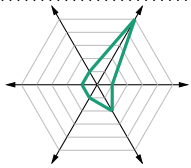

Energy controllers

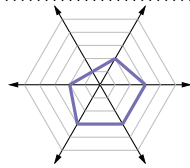

Low order harmonics at terminals

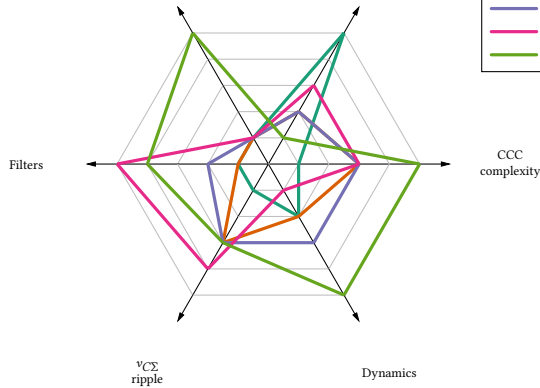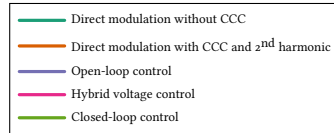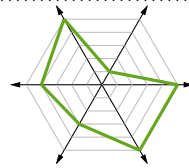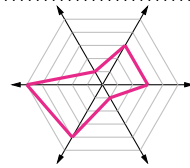

⇒ the final choice depends on the application requirements / acceptable compromises between complexity and performance


# MMC MODULATION METHODS

*Variety of options are available...*
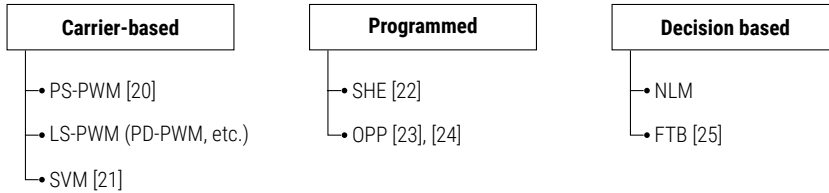
# CLASSIFICATION

---

- ▶ Choice and motivations for the choice completely different for an HVDC design compared to MVDC!




# NUMBER OF VOLTAGE LEVELS PER BRANCH

- ▶ Assuming no required action from circulating current control!
- ▶ Unipolar cells as base case

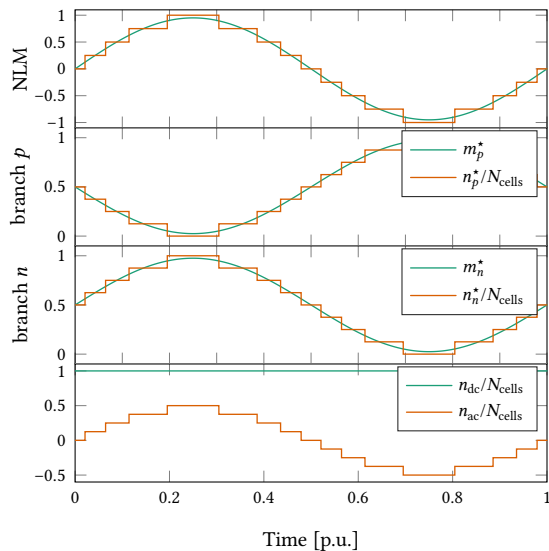
## $N + 1$ modulation

- ▶ Synchronous switching of the branches within the same phase-leg


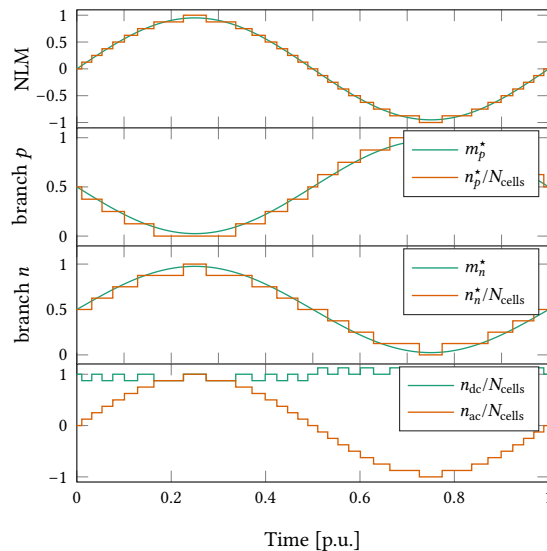
## $2N + 1$ modulation


- ▶ Asynchronous switching of the branches within the same phase-leg



# MAXIMUM LEVEL OF CONTROL DECENTRALIZATION


## Branch level modulation

- ▶ Each branch handled separately

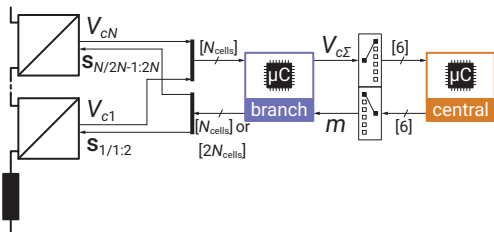

## Cell level modulation


- ▶ Each cell has its own modulator

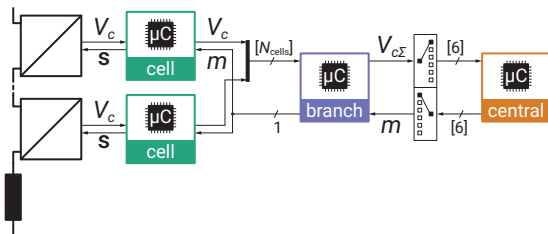

**Remark**  $\mu\text{C}$  denotes either a microcontroller, an FPGA, or a combination of both.
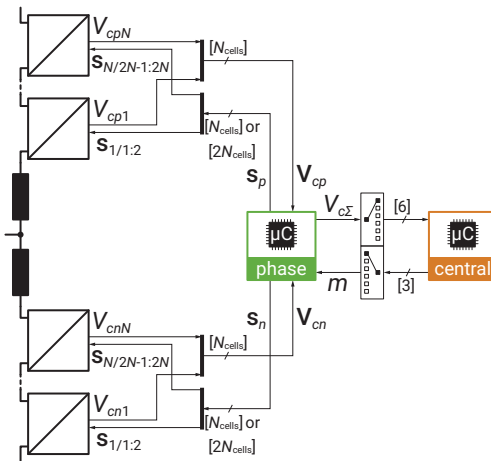
## Phase-leg level modulation

- ▶ Aim at improving ac-side spectrum and unlocking full modulation method harmonic performance
- ▶ Compromises in the circulating current control
- ▶ SHE / OPP / SVM with  $2N_{\text{cells}} + 1$  modulation







# CARRIER-BASED MODULATION

## PD-PWM

- ▶ Phase switching pattern with high harmonic at switching frequency
- ▶ Line switching pattern with low harmonic peak
- ▶ Lower THD
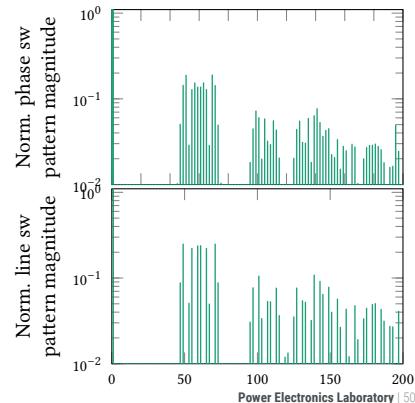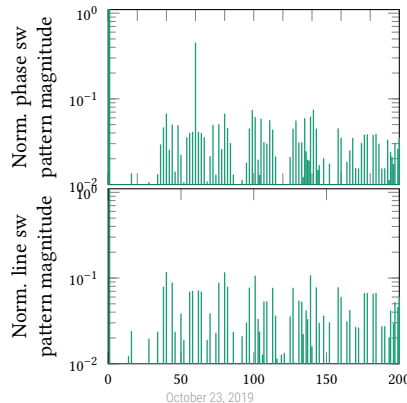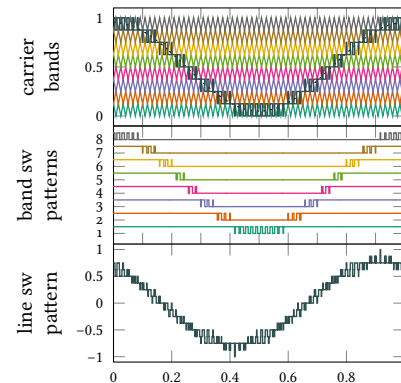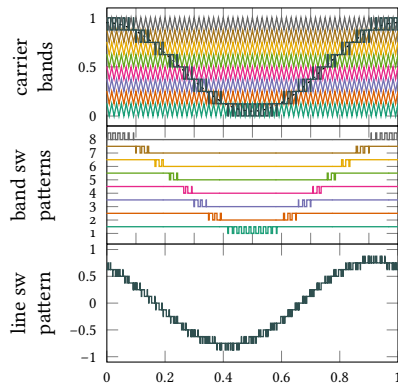
## APOD-PWM

- ▶ Phase switching pattern without strong harmonic at switching frequency
- ▶ Line switching pattern with distinctive carrier side bands
- ▶ Higher THD






## Selective Harmonic Elimination

- ▶ Cancel one harmonic per switching angle plus 1 angle to set the modulation index over a quarter fundamental period
- ▶ Results in continuous switching angles  $\Rightarrow$  linear grid current controller
- ▶  $2N + 1$  modulation preferred when it comes to the circulating current control [26]

## Optimized Pulse Patterns

- ▶ Cancel low order harmonics and incorporate user settable constraints on individual harmonics for a given number of switching angles over a quarter fundamental period
- ▶ Results in discontinuous switching angles  $\Rightarrow$  non-linear grid current controller
- ▶ Different circulating current control methods for  $N + 1$  and  $2N + 1$  modulation [24]

## Results with OPPs from [24]

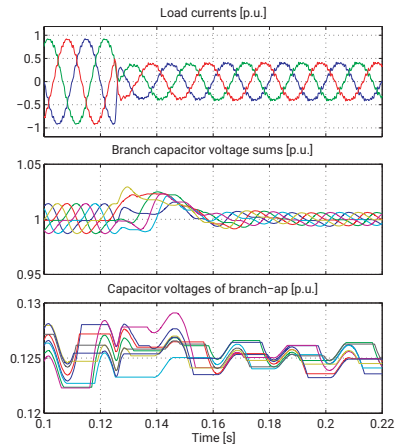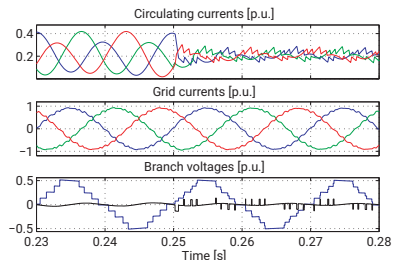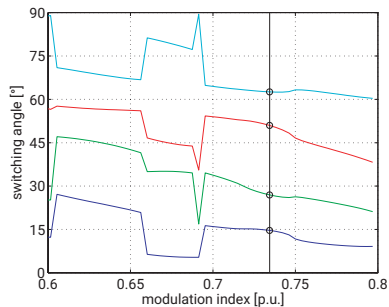



$\Rightarrow$  maximum performance without compromising the switching frequency



# SORTING ALGORITHMS

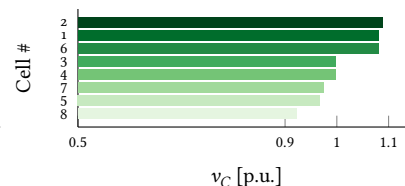
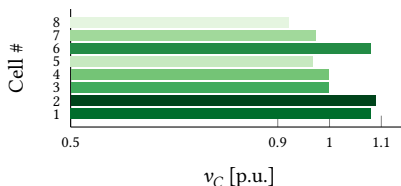
## Principle

- ▶ Depending on the branch current polarity (and switching state), the inserted cells are either charged or discharged



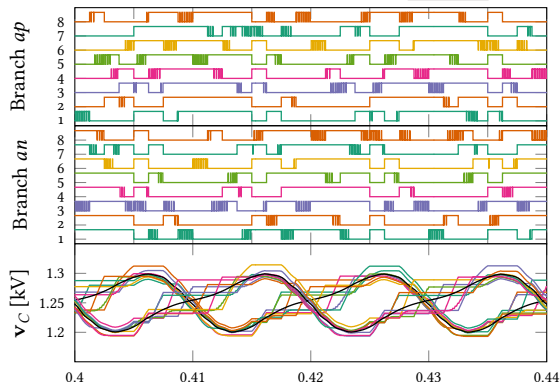
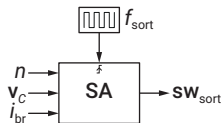
## Simple sorting

- ▶ The sorting algorithm is triggered at  $f_{\text{sort}}$
- ▶ All switching signals can be modified


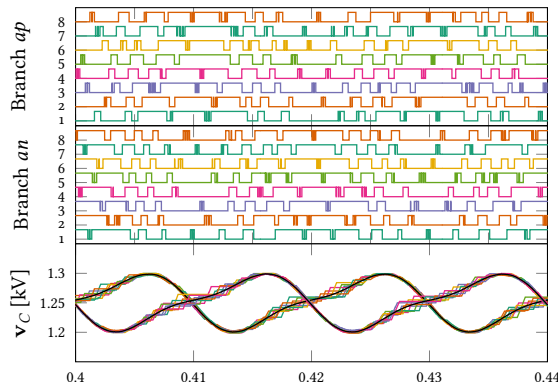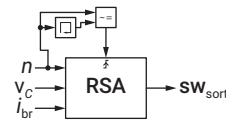
## Restricted sorting [27]


- ▶ The sorting algorithm is triggered when a switching transition occur
- ▶ No additional switching events!



# ENHANCEMENTS
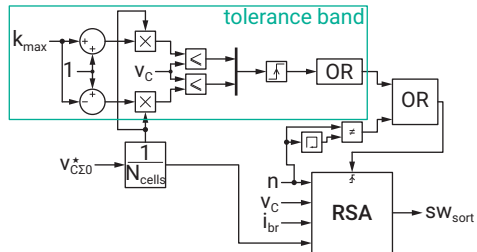
## Tolerance band [25]

- ▶ With very low switching frequency, the restricted algorithm cannot maintain the cell capacitor voltages within their limits
- ▶ Another condition forces the swapping of two cells when the bands are exceeded



▲ Restricted Sorting Algorithm with tolerance band



# CELL BALANCING WITH DISTRIBUTED MODULATORS

## Principle

- ▶ The proportional control action cancel out at the branch level

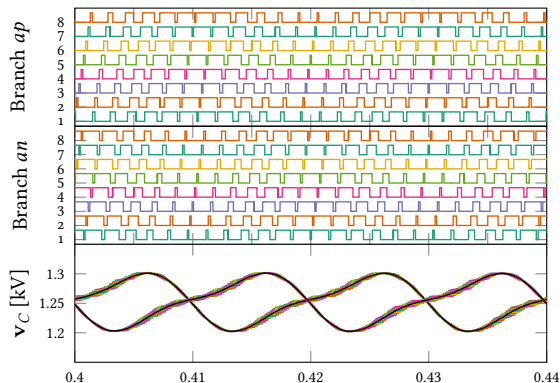
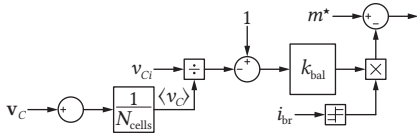
## Branch average based

- ▶ The *instantaneous* summed branch capacitor average is sent by the branch controller [20]



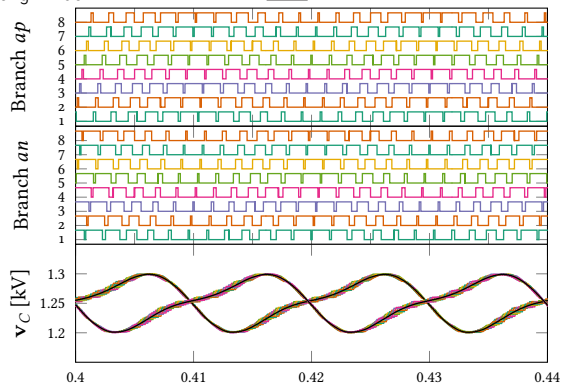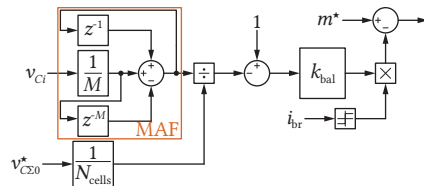
## Moving average filter based

- ▶ The summed branch capacitor average is retrieved by a moving average filter with a long window



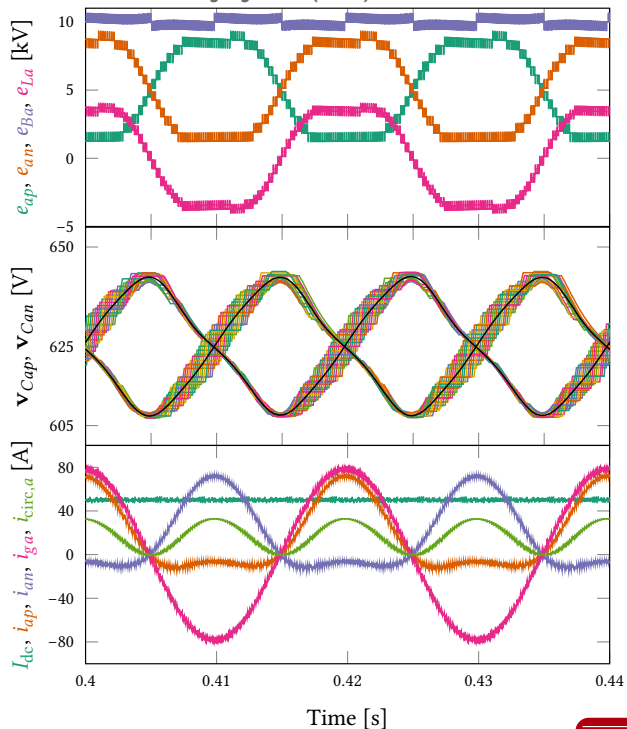
# HIGH PERFORMANCE PWM MODULATION METHODS

Enhanced restricted sorting algorithm ( $N + 1$ )



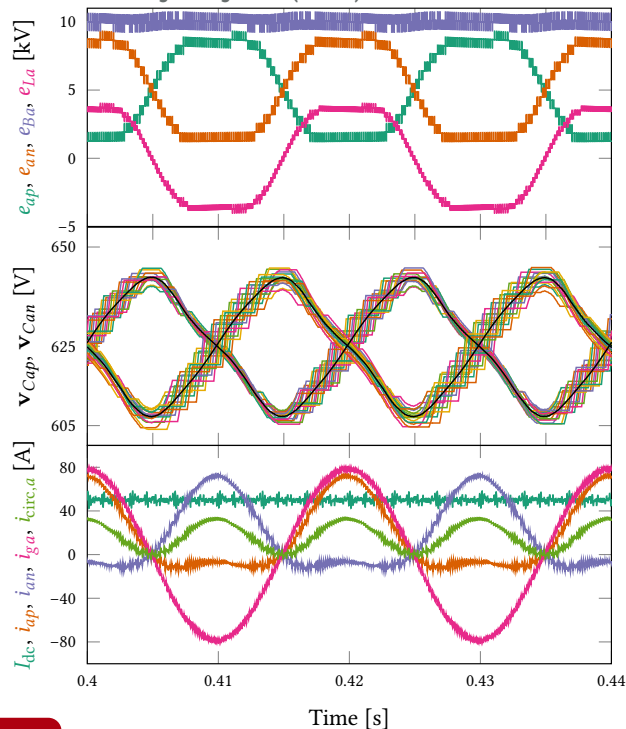
PS-PWM with moving average filter ( $2N + 1$ )




$f_{sw,cell} = 375 \text{ Hz}$
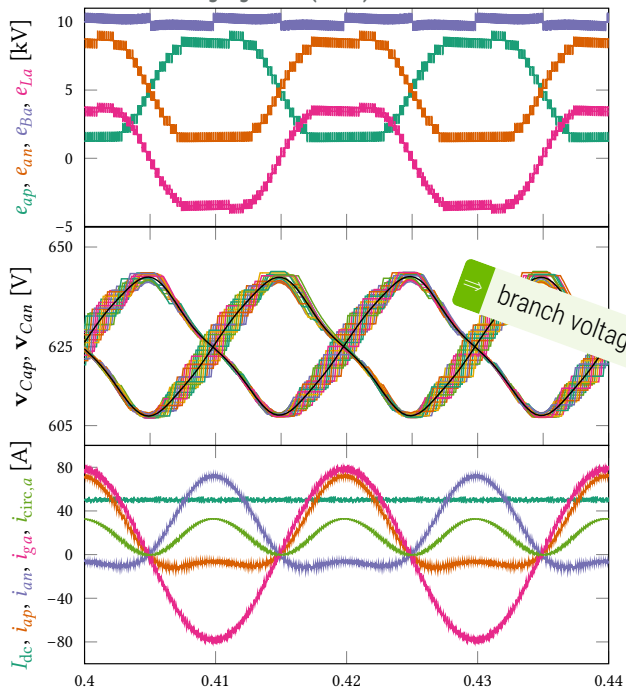
# HIGH PERFORMANCE PWM MODULATION METHODS

Enhanced restricted sorting algorithm ( $N + 1$ )



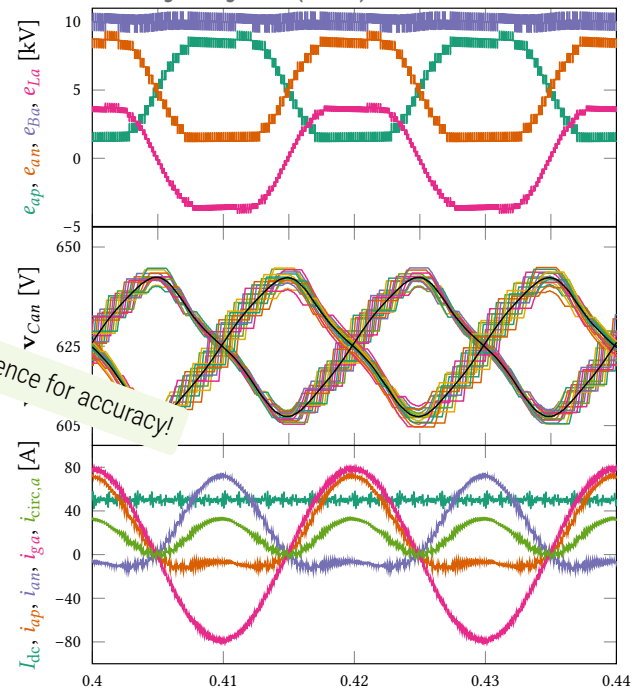PS-PWM with moving average filter ( $2N + 1$ )



branch voltage reference for accuracy!

$$f_{sw,cell} = 375 \text{ Hz}$$

# COFFEE BREAK

*Well deserved...*

## Before the Coffee

### 1) Introduction and Motivation - MVDC

- ▶ MVDC Applications and Technologies
- ▶ MVDC Conversion Technologies
- ▶ Solid State Transformers

### 2) Modular Multilevel Converter Fundamentals

- ▶ Operating principles
- ▶ Modeling and Control
- ▶ Performance Benchmark

### 3) MMC Modulation Methods

- ▶ Carrier-based PWM, SVPWM
- ▶ Centralized vs. Distributed PWM
- ▶ SHE and OPPs



## After the Coffee

### 4) High Power MMCs

- ▶ Branch Energy Balancing
- ▶ Power Extension
- ▶ Pulse Width Modulation

### 5) High Power DC-DC Conversion

- ▶ MMC-based DAB Topologies
- ▶ Quasi-Two-Level Converters
- ▶ Design and Control

### 6) MMC Research Platform

- ▶ MMC system level design
- ▶ MMC RT-HIL development
- ▶ Questions and Discussion


⇒ Tutorial pdf can be downloaded from: (Source: [https://pe1.epfl.ch/publications\\_talks\\_en](https://pe1.epfl.ch/publications_talks_en))

# MMC POWER CAPACITY EXTENSION

*Boosting the power through branch paralleling...*



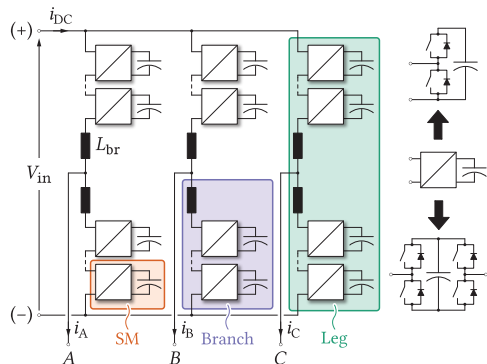
# MODULAR MULTILEVEL CONVERTER POWER SCALING




▲ Modular Multilevel Converter

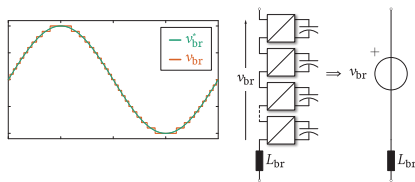- ▶ Series connection of HB/FB Submodules (SMs)
- ▶ Flexible in terms of voltage scaling
- ▶ High quality voltage waveforms




▲ Branch equivalent circuit with its voltage waveform
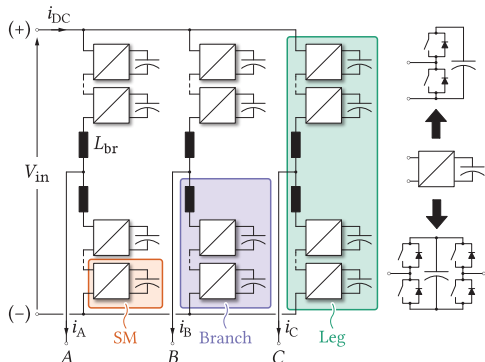
# MODULAR MULTILEVEL CONVERTER POWER SCALING




▲ Modular Multilevel Converter

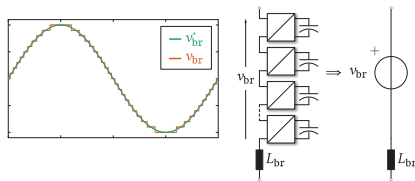- ▶ Series connection of HB/FB Submodules (SMs)
- ▶ Flexible in terms of voltage scaling
- ▶ High quality voltage waveforms



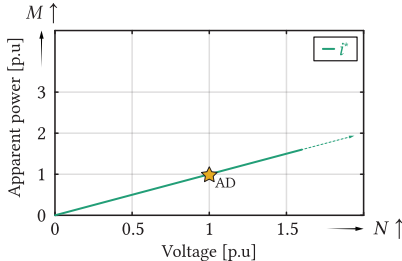▲ Branch equivalent circuit with its voltage waveform




▲ MMC power scaling

- ▶ Existing SM design is assumed




▲ MMC branch voltage scaling

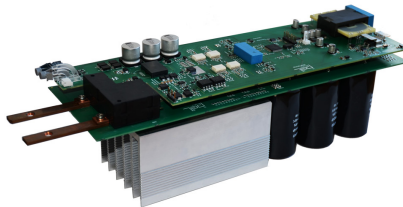


▲ SM designed at PEL
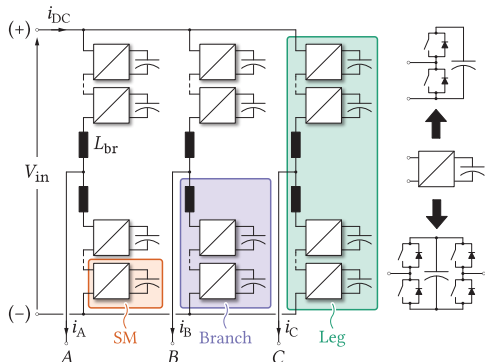
# MODULAR MULTILEVEL CONVERTER POWER SCALING




▲ Modular Multilevel Converter

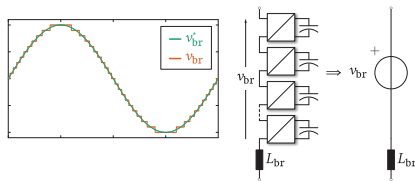- ▶ Series connection of HB/FB Submodules (SMs)
- ▶ Flexible in terms of voltage scaling
- ▶ High quality voltage waveforms




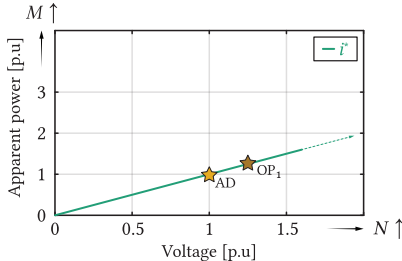▲ Branch equivalent circuit with its voltage waveform




▲ MMC power scaling

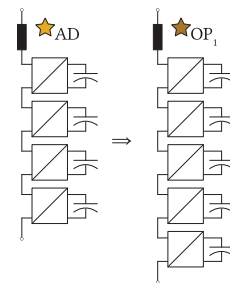- ▶ Existing SM design is assumed
- ▶ **Linear S=f(V) change for a given current rating**




▲ MMC branch voltage scaling

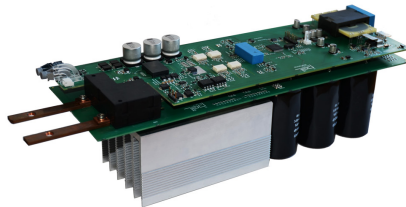


▲ SM designed at PEL
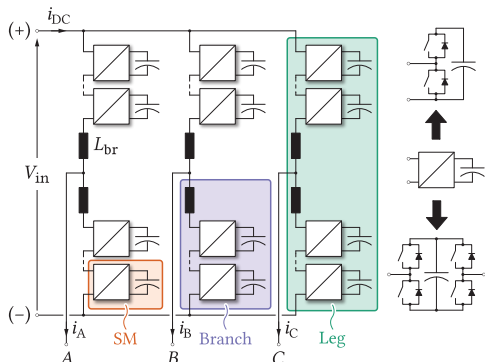
# MODULAR MULTILEVEL CONVERTER POWER SCALING




▲ Modular Multilevel Converter

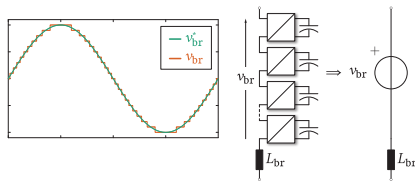- ▶ Series connection of HB/FB Submodules (SMs)
- ▶ Flexible in terms of voltage scaling
- ▶ High quality voltage waveforms




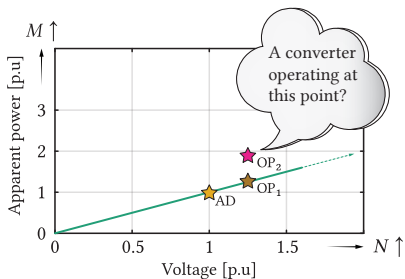▲ Branch equivalent circuit with its voltage waveform




▲ MMC power scaling

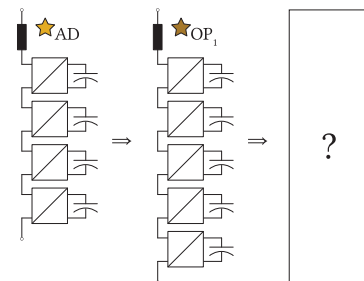- ▶ Existing SM design is assumed
- ▶ **Linear S=f(V) change for a given current rating**




▲ MMC branch voltage scaling

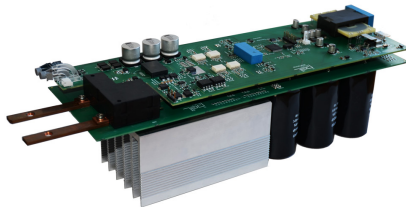


▲ SM designed at PEL
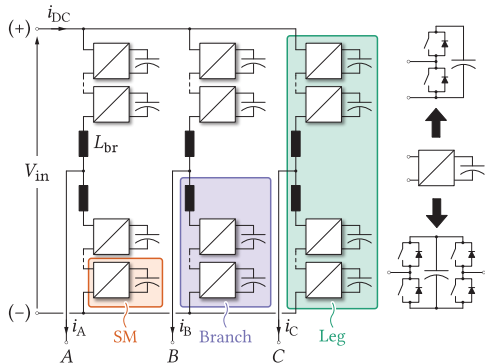
# MODULAR MULTILEVEL CONVERTER POWER SCALING




▲ Modular Multilevel Converter

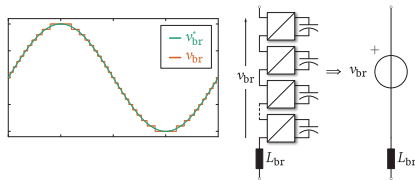- ▶ Series connection of HB/FB Submodules (SMs)
- ▶ Flexible in terms of voltage scaling
- ▶ High quality voltage waveforms




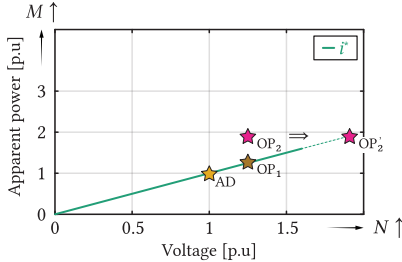▲ Branch equivalent circuit with its voltage waveform




▲ MMC power scaling

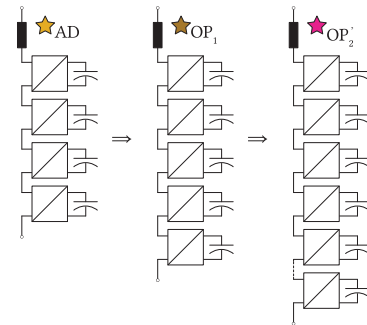- ▶ Existing SM design is assumed
- ▶ **Linear S=f(V) change for a given current rating**




▲ MMC branch voltage scaling

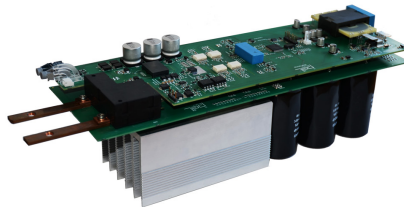


▲ SM designed at PEL
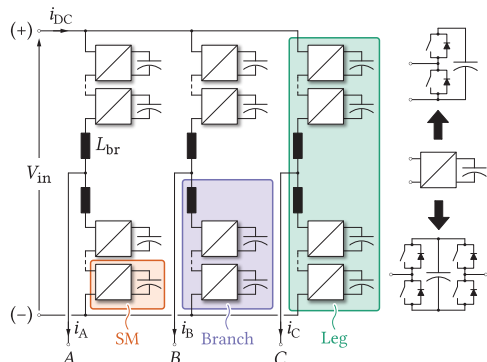
# MODULAR MULTILEVEL CONVERTER POWER SCALING




▲ Modular Multilevel Converter

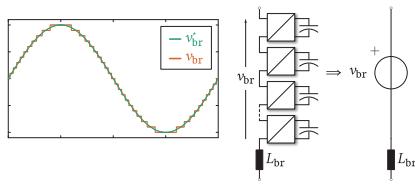- ▶ Series connection of HB/FB Submodules (SMs)
- ▶ Flexible in terms of voltage scaling
- ▶ High quality voltage waveforms




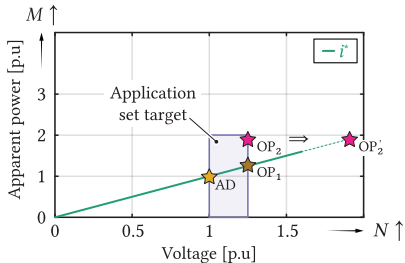▲ Branch equivalent circuit with its voltage waveform




▲ MMC power scaling

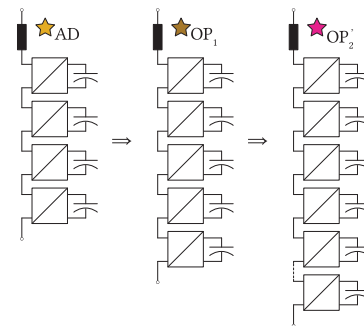- ▶ Existing SM design is assumed
- ▶ **Linear S=f(V) change for a given current rating**




▲ MMC branch voltage scaling

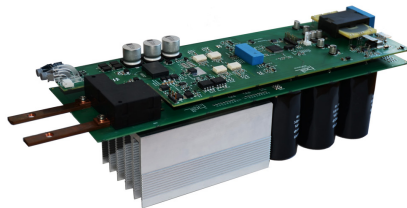


▲ SM designed at PEL
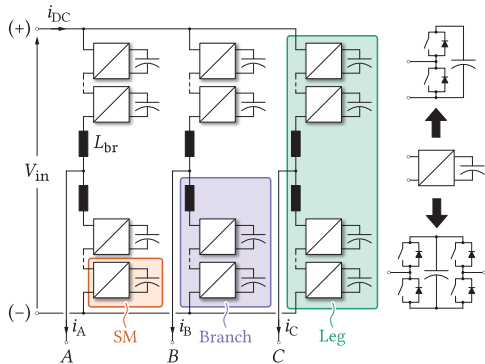
# MODULAR MULTILEVEL CONVERTER POWER SCALING




▲ Modular Multilevel Converter

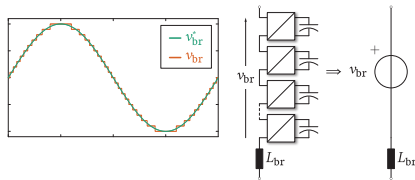- ▶ Series connection of HB/FB Submodules (SMs)
- ▶ Flexible in terms of voltage scaling
- ▶ High quality voltage waveforms




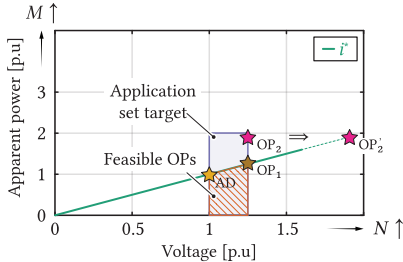▲ Branch equivalent circuit with its voltage waveform




▲ MMC power scaling

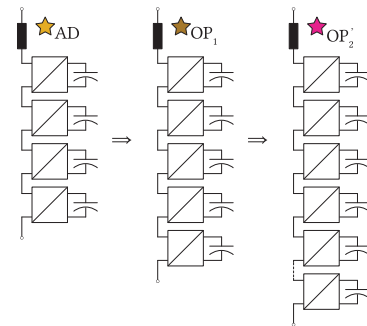- ▶ Existing SM design is assumed
- ▶ **Linear  $S=f(V)$  change for a given current rating**




▲ MMC branch voltage scaling

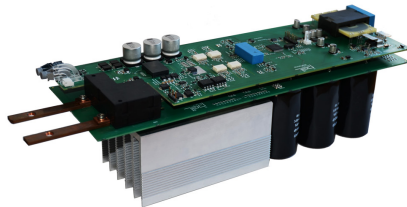


▲ SM designed at PEL
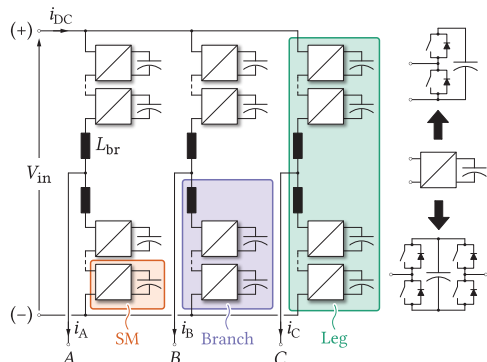
# MODULAR MULTILEVEL CONVERTER POWER SCALING




▲ Modular Multilevel Converter

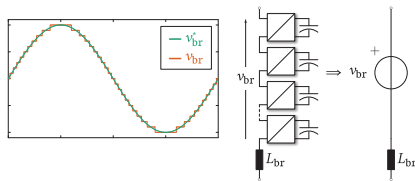- ▶ Series connection of HB/FB Submodules (SMs)
- ▶ Flexible in terms of voltage scaling
- ▶ High quality voltage waveforms




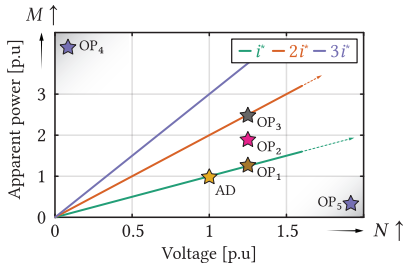▲ Branch equivalent circuit with its voltage waveform




▲ MMC power scaling

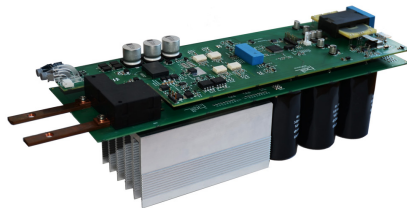- ▶ Existing SM design is assumed
- ▶ **Linear**  $S=f(V)$  change **for a given current rating**
- ▶ Current capacity  $\uparrow \Rightarrow$  new characteristics



▲ SM designed at PEL

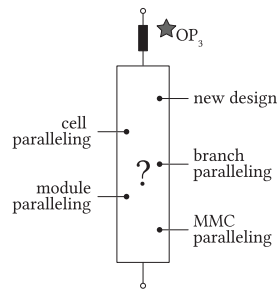


▲ MMC branch voltage scaling


? How to increase current capacity?



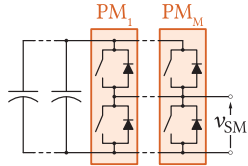
# COMMON MMC CURRENT CAPACITY INCREASE METHODS



▲ Paralleling semiconductor modules

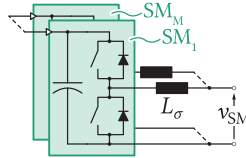


▲ Paralleling SMs

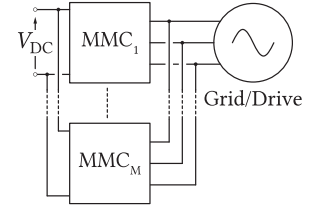


▲ Paralleling converters

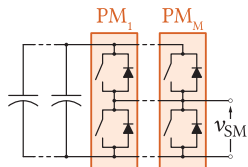
# COMMON MMC CURRENT CAPACITY INCREASE METHODS




▲ Paralleling semiconductor modules

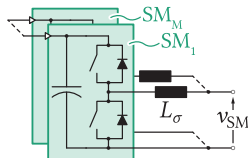

▲ Paralleling SMs

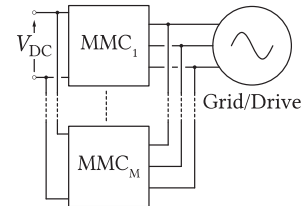


▲ Paralleling converters

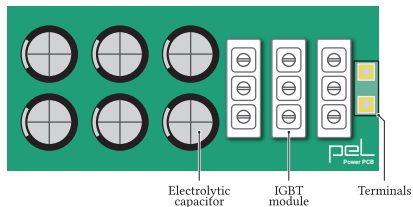


▲ Exemplary cell design; Current capacity -  $3I_{rated}$

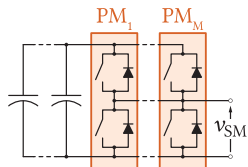
# COMMON MMC CURRENT CAPACITY INCREASE METHODS




▲ Paralleling semiconductor modules

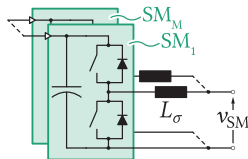

▲ Paralleling SMs

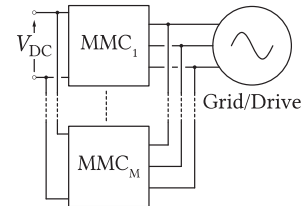


▲ Paralleling converters

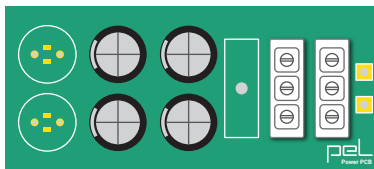


▲ Exemplary cell design; Current capacity -  $2I_{rated}$

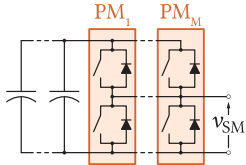
# COMMON MMC CURRENT CAPACITY INCREASE METHODS




▲ Paralleling semiconductor modules

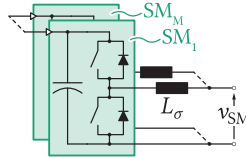

▲ Paralleling SMs

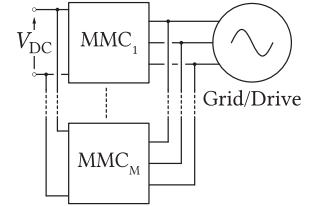


▲ Paralleling converters

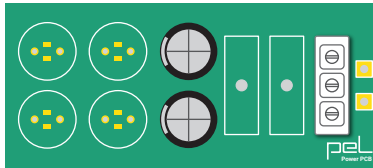


▲ Exemplary cell design; Current capacity -  $I_{rated}$

- ▶ Special design considerations
- ▶ Cell frame size does not change
- ▶ Possible heat sink oversizing?

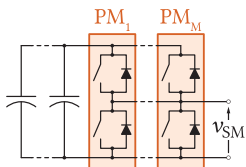
# COMMON MMC CURRENT CAPACITY INCREASE METHODS




▲ Paralleling semiconductor modules

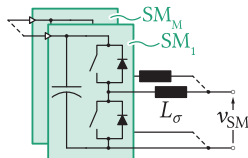


▲ Paralleling SMs

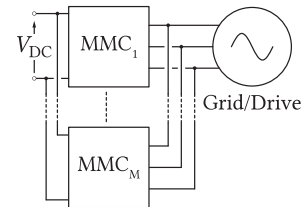

▲ Paralleling converters

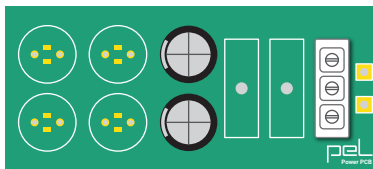

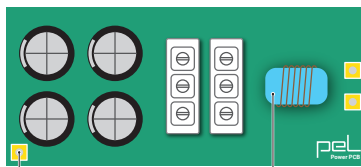▲ Exemplary cell design; Current capacity -  $I_{rated}$



Additional terminal


Inductor

▲ Cell designed for paralleling


- ▶ Special design considerations
- ▶ Cell frame size does not change
- ▶ Possible heat sink oversizing?

- ▶ Additional inductor is needed
- ▶ Additional terminal for the capacitors
- ▶ Special gate driver structure

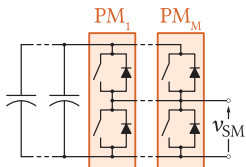
# COMMON MMC CURRENT CAPACITY INCREASE METHODS




▲ Paralleling semiconductor modules

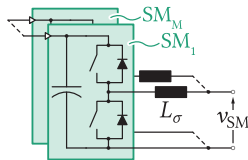


▲ Paralleling SMs

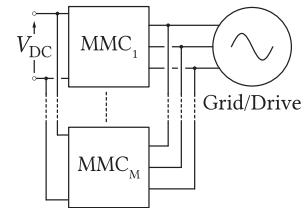

▲ Paralleling converters

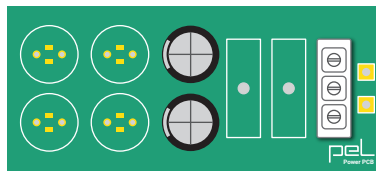

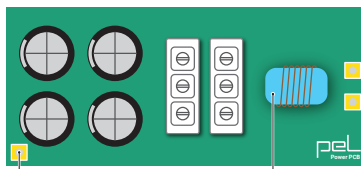▲ Exemplary cell design; Current capacity -  $I_{rated}$



Additional terminal

Inductor


▲ Cell designed for paralleling

- ▶ Special design considerations
- ▶ Cell frame size does not change
- ▶ Possible heat sink oversizing?

- ▶ Additional inductor is needed
- ▶ Additional terminal for the capacitors
- ▶ Special gate driver structure


- ▶ Well known principle
- ▶ Problem is shifted to the control domain

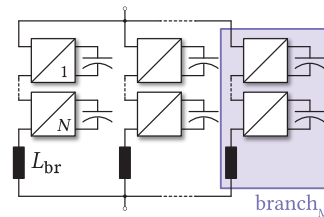Paralleled MMC branches  $\Rightarrow$  System simplification




▲ Paralleling branches

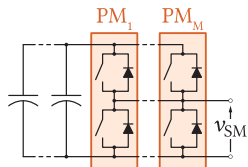
# COMMON MMC CURRENT CAPACITY INCREASE METHODS




▲ Paralleling semiconductor modules

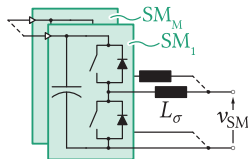


▲ Paralleling SMs

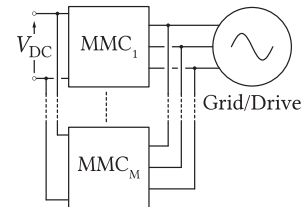

▲ Paralleling converters

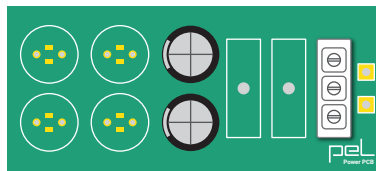

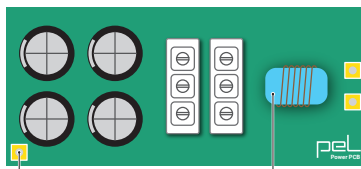▲ Exemplary cell design; Current capacity -  $I_{rated}$



Additional terminal

Inductor


▲ Cell designed for paralleling

- ▶ Special design considerations
- ▶ Cell frame size does not change
- ▶ Possible heat sink oversizing?

- ▶ Additional inductor is needed
- ▶ Additional terminal for the capacitors
- ▶ Special gate driver structure

- ▶ Well known principle
- ▶ Problem is shifted to the control domain

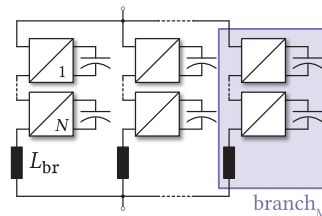Paralleled MMC branches  $\Rightarrow$  System simplification



▲ Paralleling branches


$\Rightarrow$  If the branches are paralleled, there is no need to go through a new design process to accomplish the MMC power extension

# MODELING AND CONTROL


*Deriving the additional control layer...*



# MODELING

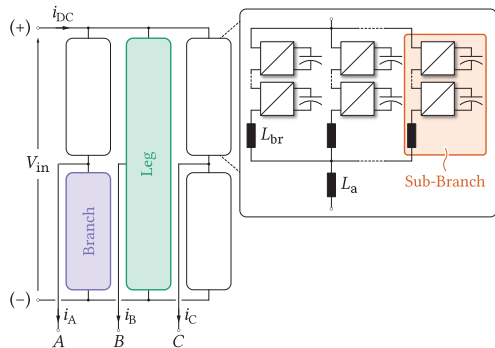

▲ MMC with paralleled (sub)branches

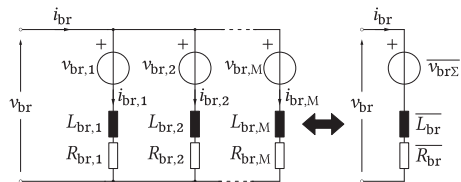


▲ Branch equivalent circuit


$$\overline{v_{br\Sigma}} = \frac{1}{M} \sum_{i=1}^M v_{br,i}$$

$$\overline{Z_{br}} = \frac{1}{M} Z_{br,i}$$

# MODELING

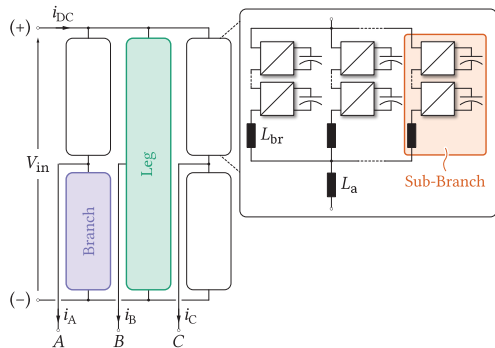


▲ MMC with paralleled (sub)branches

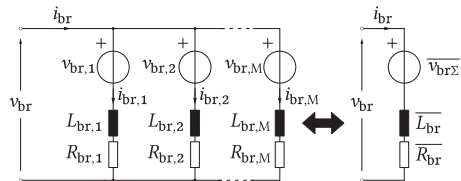

▲ Branch equivalent circuit


$$\overline{v_{br\Sigma}} = \frac{1}{M} \sum_{i=1}^M v_{br,i}$$
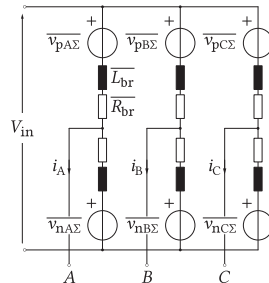
$$\overline{Z_{br}} = \frac{1}{M} Z_{br,i}$$




▲ Equivalent circuit of the converter operating with paralleled (sub)branches

# MODELING

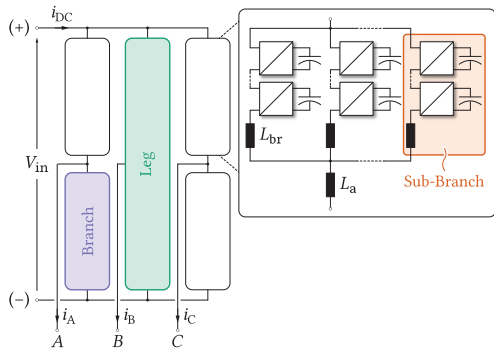


▲ MMC with paralleled (sub)branches

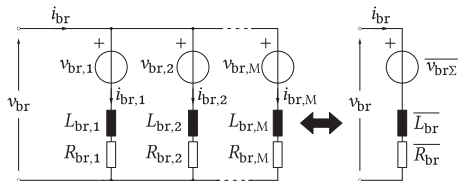

▲ Branch equivalent circuit

$$\overline{v_{br\Sigma}} = \frac{1}{M} \sum_{i=1}^M v_{br,i}$$

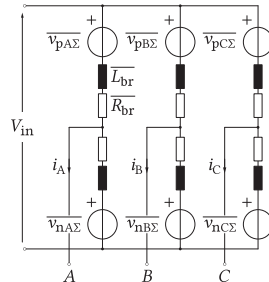
$$\overline{Z_{br}} = \frac{1}{M} Z_{br,i}$$




▲ Equivalent circuit of the converter operating with paralleled (sub)branches

⇒ Equivalent circuit ≡ Conventional MMC

# MODELING

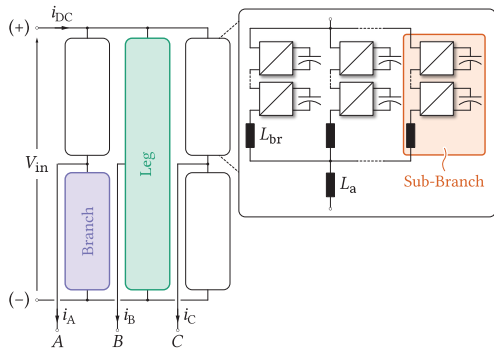


▲ MMC with paralleled (sub)branches

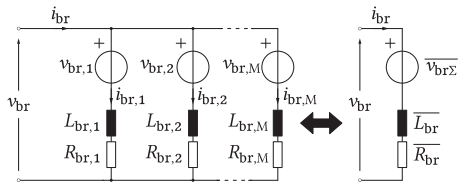

▲ Branch equivalent circuit

$$\overline{v_{br\Sigma}} = \frac{1}{M} \sum_{i=1}^M v_{br,i}$$
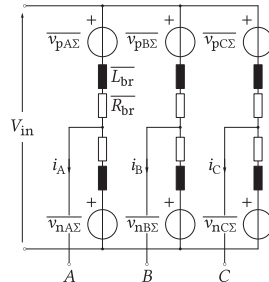
$$\overline{Z_{br}} = \frac{1}{M} Z_{br,i}$$




▲ Equivalent circuit of the converter operating with paralleled (sub)branches

⇒ Equivalent circuit ≡ Conventional MMC

- ▶ All state of the art control considerations still hold
- ▶ New layers of control to be added?
  - ▶ Unequal SBR parameters
  - ▶ SBR energy balance
  - ▶ SBR current balance
- ▶ Voltage quality improvement due to paralleling
  - ▶ (N+1)-level modulation
  - ▶ (2N+1)-level modulation
  - ▶ (NM+1)-level modulation
  - ▶ (2NM+1)-level modulation

# CONTROL - HIGHER CONTROL LAYERS

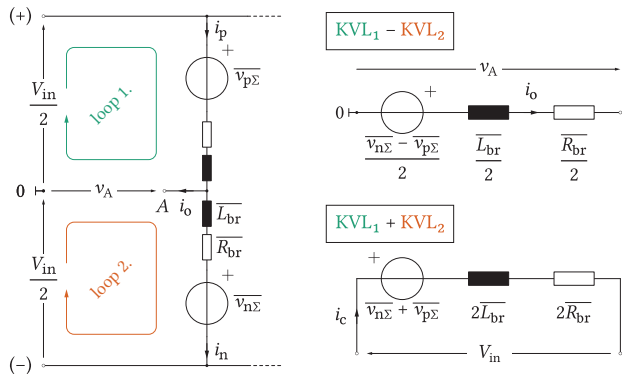


▲ Equivalent circuit of a leg


## Definition of variables identical to the 3PH-MMC

- ▶  $i_c = \frac{i_p + i_n}{2}$  - Leg common-mode current
- ▶  $i_o = i_p - i_n$  - Leg output current
- ▶  $v_c = \frac{\overline{v_{n\Sigma}} + \overline{v_{p\Sigma}}}{2}$  - Leg common-mode voltage
- ▶  $v_s = \frac{\overline{v_{n\Sigma}} - \overline{v_{p\Sigma}}}{2}$  - Leg differential voltage

# CONTROL - HIGHER CONTROL LAYERS

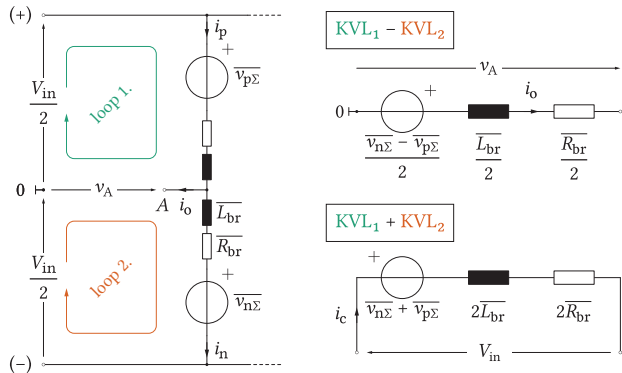

▲ Equivalent circuit of a leg

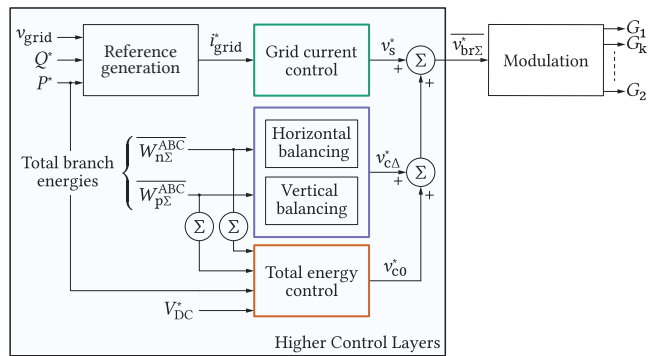

▲ Higher Control Layers

## Definition of variables identical to the 3PH-MMC


- ▶  $i_c = \frac{i_p + i_n}{2}$  - Leg common-mode current
- ▶  $i_o = i_p - i_n$  - Leg output current
- ▶  $v_c = \frac{v_{n\Sigma} + v_{p\Sigma}}{2}$  - Leg common-mode voltage
- ▶  $v_s = \frac{v_{n\Sigma} - v_{p\Sigma}}{2}$  - Leg differential voltage

⇒ Well known 3PH-MMC control logic is retained!


## Standard balancing directions

- ▶ HB ⇒ **total** energies stored within the **legs**
- ▶ VB ⇒ **total** energies stored within the **branches** belonging to the same leg

# CONTROL - HIGHER CONTROL LAYERS

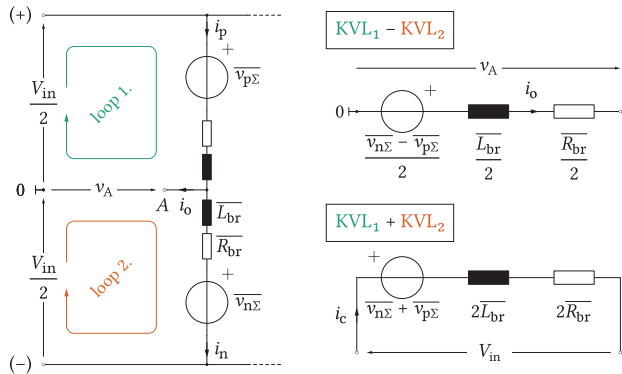

▲ Equivalent circuit of a leg

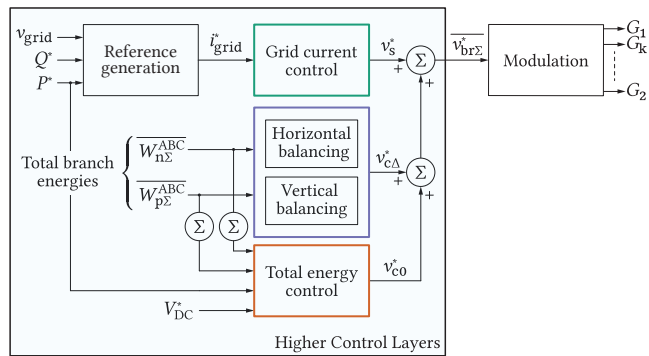

▲ Higher Control Layers

## Definition of variables identical to the 3PH-MMC

- ▶  $i_c = \frac{i_p + i_n}{2}$  - Leg common-mode current
- ▶  $i_o = i_p - i_n$  - Leg output current
- ▶  $v_c = \frac{v_{n\Sigma} + v_{p\Sigma}}{2}$  - Leg common-mode voltage
- ▶  $v_s = \frac{v_{n\Sigma} - v_{p\Sigma}}{2}$  - Leg differential voltage


⇒ Well known 3PH-MMC control logic is retained!

## Standard balancing directions

- ▶ HB ⇒ **total** energies stored within the **legs**
- ▶ VB ⇒ **total** energies stored within the **branches** belonging to the same leg

? Is this enough to keep the whole structure balanced?

# CONTROL - SBR BALANCING

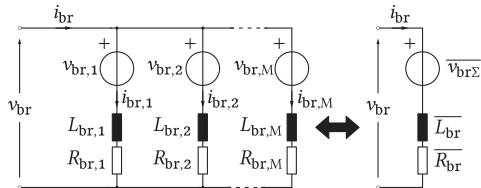

$$Z_{br,1} \neq \dots \neq Z_{br,M} \Rightarrow i_{br,1} \neq \dots \neq i_{br,M}$$

- ▲ Equivalent circuit of the branch

$$L_{br} \frac{d}{dt} \underbrace{\left( i_{br,i} - \frac{i_{br}}{M} \right)}_{\Delta i_{br,i}} + R_{br} \left( i_{br,i} - \frac{i_{br}}{M} \right) = \overline{v_{br\Sigma}} - v_{br,i}$$

Should  $v_{br,i}$  be chosen like:  $v_{br,i} = \overline{v_{br\Sigma}^*} + \Delta v_{br,i}$

$$L_{br} \frac{d}{dt} \Delta i_{br,i} + R_{br} \Delta i_{br,i} = -\Delta v_{br,i}$$

- ▶ Current split can be controlled by means of  $\Delta v_{br,i}$
- ▶ Total branch voltage must not be corrupted!


$$\sum_{i=1}^M \Delta v_{br,i} = 0$$



- ▲ SBR current balancing controller



# CONTROL - SBR BALANCING

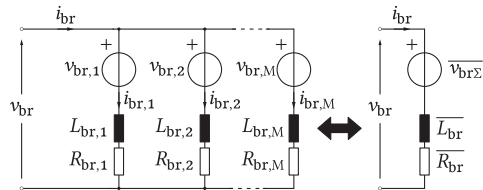

$$Z_{br,1} \neq \dots \neq Z_{br,M} \Rightarrow i_{br,1} \neq \dots \neq i_{br,M}$$

▲ Equivalent circuit of the branch

$$L_{br} \frac{d}{dt} \left( i_{br,i} - \frac{i_{br}}{M} \right) + R_{br} \left( i_{br,i} - \frac{i_{br}}{M} \right) = \overline{v_{br\Sigma}} - v_{br,i}$$

Should  $v_{br,i}$  be chosen like:  $v_{br,i} = \overline{v_{br\Sigma}^*} + \Delta v_{br,i}$

$$L_{br} \frac{d}{dt} \Delta i_{br,i} + R_{br} \Delta i_{br,i} = -\Delta v_{br,i}$$


- ▶ Current split can be controlled by means of  $\Delta v_{br,i}$
- ▶ Total branch voltage must not be corrupted!

$$\sum_{i=1}^M \Delta v_{br,i} = 0$$




▲ SBR current balancing controller


## Energy vs. current balance

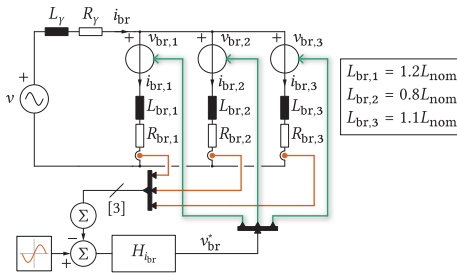
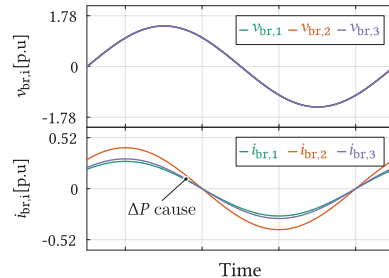
$$\begin{aligned} L_{br,1} &= 1.2 L_{nom} \\ L_{br,2} &= 0.8 L_{nom} \\ L_{br,3} &= 1.1 L_{nom} \end{aligned}$$



# CONTROL - SBR BALANCING

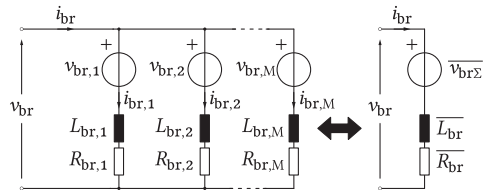

$$Z_{br,1} \neq \dots \neq Z_{br,M} \Rightarrow i_{br,1} \neq \dots \neq i_{br,M}$$

▲ Equivalent circuit of the branch


$$L_{br} \frac{d}{dt} \left( i_{br,i} - \frac{i_{br}}{M} \right) + R_{br} \left( i_{br,i} - \frac{i_{br}}{M} \right) = \overline{v_{br\Sigma}} - v_{br,i}$$

Should  $v_{br,i}$  be chosen like:  $v_{br,i} = \overline{v_{br\Sigma}} + \Delta v_{br,i}$

$$L_{br} \frac{d}{dt} \Delta i_{br,i} + R_{br} \Delta i_{br,i} = -\Delta v_{br,i}$$


- ▶ Current split can be controlled by means of  $\Delta v_{br,i}$
- ▶ Total branch voltage must not be corrupted!

$$\sum_{i=1}^M \Delta v_{br,i} = 0$$

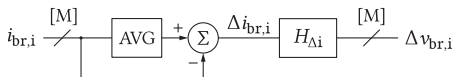


▲ SBR current balancing controller

## Energy vs. current balance

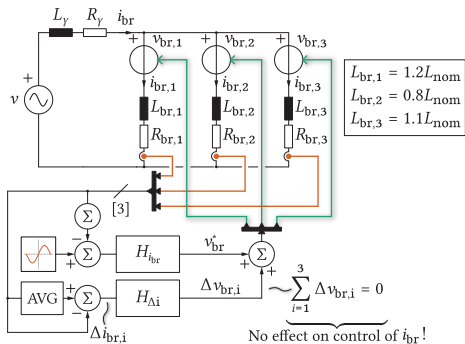

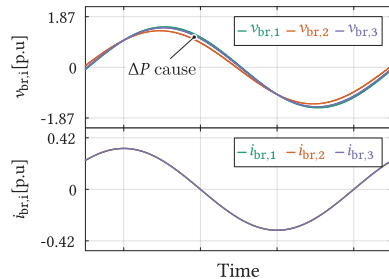
$$\begin{aligned} L_{br,1} &= 1.2L_{nom} \\ L_{br,2} &= 0.8L_{nom} \\ L_{br,3} &= 1.1L_{nom} \end{aligned}$$



### ⚡ Current balancing is not enough!

SBR powers are different  $\Rightarrow$  capacitor energy (voltage) divergence

# CONTROL - SBR BALANCING

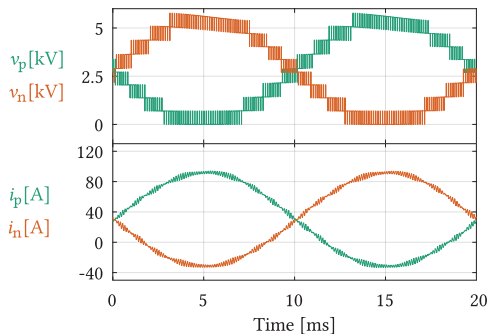

▲ Typical voltage/current waveforms of a (sub)branch

(Sub)branch power equation


$$P_{sbr} = \overline{v_{sbr} i_{sbr}}$$

$$= \overline{V_{sbr}^{DC} i_{sbr}^{DC}} + \overline{v_{sbr} i_{sbr}}$$

Taylor series expansion

$$P_{sbr} = P_{sbr}^{nom} + \underbrace{\Delta P_{sbr}^{DC}}_{\approx \frac{1}{2} V_{DC}^* \Delta i_{sbr}^{DC}} + \underbrace{\Delta P_{sbr}^{AC}}_{\text{depends on } \Delta L_{br}}$$

# CONTROL - SBR BALANCING

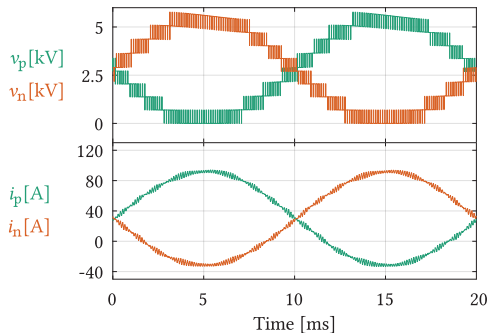

▲ Typical voltage/current waveforms of a (sub)branch

(Sub)branch power equation

$$P_{sbr} = \overline{v_{sbr} i_{sbr}}$$


$$= \overline{V_{sbr}^{DC} i_{sbr}^{DC}} + \overline{v_{sbr} i_{sbr}}$$

Taylor series expansion

$$P_{sbr} = P_{sbr}^{nom} + \underbrace{\Delta P_{sbr}^{DC}}_{\approx \frac{1}{2} V_{DC}^* \Delta i_{sbr}^{DC}} + \underbrace{\Delta P_{sbr}^{AC}}_{\text{depends on } \Delta L_{br}}$$

⇒ SBR energy control through SBR currents mismatches

# CONTROL - SBR BALANCING

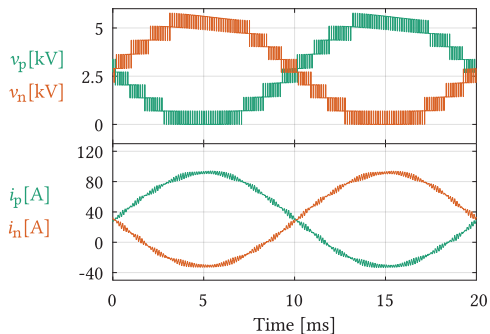

▲ Typical voltage/current waveforms of a (sub)branch

(Sub)branch power equation

$$P_{sbr} = \overline{v_{sbr} i_{sbr}}$$

$$= \overline{v_{sbr}^{DC} i_{sbr}^{DC}} + \overline{v_{sbr} i_{sbr}}$$

Taylor series expansion

$$P_{sbr} = P_{sbr}^{nom} + \underbrace{\Delta P_{sbr}^{DC}}_{\approx \frac{1}{2} V_{DC}^* \Delta i_{sbr}^{DC}} + \underbrace{\Delta P_{sbr}^{AC}}_{\text{depends on } \Delta L_{br}}$$


Reminder

$$L_{br} \frac{d}{dt} \Delta i_{br,i} + R_{br} \Delta i_{br,i} = -\Delta v_{br,i}$$

$$\overline{v_{br\Sigma}} = \frac{1}{M} \sum_{i=1}^M v_{br,i} = \frac{1}{M} \sum_{i=1}^M \left[ \underbrace{\overline{v_{br\Sigma}^*}}_{CMV} + \Delta v_{br,i} \right]$$

⇒ SBR energy control through SBR currents mismatches

# CONTROL - SBR BALANCING

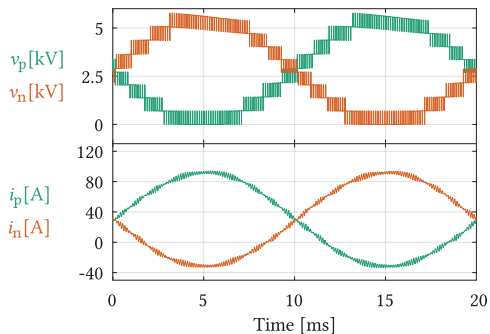

▲ Typical voltage/current waveforms of a (sub)branch

(Sub)branch power equation

$$P_{sbr} = \overline{v_{sbr} i_{sbr}}$$

$$= \sqrt{V_{sbr}^{DC}} \overline{i_{sbr}^{DC}} + \overline{v_{sbr} i_{sbr}^{AC}}$$

Taylor series expansion

$$P_{sbr} = P_{sbr}^{nom} + \underbrace{\Delta P_{sbr}^{DC}}_{\approx \frac{1}{2} V_{DC}^* \Delta i_{sbr}^{DC}} + \underbrace{\Delta P_{sbr}^{AC}}_{\text{depends on } \Delta L_{br}}$$


⇒ SBR energy control through SBR currents mismatches

Reminder

$$L_{br} \frac{d}{dt} \Delta i_{br,i} + R_{br} \Delta i_{br,i} = -\Delta v_{br,i}$$

$$\overline{v_{br,\Sigma}} = \frac{1}{M} \sum_{i=1}^M v_{br,i} = \frac{1}{M} \sum_{i=1}^M \left[ \underbrace{\overline{v_{br,\Sigma}^*}}_{CMV} + \Delta v_{br,i} \right]$$

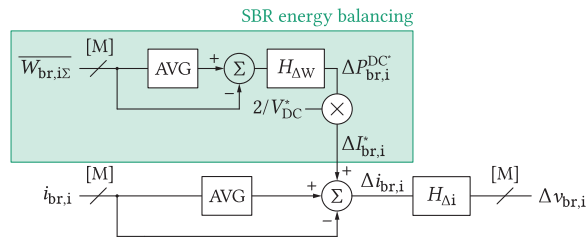
⚡  $\sum_{i=1}^M \Delta v_{br,i} = 0$  must be respected at all times!



▲ SBR energy controller

$$\sum_{i=1}^M \Delta v_{br,i} = H_{\Delta i} H_{\Delta W} \left( \underbrace{\frac{1}{M} \sum_{i=1}^M \overline{W_{br,i\Sigma}}}_{W_{avg}} - \sum_{i=1}^M \overline{W_{br,i\Sigma}} \right) + H_{\Delta i} \left( M \cdot \underbrace{\frac{1}{M} \sum_{i=1}^M i_{br,i}}_{i_{avg}} - \sum_{i=1}^M i_{br,i} \right) = 0$$

# CONTROL - SBR BALANCING

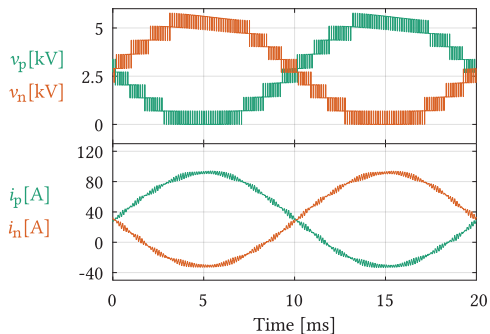

▲ Typical voltage/current waveforms of a (sub)branch

(Sub)branch power equation

$$P_{sbr} = \overline{v_{sbr} i_{sbr}}$$

$$= \sqrt{V_{sbr}^{DC}} \overline{i_{sbr}^{DC}} + \overline{v_{sbr} i_{sbr}}$$

Taylor series expansion

$$P_{sbr} = P_{sbr}^{nom} + \underbrace{\Delta P_{sbr}^{DC}}_{\approx \frac{1}{2} V_{DC}^* \Delta i_{sbr}^{DC}} + \underbrace{\Delta P_{sbr}^{AC}}_{\text{depends on } \Delta L_{br}}$$


⇒ SBR energy control through SBR currents mismatches

Reminder

$$L_{br} \frac{d}{dt} \Delta i_{br,i} + R_{br} \Delta i_{br,i} = -\Delta v_{br,i}$$

$$\overline{v_{br\Sigma}} = \frac{1}{M} \sum_{i=1}^M v_{br,i} = \frac{1}{M} \sum_{i=1}^M \left[ \underbrace{\overline{v_{br\Sigma}^*}}_{CMV} + \Delta v_{br,i} \right]$$

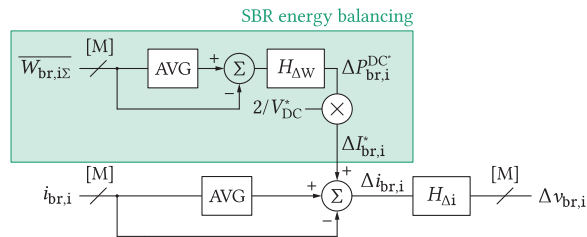
⚡  $\sum_{i=1}^M \Delta v_{br,i} = 0$  must be respected at all times!



▲ SBR energy controller

$$\sum_{i=1}^M \Delta v_{br,i} = H_{\Delta i} H_{\Delta W} \left( \underbrace{\frac{1}{M} \sum_{i=1}^M \overline{W_{br,i\Sigma}}}_{W_{avg}} - \sum_{i=1}^M \overline{W_{br,i\Sigma}} \right) + H_{\Delta i} \left( M \cdot \underbrace{\frac{1}{M} \sum_{i=1}^M i_{br,i}}_{i_{avg}} - \sum_{i=1}^M i_{br,i} \right) = 0$$

# CONTROL - SBR BALANCING

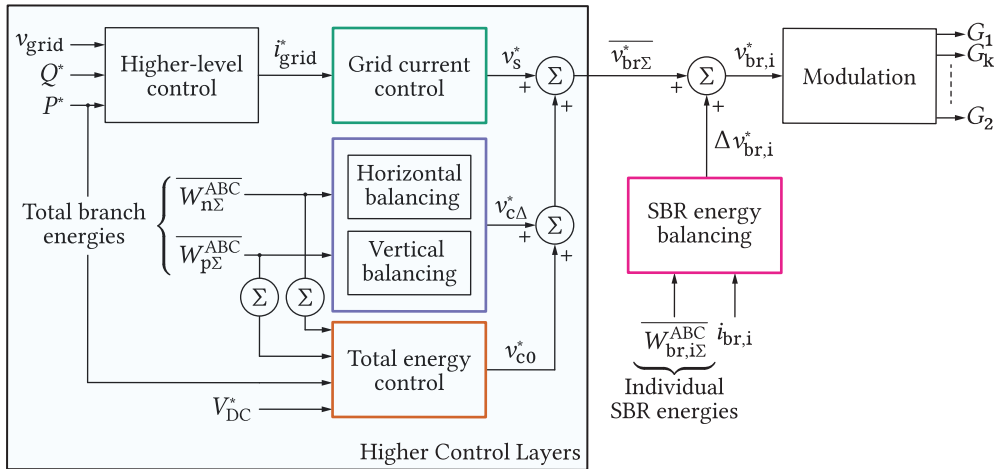

▲ Converter control layers


- ▶ Additional control layer (conventional MMC control is retained as can be seen on the left-hand side)
- ▶ Decoupling from the higher control levels ensured by means of  $\sum_{i=1}^M \Delta v_{\text{br},i} = 0$
- ▶ Independent on the number of paralleled SBRs (the same approach for both odd and even  $M$ )
- ▶ Power scalability depending solely upon the control system limitations




# SIMULATION RESULTS

*General solution for arbitrary number of Sub-Branches*


# SIMULATION SCENARIO

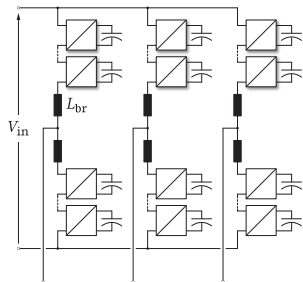

▲ Available converter design

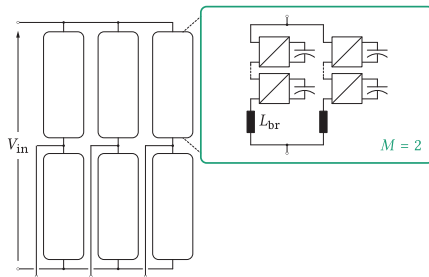


▲ Doubling the converter rated power

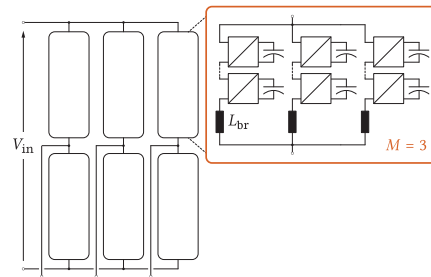

▲ Tripling the converter rated power


	Simulation 1	Simulation 2
Rated power ( $P$ )	1MW	1.5MW
Input voltage ( $V_{in}$ )	5kV	5kV
No. of cells/SBR ( $N$ )	5	5
Cell rated voltage ( $V_{SM}$ )	1kV	1kV
Cell capacitance ( $C_{SM}$ )	0.83mF	0.83mF
Number of paralleled SBRs ( $M$ )	2	3
SBR inductance ( $L_{br}$ )	5mH	7.5mH
SBR resistance ( $R_{br}$ )	60m $\Omega$	60m $\Omega$
Switching frequency ( $f_c$ )	999Hz	999Hz

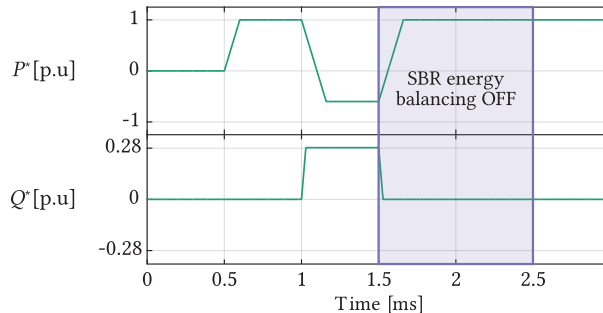


▲ Power profile used to test SBR energy balancing control

# SIMULATION RESULTS

	Rated power ( $P$ )	Input voltage ( $V_{in}$ )	No. of cells/SBR ( $N$ )	Cell rated voltage ( $V_{cell}$ )	Cell capacitance ( $C_{cell}$ )	No. of paralleled SBRs ( $M$ )	SBR inductance ( $L_{br}$ )	SBR resistance ( $R_{br}$ )	Sw. frequency ( $f_{sw}$ )
Left	1MW	5kV	5	1kV	0.83mF	2	5mH	60m $\Omega$	999Hz
Right	1.5MW	5kV	5	1kV	0.83mF	3	5mH	60m $\Omega$	999Hz

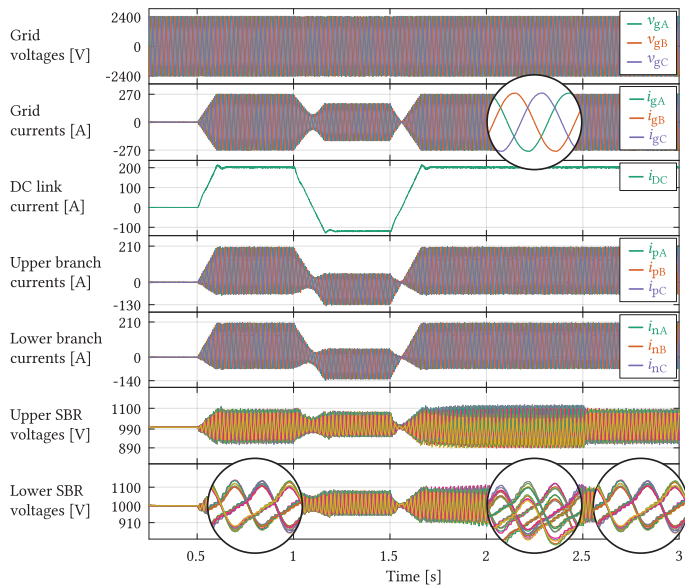


▲ Simulation results in case  $M = 2$

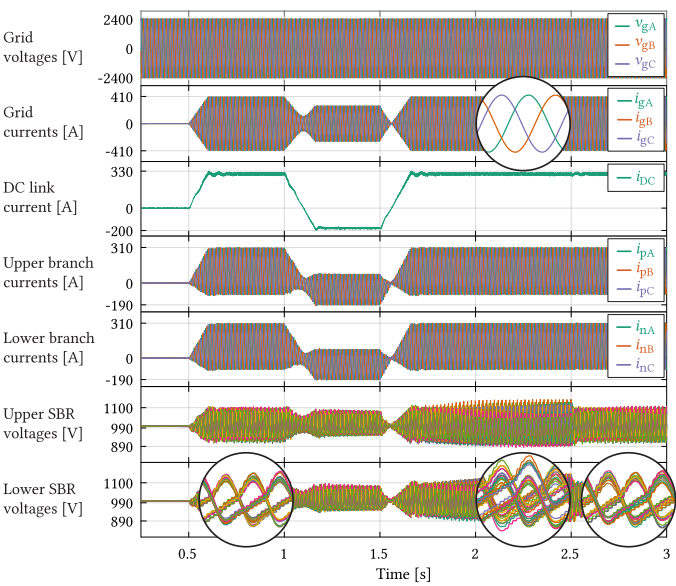


▲ Simulation results in case  $M = 3$

# SIMULATION RESULTS

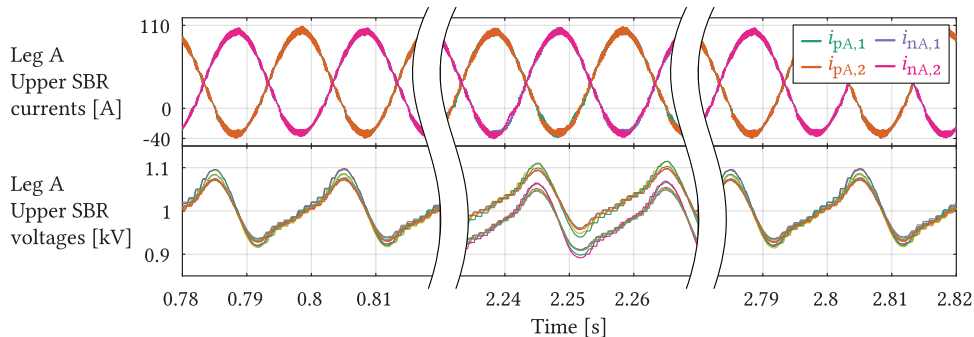

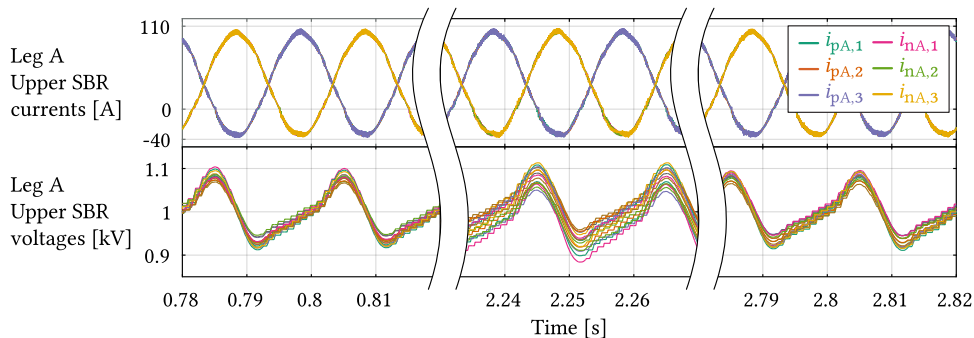▲ Leg A upper and lower SBR currents (top) along with SBR voltages (bottom) in case  $M = 2$



▲ Leg A upper and lower SBR currents (top) along with SBR voltages (bottom) in case  $M = 3$

# SIMULATION RESULTS

---

There are two relevant questions one might ask:


- ▶ How aggressive is the SBR energy balancing controller?
- ▶ Should current rating of the SMs be increased owing to the presence of SBR energy balancing?

# SIMULATION RESULTS

There are two relevant questions one might ask:

- ▶ How aggressive is the SBR energy balancing controller?
- ▶ Should current rating of the SMs be increased owing to the presence of SBR energy balancing?
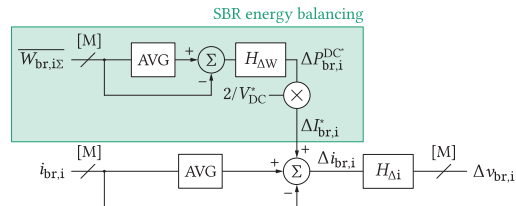
$$\Delta I_{br,i}^* = \underbrace{\Delta W_{br,i\Sigma}}_{\text{Energy error}} \cdot \underbrace{H_{\Delta W}}_{\text{Controller TF}} \cdot \underbrace{\frac{2}{V_{DC}^*}}_{\text{several kV}}$$




# SIMULATION RESULTS


There are two relevant questions one might ask:

- ▶ How aggressive is the SBR energy balancing controller?
- ▶ Should current rating of the SMs be increased owing to the presence of SBR energy balancing?

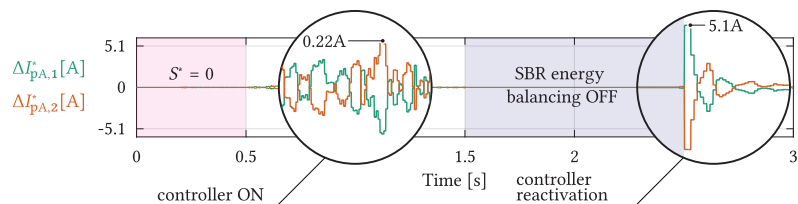
$$\Delta I_{br,i}^* = \underbrace{\Delta W_{br,i\Sigma}}_{\text{Energy error}} \cdot \underbrace{H_{\Delta W}}_{\text{Controller TF}} \cdot \underbrace{\frac{2}{V_{DC}^*}}_{\text{several kV}}$$



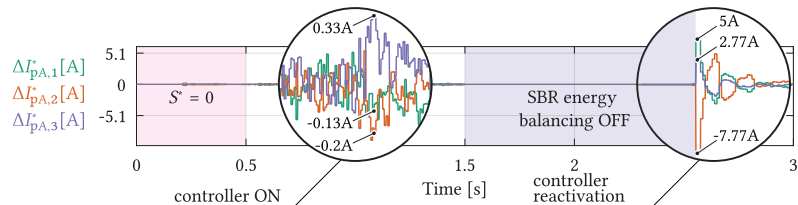- ▲ References provided by the SBR energy balancing controller ( $M = 2$ )



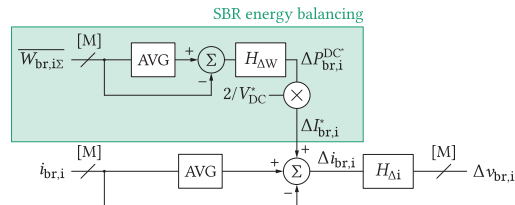- ▲ References provided by the SBR energy balancing controller ( $M = 3$ )




# SIMULATION RESULTS


There are two relevant questions one might ask:

- How aggressive is the SBR energy balancing controller?
- Should current rating of the SMs be increased owing to the presence of SBR energy balancing?

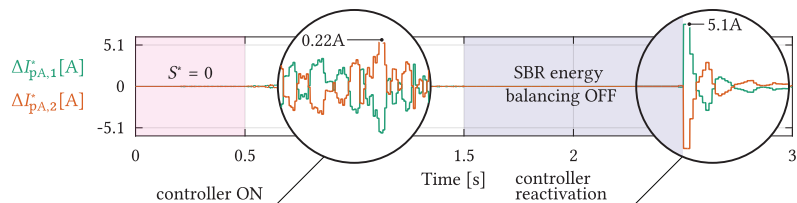
$$\Delta I_{br,i}^* = \underbrace{\Delta W_{br,i\Sigma}}_{\text{Energy error}} \cdot \underbrace{H_{\Delta W}}_{\text{Controller TF}} \cdot \underbrace{\frac{2}{V_{DC}^*}}_{\text{several kV}}$$



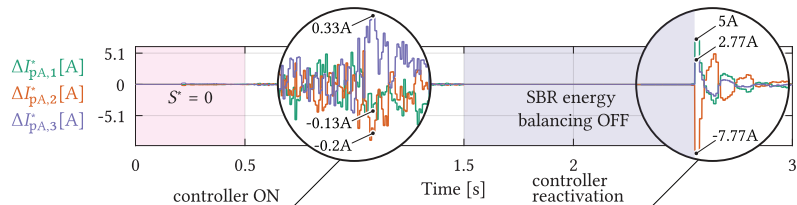▲ References provided by the SBR energy balancing controller ( $M = 2$ )



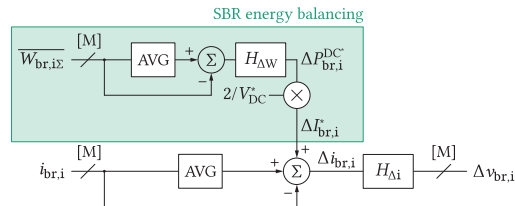▲ References provided by the SBR energy balancing controller ( $M = 3$ )



- $\Delta I_{br,i}^* < 10\% \hat{i}_{br}$  (**Modest response!**)




# SIMULATION RESULTS


There are two relevant questions one might ask:

- ▶ How aggressive is the SBR energy balancing controller?
- ▶ Should current rating of the SMs be increased owing to the presence of SBR energy balancing?

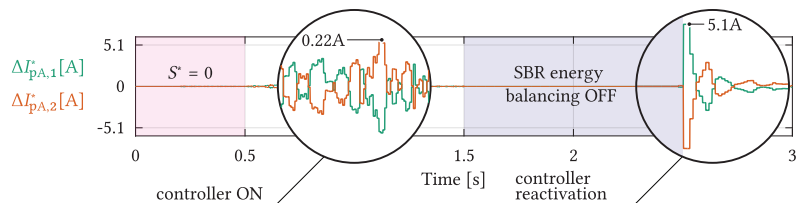
$$\Delta I_{br,i}^* = \underbrace{\Delta W_{br,i\bar{z}}}_{\text{Energy error}} \cdot \underbrace{H_{\Delta W}}_{\text{Controller TF}} \cdot \underbrace{\frac{2}{V_{DC}^*}}_{\text{several kV}}$$



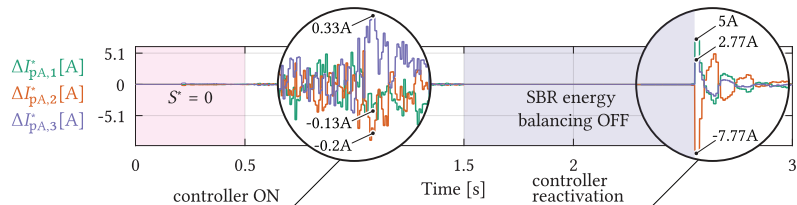- ▲ References provided by the SBR energy balancing controller ( $M = 2$ )



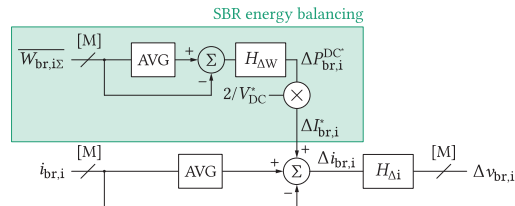- ▲ References provided by the SBR energy balancing controller ( $M = 3$ )




- ▶  $\Delta I_{br,i}^* < 10\% \hat{i}_{br}$  (Modest response!)
- ▶  $\sum_{i=1}^M \Delta I_{br,i}^* = 0$

# SIMULATION RESULTS


There are two relevant questions one might ask:

- ▶ How aggressive is the SBR energy balancing controller?
- ▶ Should current rating of the SMs be increased owing to the presence of SBR energy balancing?

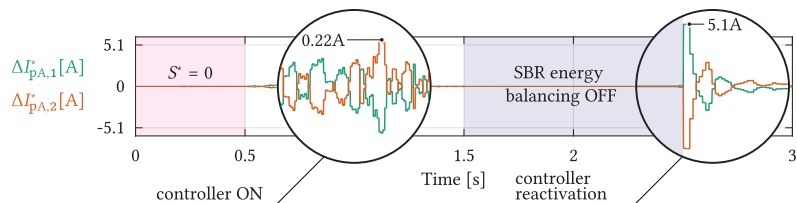
$$\Delta I_{br,i}^* = \underbrace{\Delta W_{br,i\Sigma}}_{\text{Energy error}} \cdot \underbrace{H_{\Delta W}}_{\text{Controller TF}} \cdot \underbrace{\frac{2}{V_{DC}^*}}_{\text{several kV}}$$



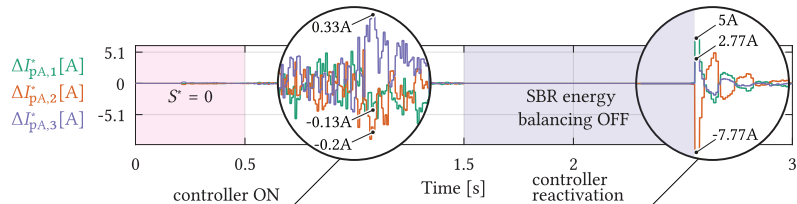▲ References provided by the SBR energy balancing controller ( $M = 2$ )



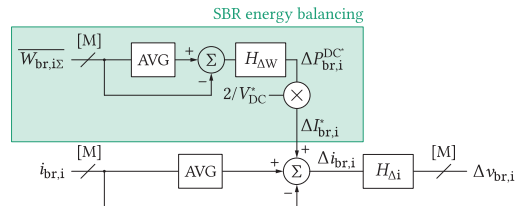▲ References provided by the SBR energy balancing controller ( $M = 3$ )




- ▶  $\Delta I_{br,i}^* < 10\% \hat{i}_{br}$  (**Modest response!**)
- ▶  $\sum_{i=1}^M \Delta I_{br,i}^* = 0$
- ▶  $\sum_{i=1}^M \Delta v_{br,i}^* = 0 \Rightarrow$  no interference with higher control loops

# SIMULATION RESULTS


There are two relevant questions one might ask:

- ▶ How aggressive is the SBR energy balancing controller?
- ▶ Should current rating of the SMs be increased owing to the presence of SBR energy balancing?

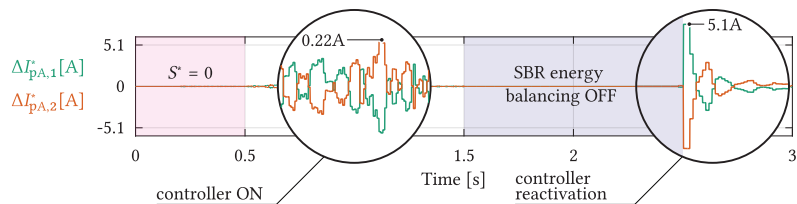
$$\Delta i_{br,i}^* = \underbrace{\Delta W_{br,i\Sigma}}_{\text{Energy error}} \cdot \underbrace{H_{\Delta W}}_{\text{Controller TF}} \cdot \underbrace{\frac{2}{V_{DC}^*}}_{\text{several kV}}$$



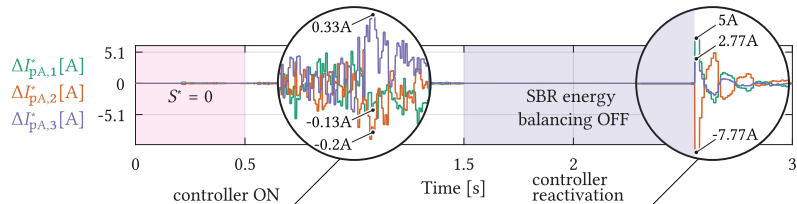▲ References provided by the SBR energy balancing controller ( $M = 2$ )



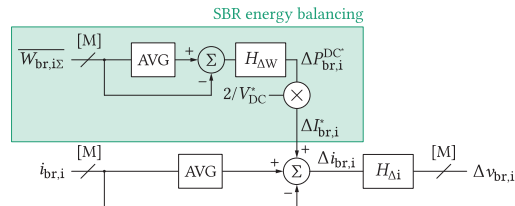▲ References provided by the SBR energy balancing controller ( $M = 3$ )




- ▶  $\Delta i_{br,i}^* < 10\% \hat{i}_{br}$  (**Modest response!**)
- ▶  $\sum_{i=1}^M \Delta i_{br,i}^* = 0$
- ▶  $\sum_{i=1}^M \Delta v_{br,i}^* = 0 \Rightarrow$  no interference with higher control loops

⇒ No need for SM current rating upgrade!

# MODULATION CONSIDERATIONS


*...impact on the voltage quality*

# PRELIMINARY CONSIDERATIONS

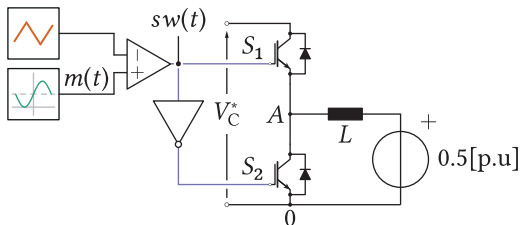


$$\begin{aligned}
 v_{A0} &= sw(t) \cdot V_{C,1} \\
 &= [m_1(t) + \underbrace{st(\theta_1) + st(\theta_2)}_{\text{higher order harmonics}}] V_{C,1} \\
 &= \frac{V_C^*}{2} + \hat{m} \frac{V_C^*}{2} \cos(\omega t) + H_1(\omega t)
 \end{aligned}$$
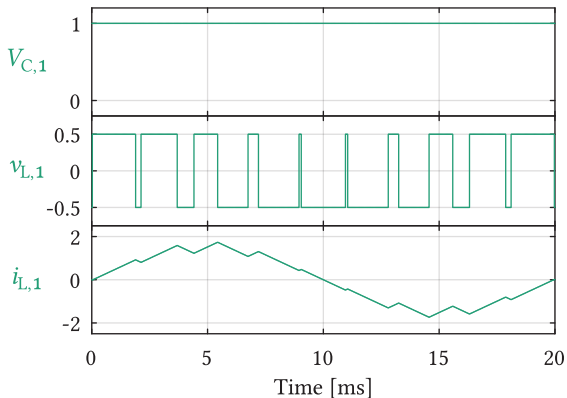
$$m_1(t) = \frac{1}{2} + \frac{\hat{m}}{2} \cos(\omega t)$$




▲ PSC modulation example with one HB module

# PRELIMINARY CONSIDERATIONS

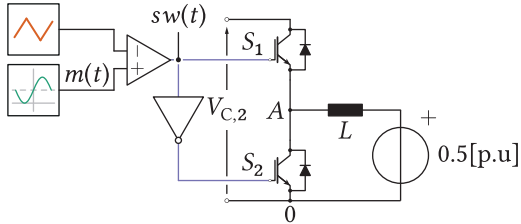


$$\begin{aligned}
 v_{A0} &= sw(t) \cdot V_{C,2} \\
 &= [m_2(t) + \underbrace{st(\theta_1) + st(\theta_2)}_{\text{higher order harmonics}}] V_{C,2} \\
 &= \underbrace{\frac{V_C^* + \Delta v_C}{2}}_{\text{DC + osc.}} + \underbrace{(V_C^* + \Delta v_C) \frac{\hat{m}}{2} \cos(\omega t) + H_2(\omega t)}_{\text{DC + osc.}}
 \end{aligned}$$
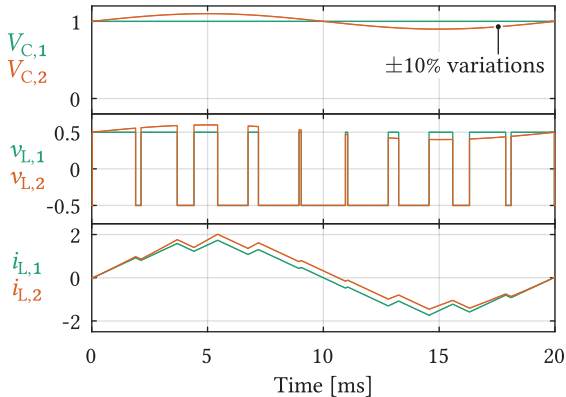
$$m_2(t) = \frac{1}{2} + \frac{\hat{m}}{2} \cos(\omega t)$$




▲ PSC modulation example with one HB module

# PRELIMINARY CONSIDERATIONS

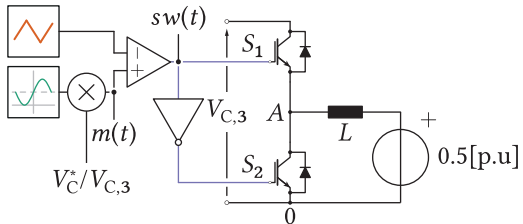


$$\begin{aligned}
 v_{A0} &= sw(t) \cdot V_{C,3} \\
 &= [m_3(t) + \underbrace{st(\theta_1) + st(\theta_2)}_{\text{higher order harmonics}}] V_{C,3} \\
 &= \frac{V_C^*}{2} + \hat{m} \frac{V_C^*}{2} \cos(\omega t) + H_3(\omega t)
 \end{aligned}$$
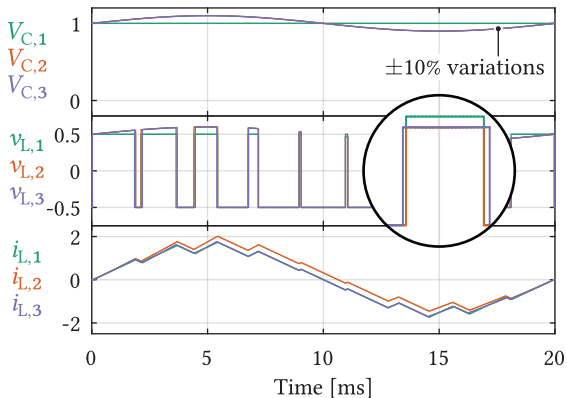
$$m_3(t) = \left\{ \frac{1}{2} + \frac{\hat{m}}{2} \cos(\omega t) \right\} \frac{V_C^*}{V_{C,3}}$$



▲ PSC modulation example with one HB module


# PRELIMINARY CONSIDERATIONS

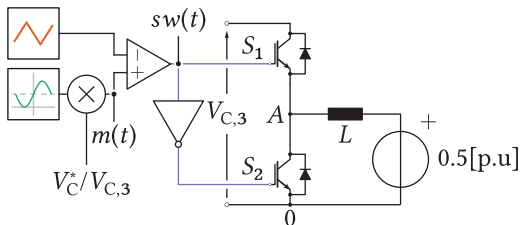

$$m_3(t) = \left\{ \frac{1}{2} + \frac{\hat{m}}{2} \cos(\omega t) \right\} \frac{V_C^*}{V_{C,3}}$$

$$\begin{aligned} v_{A0} &= sw(t) \cdot V_{C,3} \\ &= [m_3(t) + \underbrace{st(\theta_1) + st(\theta_2)}_{\text{higher order harmonics}}] V_{C,3} \\ &= \frac{V_C^*}{2} + \hat{m} \frac{V_C^*}{2} \cos(\omega t) + H_3(\omega t) \end{aligned}$$

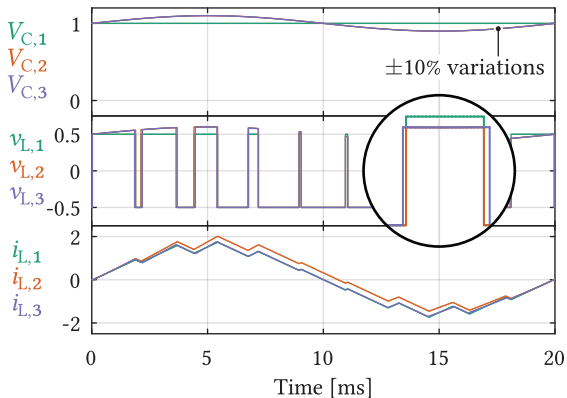
⇒ Correction of  $m(t)$  ensures DC link voltage ripple effect mitigation!



▲ PSC modulation example with one HB module




# PRELIMINARY CONSIDERATIONS

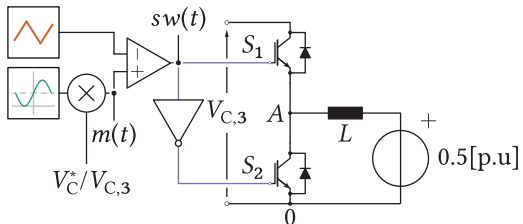

$$\begin{aligned}
 v_{A0} &= sw(t) \cdot V_{C,3} \\
 &= [m_3(t) + \underbrace{st(\theta_1) + st(\theta_2)}_{\text{higher order harmonics}}] V_{C,3} \\
 &= \frac{V_C^*}{2} + \hat{m} \frac{V_C^*}{2} \cos(\omega t) + H_3(\omega t)
 \end{aligned}$$
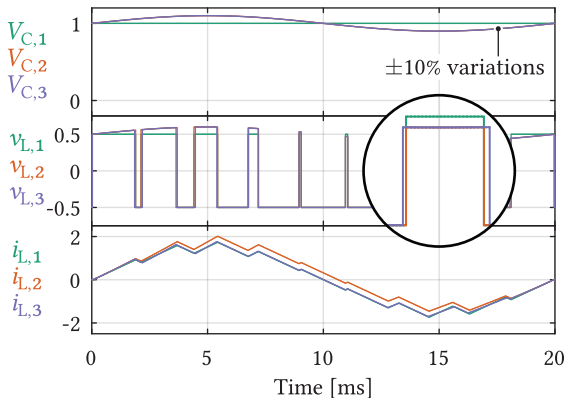
$$m_3(t) = \left\{ \frac{1}{2} + \frac{\hat{m}}{2} \cos(\omega t) \right\} \frac{V_C^*}{V_{C,3}}$$




▲ PSC modulation example with one HB module

⇒ Correction of  $m(t)$  ensures DC link voltage ripple effect mitigation!

Closed loop control of the MMC utilizes similar procedure, where


$$m_{i[n,p]} = \frac{V_C^* \pm V_S^*}{V_{[n,p]\Sigma}}$$

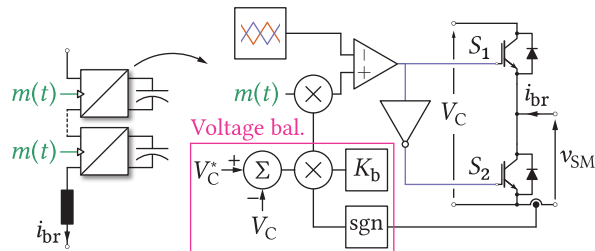However, not all of the SMs are the same ⇒ Additional  $m(t)$  compensation is needed!




▲ Additional compensation of modulation index

# PRELIMINARY CONSIDERATIONS

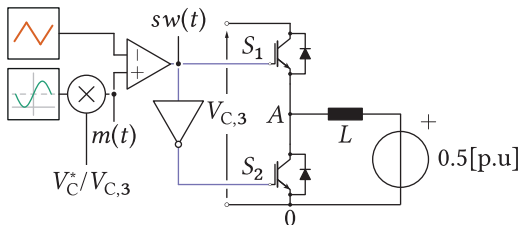
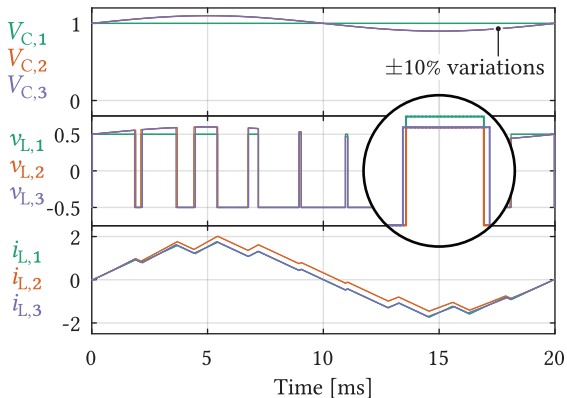
$$m_3(t) = \left\{ \frac{1}{2} + \frac{\hat{m}}{2} \cos(\omega t) \right\} \frac{V_C^*}{V_{C,3}}$$



▲ PSC modulation example with one HB module


$$\begin{aligned} v_{A0} &= sw(t) \cdot V_{C,3} \\ &= [m_3(t) + \underbrace{st(\theta_1) + st(\theta_2)}_{\text{higher order harmonics}}] V_{C,3} \\ &= \frac{V_C^*}{2} + \hat{m} \frac{V_C^*}{2} \cos(\omega t) + H_3(\omega t) \end{aligned}$$

⇒ Correction of  $m(t)$  ensures DC link voltage ripple effect mitigation!

Closed loop control of the MMC utilizes similar procedure, where

$$m_{[n,p]} = \frac{V_C^* \pm V_S^*}{V_{[n,p]\Sigma}}$$

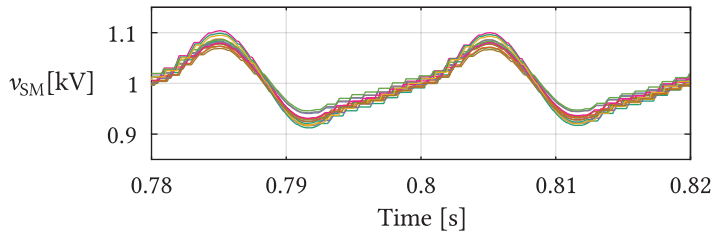However, not all of the SMs are the same ⇒ Additional  $m(t)$  compensation is needed!




▲ MMC SM voltages in case PSC modulation is used

# PSC MODULATION APPLIED TO A SINGLE BRANCH

For the purpose of qualitative analysis, three assumptions are made:

- ▶ Closed-loop control of the internal quantities
- ▶ Voltage across all the SMs is approximately the same (PSC modulation)
- ▶ Active balancing contribution to modulation index corrections is negligible

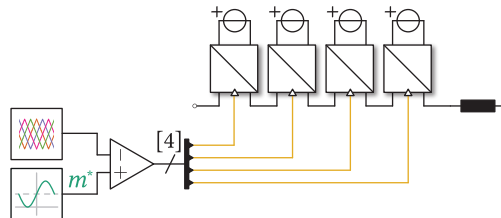⇒ **every SM capacitor is perceived as a stiff voltage source**




▲ A branch with  $N = 4$  SMs (an exemplary case)

# PSC MODULATION APPLIED TO A SINGLE BRANCH


For the purpose of qualitative analysis, three assumptions are made:

- ▶ Closed-loop control of the internal quantities
- ▶ Voltage across all the SMs is approximately the same (PSC modulation)
- ▶ Active balancing contribution to modulation index corrections is negligible

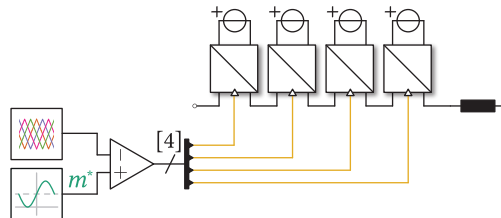⇒ **every SM capacitor is perceived as a stiff voltage source**



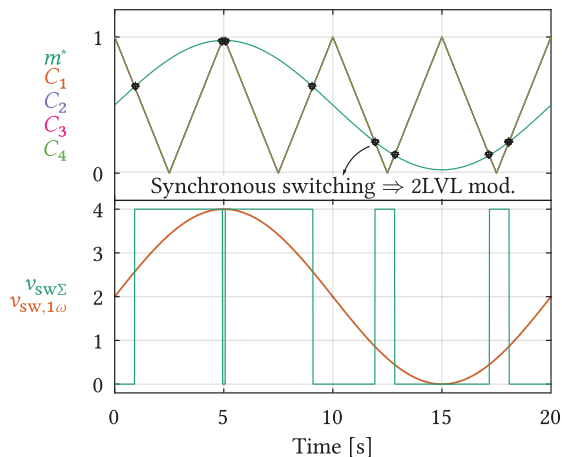▲ A branch with  $N = 4$  SMs (an exemplary case)




▲ Obtained voltage waveform in case  $m(t) = \frac{1}{2} + \frac{0.95}{2} \cos(2\pi 50t)$  and  $\theta_c = 0$

# PSC MODULATION APPLIED TO A SINGLE BRANCH


For the purpose of qualitative analysis, three assumptions are made:

- ▶ Closed-loop control of the internal quantities
- ▶ Voltage across all the SMs is approximately the same (PSC modulation)
- ▶ Active balancing contribution to modulation index corrections is negligible

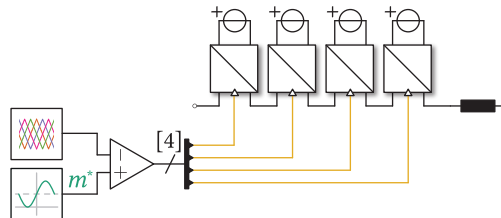
⇒ **every SM capacitor is perceived as a stiff voltage source**



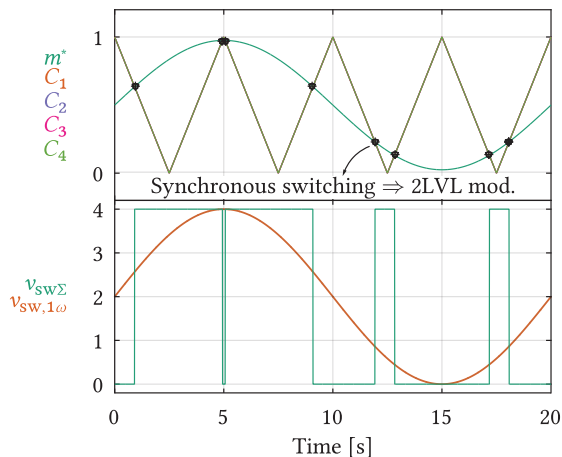▲ A branch with  $N = 4$  SMs (an exemplary case)



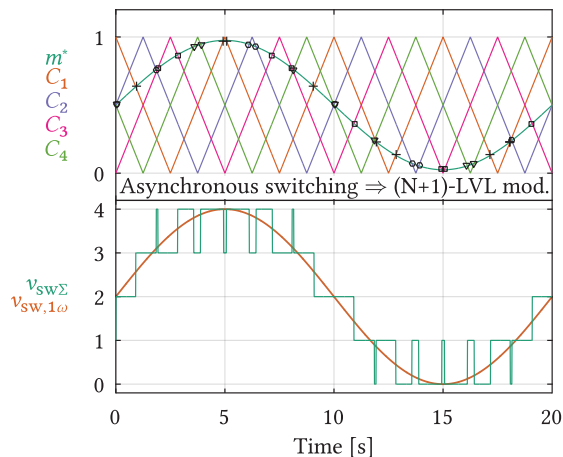▲ Obtained voltage waveform in case  $m(t) = \frac{1}{2} + \frac{0.95}{2} \cos(2\pi 50t)$  and  $\theta_c = 0$





▲ Obtained voltage waveform in case  $m(t) = \frac{1}{2} + \frac{0.95}{2} \cos(2\pi 50t)$  and  $\theta_c = \frac{2\pi}{4}$
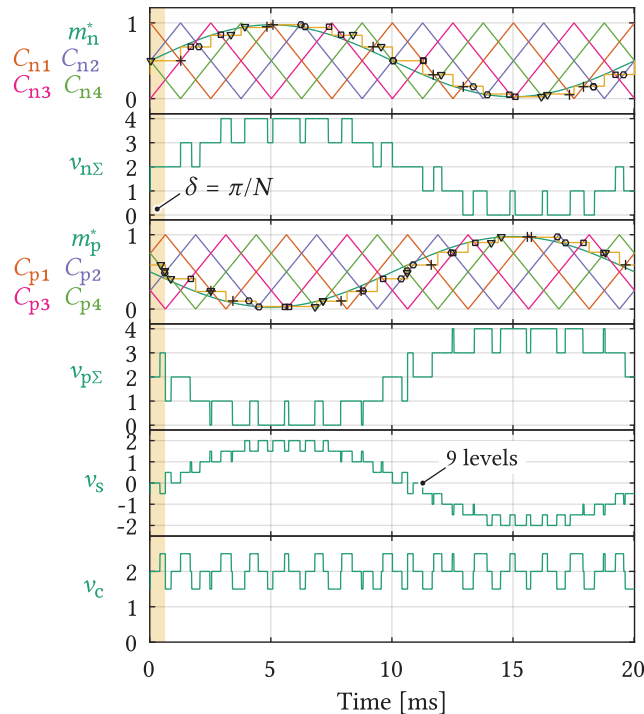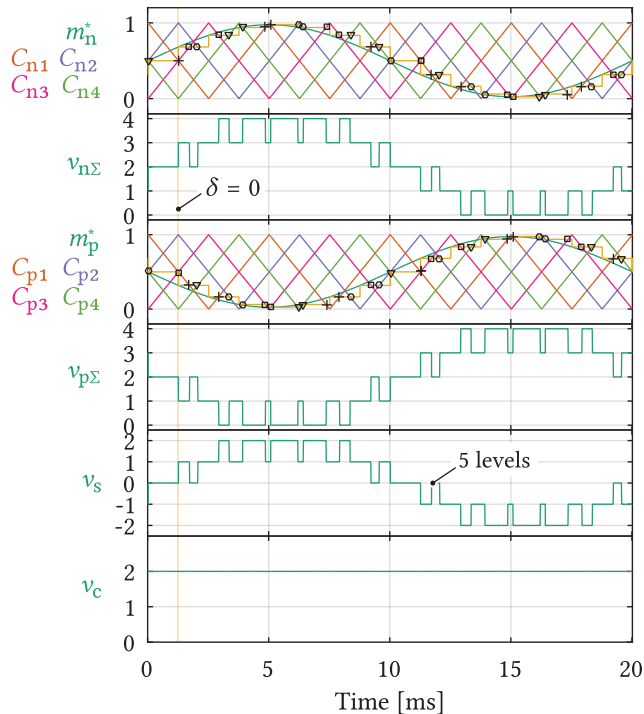
# PSC MODULATION APPLIED TO A REGULAR MMC LEG

Synchronous switching of branches  $\Rightarrow (N + 1)$ -level modulation



Asynchronous switching of branches  $\Rightarrow (2N + 1)$ -level modulation


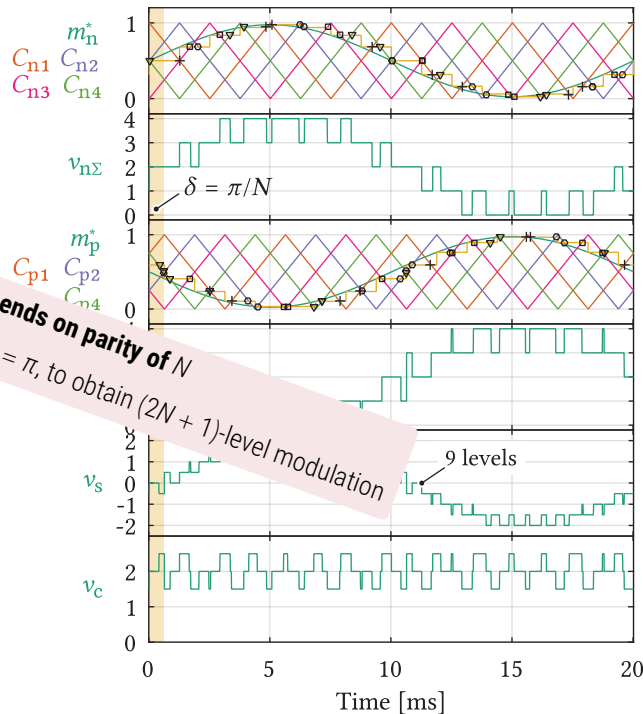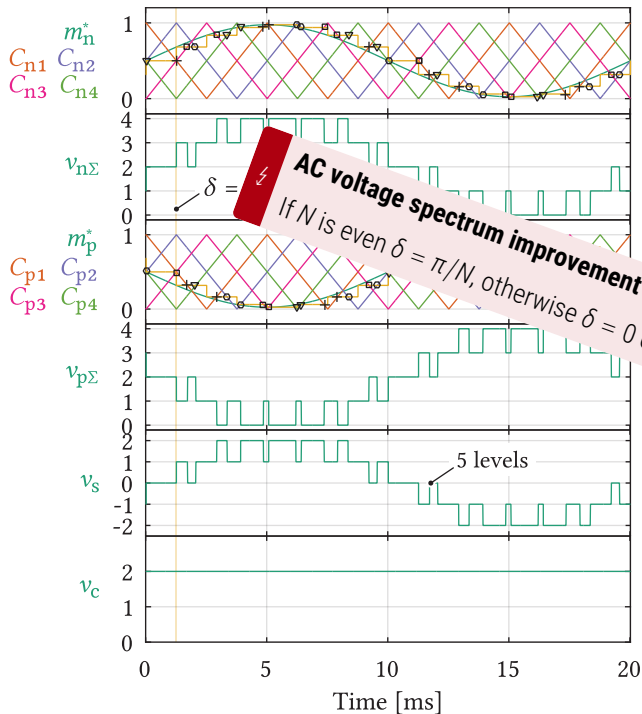
# PSC MODULATION APPLIED TO A REGULAR MMC LEG


Synchronous switching of branches  $\Rightarrow (N + 1)$ -level modulation

Asynchronous switching of branches  $\Rightarrow (2N + 1)$ -level modulation



**AC voltage spectrum improvement depends on parity of  $N$**   
 If  $N$  is even  $\delta = \pi/N$ , otherwise  $\delta = 0$  or  $\delta = \pi$ , to obtain  $(2N + 1)$ -level modulation

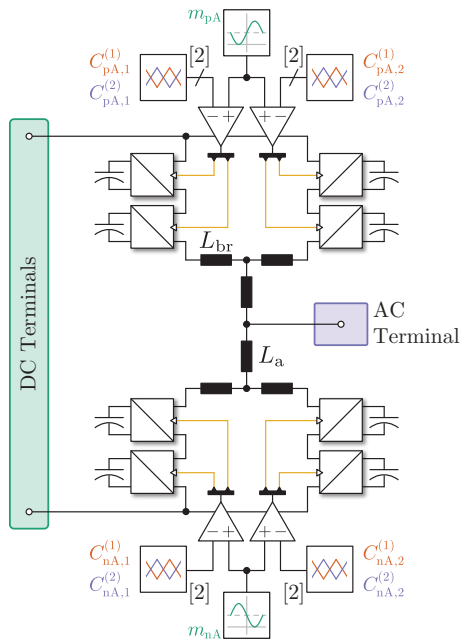
# PSC MODULATION APPLIED TO A MMC LEG WITH TWO PARALLEL SBRs



▲ MMC leg utilizing two parallel SBRs (an exemplary case)

There are two relevant phase-shifts:

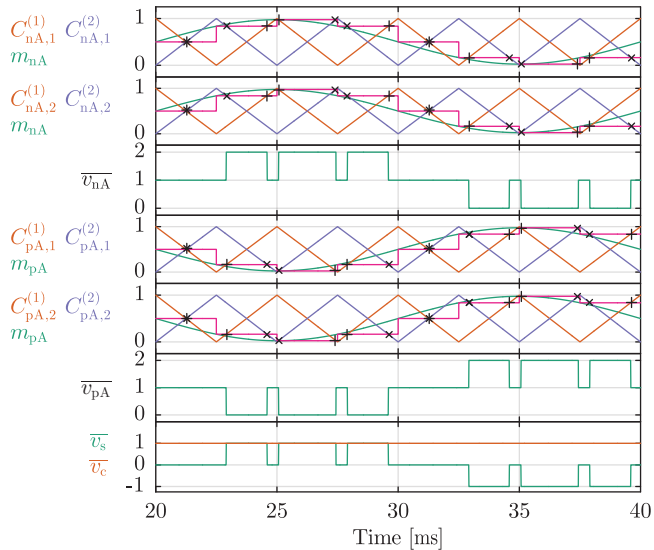
- ▶  $\delta$  - phase shift between two carrier sets within two SBRs belonging to adjacent branches
- ▶  $\beta$  - phase shift between two carrier sets within two SBRs belonging to the same branch



▲  $(N + 1)$ -level modulation



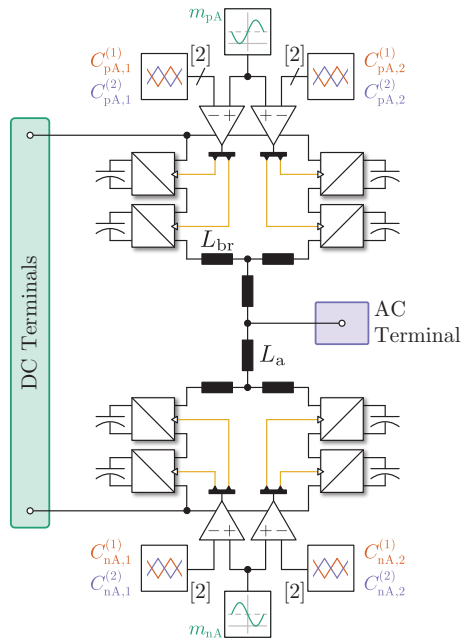
# PSC MODULATION APPLIED TO A MMC LEG WITH TWO PARALLEL SBRs



▲ MMC leg utilizing two parallel SBRs (an exemplary case)


There are two relevant phase-shifts:

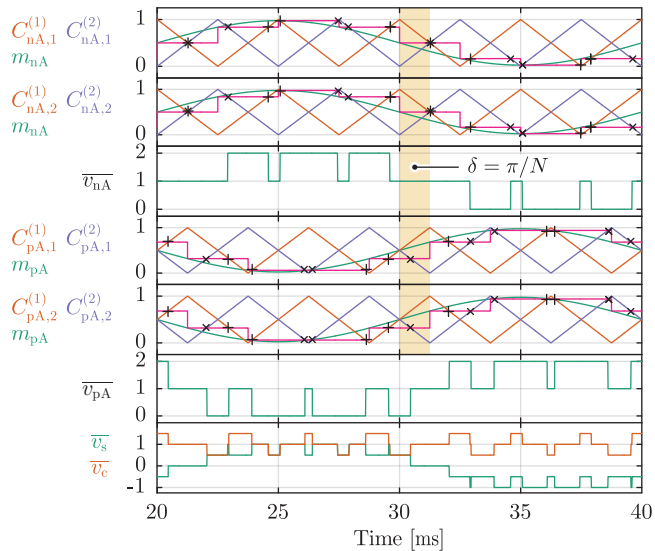- ▶  $\delta$  - phase shift between two carrier sets within two SBRs belonging to adjacent branches
- ▶  $\beta$  - phase shift between two carrier sets within two SBRs belonging to the same branch



▲  $(2N + 1)$ -level modulation

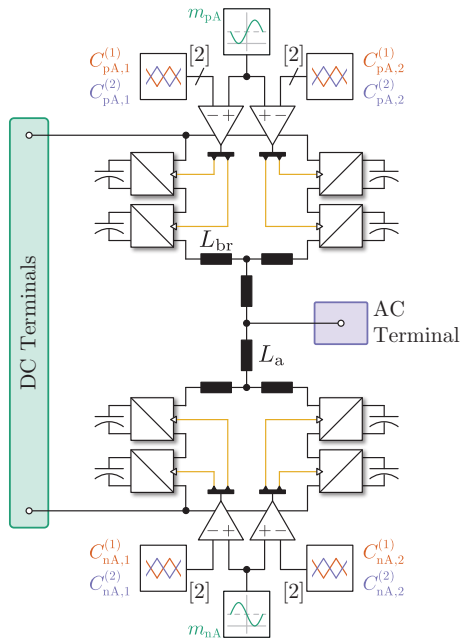
# PSC MODULATION APPLIED TO A MMC LEG WITH TWO PARALLEL SBRs



▲ MMC leg utilizing two parallel SBRs (an exemplary case)


There are two relevant phase-shifts:

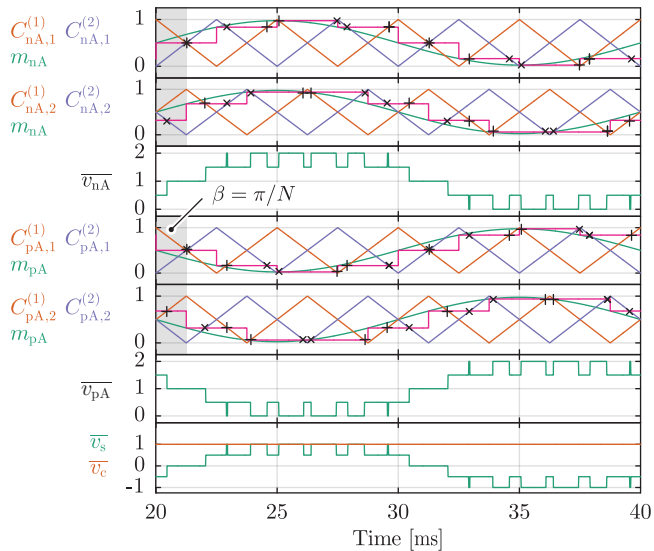- ▶  $\delta$  - phase shift between two carrier sets within two SBRs belonging to adjacent branches
- ▶  $\beta$  - phase shift between two carrier sets within two SBRs belonging to the same branch



▲  $(MN + 1)$ -level modulation

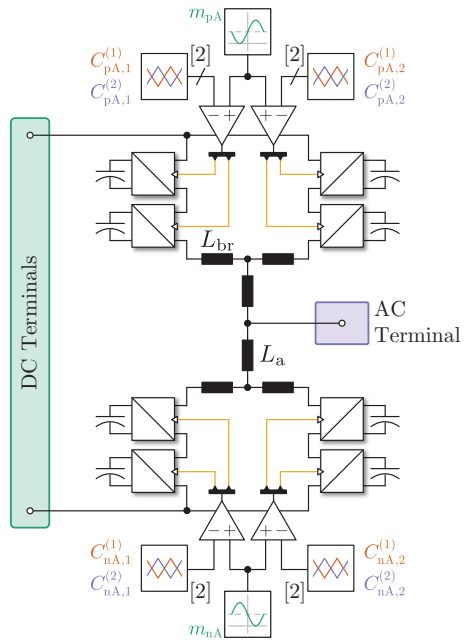
# PSC MODULATION APPLIED TO A MMC LEG WITH TWO PARALLEL SBRs



▲ MMC leg utilizing two parallel SBRs (an exemplary case)

There are two relevant phase-shifts:

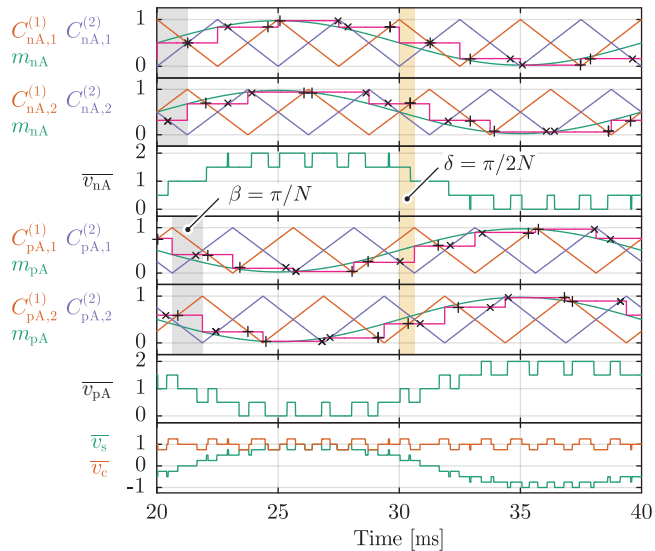- ▶  $\delta$  - phase shift between two carrier sets within two SBRs belonging to adjacent branches
- ▶  $\beta$  - phase shift between two carrier sets within two SBRs belonging to the same branch




▲  $(2MN + 1)$ -level modulation

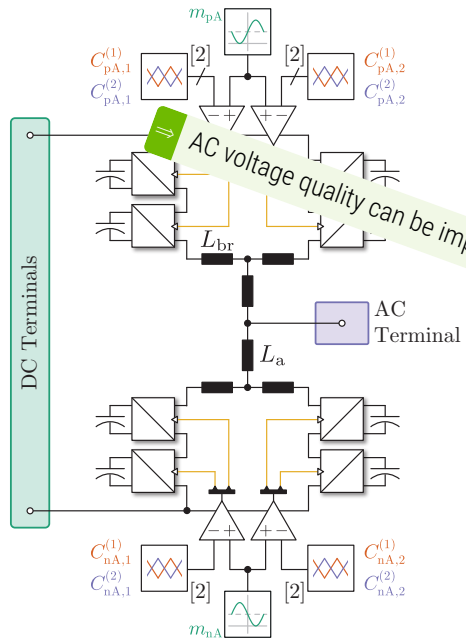
# PSC MODULATION APPLIED TO A MMC LEG WITH TWO PARALLEL SBRs

There are two relevant phase-shifts:

- ▶  $\delta$  - phase shift between two carrier sets within two SBRs belonging to adjacent branches
- ▶  $\beta$  - phase shift between two carrier sets within two SBRs belonging to the same branch



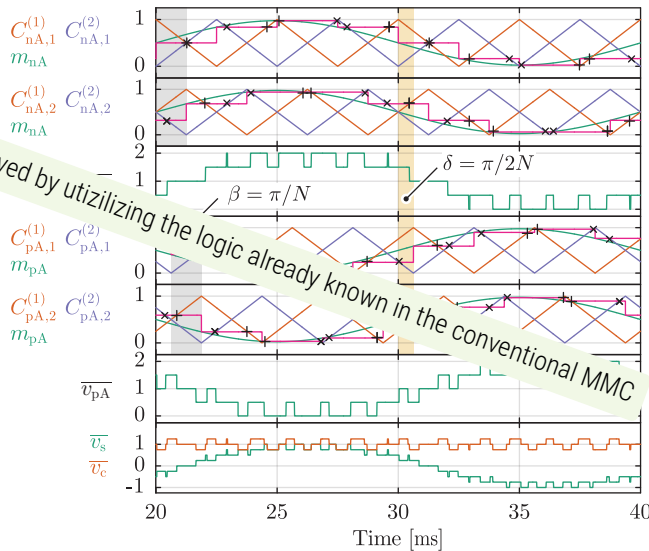▲ MMC leg utilizing two parallel SBRs (an exemplary case)






▲  $(2MN + 1)$ -level modulation

AC voltage quality can be improved by utilizing the logic already known in the conventional MMC
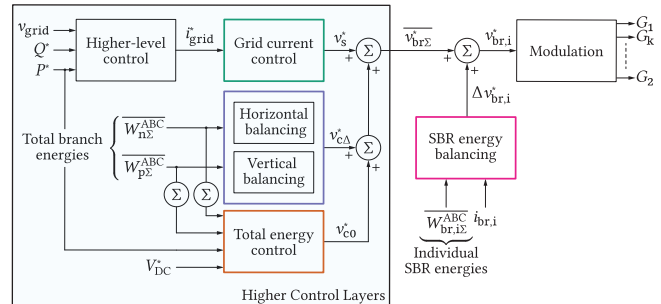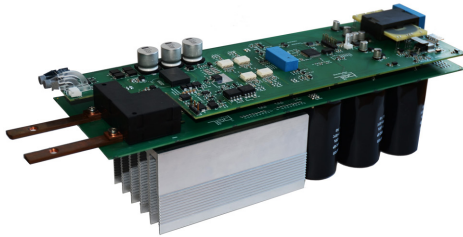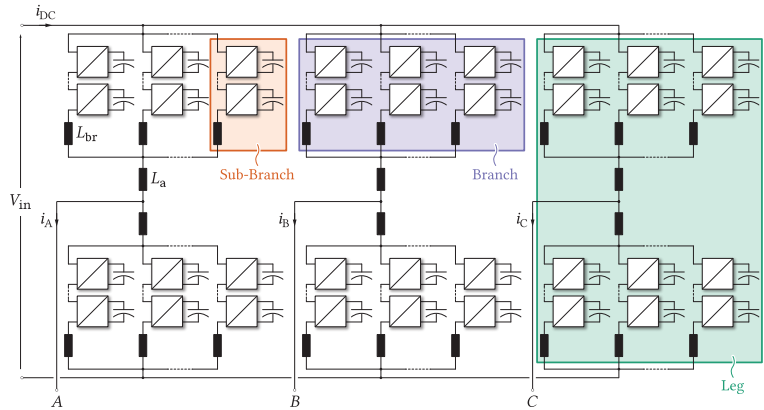
# CONCLUSION

- ▶ **MMC power extension** as a main motivation
- ▶ **Simple and cheap** (no need for major redesign of the converter parts)
- ▶ The challenge is shifted to the **control domain**
- ▶ State of the art control methods + **Additional loops**
- ▶ Possible AC **voltage quality improvement**



# DC-DC CONVERTERS

*Building blocks of Solid State Transformers*


# SOLID-STATE TRANSFORMER (SST)

## Concept and motivation?


- ▶ SST = Switching stages + Isolation
- ▶ Firstly envisioned within AC grids
- ▶ Power Electronic Building Blocks (PEBBs)
- ▶ Conventional transformer vs SST?
- ▶ Operating frequency increase (**MFT**)

	Grid Tx	SST
Controlability	No	Yes
Efficiency	$\eta \geq 99\%$	$P_\gamma$
Q compensation	No	Yes
Fault tolerance	No	Yes
Size	Bulky	Compact

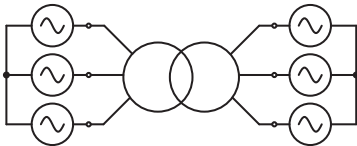**Advantages at the expense of reduced efficiency!**




▲ Conventional AC grid transformer

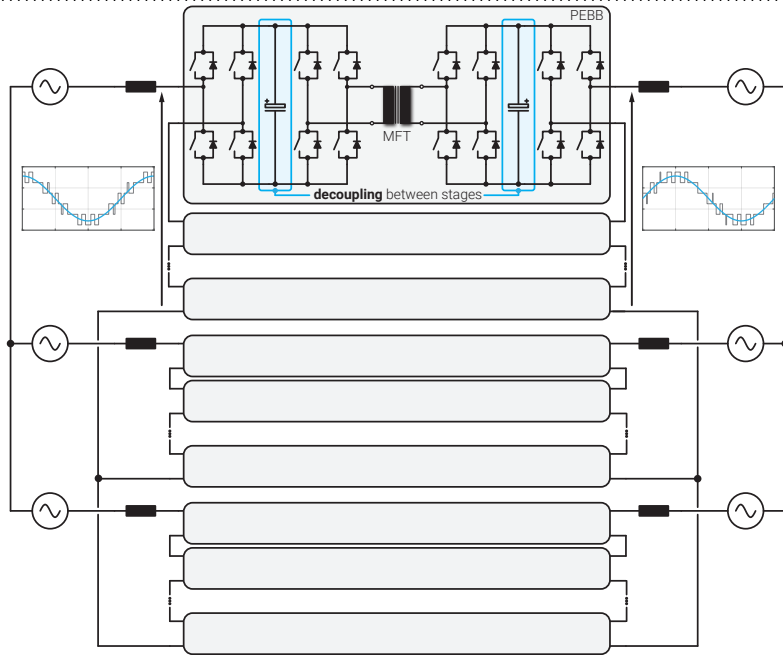


▲ Solid-State Transformer employed with the aim of interfacing two AC systems [28], [29]
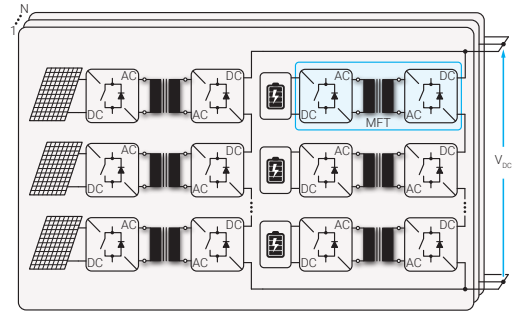
# DC-DC SST


- ▶ Inherent part of the AC-AC SST
- ▶ Expansion of the existing power system
- ▶ Enabling technology for MVDC
- ▶ Penetration of renewable energy sources
- ▶ Fast / Ultra Fast EV charging
- ▶ **Medium Frequency** conversion



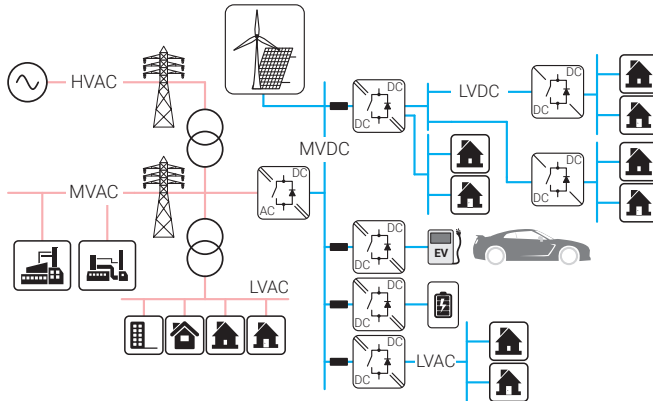▲ Employment of a DC-DC SST within RES-based systems



▲ Concept of a modern power system



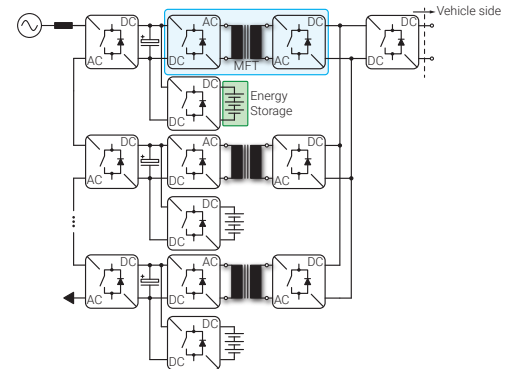


▲ Fast EV charging concept


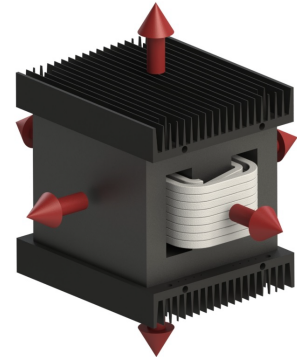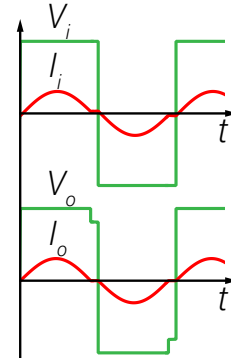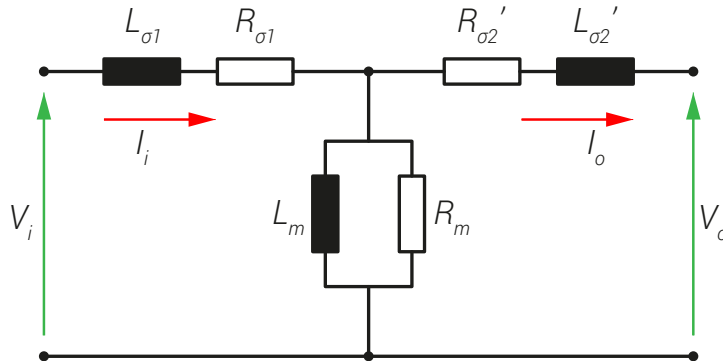
# MFT CHALLENGES

- ▶ **Skin and proximity effect losses:** impact on efficiency and heating
- ▶ **Cooling:** increase of power density  $\Rightarrow$  decrease in size  $\Rightarrow$  less cooling surface  $\Rightarrow$  higher  $R_{th}$   $\Rightarrow$  higher temperature gradients
- ▶ **Non-sinusoidal excitation:** impact on core and winding losses and insulation
- ▶ **Insulation:** coordination and testing taking into account high  $\frac{dV}{dt}$  characteristic for power electronic converters
- ▶ **Accurate electric parameter control:** especially in case of resonant converter applications




▲ Medium Frequency Transformer challenges


⇒ MFT design is generally challenging and requires multiphysics considerations and multiobjective optimization

# MFT NONSINUSOIDAL POWER ELECTRONIC WAVEFORMS


## DAB Converter:

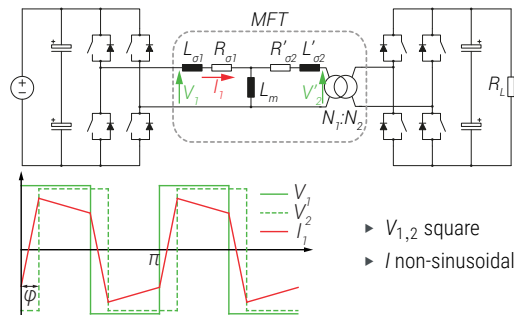

## Series Resonant Converter:

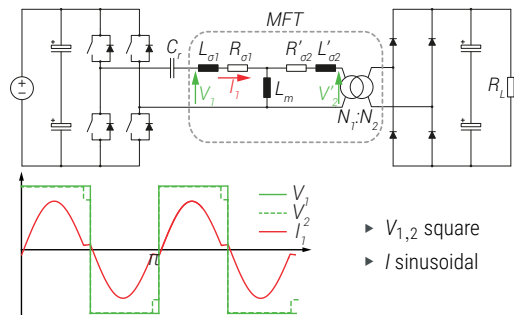


## Core Losses:

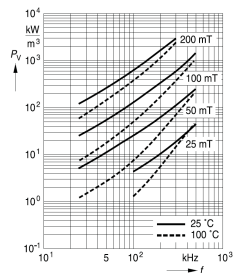

▲ Specific AC core losses

- ▶ Data-sheet - sinusoidal excitation
- ▶ Steinmetz - sinusoidal excitation losses
- ▶ Core is excited with square pulses!
- ▶ Losses must be correctly evaluated
- ▶ Generalization of Steinmetz model



## Winding Losses:

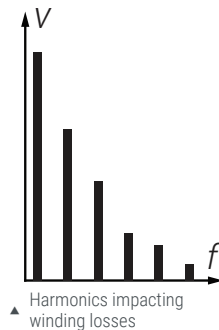

- ▶ Current waveform impacts the winding losses
- ▶ Copper is a linear material
- ▶ Losses can be evaluated in harmonic basis
- ▶ Current harmonic content must be evaluated
- ▶ Losses are the sum of the individual harmonic losses



# MFT ACCURATE PARAMETERS CONTROL

## DAB Converter:

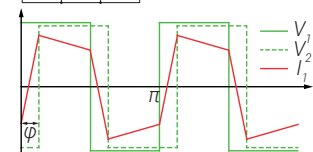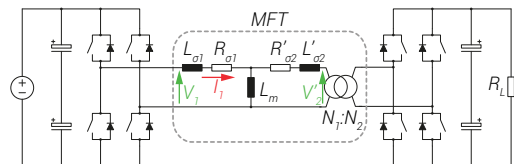

- ▶  $V_{1,2}$  square
- ▶  $I$  non-sinusoidal

## Series Resonant Converter:

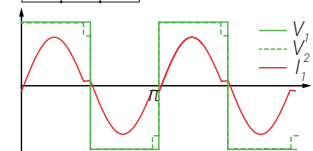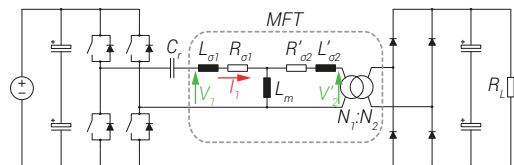

- ▶  $V_{1,2}$  square
- ▶  $I$  sinusoidal

## DAB

- ▶ Leakage Inductance
- ▶ Controllability of the power flow
- ▶ Higher than  $L_{\sigma.min}$  :

$$L_{\sigma.min} = \frac{V_{DC1} V_{DC2} \varphi_{min} (\pi - \varphi_{min})}{2P_{out} \pi^2 f_s n}$$

- ▶ Magnetizing Inductance is normally high

## SRC

- ▶ Leakage inductance is part of resonant circuit
- ▶ Must match the reference:

$$L_{\sigma.ref} = \frac{1}{\omega_0^2 C_r}$$

- ▶ Magnetizing inductance is normally high
- ▶ Reduced in case of LLC
- ▶ Limits the magnetization current to the reference  $I_{m.ref}$
- ▶ Limits the switch-off current and losses

$$L_m = \frac{n V_{DC2}}{4 f_s I_{m.ref}}$$

- ▶  $I_{m.ref}$  has to be sufficiently high to maintain ZVS

# MFT VARIETY OF DESIGNS...

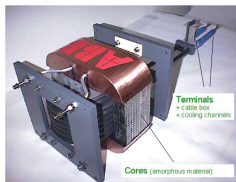


ABB: 350kW, 10kHz



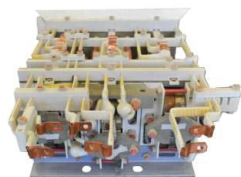


ABB: 3x150kW, 1.8kHz

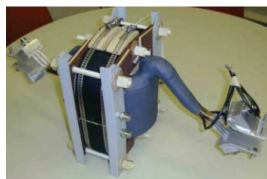


BOMBARDIER: 350kW, 8kHz

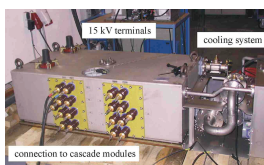


ALSTOM: 1500kW, 5kHz



IKERLAN: 400kW, 5kHz

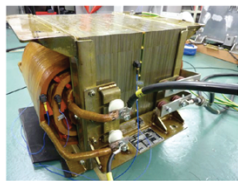


IKERLAN: 400kW, 1kHz

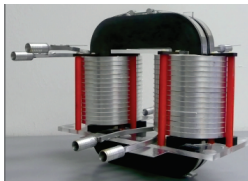


FAU-EN: 450kW, 5.6kHz




CHALMERS: 50kW, 5kHz

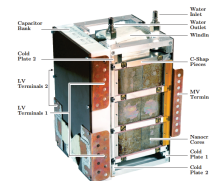


ETHZ: 166kW, 20kHz

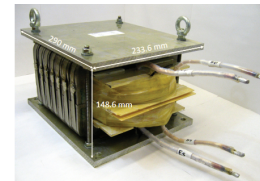


EPFL: 300kW, 2kHz

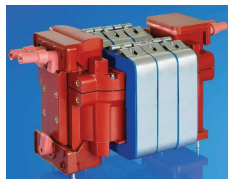


STS: 450kW, 8kHz

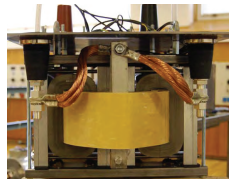

KTH: 170kW, 4kHz

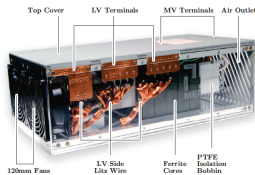

ETHZ: 166kW, 20kHz

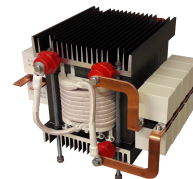

EPFL: 100kW, 10kHz

?

ACME: ???kW, ???kHz


# HP DC-DC CONVERTERS

*Going into Medium Voltage..*

# DC-DC SST - BASIC CONCEPTS
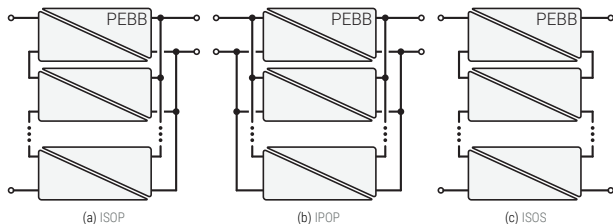
## Fractional power processing


- ▶ Multiple MFTs
- ▶ Equal power distribution among PEBBs
- ▶ MFT isolation?
- ▶ Various PEBB configurations




- ▲ Different structures employed depending upon the voltage level
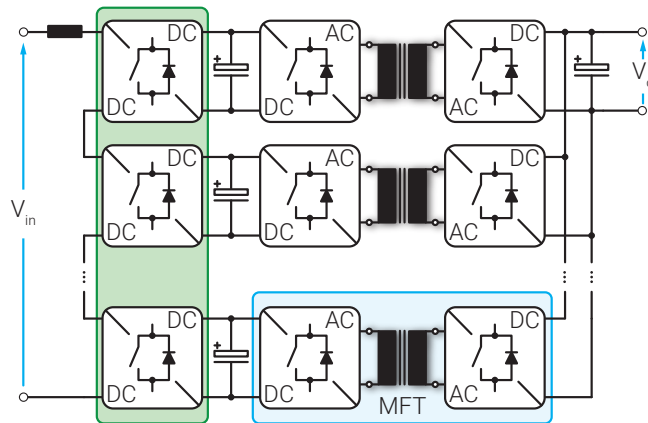
## Bulk power processing

- ▶ Single MFT
- ▶ Isolation solved only once
- ▶ Various configurations/operating principles





- ▲ ISOP Structure

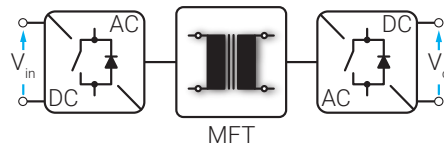

- ▲ Bulk power processing concept



# COMMON PEBB CONFIGURATIONS

## Dual-Active Bridge

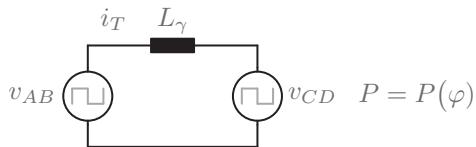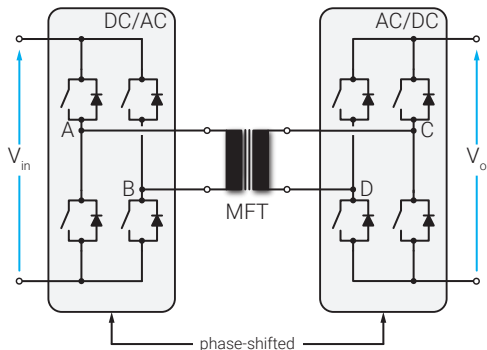

▲ Dual Active Bridge [30]

## Resonant Converters

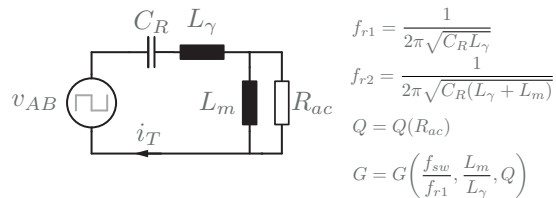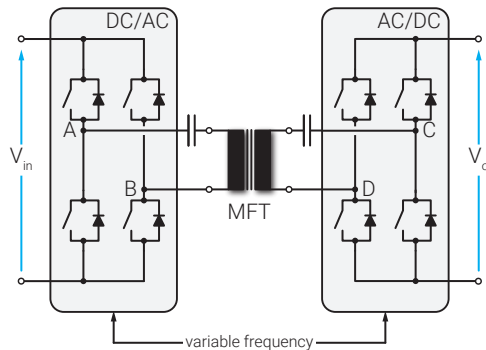


▲ LCL Resonant Converter

# 1-PHASE DAB

*Basic operating principles*



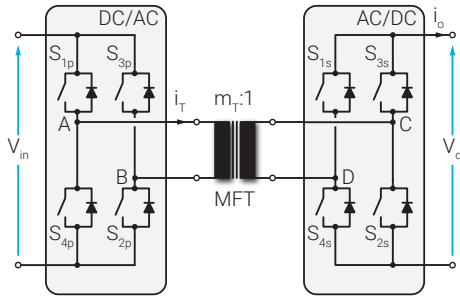
# SINGLE-PHASE (1PH) DUAL ACTIVE BRIDGE (DAB)



## Power equation



$$P = \frac{1}{T} \int_0^T v_{AB} i_T dt$$

$$= m_T \frac{V_{in} V_o}{\omega L_{\Sigma}} \varphi \left( 1 - \frac{|\varphi|}{\pi} \right)$$

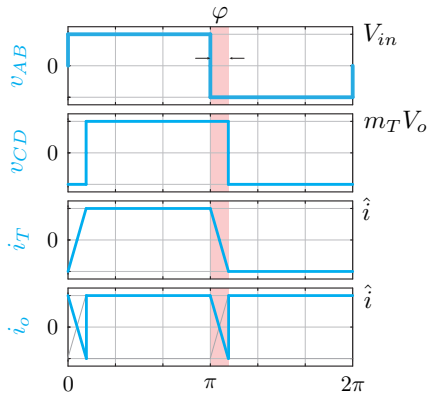

▲ 1PH-DAB with its relevant waveforms
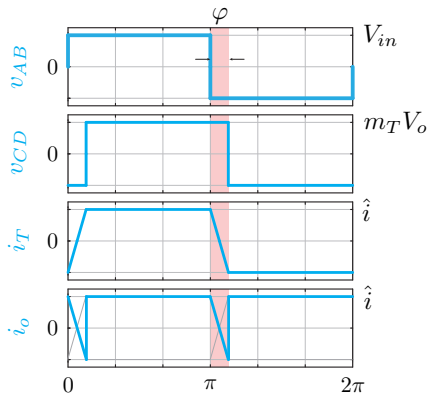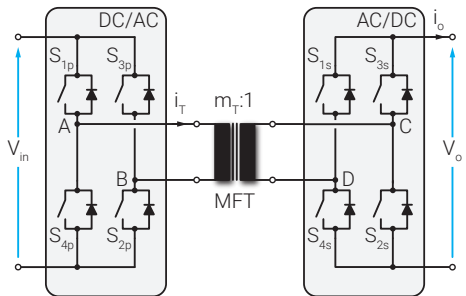
# SINGLE-PHASE (1PH) DUAL ACTIVE BRIDGE (DAB)




▲ 1PH-DAB with its relevant waveforms

## Power equation



$$P = \frac{1}{T} \int_0^T v_{AB} i_T dt$$

$$= m_T \frac{V_{in} V_o}{\omega L_{\Sigma}} \varphi \left( 1 - \frac{|\varphi|}{\pi} \right)$$

## Switching cycle

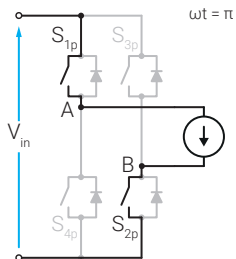
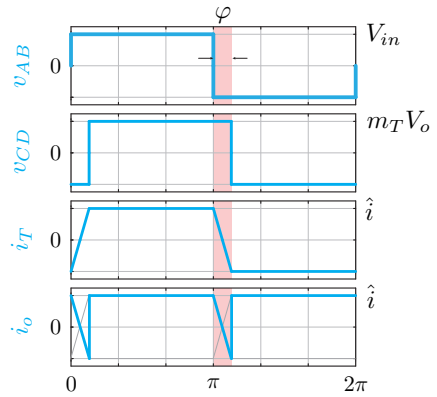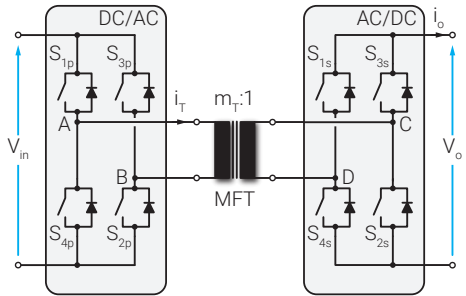
# SINGLE-PHASE (1PH) DUAL ACTIVE BRIDGE (DAB)




▲ 1PH-DAB with its relevant waveforms

## Power equation



$$P = \frac{1}{T} \int_0^T v_{AB} i_T dt$$

$$= m_T \frac{V_{in} V_o}{\omega L_{\Sigma}} \varphi \left( 1 - \frac{|\varphi|}{\pi} \right)$$

## Switching cycle

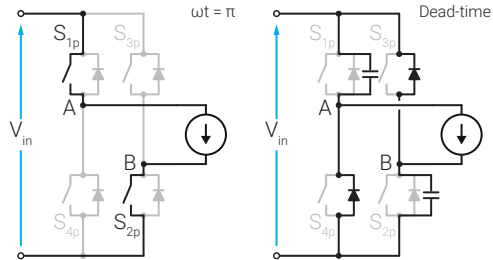
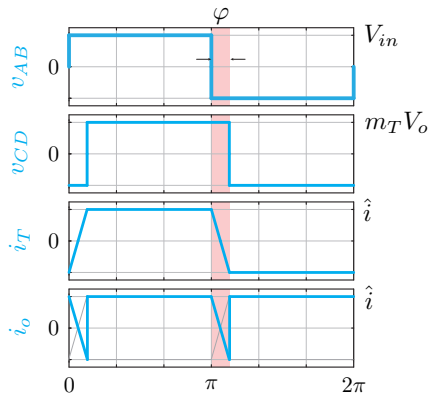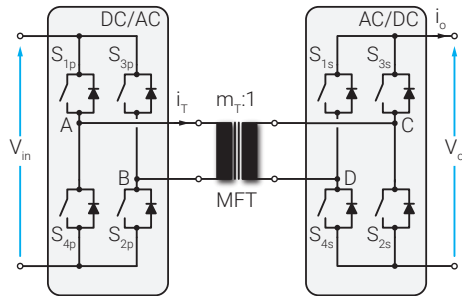
# SINGLE-PHASE (1PH) DUAL ACTIVE BRIDGE (DAB)




▲ 1PH-DAB with its relevant waveforms

## Power equation



$$P = \frac{1}{T} \int_0^T v_{AB} i_T dt$$

$$= m_T \frac{V_{in} V_o}{\omega L_{\Sigma}} \varphi \left( 1 - \frac{|\varphi|}{\pi} \right)$$

## Switching cycle

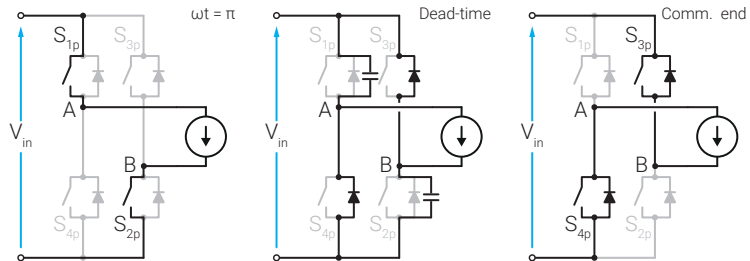
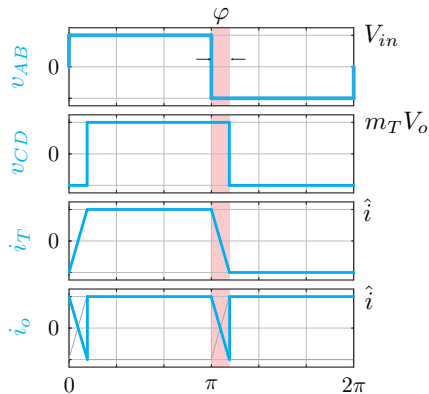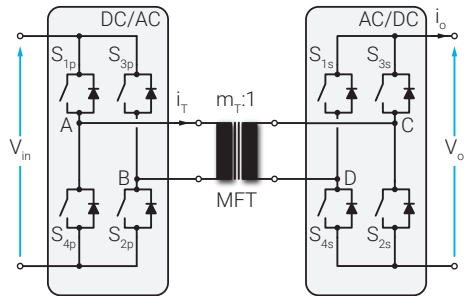
# SINGLE-PHASE (1PH) DUAL ACTIVE BRIDGE (DAB)




▲ 1PH-DAB with its relevant waveforms

## Power equation



$$P = \frac{1}{T} \int_0^T v_{AB} i_T dt$$

$$= m_T \frac{V_{in} V_o}{\omega L_{\Sigma}} \varphi \left( 1 - \frac{|\varphi|}{\pi} \right)$$

## Switching cycle

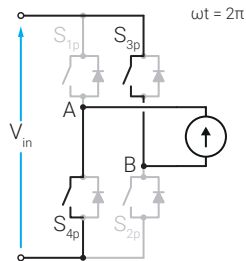
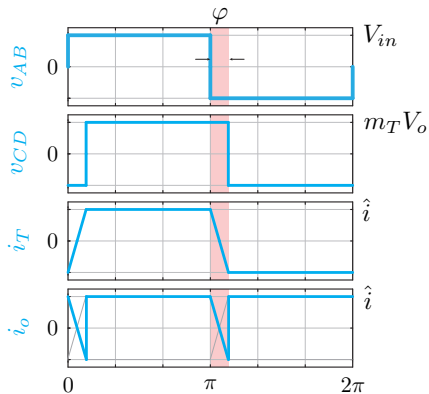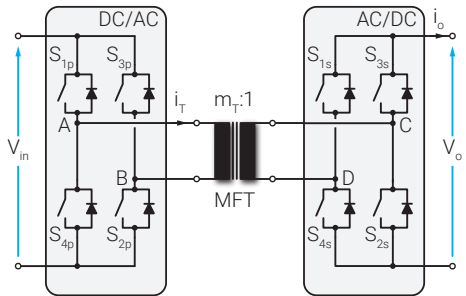
# SINGLE-PHASE (1PH) DUAL ACTIVE BRIDGE (DAB)




▲ 1PH-DAB with its relevant waveforms

## Power equation



$$P = \frac{1}{T} \int_0^T v_{AB} i_T dt$$

$$= m_T \frac{V_{in} V_o}{\omega L_{\Sigma}} \varphi \left( 1 - \frac{|\varphi|}{\pi} \right)$$

## Switching cycle

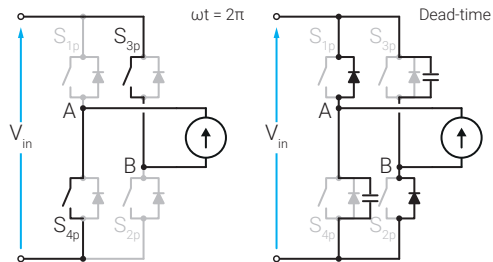
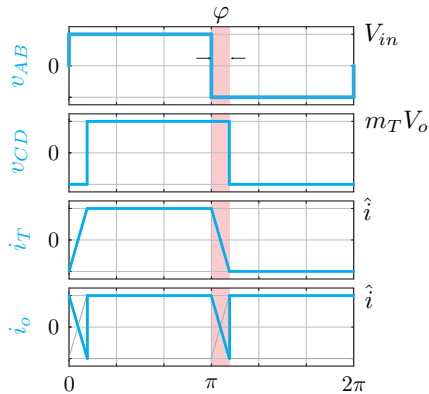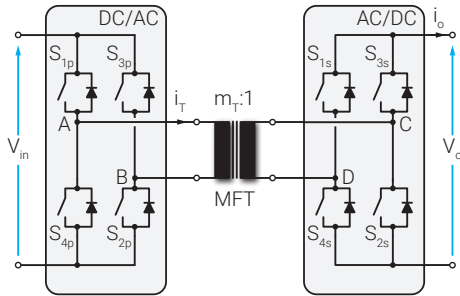
# SINGLE-PHASE (1PH) DUAL ACTIVE BRIDGE (DAB)




▲ 1PH-DAB with its relevant waveforms

## Power equation

$$P = \frac{1}{T} \int_0^T v_{AB} i_T dt$$

$$= m_T \frac{V_{in} V_o}{\omega L_{\Sigma}} \varphi \left( 1 - \frac{|\varphi|}{\pi} \right)$$

## Switching cycle

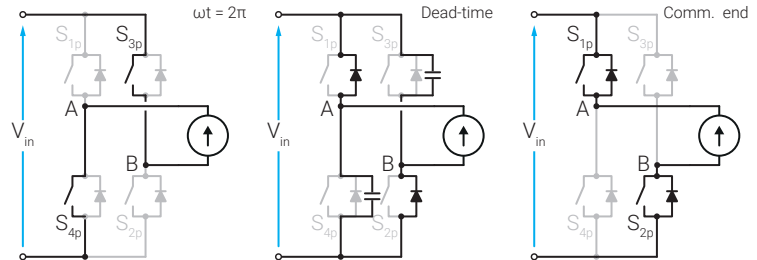

## Main features



- ▶ Phase-Modulated converter
- ▶ Simple power flow control
- ▶ Soft-switching capability

# 3-PHASE DAB


*Somewhat more complicated...*




# THREE-PHASE (3PH) DAB

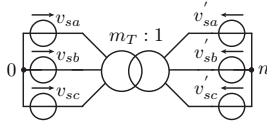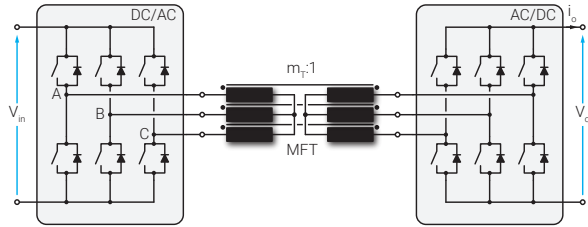
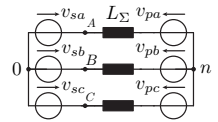
$$v_{an} = \frac{2v_{sa} - v_{sb} - v_{sc}}{3}$$


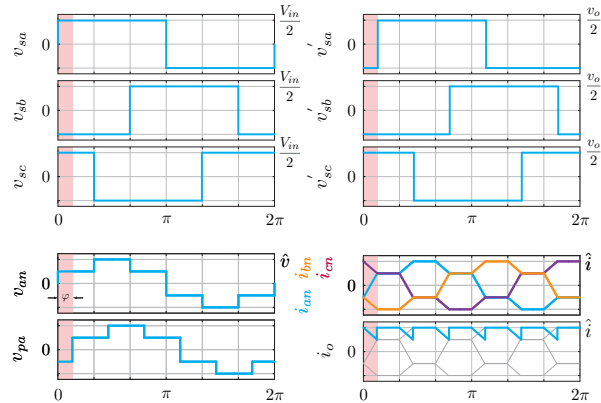
$$v_{pa} = m_T \frac{2v'_{sa} - v'_{sb} - v'_{sc}}{3}$$



▲ 3PH-DAB with its relevant waveforms

## Power Equation



$$P = \frac{3}{T} \int_0^T v_{an} i_{an} dt$$

$$= m_T \frac{4}{3} \frac{V_{in} V_o}{\omega L_{\Sigma}} \varphi \left( \frac{1}{2} - \frac{3|\varphi|}{8\pi} \right)$$


## 1-PH vs 3-PH DAB

	Control Simplicity	Tx utilization	Soft Switching	In/Out current ripple
1-PH DAB	☹️	☹️	☺️	☹️
3-PH DAB	☺️	☺️	☺️	☺️


# THREE-PHASE (3PH) DAB

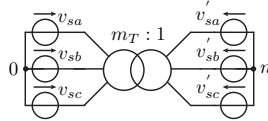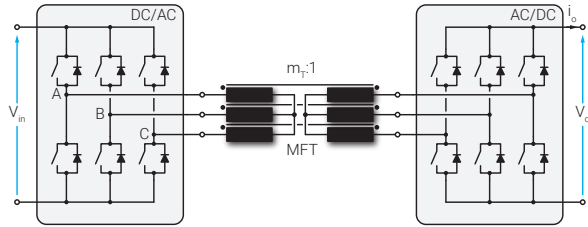
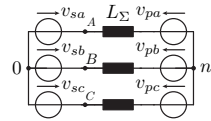
$$v_{an} = \frac{2v_{sa} - v_{sb} - v_{sc}}{3}$$


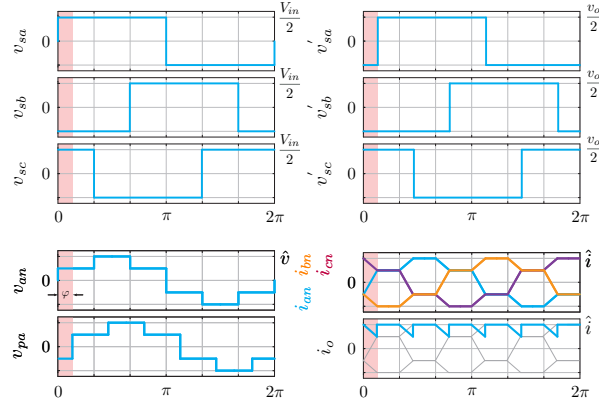
$$v_{pa} = m_T \frac{2v'_{sa} - v'_{sb} - v'_{sc}}{3}$$



▲ 3PH-DAB with its relevant waveforms

## Power Equation

$$P = \frac{3}{T} \int_0^T v_{an} i_{an} dt$$


$$= m_T \frac{4}{3} \frac{V_{in} V_o}{\omega L_{\Sigma}} \varphi \left( \frac{1}{2} - \frac{3|\varphi|}{8\pi} \right)$$

## 1-PH vs 3-PH DAB

	Control Simplicity	Tx utilization	Soft Switching	In/Out current ripple
1-PH DAB	☹️	☹️	☺️	☹️
3-PH DAB	☺️	☺️	☺️	☺️

⇒ 3PH-DAB is considered favorable!

# 3PH-DAB CONTROL

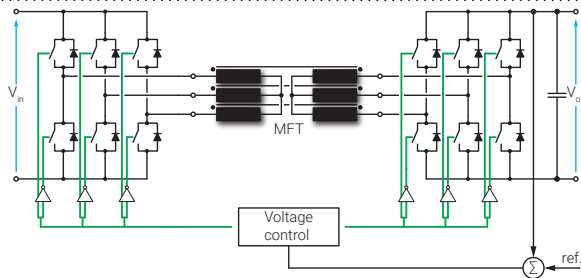


▲ Observed DAB-based system


Assuming  $P_{in} = P_{out}$ :

$$\begin{aligned} \forall \varphi i_o &= \frac{4m_T V_{in} V_o}{3\omega L} \varphi \left( \frac{1}{2} - \frac{3|\varphi|}{8\pi} \right) \\ \Rightarrow i_o &= \frac{4m_T V_{in} V_o}{3\omega L} \varphi \left( \frac{1}{2} - \frac{3|\varphi|}{8\pi} \right) \end{aligned}$$



⇒ Controlled current source behavior!

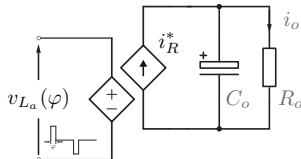

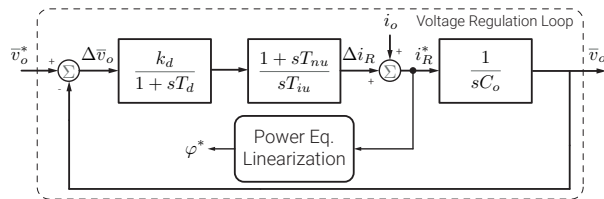
▲ DAB equivalent circuit seen from the controlled side



▲ Output voltage control loop

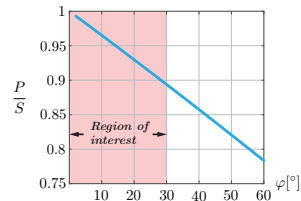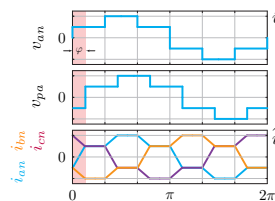

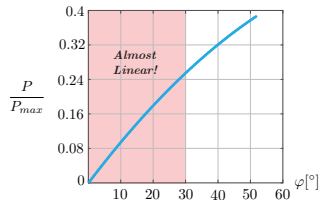
$$\frac{P}{S} = \frac{4\pi - 3\varphi}{2\pi \sqrt{\frac{4\pi - \varphi}{\pi}}}$$



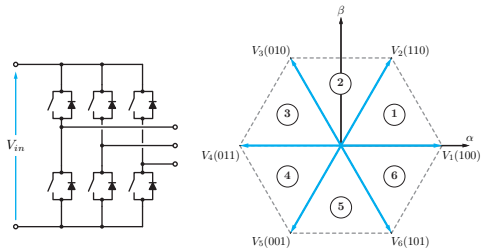
# ABRUPT PHASE ANGLE CHANGES? (I)

- ▶ Six step modulation
- ▶ Limited number of voltage states

For  $\omega t \in [(k-1)\frac{\pi}{3}, k\frac{\pi}{3}]$



▶ Either side of the 3PH-DAB

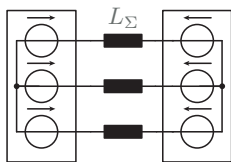

$$\mathbf{v}_p = \hat{V} \angle \varphi \quad \mathbf{v}_s = \hat{V} \angle 0$$

▶ DAB equivalent circuit


$$\mathbf{V}_p = \mathbf{V}_k$$

$$\mathbf{V}_s = \begin{cases} \mathbf{V}_{k-1}, & \omega t \in [(k-1)\frac{\pi}{3}, (k-1)\frac{\pi}{3} + \varphi] \\ \mathbf{V}_k, & \omega t \in [(k-1)\frac{\pi}{3} + \varphi, k\frac{\pi}{3}] \end{cases}$$

$$L \frac{d\mathbf{i}}{dt} = \mathbf{V}_p - \mathbf{V}_s$$

$$= \begin{cases} \hat{V} e^{j(k+1)\frac{\pi}{3}}, & \omega t \in [(k-1)\frac{\pi}{3}, (k-1)\frac{\pi}{3} + \varphi] \\ 0, & \omega t \in [(k-1)\frac{\pi}{3} + \varphi, k\frac{\pi}{3}] \end{cases}$$
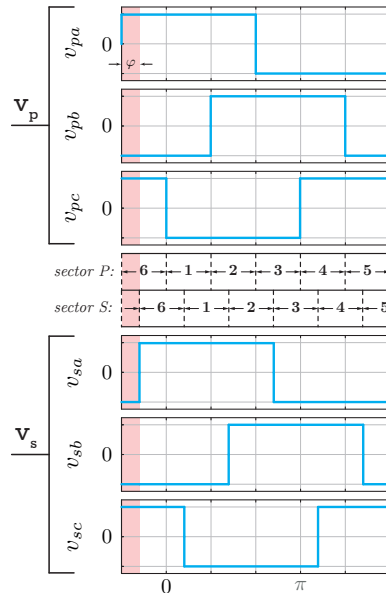
$$\mathbf{i} = \begin{cases} \mathbf{i}_{0,k} + \frac{\hat{V}}{L\omega} t e^{j(k+1)\frac{\pi}{3}}, & \omega t \in [(k-1)\frac{\pi}{3}, (k-1)\frac{\pi}{3} + \varphi] \\ \mathbf{i}_{0,k} + \frac{\hat{V}}{\omega L} \varphi e^{j(k+1)\frac{\pi}{3}}, & \omega t \in [(k-1)\frac{\pi}{3} + \varphi, k\frac{\pi}{3}] \end{cases}$$




▶ DAB switching signals

? Current shape in the  $\alpha\beta$  plane?

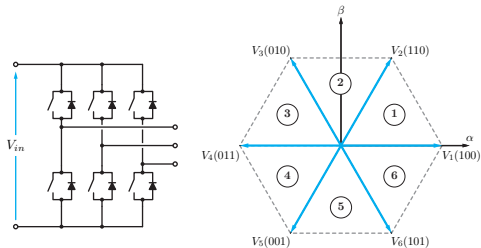
# ABRUPT PHASE ANGLE CHANGES? (I)

- ▶ Six step modulation
- ▶ Limited number of voltage states

For  $\omega t \in [(k-1)\frac{\pi}{3}, k\frac{\pi}{3}]$



▲ Either side of the 3PH-DAB

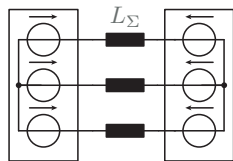

$$\mathbf{v}_p = \hat{V} \angle \varphi \quad \mathbf{v}_s = \hat{V} \angle 0$$

▲ DAB equivalent circuit

$$\mathbf{V}_p = \mathbf{V}_k$$


$$\mathbf{V}_s = \begin{cases} \mathbf{V}_{k-1}, & \omega t \in [(k-1)\frac{\pi}{3}, (k-1)\frac{\pi}{3} + \varphi] \\ \mathbf{V}_k, & \omega t \in [(k-1)\frac{\pi}{3} + \varphi, k\frac{\pi}{3}] \end{cases}$$

$$L \frac{d\mathbf{i}}{dt} = \mathbf{V}_p - \mathbf{V}_s$$

$$= \begin{cases} \hat{V} e^{j(k+1)\frac{\pi}{3}}, & \omega t \in [(k-1)\frac{\pi}{3}, (k-1)\frac{\pi}{3} + \varphi] \\ 0, & \omega t \in [(k-1)\frac{\pi}{3} + \varphi, k\frac{\pi}{3}] \end{cases}$$

$$\mathbf{i} = \begin{cases} \mathbf{i}_{0,k} + \frac{\hat{V}}{L\omega} t e^{j(k+1)\frac{\pi}{3}}, & \omega t \in [(k-1)\frac{\pi}{3}, (k-1)\frac{\pi}{3} + \varphi] \\ \mathbf{i}_{0,k} + \frac{\hat{V}}{\omega L\omega} \varphi e^{j(k+1)\frac{\pi}{3}}, & \omega t \in [(k-1)\frac{\pi}{3} + \varphi, k\frac{\pi}{3}] \end{cases}$$

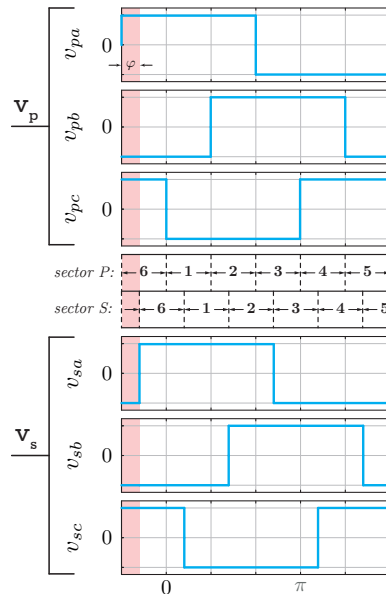- ▶ Amplitude of the change proportional to  $\varphi$
- ▶ Phase change in  $60^\circ$  steps



▲ DAB switching signals

? Current shape in the  $\alpha\beta$  plane?

⇒ Current slides along a hexagon!

# ABRUPT PHASE ANGLE CHANGES? (II)

---

## Recap

- ▶ Limited number of voltage states  $V_p$  and  $V_s$
- ▶ Current vector stepwise phase changes ( $60^\circ$ )
- ▶ Current vector magnitude directly proportional to phase angle
- ▶ Current vector slides along the hexagon [31], [32]

# ABRUPT PHASE ANGLE CHANGES? (II)

---

## Recap

- ▶ Limited number of voltage states  $V_p$  and  $V_s$
- ▶ Current vector stepwise phase changes ( $60^\circ$ )
- ▶ Current vector magnitude directly proportional to phase angle
- ▶ Current vector slides along the hexagon [31], [32]

? What if the phase angle gets abruptly changed?

# ABRUPT PHASE ANGLE CHANGES? (II)

## Recap

- ▶ Limited number of voltage states  $V_p$  and  $V_s$
- ▶ Current vector stepwise phase changes ( $60^\circ$ )
- ▶ Current vector magnitude directly proportional to phase angle
- ▶ Current vector slides along the hexagon [31], [32]

? What if the phase angle gets abruptly changed?

- ▶ New current vector trajectory
- ▶ Hexagon decentralization  $\Rightarrow$  Transformer currents asymmetry!

Inverse  $\alpha\beta 0$  transformation:

$$\begin{bmatrix} i_a^{off} \\ i_b^{off} \\ i_b^{off} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 1 \\ -\frac{1}{2} & \frac{\sqrt{3}}{2} & 1 \\ -\frac{1}{2} & -\frac{\sqrt{3}}{2} & 1 \end{bmatrix} \cdot \begin{bmatrix} i_{a,hex}^{off} \\ i_{\beta,hex}^{off} \\ 0 \end{bmatrix}$$


⚡ Time constant  $L_\Sigma/R_\Sigma$  determines asymmetric components decay!



# ABRUPT PHASE ANGLE CHANGES? (III)


- ▲ Safe way of achieving phase angle change (I)

## Applied phase angle sequence:

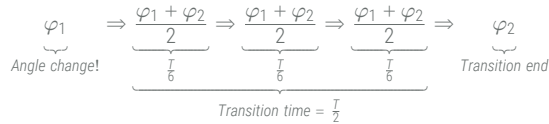

- ▲ Safe way of achieving phase angle change (II)


## Applied phase angle sequence:

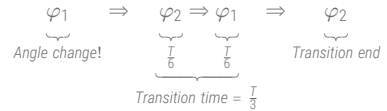

# MEDIUM VOLTAGE DC-DC


*Extending previously presented concepts...*

# HOW TO HANDLE HIGH/MEDIUM VOLTAGES?

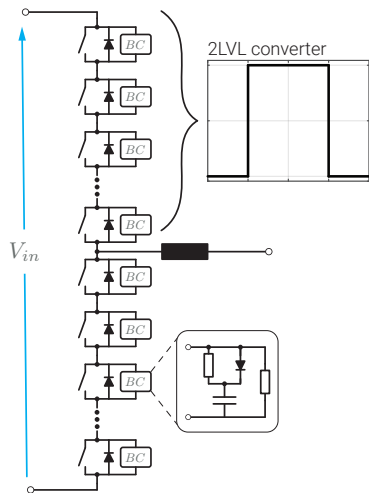


▲ Series connection of switches [33]

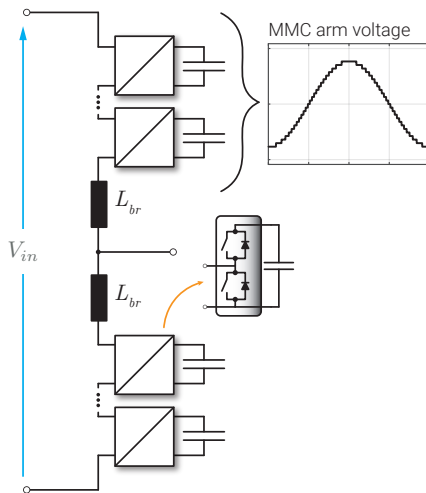- ▶ Series connection of switches with snubbers
- ▶ Two voltage levels ( $n_{LVL} = 2$ )
- ▶ Two-Level voltage waveforms



▲ Modular Multilevel Converter (MMC)

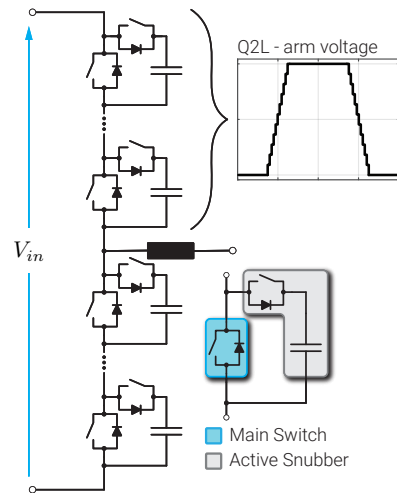- ▶ Series connection of Submodules (SM)
- ▶  $n_{LVL}$  depending upon number of SMs
- ▶ Arbitrary voltage waveform generation




▲ Quasi Two-Level (Q2L) Converter [34], [35]


- ▶ Series connection of MMC-alike SMs
- ▶  $n_{LVL}$  depending upon number of SMs
- ▶ Quasi Two-Level (trapezoidal) voltage waveform
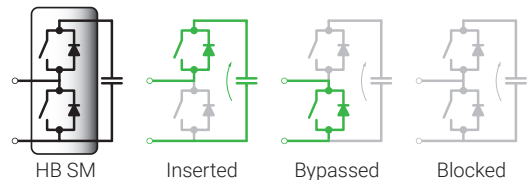
# MODULAR MULTILEVEL CONVERTER (MMC)


- ▶ Variety of conversion possibilities
- ▶ Variety of modulations
- ▶ Different types of submodules (SMs)
  - ▶ Half-Bridge (HB)
  - ▶ Full-Bridge (FB)
  - ▶ Others...
- ▶ Arbitrary voltage waveform generation



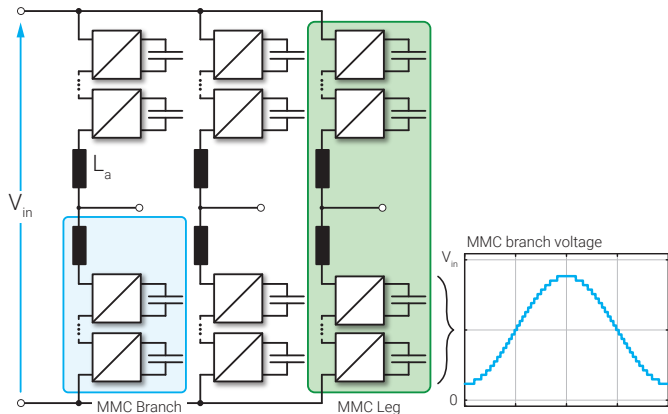▶ Half-Bridge submodule and its allowed states




▶ Modular Multilevel Converter (MMC)

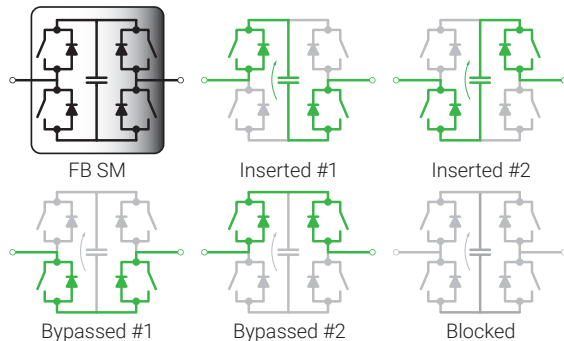

▶ Full-Bridge submodule and its allowed states

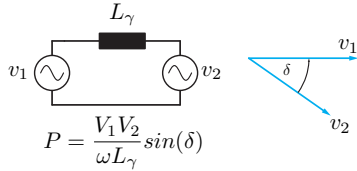
# MMC-BASED DUAL ACTIVE BRIDGE (DAB)

- ▶ Basic operation principles are retained
- ▶ Easy to comprehend (AC equivalent)




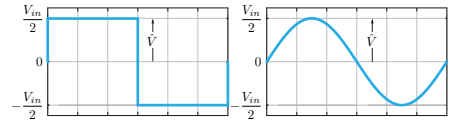
## Challenges?

- ▶ Modulation choice (sine, square, etc ... ?)
- ▶ System design ( $N$  vs  $V_{grid}$ )
- ▶ Energy balancing
- ▶ Q2L mode & capacitors sizing
- ▶ Engagement within bipolar grids




$$P_{sq} = \frac{\hat{V}^2}{\omega L} \varphi \left(1 - \frac{\varphi}{\pi}\right)$$
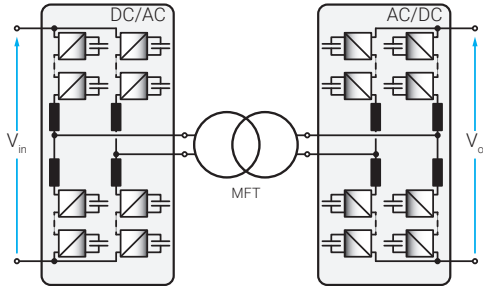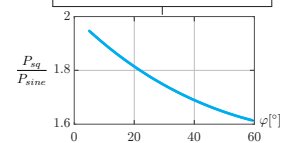
$$P_{sine} = \frac{\hat{V}^2}{2\omega L} \sin(\varphi)$$




▲ MMC-based 1PH-DAB [36]

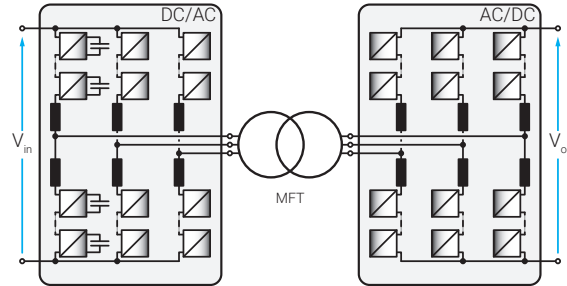

▲ MMC-based 3PH-DAB


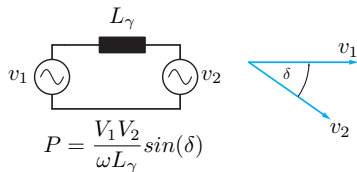
# MMC-BASED DUAL ACTIVE BRIDGE (DAB)

- ▶ Basic operation principles are retained
- ▶ Easy to comprehend (AC equivalent)



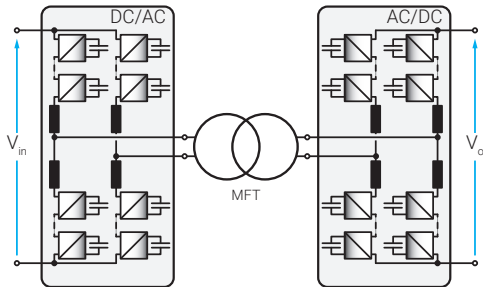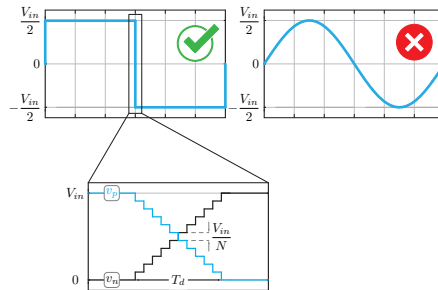
## Challenges?

- ▶ Modulation choice (sine, square, etc ... ?)
- ▶ System design ( $N$  vs  $V_{grid}$ )
- ▶ Energy balancing
- ▶ Q2L mode & capacitors sizing
- ▶ Engagement within bipolar grids




▲ MMC-based 1PH-DAB [36]

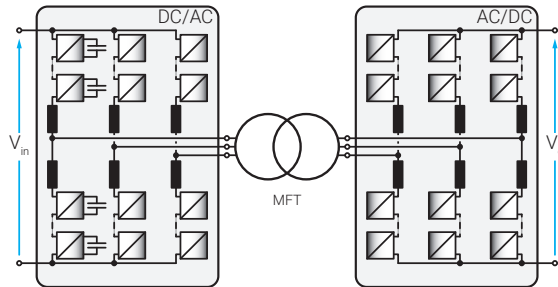

▲ MMC-based 3PH-DAB

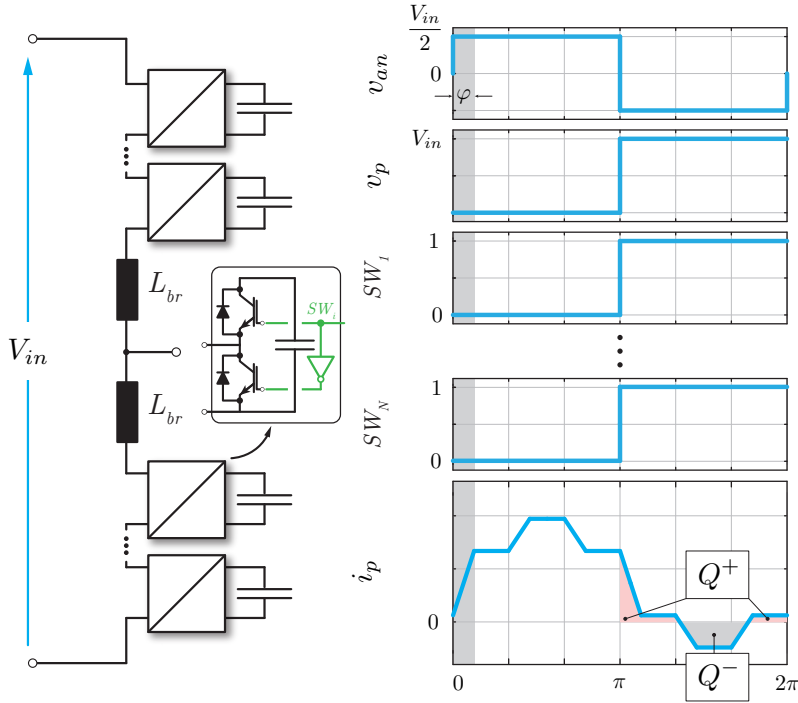
# MMC ENERGY BALANCING AND QUASI SQUARE WAVE OPERATION (I)




▲ MMC operating as a two level converter and its relevant waveforms

Ideally,  $Q^+ = Q^- \Rightarrow$  **Natural balancing** 😊  
 However, reality is different... 😞

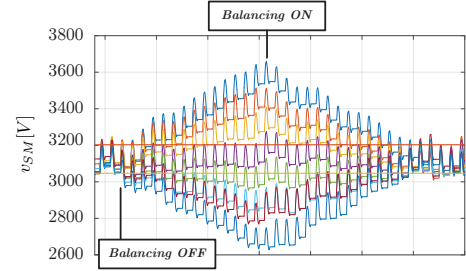- ▶ Branch resistances affect the MMC current
- ▶ Not all the switches are gated at the same time



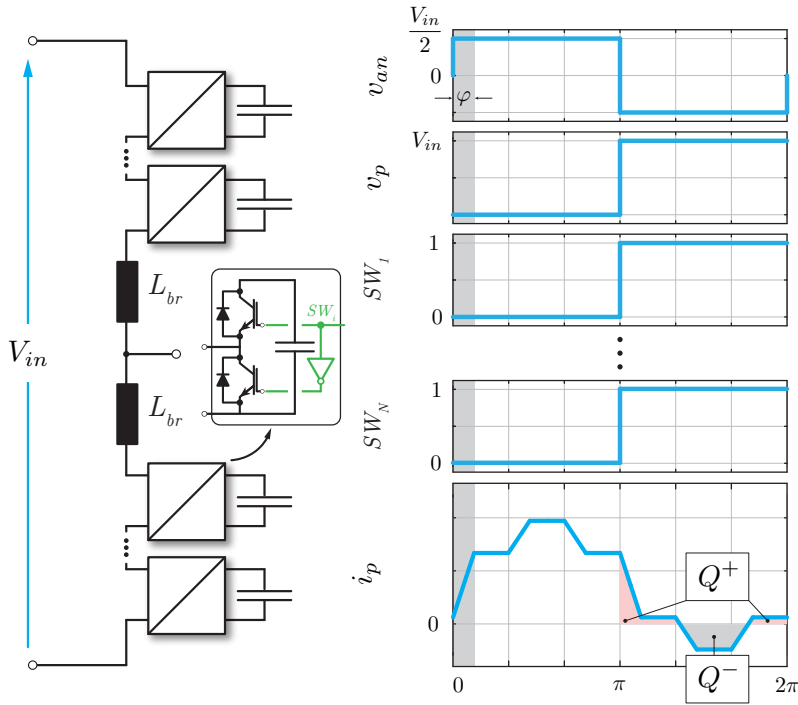
# MMC ENERGY BALANCING AND QUASI SQUARE WAVE OPERATION (I)



▲ MMC operating as a two level converter and its relevant waveforms

Ideally,  $Q^+ = Q^- \Rightarrow$  **Natural balancing** 😊  
 However, reality is different... 😞

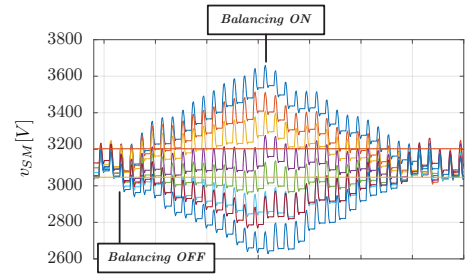
- ▶ Branch resistances affect the MMC current
- ▶ Not all the switches are gated at the same time



⚡ Balancing algorithm must be employed!


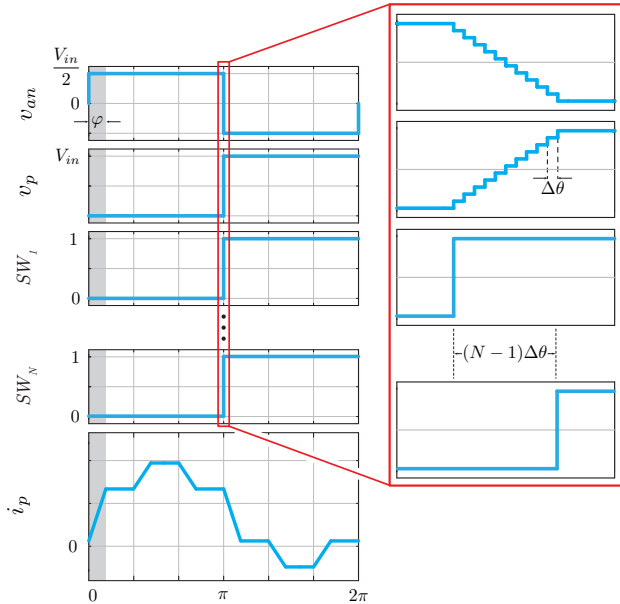
# MMC ENERGY BALANCING AND QUASI SQUARE WAVE OPERATION (II)




▲ MMC operating with quasi square voltages and its relevant waveforms

## Quasi Square Wave operation

- ▶ Intentional displacement among gating signals
- ▶ Control of MFT voltage slopes ( $dV/dt$ )
- ▶ Control of SMs' voltages!


$$G = \frac{V_o m_T}{V_{in}}$$

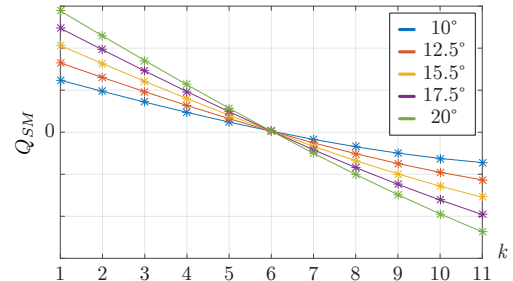For  $G = 1$ , SMs charge distribution can be derived.



▲ Charge received by a SM depending upon the gate signal [37]
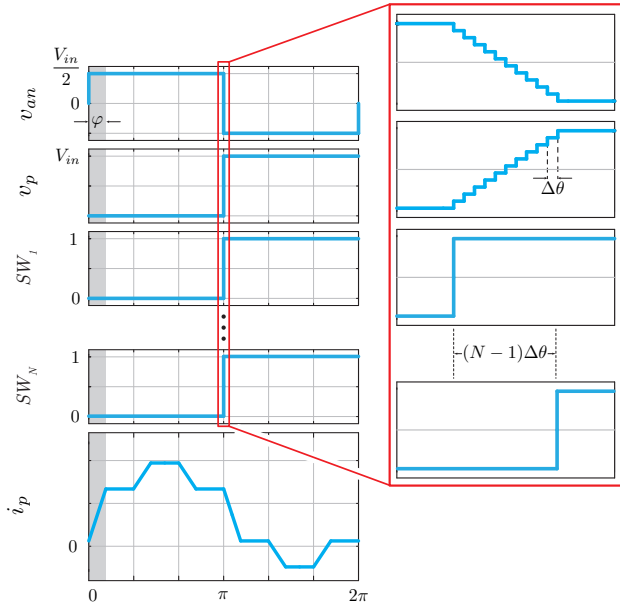
# MMC ENERGY BALANCING AND QUASI SQUARE WAVE OPERATION (II)




▲ MMC operating with quasi square voltages and its relevant waveforms

## Quasi Square Wave operation

- ▶ Intentional displacement among gating signals
- ▶ Control of MFT voltage slopes ( $dV/dt$ )
- ▶ Control of SMs' voltages!

$$G = \frac{V_o m_T}{V_{in}}$$

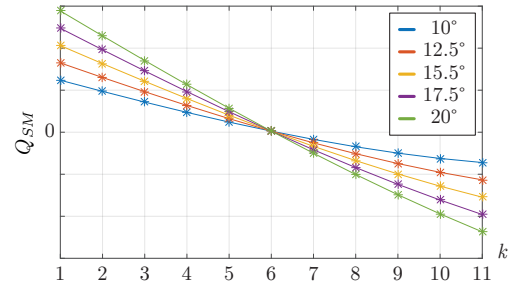For  $G = 1$ , SMs charge distribution can be derived.



▲ Charge received by a SM depending upon the gate signal [37]

⇒ Different charge distribution enables balancing!


# MMC-BASED DAB SORTING FOR N = 3 (EXAMPLE)

- ▶  $V_{SM}(k)$  - SMs voltages measured in the observed switching period
- ▶  $V_{SM}(k - 1)$  - SMs voltages measured in the previous switching period
- ▶  $Gate(k - 1)$  - Gate signals assigned in the previous switching period
- ▶  $\Delta V_{SM}$  - SM voltage change with respect to the previous switching period

	$SM_1$	$SM_2$	$SM_3$
$V_{SM}(k)$	1200	1050	1150
$V_{SM}(k-1)$	1100	1150	1200
Gate (k-1)	Signal 2	Signal 3	Signal 1
$\Delta V_{SM}$	100	-100	-50

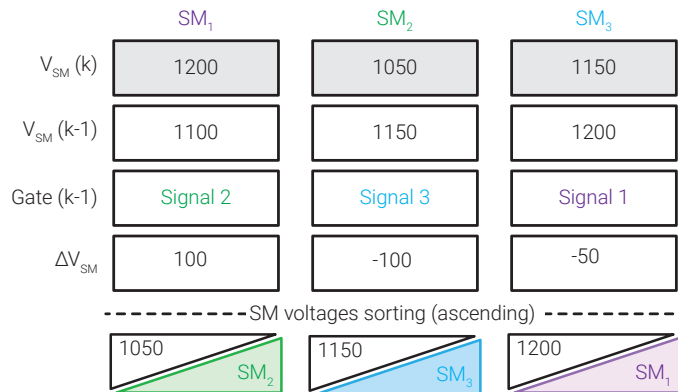
# MMC-BASED DAB SORTING FOR N = 3 (EXAMPLE)

- ▶  $V_{SM}(k)$  - SMs voltages measured in the observed switching period
- ▶  $V_{SM}(k - 1)$  - SMs voltages measured in the previous switching period
- ▶  $Gate(k - 1)$  - Gate signals assigned in the previous switching period
- ▶  $\Delta V_{SM}$  - SM voltage change with respect to the previous switching period



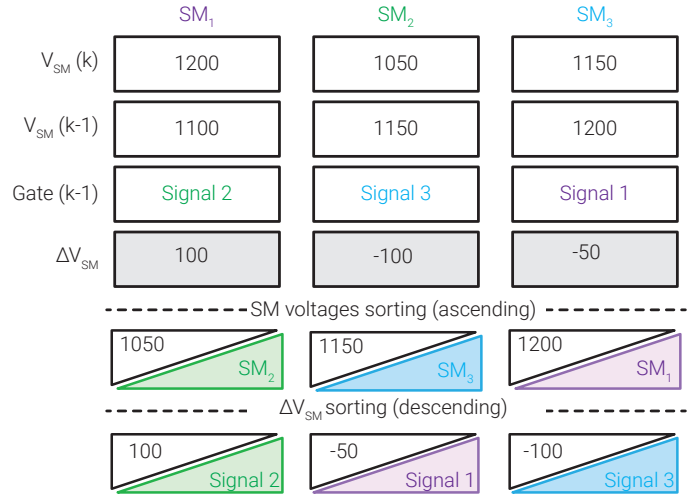
# MMC-BASED DAB SORTING FOR N = 3 (EXAMPLE)

- ▶  $V_{SM}(k)$  - SMs voltages measured in the observed switching period
- ▶  $V_{SM}(k - 1)$  - SMs voltages measured in the previous switching period
- ▶  $Gate(k - 1)$  - Gate signals assigned in the previous switching period
- ▶  $\Delta V_{SM}$  - SM voltage change with respect to the previous switching period



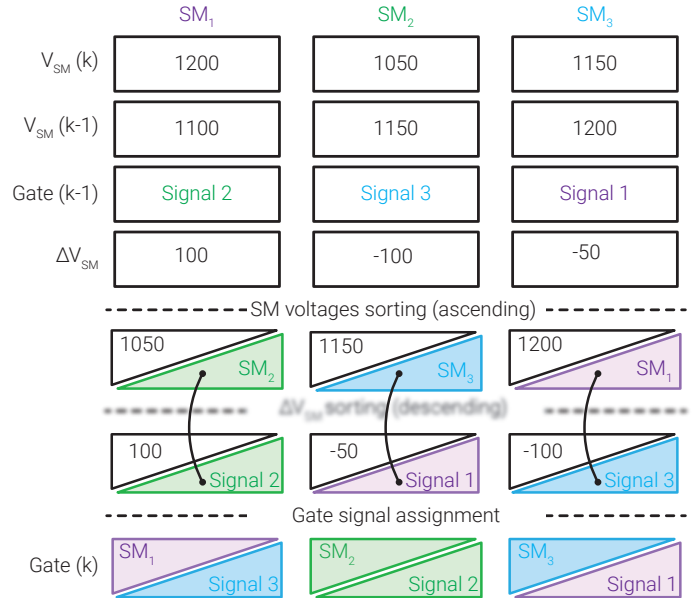
# MMC-BASED DAB SORTING FOR N = 3 (EXAMPLE)

- ▶  $V_{SM}(k)$  - SMs voltages measured in the observed switching period
- ▶  $V_{SM}(k - 1)$  - SMs voltages measured in the previous switching period
- ▶  $Gate(k - 1)$  - Gate signals assigned in the previous switching period
- ▶  $\Delta V_{SM}$  - SM voltage change with respect to the previous switching period
- ▶  $Gate(k)$  - Gate signal assigned to a SM in the observed switching period



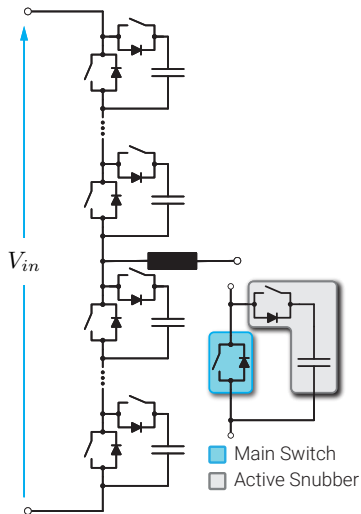
# QUASI TWO-LEVEL (Q2L) CONVERTER

- ▶ MMC-like structure
- ▶ Branch inductors removed!
- ▶ **SM** = Main Switch + Active Snubber
- ▶ Sequential insertion/bypassing of SMs




▲ Quasi Two-Level Converter

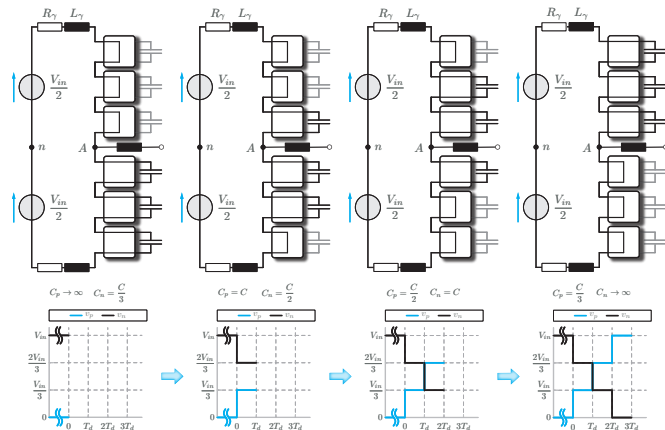


▲ Example of the Q2L Converter transition (N=3)
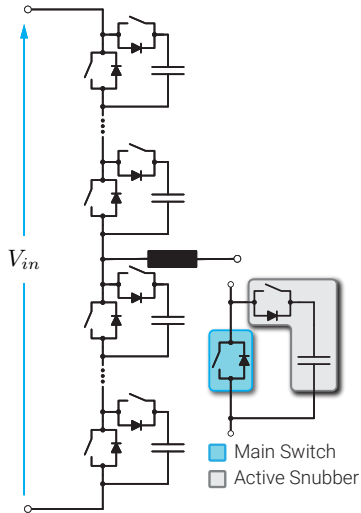
# QUASI TWO-LEVEL (Q2L) CONVERTER

- ▶ MMC-like structure
- ▶ Branch inductors removed!
- ▶ **SM** = **Main Switch** + **Active Snubber**
- ▶ Sequential insertion/bypassing of SMs



▲ Quasi Two-Level Converter

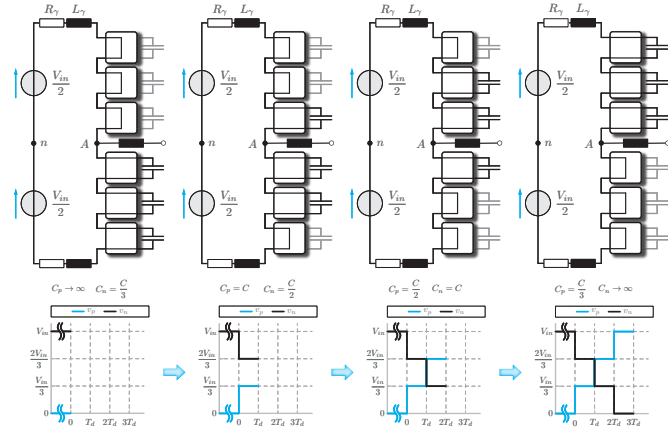


▲ Example of the Q2L Converter transition (N=3)

**⚡** Every dwell interval introduces new resonant parameters to the circuit!



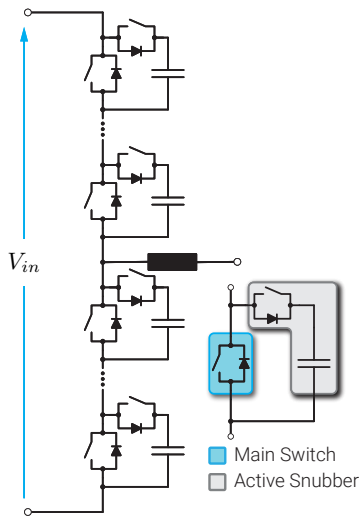
# QUASI TWO-LEVEL (Q2L) CONVERTER


- ▶ MMC-like structure
- ▶ Branch inductors removed!
- ▶ **SM** = **Main Switch** + **Active Snubber**
- ▶ Sequential insertion/bypassing of SMs



▲ Quasi Two-Level Converter

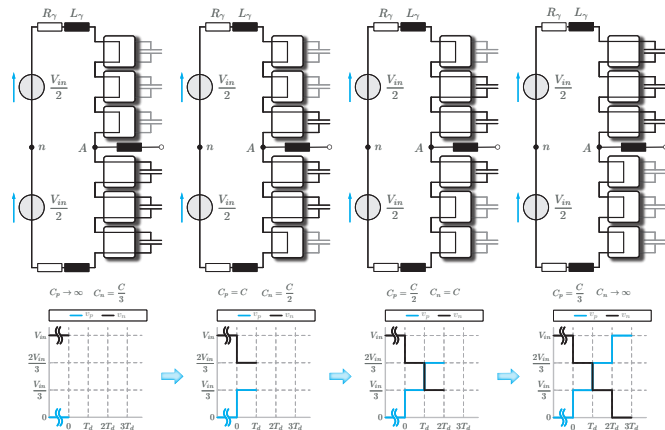


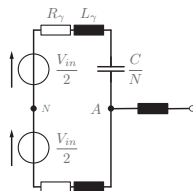▲ Example of the Q2L Converter transition (N=3)



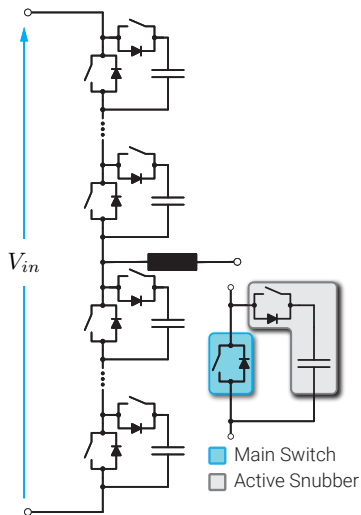
# QUASI TWO-LEVEL (Q2L) CONVERTER


- ▶ MMC-like structure
- ▶ Branch inductors removed!
- ▶ SM = Main Switch + Active Snubber
- ▶ Sequential insertion/bypassing of SMs



▲ Quasi Two-Level Converter

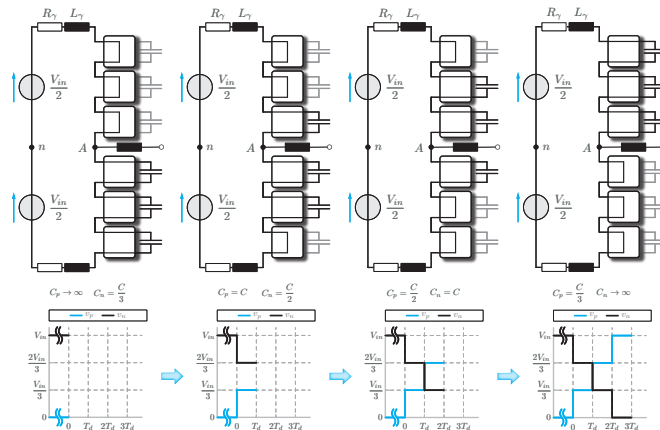


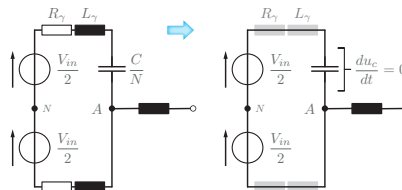▲ Example of the Q2L Converter transition (N=3)



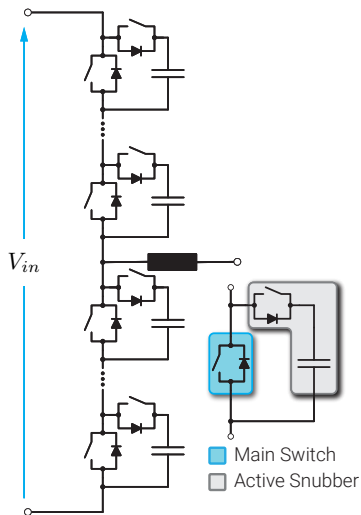
# QUASI TWO-LEVEL (Q2L) CONVERTER


- ▶ MMC-like structure
- ▶ Branch inductors removed!
- ▶ **SM** = **Main Switch** + **Active Snubber**
- ▶ Sequential insertion/bypassing of SMs



▶ Quasi Two-Level Converter


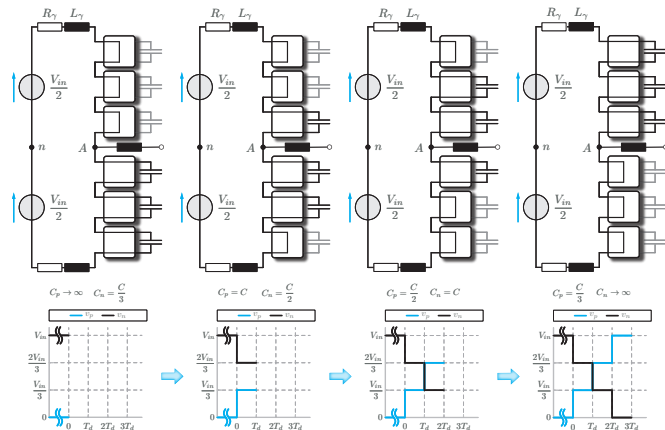


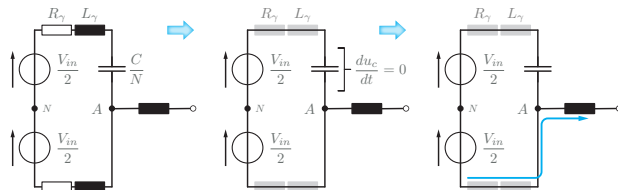▶ Example of the Q2L Converter transition (N=3)




⇒ Output current drifts to a single branch. Common mode current does not exist!

# Q2L CONVERTER - PROS AND CONS

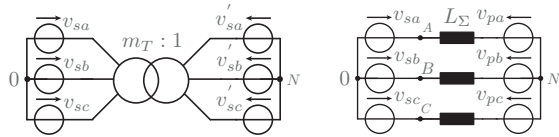
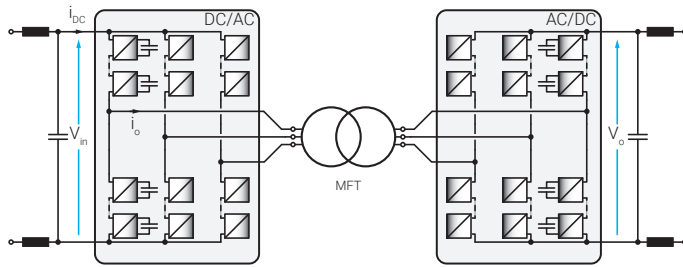


▲ Observed Q2L configuration

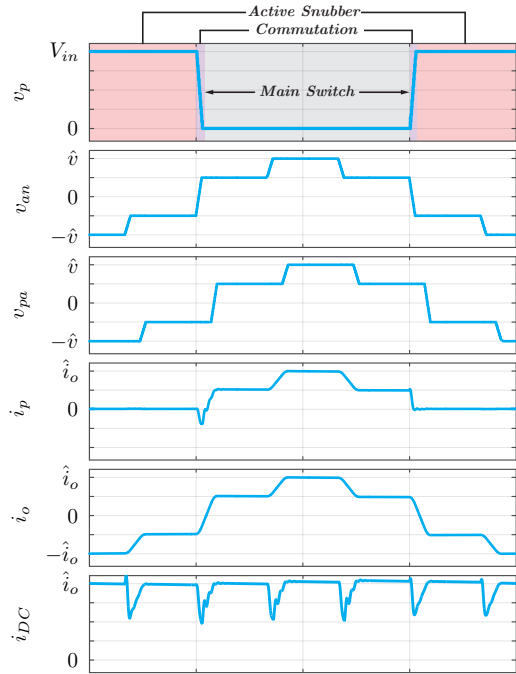


▲ Relevant waveforms of the Q2L converter operating as the 3PH-DAB

# Q2L CONVERTER - PROS AND CONS

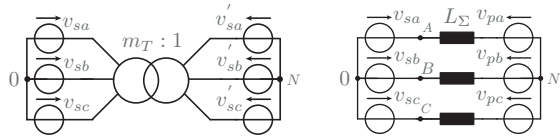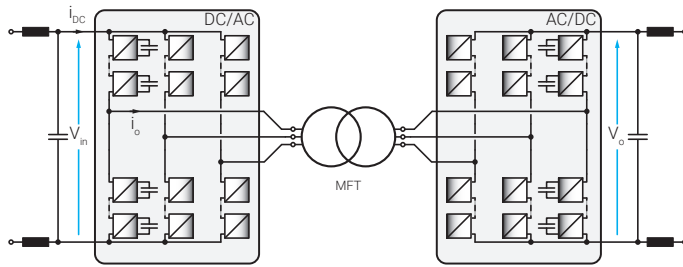


▲ Observed Q2L configuration

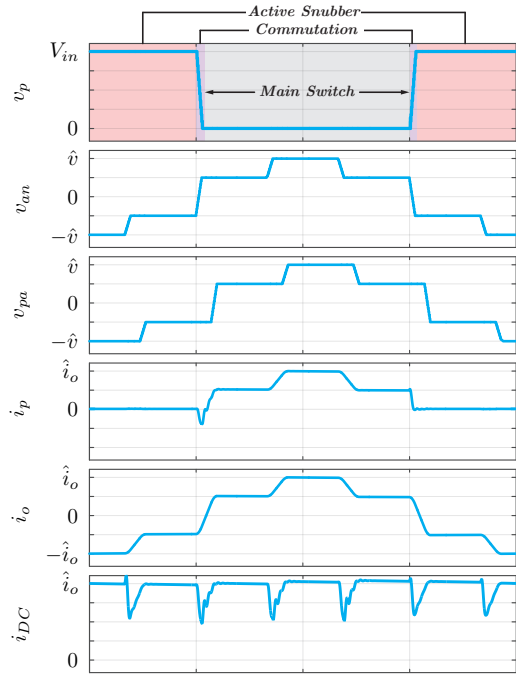→ SM capacitor = "short-interval" energy buffer



▲ Relevant waveforms of the Q2L converter operating as the 3PH-DAB

# Q2L CONVERTER - PROS AND CONS

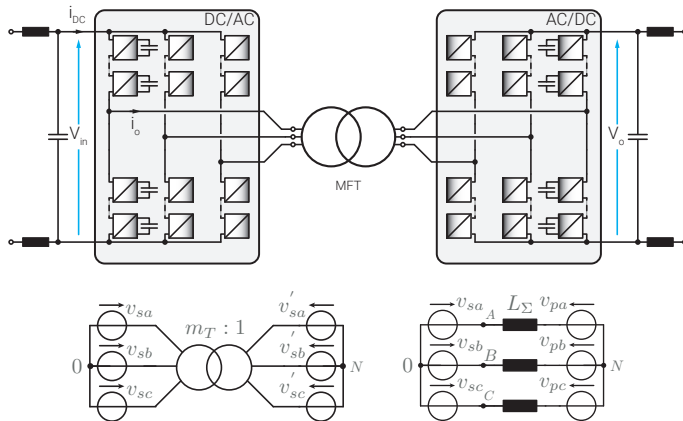


▲ Observed Q2L configuration

## Pros

- ▶ Significant reduction in submodule capacitance
- ▶ Converter size reduction (no branch inductors, small SM capacitance)
- ▶ Active snubber switch can be sized for half the rated current
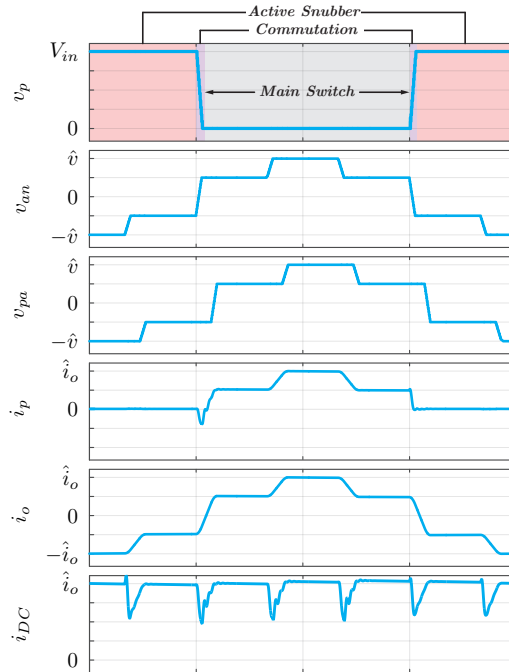
## Cons

- ▶ Need for HV/MV input/output capacitor
- ▶ Complicated analysis of transition process/SM capacitance sizing
- ▶ SM capacitance sizing influenced by the branch stray inductance



▲ Relevant waveforms of the Q2L converter operating as the 3PH-DAB

# MV MMC CONVERTER PLATFORM

*University lab prototype*

# ONGOING MMC – RELATED ACTIVITIES

## Pump Hydro Storage Research Platform

- ▶ MMC based AC/AC converter
- ▶ Interface between SG and local AC grid




- ▲ MMC-Based AC/AC Converter for Pump Hydro Applications

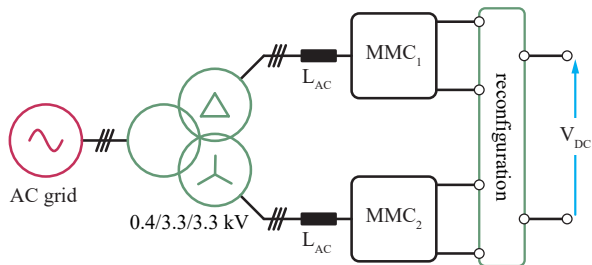
## Flexible DC Source (FlexDCS)

- ▶ MMC Based DC Source rated at 0.5 MVA
- ▶ Reconfiguration unit allows series/parallel operation
- ▶ Four quadrant operation

- ▶ Flexible voltage source in a range  $\pm 10$  kV DC
- ▶ Flexible current source in a range  $\pm 100$  A DC



- ▲ Flexible DC Source Topology

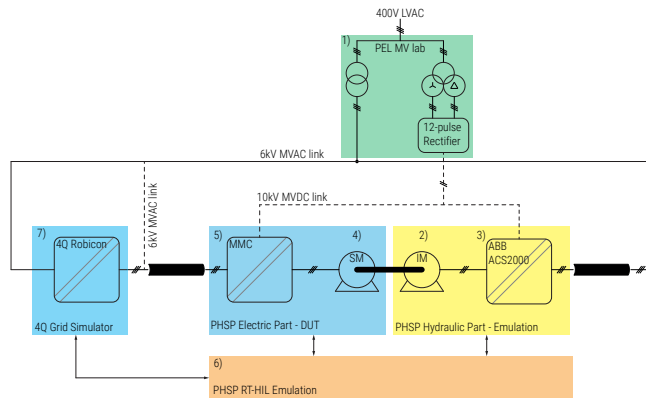


- ▲ Pumped Hydro Storage Plants - Research Platform


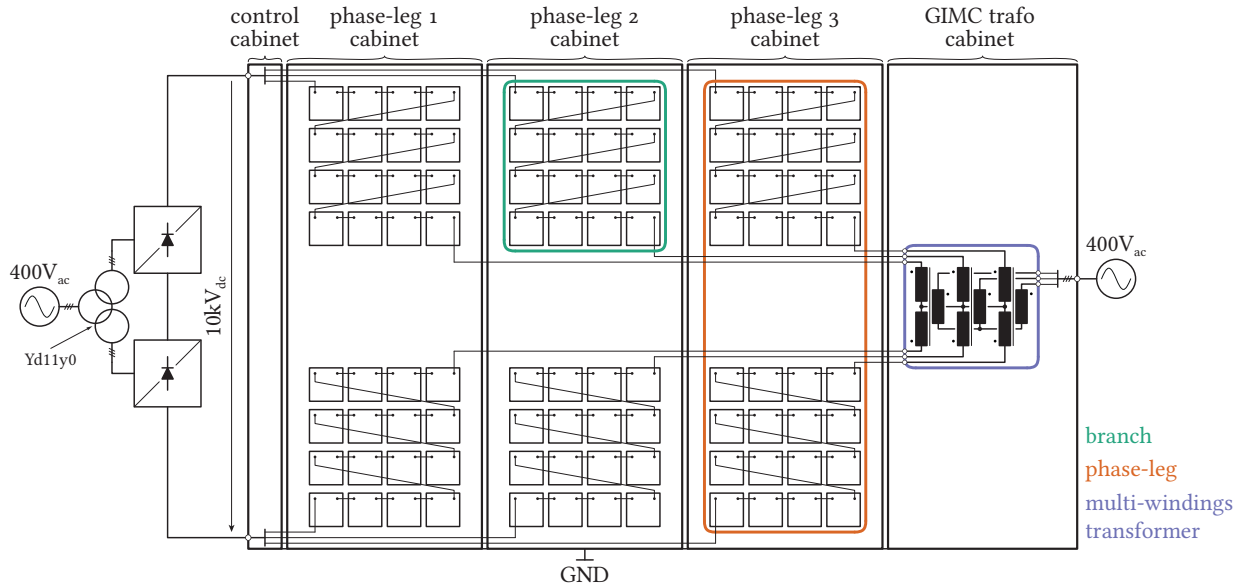
# GIMC - CONVERTER LAYOUT

MMC demonstrator ratings are:

- ▶ 500 kVA
- ▶  $10\text{ kV}_{\text{dc}} \leftrightarrow 400\text{ V}_{\text{ac}}$  or  $6.6\text{ kV}_{\text{ac}}$
- ▶ 16 low voltage cells per branch  $\Rightarrow$  32 cells per phase (cabinet)  $\Rightarrow$  96 cells in total
- ▶ Industrial central controller and communication (ABB AC PEC 800)




▲ DC/3-AC MMC Converter Layout
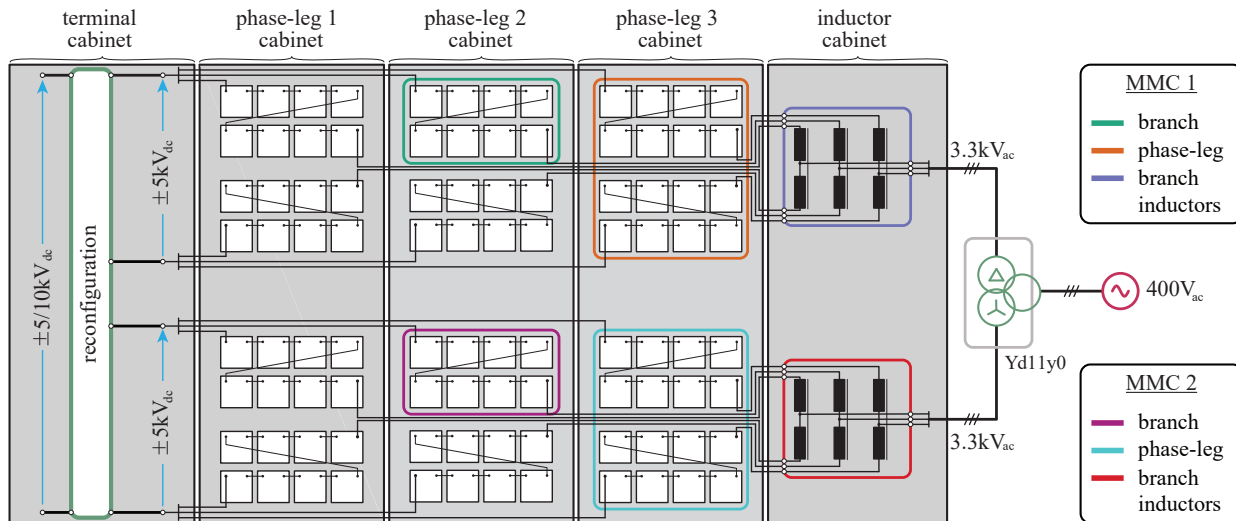
# MMC – CONVERTER LAYOUT

MMC demonstrator ratings are:

- ▶ 500 kVA
- ▶  $\pm 10 \text{ kV}_{\text{dc}} \leftrightarrow 2 \times 3.3 \text{ kV}_{\text{ac}}$
- ▶ 8 low voltage cells per branch  $\Rightarrow$  16 cells per MMC phase  $\Rightarrow$  96 cells in total
- ▶ Industrial central controller and communication (ABB AC PEC 800)



▲ Flexible DC Source Converter Layout




# MMC – SUBMODULE OPTIMIZATION

## Submodule

- ▶ 1.2 kV / 50 A full-bridge IGBT module
- ▶  $C_{cell} = 2.25$  mF
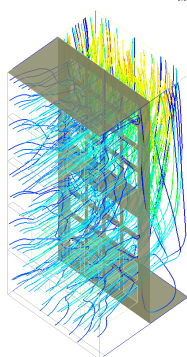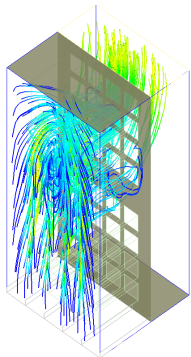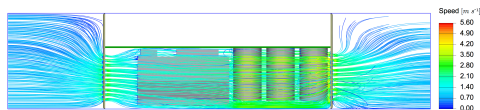
## Thermal design



- ▶ Cell level: detailed FEM
- ▶ Cabinet level: simplified FEM



▲ CFD simulations of submodule and cabinet
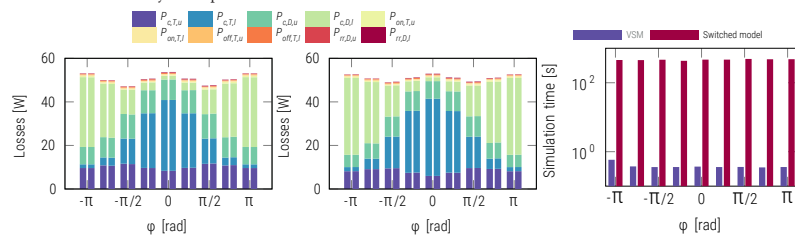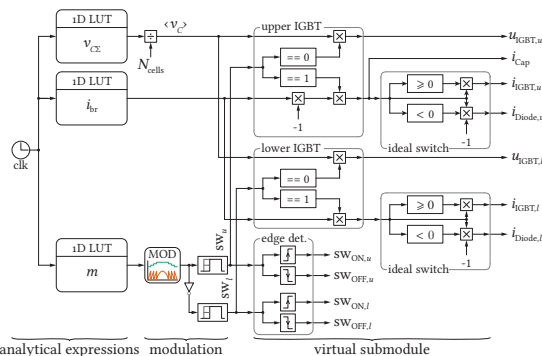
## Semiconductor losses

- ▶ Virtual Submodule concept has been utilized [8]
- ▶ Closed-loop waveforms are approached by analytical waveforms




▲ PS-PWM, DC circ

▲ PS-PWM, DC+2<sup>nd</sup> circ

▲ Time benchmark

# INSULATION COORDINATION OF A MV CONVERTER PROTOTYPE (I)


## System partitioning

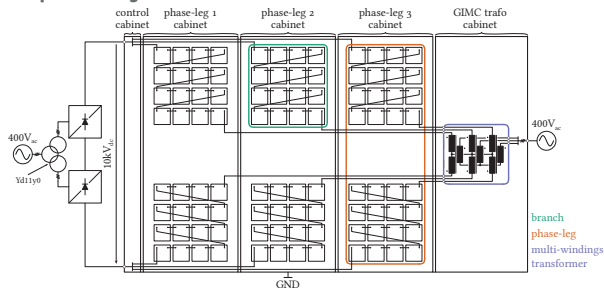

## Standards




- ▶ UL840 for cell PCB (< 1 kV)
- ▶ IEC61800-5-1 (AC motor drives)
  - ▶ Pollution degree 2: "Normally, only non-conductive pollution occurs. Occasionally, however, a temporary conductivity caused by condensation is to be expected, when the PDS is out of operation."
  - ▶ Overvoltage category II: "Equipment not permanently connected to the fixed installation. Examples are appliances, portable tools and other plug-connected equipment."

## Zones definition

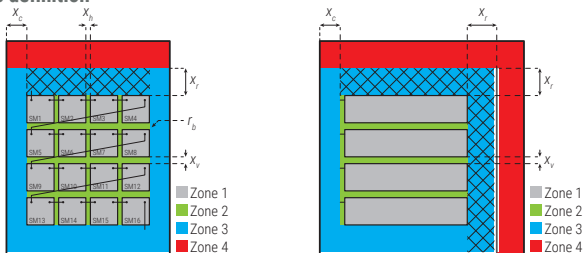
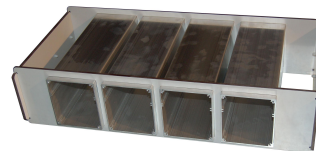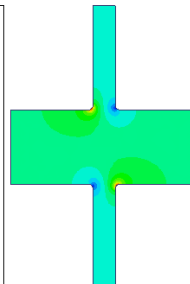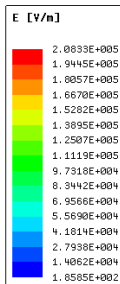
## Zone 2

- ▶ Box at dc- cell's potential (floating)
- ▶ Box corner radius: 3 mm
- ▶ MKHP (high CTI material) drawer holding 4 cells



Zone 1 (ins. coord. inside a SM's enclosure) system voltage: 1 kV<sub>ac</sub>

Zone 2 (ins. coord. branch)


- ▶ Horizontal system voltage: 1 kV<sub>ac</sub>
- ▶ Vertical system voltage: 3.6 kV<sub>ac</sub>

Zone 3 (ins. coord. branch - cabinet (at GND)) system voltage: 6.6 kV<sub>ac</sub>


Zone 4 (ins. coord. for LV circuits) system voltage: 0.4 kV<sub>ac</sub>
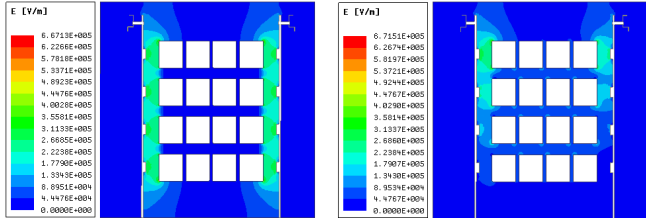
# INSULATION COORDINATION OF A MV CONVERTER PROTOTYPE (II)

Zone 3 (2 out of  $2^{16}$  combinations)



## Ac dielectric withstand test

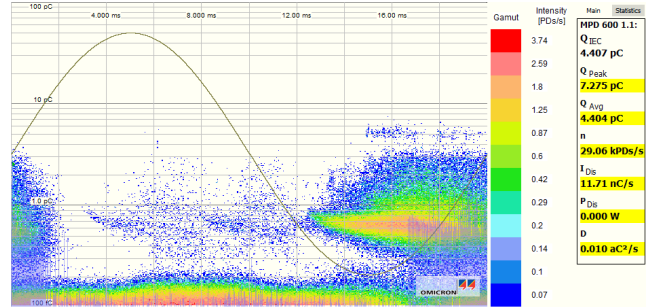

## Design recap

Variable	Minimal value [mm]	Actual design value [mm]
$r_b$		3
$d_{L,h}$	6.8	15
$d_{C,h}$	3.2	15
$d_{L,v}$	30	50
$d_{C,v}$	12.5	275
$d_{L,c}$	60	81.5
$d_{C,c}$	60	93
$d_{L,r}$	102	120



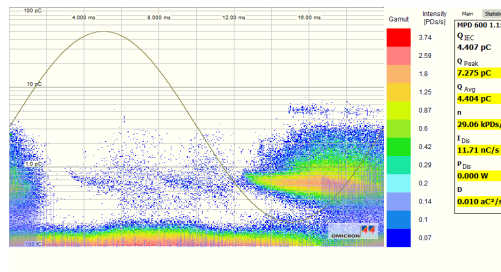
# MMC – CONVERTER DESIGN


- ✓ MV MMC converter laboratory prototype layout compliant with:
  - ▶ UL840 (for cell)
  - ▶ IEC 61800-5-1
- ✓ Complete AC dielectric withstand tests on real prototype [9]



▲ Cabinet of one phase-leg (32 cells) in Faraday cage during insulation coordination testing



▲ AC dielectric withstand test result

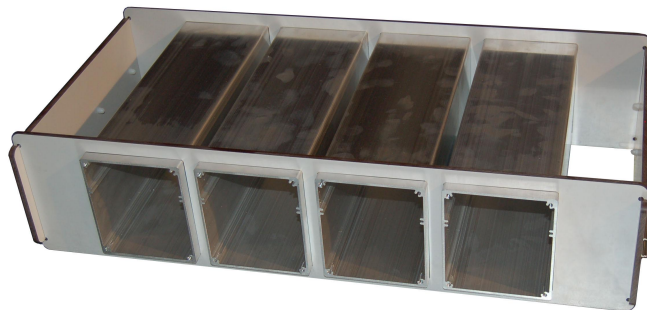


▲ Drawer holding 4 cell (MKHP material)


# MMC SUBMODULE – STRUCTURE
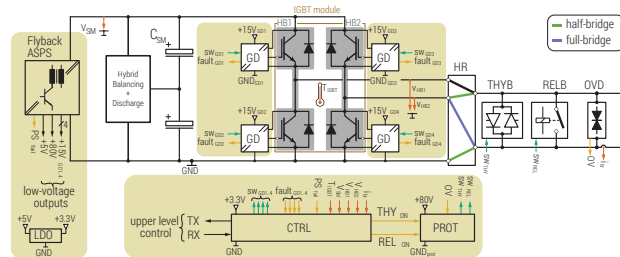
## Key Features

- ▶ Low voltage power components
- ▶ Full-bridge submodule structure
- ▶ Submodule rated voltage - 625 V
- ▶ Submodule insulation coordination - 900 V
- ▶ Two interconnected PCBs: **Power PCB** and **Control PCB**



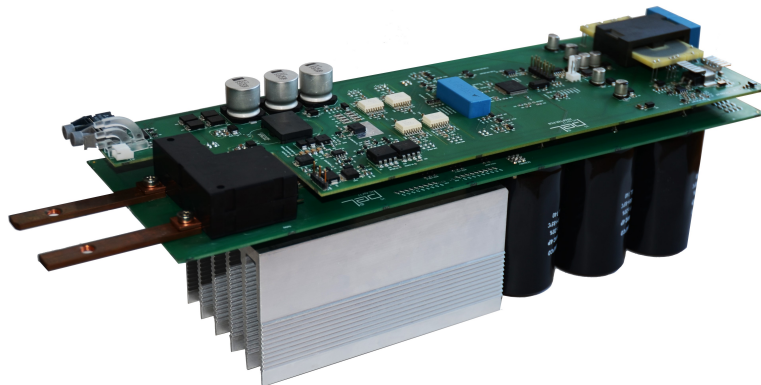
▲ MMC Submodule Structure: Yellow parts - Control PCB




▲ Developed MMC submodule
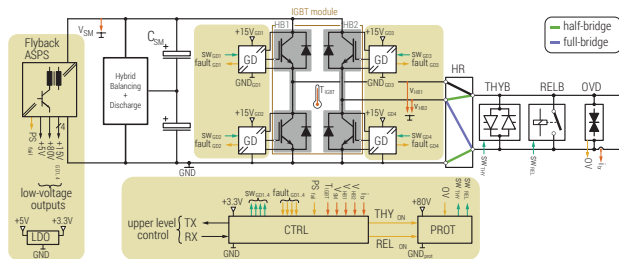
# MMC SUBMODULE – POWER PCB

- ▶ Power processing part
- ▶ Semikron full-bridge IGBT module 1.2 kV/50 A
- ▶ Bank of electrolytic capacitors  $C_{sm} = 2.25 \text{ mF}$
- ▶ Protection devices: Bypass thyristor, relay and OVD
- ▶ Current and voltage measurements
- ▶ Hybrid balancing circuitry
- ▶ Hardware reconfiguration (HR)



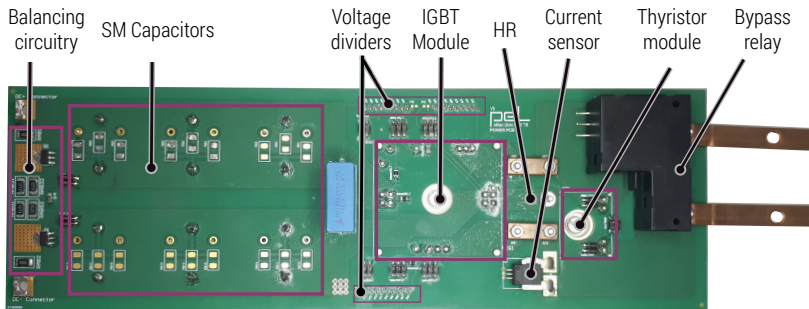▲ MMC Submodule Structure: Yellow parts - Control PCB




▲ Top overview of the Power PCB



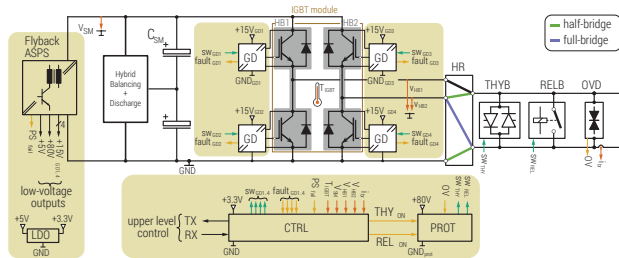
# MMC SUBMODULE – CONTROL PCB

- ▶ Flyback based auxiliary power supply
  - ▶ +5V Output, used as a control feedback
  - ▶ +80V Protection supply
  - ▶ +15V Gate drivers supplies
  - ▶ +15V Self-supply output
- ▶ DSP based main SM Controller
  - ▶ Communication with upper level control
  - ▶ Voltage and current measurements
  - ▶ Monitoring the SM condition
  - ▶ Decentralized modulation
- ▶ Gate drivers
- ▶ Protection logic
  - ▶ Protection activation from upper level control
  - ▶ Protection activation from DSP
  - ▶ Protection activation by overvoltage detection
- ▶ Fiber-optical communication link



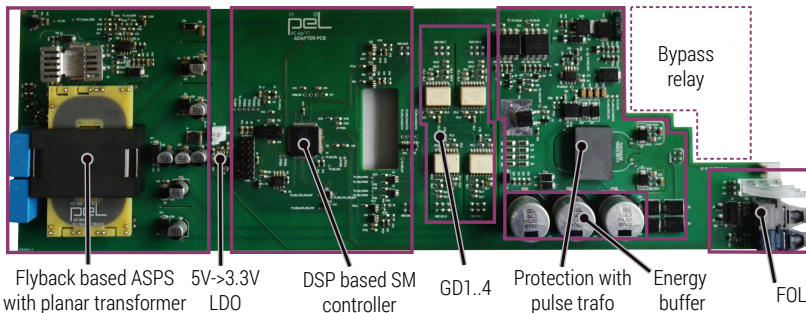▲ MMC Submodule Structure: Yellow parts- Control PCB



▲ MMC Top overview of the Control PCB


# AUXILIARY SUBMODULE POWER SUPPLY (I)

## Possible concepts

- ▶ Externally supplied
  - ▶ Single wire loop
  - ▶ Siebel
  - ▶ Inductive power transfer
- ▶ Internally supplied
  - ▶ Tapped inductor Buck
  - ▶ Flyback
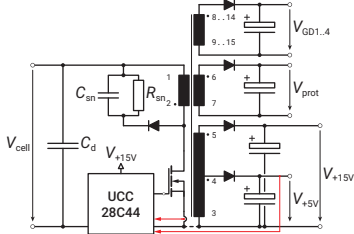
## Choice

- ▶ Flyback with 6 isolated secondaries
  - ▶  $1 \times 5V, 4W$  for the controller supply ( $V_{+5V}$ ). This output is tightly regulated in closed-loop.
  - ▶  $4 \times 15V, 1.5W$  for the IGBT gate drivers ( $V_{GD1..4}$ )
  - ▶  $1 \times 80V, 15W$  for 15 s operation when activated for the protection circuit ( $V_{prot}$ )






## Planar trafo design

- ▶ PCB windings (isolation requirements!)
- ▶ Planar ferrite cores with custom gapping (COSMO ferrites)

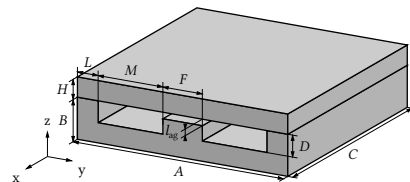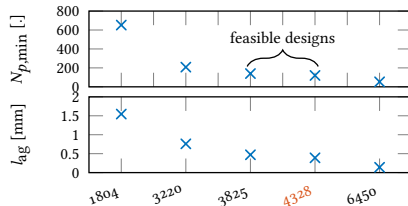
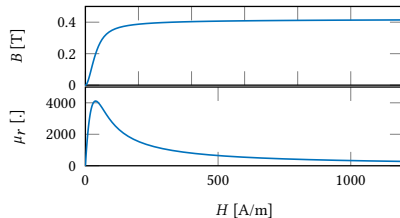
## Matlab design tool

- ▶ Account for flux fringing [38]
- ▶ BH curve for CF297
- ▶ Jiles-Atherton parametrization


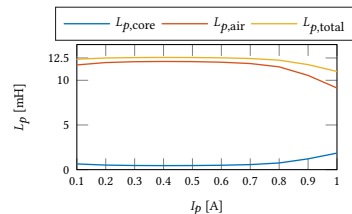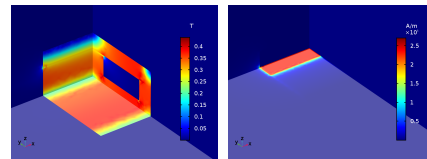
## FEM



- ▶ Validate Matlab design
- ▶ 3D model for accurate leakage flux



# AUXILIARY SUBMODULE POWER SUPPLY (II)

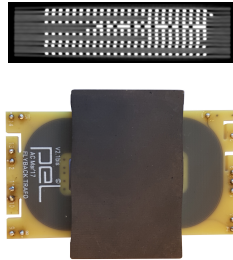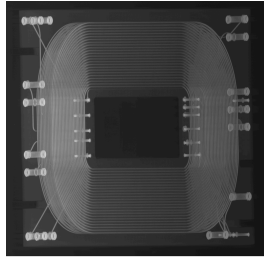
## Transformer assembly

- ▶ 14 copper layers PCB
- ▶ Custom gapped ferrite E+I core




## AC dielectric withstand test


- ▶ Way below threshold level of 10pC

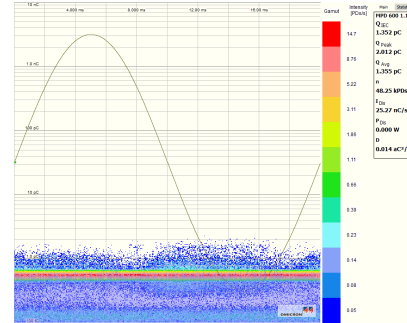


## Tests

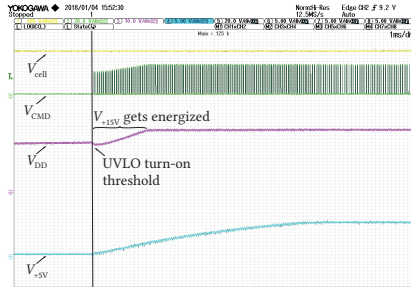

▲ Start-up

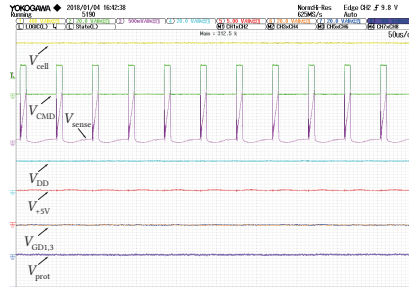


▲ Steady-state operation

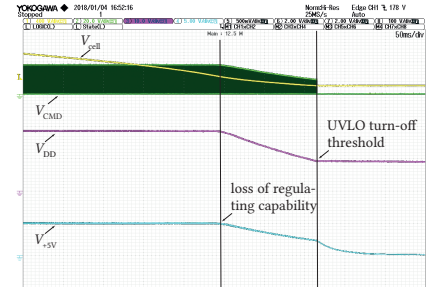


▲ Shut-down (slow dv/dt from Delta power-supply used to emulate the cell)

# MMC MECHANICS

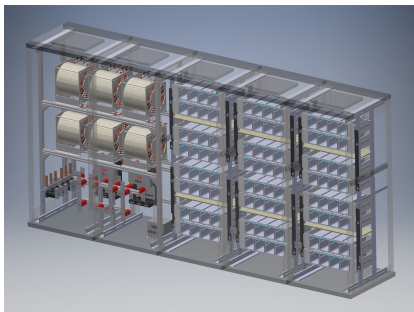


▲ MMC CAD development

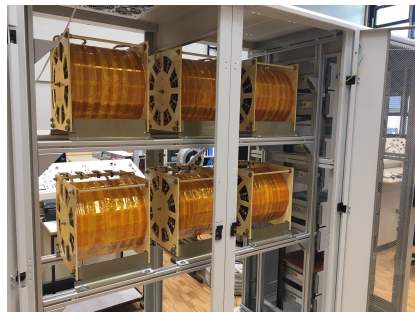

▲ MMC coupled air-core branch inductors




▲ MMC - Actual mechanical assembly

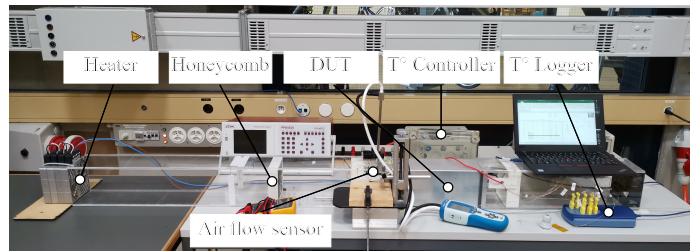


▲ MMC Submodule thermal heat-run test setup
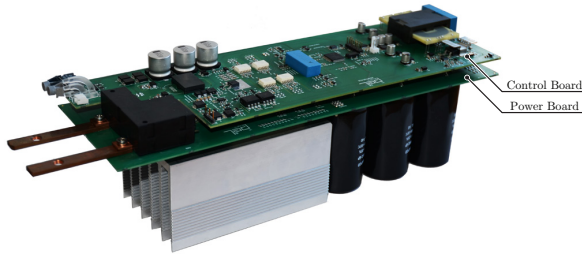
# MMC CONTROL TESTING PLATFORM BASED ON THE PLECS RT-BOX HIL

- ▶ **Digital twin** of the system being under construction
- ▶ Virtual power processing
- ▶ Safe control testing prior to commissioning
- ▶ Flexibility
- ▶ Certain adjustments need to be made
  - ▶ Adjustment of the original MMC submodule?
  - ▶ RT-Box/MMC submodule interface boards
- ▶ Two connected MMCs as the end goal (**13 RT-Boxes + 96 cells**)



▲ MMC Submodule

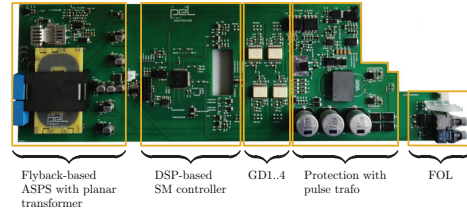


▲ MMC Submodule Control board

# MMC CONTROL TESTING PLATFORM BASED ON THE PLECS RT-BOX HIL

- ▶ **Digital twin** of the system being under construction
- ▶ Virtual power processing
- ▶ Safe control testing prior to commissioning
- ▶ Flexibility
- ▶ Certain adjustments need to be made
  - ▶ Adjustment of the original MMC submodule?
  - ▶ RT-Box/MMC submodule interface boards
- ▶ Two connected MMCs as the end goal (**13 RT-Boxes + 96 cells**)




▲ MMC Submodule

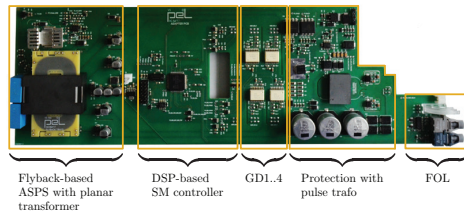

Following parts of the Control Boards are retained:

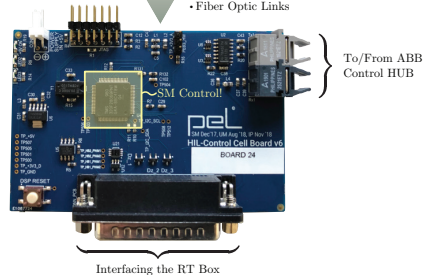
- DSP-based SM controller
- Fiber Optic Links



▲ Control board trimming ⇒ Adjusted Control card
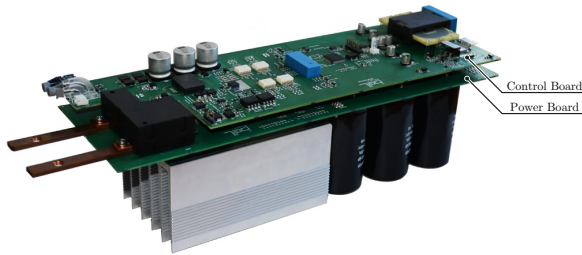
# MMC CONTROL TESTING PLATFORM BASED ON THE PLECS RT-BOX HIL

- ▶ **Digital twin** of the system being under construction
- ▶ Virtual power processing
- ▶ Safe control testing prior to commissioning
- ▶ Flexibility
- ▶ Certain adjustments need to be made
  - ▶ Adjustment of the original MMC submodule?
  - ▶ RT-Box/MMC submodule interface boards
- ▶ Two connected MMCs as the end goal (**13 RT-Boxes + 96 cells**)




▲ MMC Submodule




▲ Stack of PLECS RT-Boxes hosting the adjusted Control cards
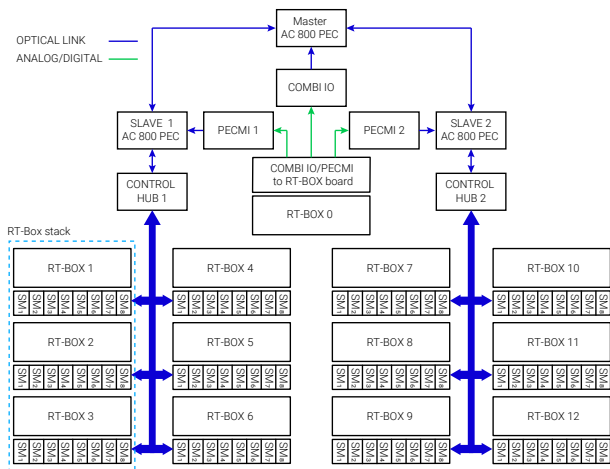
# MMC RT-HIL SYSTEM)

- ▶ **Digital twin** of real MMC
- ▶ Two connected MMCs (48 Submodules per MMC)
- ▶ 6 RT-Boxes per MMC (8 Submodules per RT-Box)
- ▶ 1 RT-Box for DC an AC side terminals (application)
- ▶ Safe control SW testing prior to commissioning
- ▶ Flexibility in SW testing
- ▶ Ability to work in parallel with HW development



▲ MMC RT-HIL complete scheme

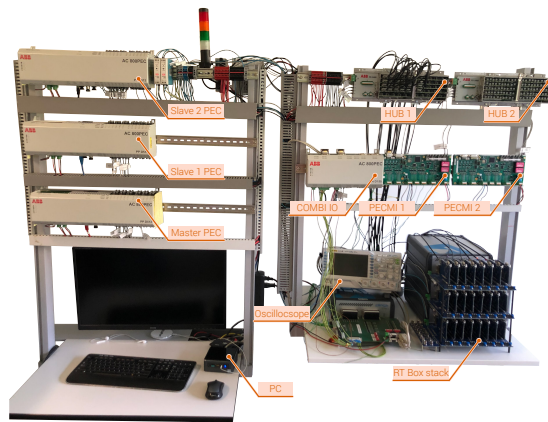

▲ MMC RT-HIL system including ABB AC 800PEC industrial controllers



# SUMMARY


# SUMMARY

## Modular Multilevel Converter


- ▶ Modular design easily scalable for higher voltages
- ▶ Flexible and adaptable for different conversion needs
- ▶ Efficient
- ▶ HVDC (early adopter)
- ▶ STATCOM, FACTS, RAIL INTERTIES, MV DRIVES
- ▶ Can serve MV and HV applications!
- ▶ Unlimited research opportunities...



▶ HVDC Light valve hall from ABB.

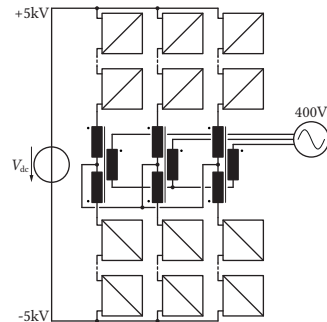

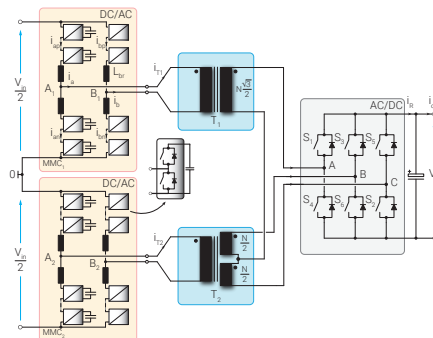▶ Galvanically Isolated Modular Converter



▶ High Power DC-DC Converter Employing Scott Transformer Connection

# REFERENCES

- [1] ABB. *Tjæreborg*. <http://new.abb.com/systems/hvdc/references/tjaereborg>.
- [2] Charles Bodel. *Paimpol-Bréhat tidal demonstrator project*. <http://eusew.eu/sites/default/files/programme-additional-docs/EUSEW1606160PresentationtoEUSEWbyEDF.pdf>. EDF.
- [3] G. Bathurst, G. Hwang, and L. Tejwani. "MVDC - The New Technology for Distribution Networks." *11th IET International Conference on AC and DC Power Transmission*. Feb. 2015, pp. 1–5.
- [4] SP Energy Networks. *Angle dc*. [https://www.spenergynetworks.co.uk/pages/angle\\_dc.aspx](https://www.spenergynetworks.co.uk/pages/angle_dc.aspx).
- [5] D. Dujic et al. "Power Electronic Traction Transformer-Low Voltage Prototype." *IEEE Transactions on Power Electronics* 28.12 (Dec. 2013), pp. 5522–5534.
- [6] C. Zhao et al. "Power Electronic Traction Transformer-Medium Voltage Prototype." *IEEE Transactions on Industrial Electronics* 61.7 (July 2014), pp. 3257–3268.
- [7] J. E. Huber and J. W. Kolar. "Volume/weight/cost comparison of a 1MVA 10 kV/400 V solid-state against a conventional low-frequency distribution transformer." *2014 IEEE Energy Conversion Congress and Exposition (ECCE)*. Sept. 2014, pp. 4545–4552.
- [8] A. Christe and D. Dujic. "Virtual Submodule Concept for Fast Semi-Numerical Modular Multilevel Converter Loss Estimation." *IEEE Transactions on Industrial Electronics* 64.7 (July 2017), pp. 5286–5294.
- [9] A. Christe, E. Coulinge, and D. Dujic. "Insulation coordination for a modular multilevel converter prototype." *2016 18th European Conference on Power Electronics and Applications (EPE'16 ECCE Europe)*. Sept. 2016, pp. 1–9.
- [10] A. Rasic et al. "Optimization of the modular multilevel converters performance using the second harmonic of the module current." *2009 13th European Conference on Power Electronics and Applications*. Sept. 2009, pp. 1–10.
- [11] Amirnaser Yazdani and Reza Iravani. *Voltage-Sourced Converters in Power Systems: Modeling, Control, and Applications*. Wiley-IEEE Press, 2010.
- [12] P. Rodriguez et al. "Decoupled Double Synchronous Reference Frame PLL for Power Converters Control." *IEEE Transactions on Power Electronics* 22.2 (Mar. 2007), pp. 584–592.
- [13] D. N. Zmood and D. G. Holmes. "Stationary frame current regulation of PWM inverters with zero steady-state error." *IEEE Transactions on Power Electronics* 18.3 (May 2003), pp. 814–822.
- [14] P. Münch et al. "Integrated current control, energy control and energy balancing of Modular Multilevel Converters." *IECON 2010 - 36th Annual Conference on IEEE Industrial Electronics Society*. Nov. 2010, pp. 150–155.
- [15] X. She et al. "AC circulating currents suppression in modular multilevel converter." *IECON 2012 - 38th Annual Conference on IEEE Industrial Electronics Society*. Oct. 2012, pp. 191–196.
- [16] S. Cui et al. "Principles and dynamics of natural arm capacitor voltage balancing of a direct modulated modular multilevel converter." *2015 9th International Conference on Power Electronics and ECCE Asia (ICPE-ECCE Asia)*. June 2015, pp. 259–267.
- [17] L. Angquist et al. "Open-Loop Control of Modular Multilevel Converters Using Estimation of Stored Energy." *IEEE Transactions on Industry Applications* 47.6 (Nov. 2011), pp. 2516–2524.
- [18] A. Antonopoulos et al. "Global Asymptotic Stability of Modular Multilevel Converters." *IEEE Transactions on Industrial Electronics* 61.2 (Feb. 2014), pp. 603–612.
- [19] L. Harnefors et al. "Global Asymptotic Stability of Current-Controlled Modular Multilevel Converters." *IEEE Transactions on Power Electronics* 30.1 (Jan. 2015), pp. 249–258.
- [20] M. Hagiwara and H. Akagi. "Control and Experiment of Pulsewidth-Modulated Modular Multilevel Converters." *IEEE Transactions on Power Electronics* 24.7 (July 2009), pp. 1737–1746.
- [21] A. Lesnicar and R. Marquardt. "An innovative modular multilevel converter topology suitable for a wide power range." *2003 IEEE Bologna Power Tech Conference Proceedings*, vol. 3. June 2003, 6 pp. Vol.3.
- [22] K. Ilves et al. "A New Modulation Method for the Modular Multilevel Converter Allowing Fundamental Switching Frequency." *IEEE Transactions on Power Electronics* 27.8 (Aug. 2012), pp. 3482–3494.
- [23] J. E. Huber and A. J. Korn. "Optimized Pulse Pattern modulation for Modular Multilevel Converter high-speed drive." *2012 15th International Power Electronics and Motion Control Conference (EPE/PEMC)*. Sept. 2012, LS1a-1.4-1-LS1a-1.4-7.
- [24] M. Vasiladiotis, A. Christe, and T. Geyer. "Model Predictive Pulse Pattern Control for Modular Multilevel Converters." *IEEE Transactions on Industrial Electronics* (2018), pp. 1–1.
- [25] A. Hassanpoor et al. "Tolerance-band modulation methods for modular multilevel converters." *2013 15th European Conference on Power Electronics and Applications (EPE)*. Sept. 2013, pp. 1–10.
- [26] A. Pérez-Basante et al. "(2N+1) Selective Harmonic Elimination-PWM for Modular Multilevel Converters: A Generalized Formulation and A Circulating Current Control Method." *IEEE Transactions on Power Electronics* 33.1 (Jan. 2018), pp. 802–818.
- [27] Q. Tu, Z. Xu, and L. Xu. "Reduced Switching-Frequency Modulation and Circulating Current Suppression for Modular Multilevel Converters." *IEEE Transactions on Power Delivery* 26.3 (July 2011), pp. 2009–2017.
- [28] S. Inoue and H. Akagi. "A Bidirectional Isolated DC-DC Converter as a Core Circuit of the Next-Generation Medium-Voltage Power Conversion System." *IEEE Transactions on Power Electronics* 22.2 (Mar. 2007), pp. 535–542.

# REFERENCES

---

- [29] Johann W Kolar and Gabriel Ortiz. "Solid-state-transformers: key components of future traction and smart grid systems." *Proc. of the International Power Electronics Conference (IPEC), Hiroshima, Japan*. 2014.
- [30] R. W. A. A. De Doncker, D. M. Divan, and M. H. Kheraluwala. "A three-phase soft-switched high-power-density DC/DC converter for high-power applications." *IEEE Transactions on Industry Applications* 27.1 (Jan. 1991), pp. 63–73.
- [31] Stefan P Engel, Nils Soltan, and Rik W De Doncker. "Instantaneous current control for the three-phase dual-active bridge DC-DC converter." *Energy Conversion Congress and Exposition (ECCE)*. IEEE. 2012, pp. 3964–3969.
- [32] Stefan P Engel et al. "Improved instantaneous current control for the three-phase dual-active bridge DC-DC converter." *ECCE Asia Downunder (ECCE Asia)*. IEEE. 2013, pp. 855–860.
- [33] R. Withanage and N. Shammass. "Series Connection of Insulated Gate Bipolar Transistors (IGBTs)." *IEEE Transactions on Power Electronics* 27.4 (Apr. 2012), pp. 2204–2212.
- [34] IA Gowaid et al. "Analysis and design of a modular multilevel converter with trapezoidal modulation for medium and high voltage DC-DC transformers." *IEEE Transactions on Power Electronics* 30.10 (2015), pp. 5439–5457.
- [35] IA Gowaid et al. "Quasi two-level operation of modular multilevel converter for use in a high-power DC transformer with DC fault isolation capability." *IEEE Transactions on Power Electronics* 30.1 (2015), pp. 108–123.
- [36] Stephan Kenzelmann et al. "Isolated DC/DC structure based on modular multilevel converter." *IEEE Transactions on Power Electronics* 30.1 (2015), pp. 89–98.
- [37] S. Shao et al. "A Capacitor Voltage Balancing Method for a Modular Multilevel DC Transformer for DC Distribution System." *IEEE Transactions on Power Electronics* 33.4 (Apr. 2018), pp. 3002–3011.
- [38] J. Muhlethaler, J. W. Kolar, and A. Ecklebe. "A novel approach for 3d air gap reluctance calculations." *8th International Conference on Power Electronics - ECCE Asia*. May 2011, pp. 446–452.



Tutorial pdf can be downloaded from:

► [https://pel.epfl.ch/publications\\_talks\\_en](https://pel.epfl.ch/publications_talks_en)